


SECTION 7: ACTIVE FILTERS

ENGR 203 – Electrical Fundamentals III

Introduction

2

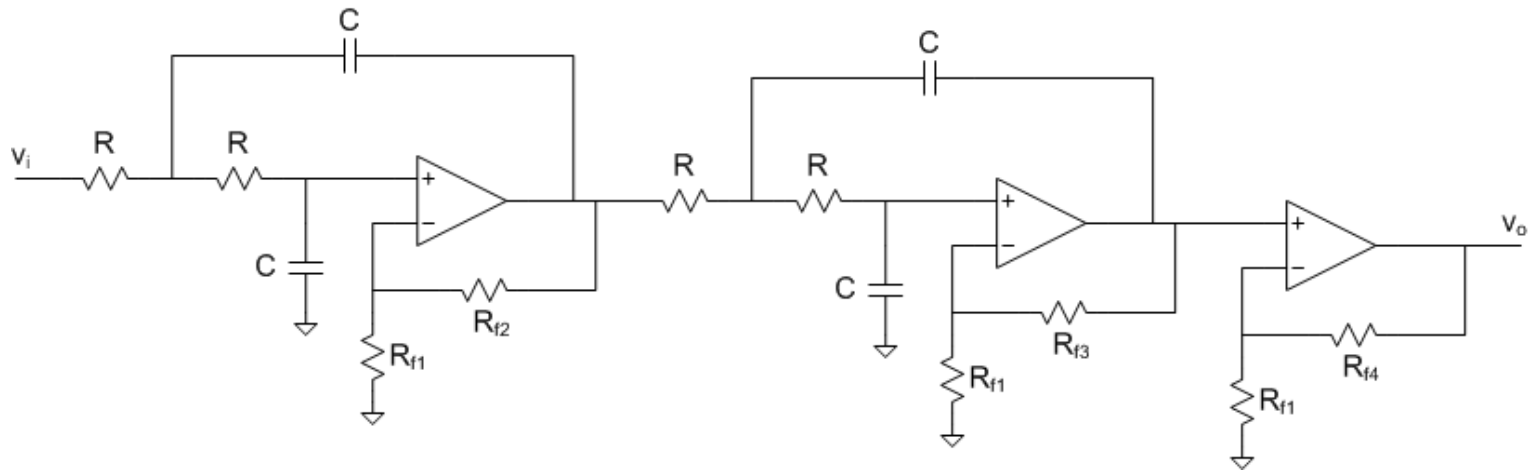- In ENGR 202 we studied different types of first- and second-order *passive* filters
 - ▣ *Passive*, because they contain only passive components:
 - Resistors, capacitors, and inductors
- Can also construct filters using opamps
 - ▣ *Active filters*



Introduction

3

- Active filters have advantages over passive filters:
 - ▣ Can build ***high-Q filters without inductors***
 - ▣ ***Low output impedance***
 - ▣ Easily ***adjustable***: f_c , Q
 - ▣ Can provide ***gain*** (> 0 dB)

- Before getting into the design of active filters, we will look at two fundamental filter building blocks:
 - ▣ Opamp integrators
 - ▣ Opamp differentiators

4

Opamp Integrators

Integrators and Differentiators

5


- Opamp circuits can perform many different ***mathematical operations***
 - ▣ ***Operational amplifiers***
- Multiplication
 - ▣ Inverting and non-inverting amplifiers
- Addition and subtraction
 - ▣ Summing and difference amplifiers
- Can also perform ***integration*** and ***differentiation***
 - ▣ Feedback controllers
 - ▣ Building block of active filters

Opamp Integrator – Time Domain

6

- Analyze the opamp integrator in the time domain
- Virtual ground at inverting input, so

$$i(t) = \frac{v_i(t)}{R}$$

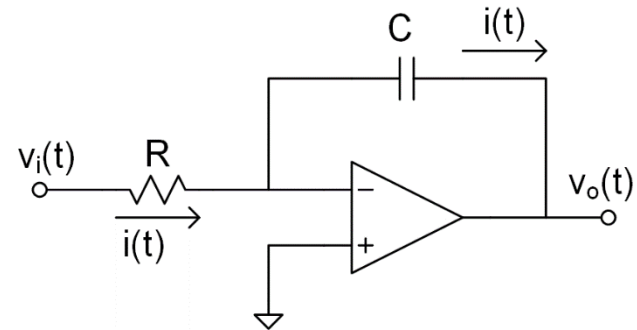

- Capacitor **integrates** input current to give output voltage

$$v_o(t) = -\frac{1}{C} \int_0^t i(\tau) d\tau \quad v_o(t) = -\frac{1}{RC} \int_0^t v_i(\tau) d\tau$$

- Output is the (scaled and inverted) integral of the input

Opamp Integrator – Laplace Domain

7


- Analyze the opamp integrator in the Laplace domain
- Again, a virtual ground at inverting input, so

$$I(s) = \frac{V_i(s)}{R}$$

- Output voltage:

$$V_o(s) = -I(s) \frac{1}{Cs} = -\frac{V_i(s)}{RCs} = -\frac{1}{s} \cdot \frac{V_i(s)}{RC}$$

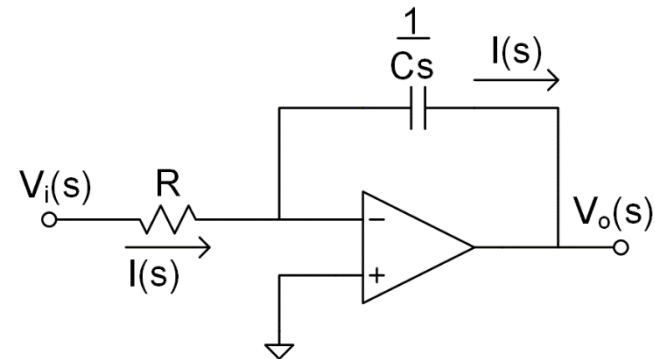- Recall that multiplication by $1/s$ in the Laplace domain corresponds to integration in the time domain





Opamp Integrator – Frequency Response

8

- Transfer function:

$$G(s) = -\frac{1}{RCs}$$

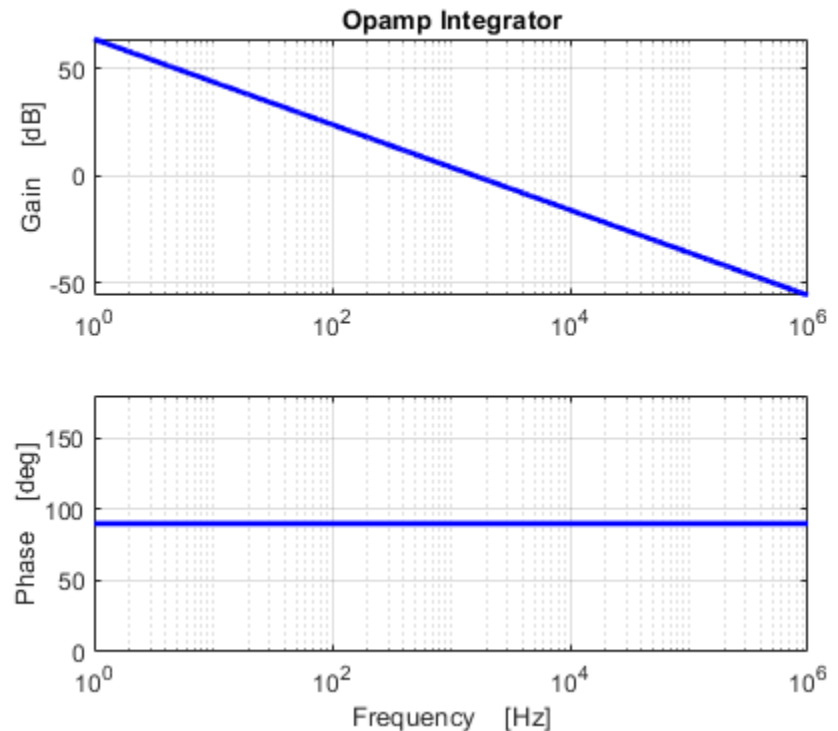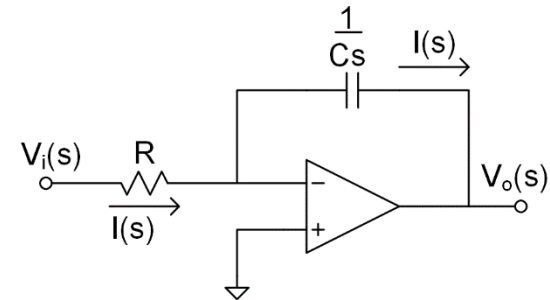- Single pole at $s = 0$
 - Gain: constant slope of -20 dB/dec
 - Infinite DC gain
 - Phase: -90° from integrator pole + 180° from inversion yields constant $+90^\circ$



Ideal Integrator - Problem

9

- Laplace domain step response of the ideal integrator

$$V_o(s) = \frac{1}{s} \cdot G(s) = -\frac{1}{RC} \cdot \frac{1}{s^2}$$

- Inverse transforming to the time domain


$$v_o(t) = -\frac{1}{RC} \cdot t$$

- Output increases linearly with time
- Opamp will quickly saturate in response *any* DC input component
 - ▣ Infinite DC gain
- Not a practical circuit
 - ▣ Inputs will always have some non-zero offset
 - ▣ Real (non-ideal) opamps have non-zero offset voltages and input bias currents

Practical Opamp Integrator

10

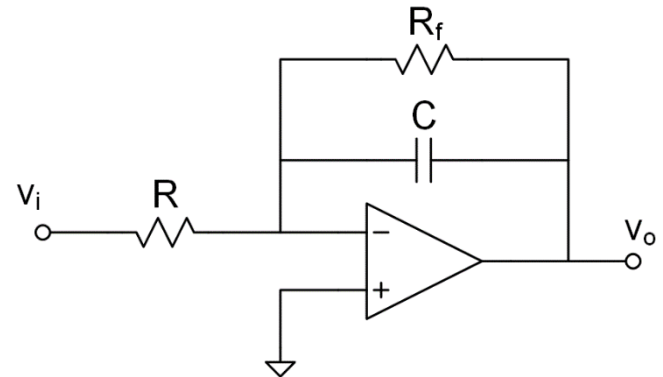- Problem with ideal integrator is infinite DC gain
 - ▣ No DC feedback
 - ▣ Open-loop at DC
- Add a feedback resistor in parallel with the capacitor
 - ▣ Now there is a feedback path for DC signals
 - ▣ DC gain limited to R_f/R
- Behaves as an inverting opamp at low frequencies
- Still behaves as an integrator at high frequencies
- A ***practical*** or ***lossy*** integrator circuit



Opamp Integrator – Frequency Response

11

- Transfer function:



$$G(s) = -\frac{\frac{R_f}{Cs}}{R_f + \frac{1}{Cs}} = -\frac{R_f}{R} \frac{1}{R_f Cs + 1}$$

- Pole (corner frequency) set by the feedback network:

$$\omega_c = \frac{1}{R_f C}$$

- For $\omega \gg \omega_c$, still behaves like an integrator

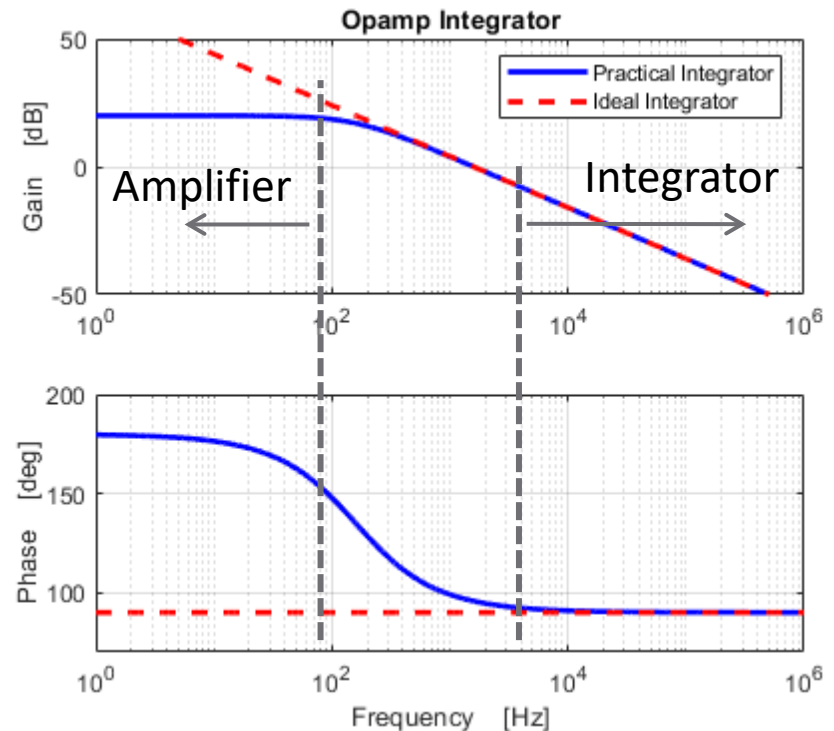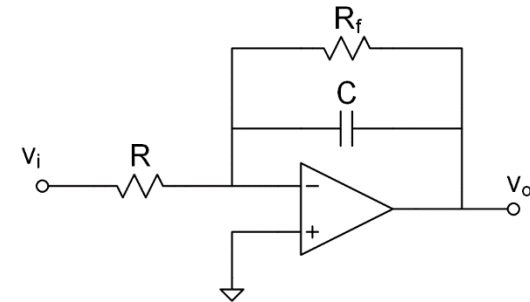- Gain: rolls off at -20 dB/dec
 - Phase: $\sim 90^\circ$



12

Opamp Differentiators

Opamp Differentiator – Time Domain

13


- Analyze the opamp differentiator in the time domain
- Virtual ground at inverting input, so

$$i(t) = C \frac{dv_i}{dt}$$

- Ohm's law gives the output voltage

$$v_o(t) = -Ri(t) = -RC \frac{dv_i}{dt}$$

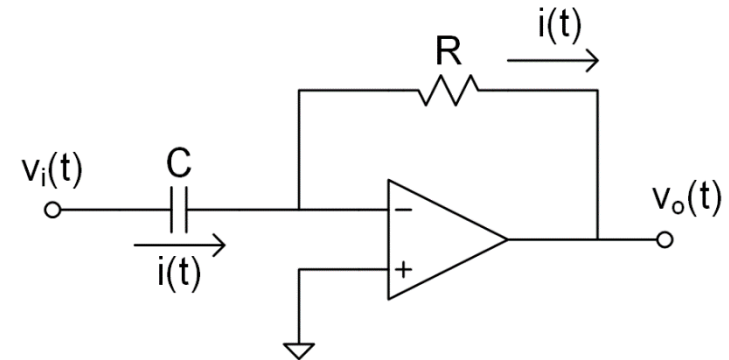- Output is the (scaled and inverted) derivative of the input



Opamp Differentiator – Laplace Domain

14


- Analyze the differentiator in the Laplace domain
- Again, a virtual ground at inverting input, so

$$I(s) = Cs \cdot V_i(s)$$

- Output voltage:

$$V_o(s) = -RI(s) = -RCsV_i(s) = -s \cdot RCV_i(s)$$

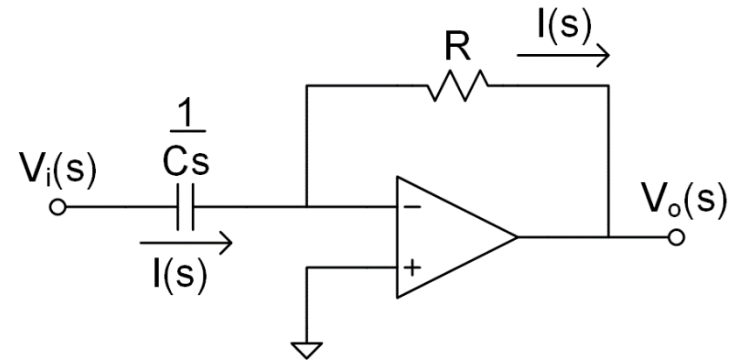- Recall that multiplication by s in the Laplace domain corresponds to differentiation in the time domain





Opamp Differentiator – Frequency Response

15

- Transfer function:

$$G(s) = -RCs$$

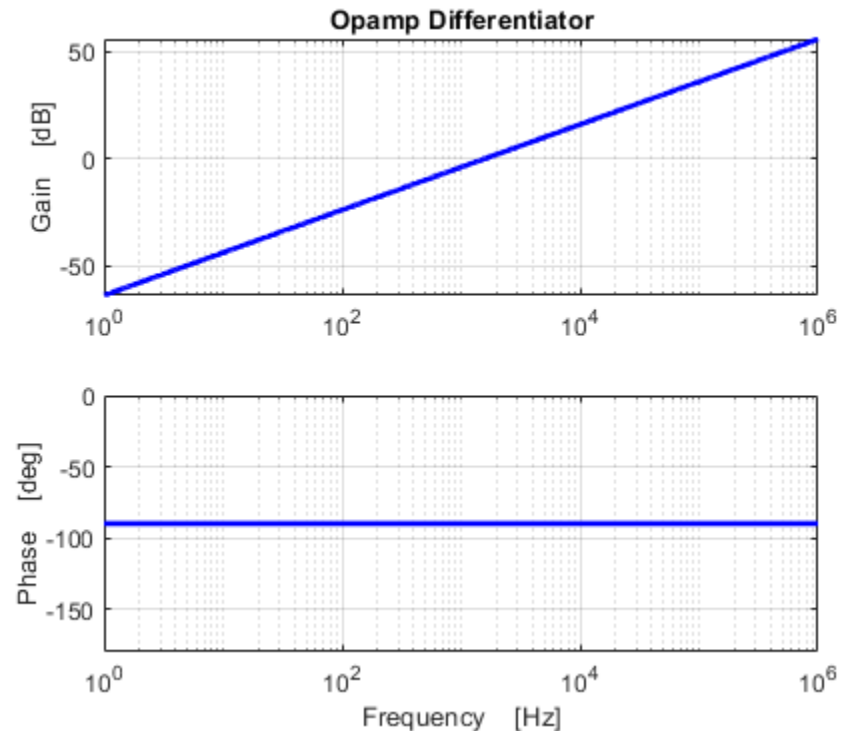
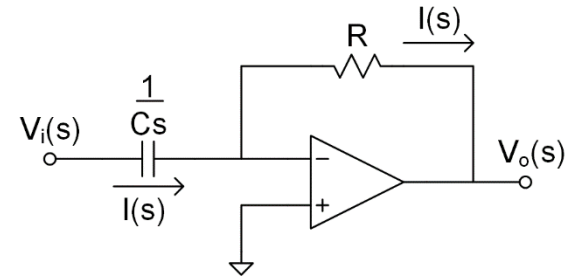
- Single zero at $s = 0$
 - Gain: constant slope of +20 dB/dec
 - Very large high-frequency gain
 - Phase: +90° from zero at the origin + 180° from inversion yields constant +270° = -90°



Ideal Differentiator - Problem

16

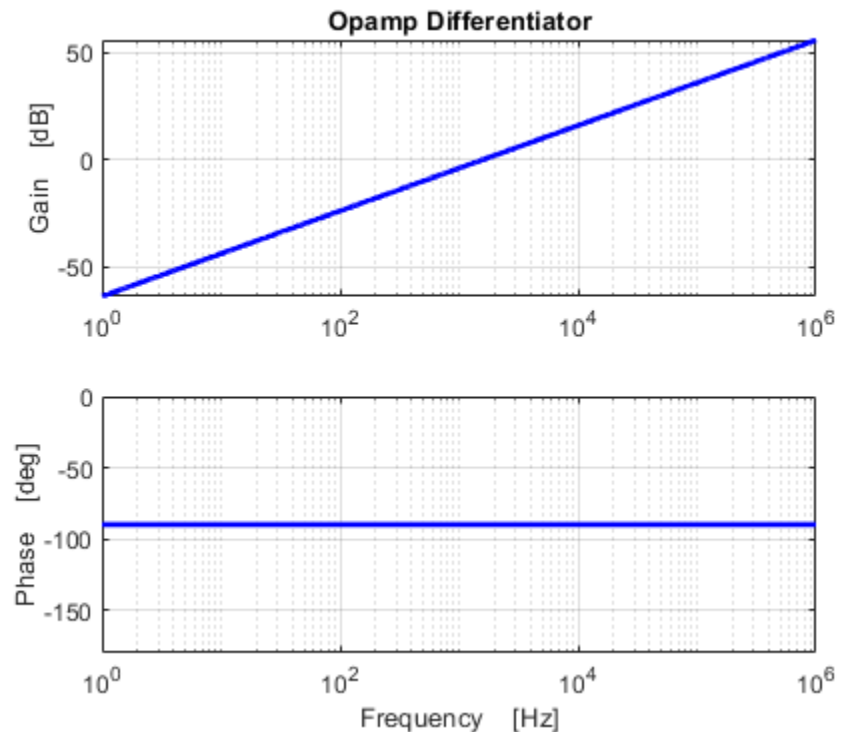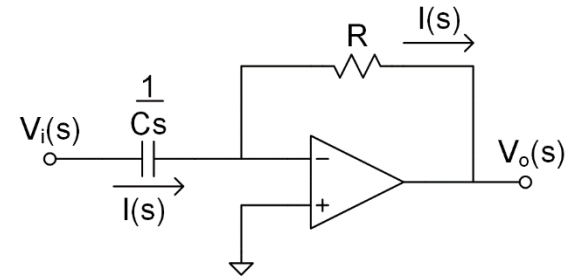
- Gain continues to increase with frequency
- High-frequency gain is very large
 - ▣ Any input signal will include some noise
- Better to limit the gain above some upper frequency



Practical Opamp Differentiator

17

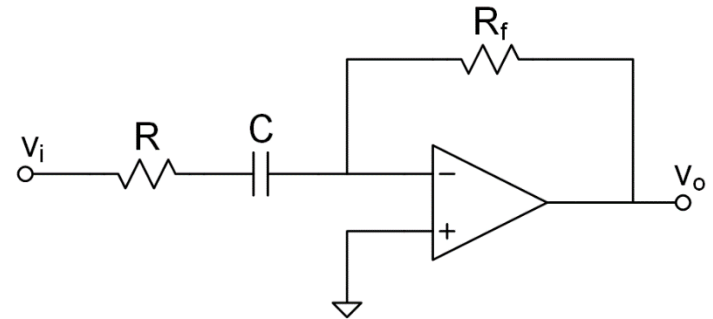- Problem with ideal differentiator:
 - ▣ Low input impedance at high frequency
 - ▣ Excessive high-frequency input current
- Add a resistor in series with the input capacitor
 - ▣ High-frequency gain limited to R_f/R
- Still behaves as a differentiator at low frequencies
- Behaves as an inverting opamp at high frequencies
- A ***practical*** or ***lossy*** differentiator circuit



Practical Opamp Differentiator

18



- Transfer function:

$$G(s) = -\frac{R_f}{R + \frac{1}{Cs}} = -\frac{R_f Cs}{RCs + 1}$$

- Pole (corner frequency) set by the input network:

$$\omega_c = \frac{1}{RC}$$

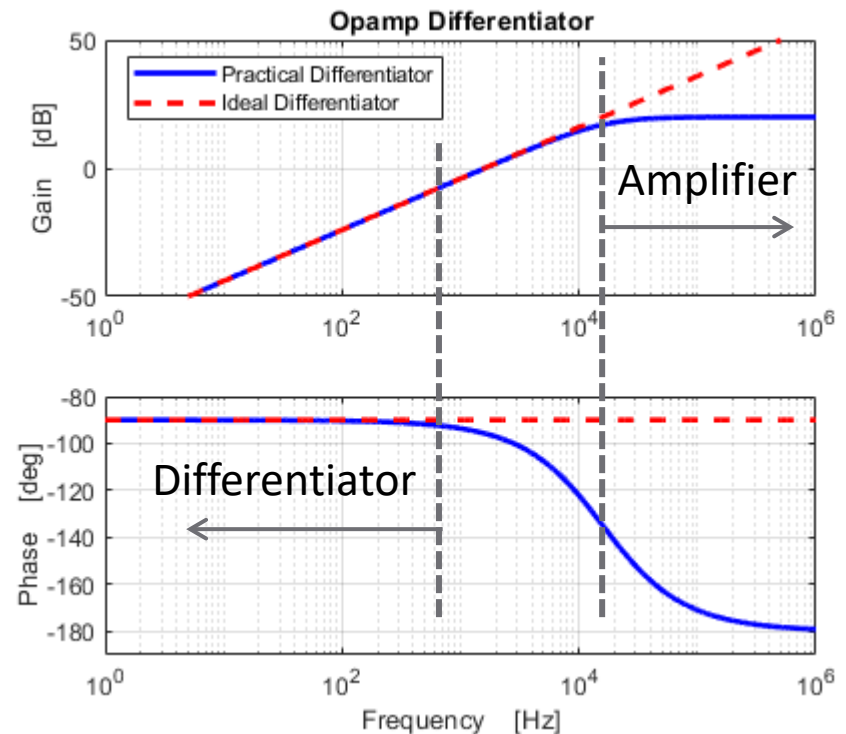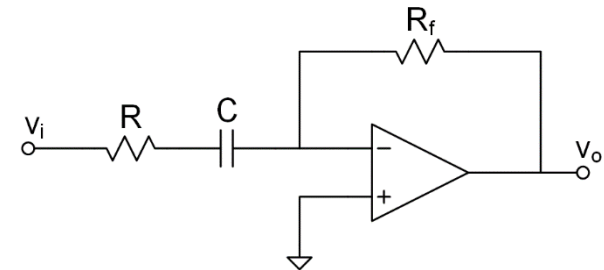- For $\omega \ll \omega_c$, still behaves like a differentiator
 - ▣ Gain: increases at +20 dB/dec
 - ▣ Phase: $\sim -90^\circ$





19

First-Order Opamp Active Filters

First-Order Active Filters

20

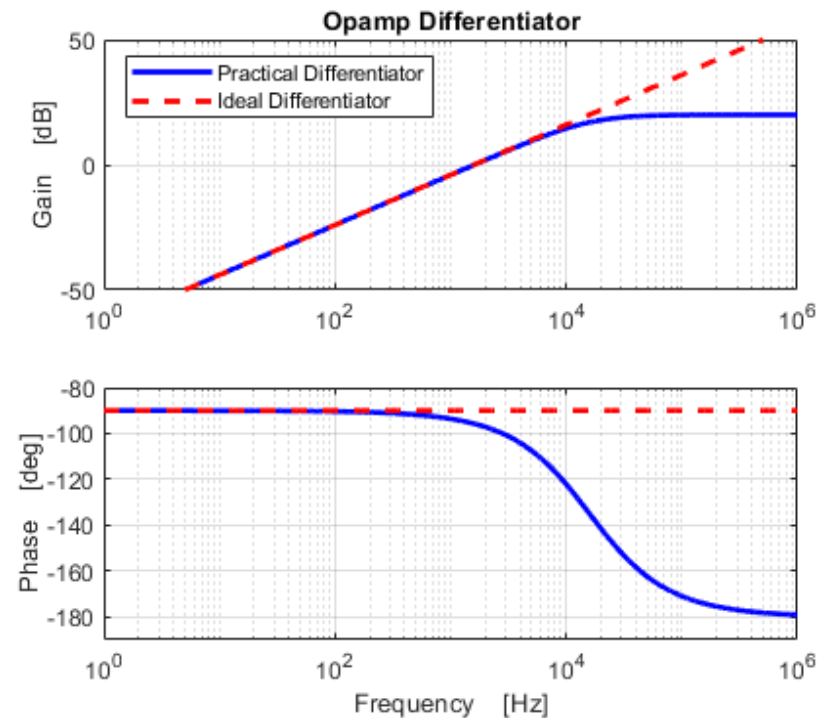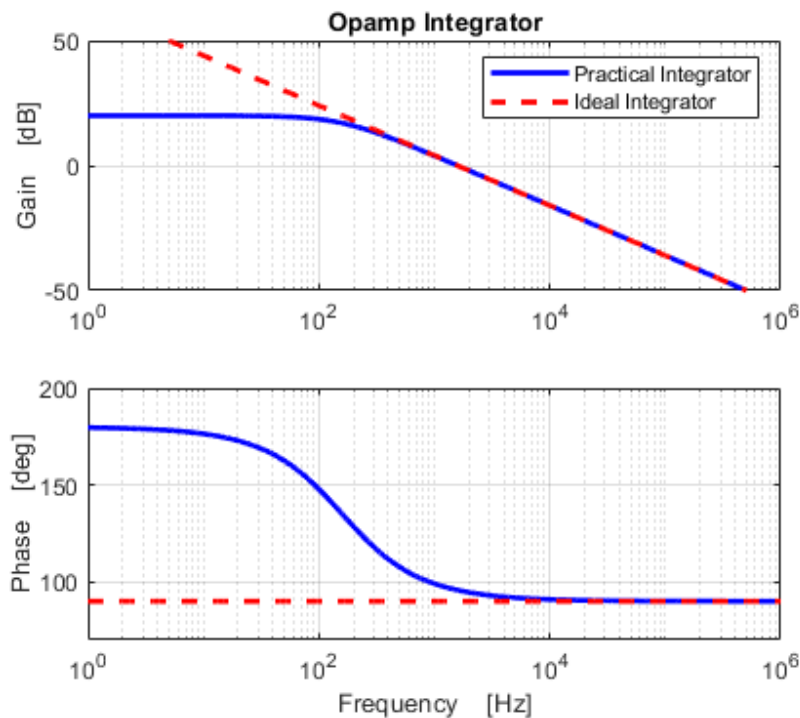- Practical integrator and differentiator circuits
 - ▣ Additional resistors fix problems with ideal circuits
 - ▣ First-order low pass and high pass filters



First-Order Low Pass Filter

21

- Transfer function

$$G(s) = -\frac{R_f}{R} \frac{1}{(R_f C s + 1)}$$




$$G(s) = -\frac{R_f}{R} \frac{\frac{1}{R_f C}}{\left(s + \frac{1}{R_f C}\right)}$$

- Corner frequency

$$f_c = \frac{1}{2\pi R_f C}$$

- Pass-band gain

$$A_v = -\frac{R_f}{R}$$

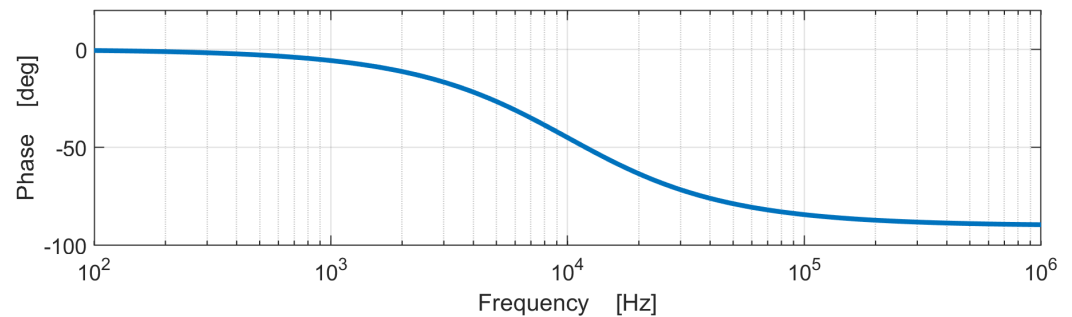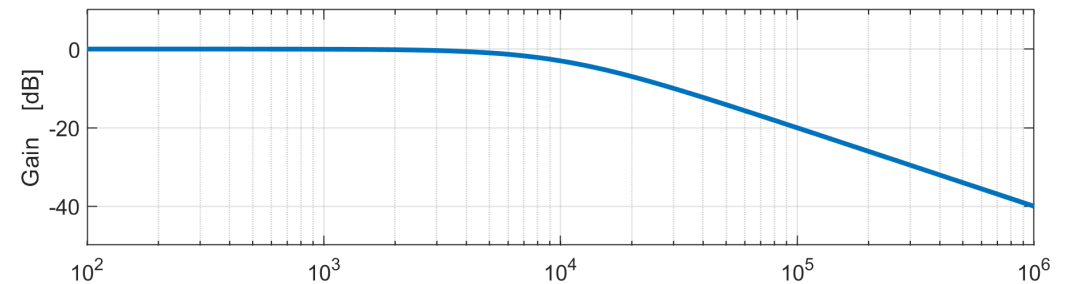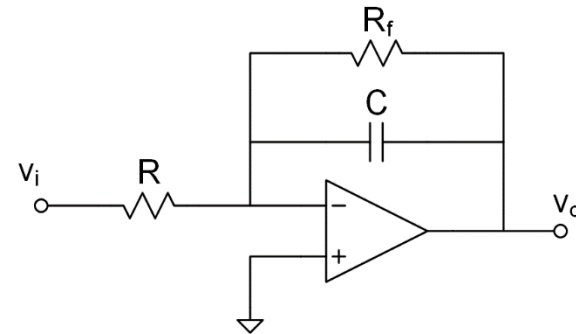

First-Order High Pass Filter

22

- Transfer function

$$G(s) = -\frac{R_f C s}{R C s + 1}$$



$$G(s) = -\frac{R_f}{R} \frac{s}{\left(s + \frac{1}{RC}\right)}$$

- Corner frequency

$$f_c = \frac{1}{2\pi RC}$$

- Pass-band gain

$$A_v = -\frac{R_f}{R}$$

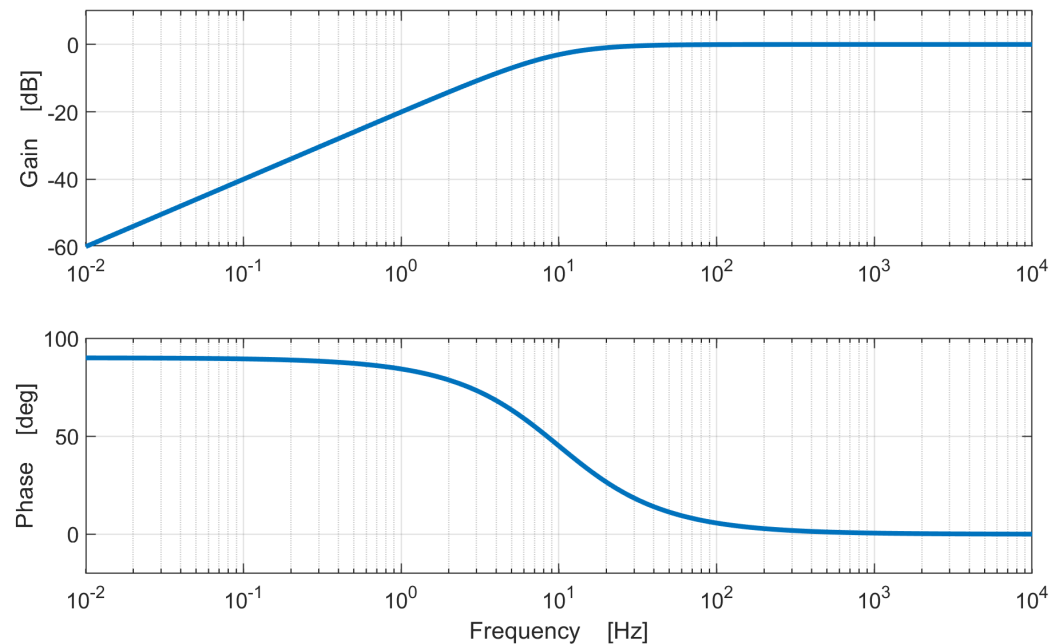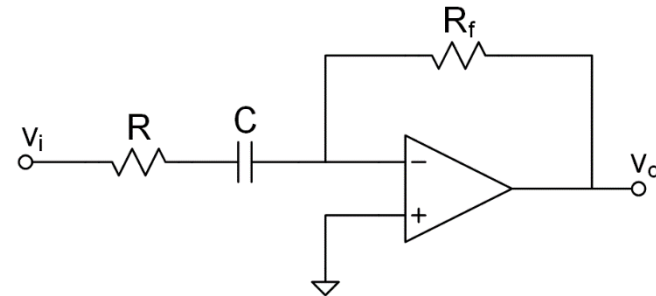

23

Higher Order Active Filters

Higher-Order Active Filters

24

- Higher order active filters can be constructed by:
 - ▣ Cascading first-order active filters
 - ▣ Using second-order active filter stages
 - ▣ Cascading second- and first-order stages
- Create higher order band pass/stop filters similarly:
 - ▣ Cascade first-order high/low pass filters
 - ▣ Use and/or cascade second-order band pass/stop stages
- Many different second-order active filter topologies
 - ▣ We'll look at the ***Sallen-Key circuit***

Sallen-Key Filter – Generalized Form

25

- Sallen-Key filter topology
 - ▣ Low pass and high pass filters
 - ▣ Band-pass, and notch filters with slight modifications
- We'll look first at the filter in its most generalized form, then consider the specific low pass and high pass filter forms
- Type of filter depends on the location of components – resistors and capacitors

Sallen-Key Filter – Generalized Form

26

□ Transfer function

▣ Nodal analysis


- KCL at V^+ and V_f
- Virtual short at opamp inputs

▣ After *a lot* of ugly algebra:

$$G(s) = \frac{1}{\beta \frac{Z_1 Z_2}{Z_3 Z_4} + \beta \frac{Z_2}{Z_4} + \beta \frac{Z_1}{Z_4} + (\beta - 1) \frac{Z_1}{Z_3} + \beta}$$

where β is the feedback path gain
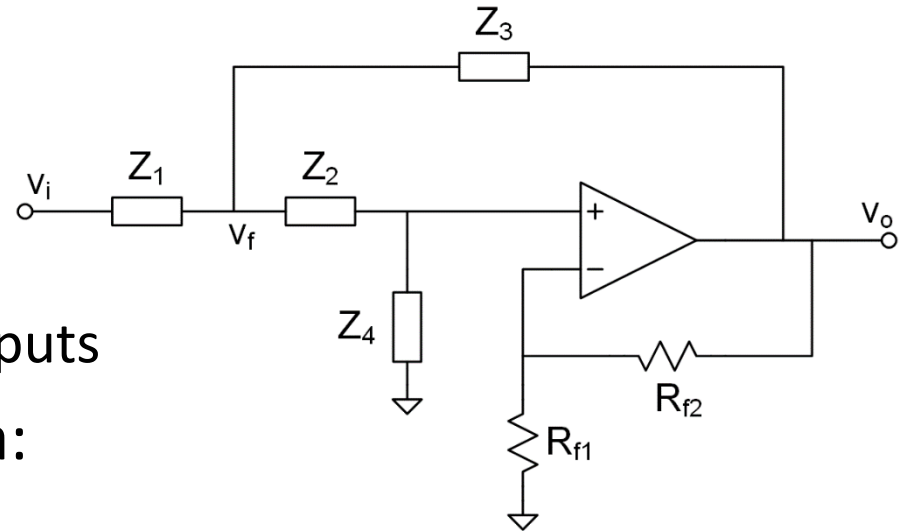
$$\beta = \frac{R_{f1}}{R_{f1} + R_{f2}}$$



27


Sallen-Key Low Pass Filter

Sallen-Key Second-Order Low Pass Filter

28

- Z_1 and Z_2 are resistors
- Z_3 and Z_4 are capacitors

- Transfer function

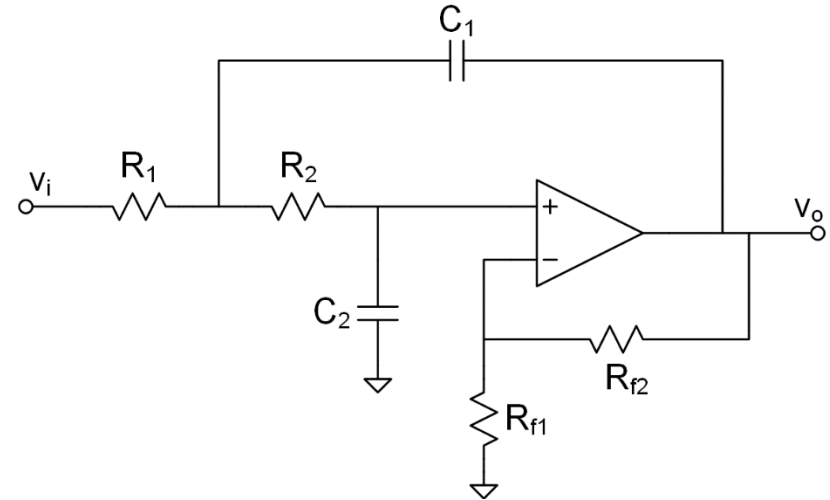

$$G(s) = \frac{1}{\beta R_1 R_2 C_1 C_2 s^2 + \beta R_2 C_2 s + \beta R_1 C_2 s + (\beta - 1) R_1 C_1 s + \beta}$$

$$G(s) = \frac{\frac{1}{\beta R_1 R_2 C_1 C_2}}{s^2 + \left(\frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{(\beta - 1)}{\beta R_2 C_2} \right) s + \frac{1}{R_1 R_2 C_1 C_2}}$$

Sallen-Key Low Pass Filter

29

- Generalized second-order low pass transfer function:

$$G(s) = K \cdot \frac{\omega_0^2}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$$

- Equating coefficients with the Sallen-Key transfer function gives
 - **Resonant frequency:**

$$\omega_0 = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$

- **Quality factor:**

$$Q = \frac{\sqrt{R_1 R_2 C_1 C_2}}{R_2 C_2 + R_1 C_1 + \left(\frac{\beta - 1}{\beta}\right) R_1 C_1}$$

- **DC gain:**

$$K = \frac{1}{\beta} = \frac{R_{f1} + R_{f2}}{R_{f1}}$$

Sallen-Key Low Pass Filter


30

- ω_0 , Q , and gain all set by appropriate component selection, but
 - ▣ There are more degrees of freedom than we need
 - ▣ Transfer function is a bit more complicated than we'd like
- Simplify by setting component values equal
- Transfer function becomes

$$G(s) = \frac{1}{\beta(RC)^2} \frac{1}{s^2 + \left(3 - \frac{1}{\beta}\right) \frac{s}{RC} + \frac{1}{(RC)^2}}$$

- ▣ Where now
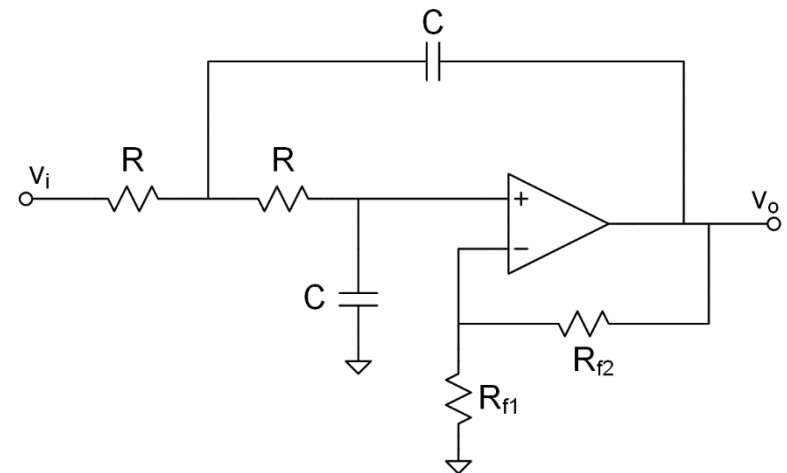
$$\omega_0 = \frac{1}{RC} \quad \text{and} \quad Q = \frac{1}{3 - \frac{1}{\beta}}$$



Sallen-Key Low Pass Filter

31

$$G(s) = \frac{1}{\beta(RC)^2} \frac{1}{s^2 + \left(\frac{3 - \frac{1}{\beta}}{RC}\right)s + \frac{1}{(RC)^2}}$$

- We can also write the transfer function in terms of DC gain, K

$$G(s) = \frac{\frac{K}{(RC)^2}}{s^2 + \left(\frac{3 - K}{RC}\right)s + \frac{1}{(RC)^2}}$$

- ω_0 and Q in terms of K :


$$\omega_0 = \frac{1}{RC} \quad \text{and} \quad Q = \frac{1}{3-K}$$

- ***The filter's DC gain is dependent on the filter's Q and vice versa***
 - For independent control of DC gain, cascade an additional gain stage

Sallen-Key Low Pass Filter

32

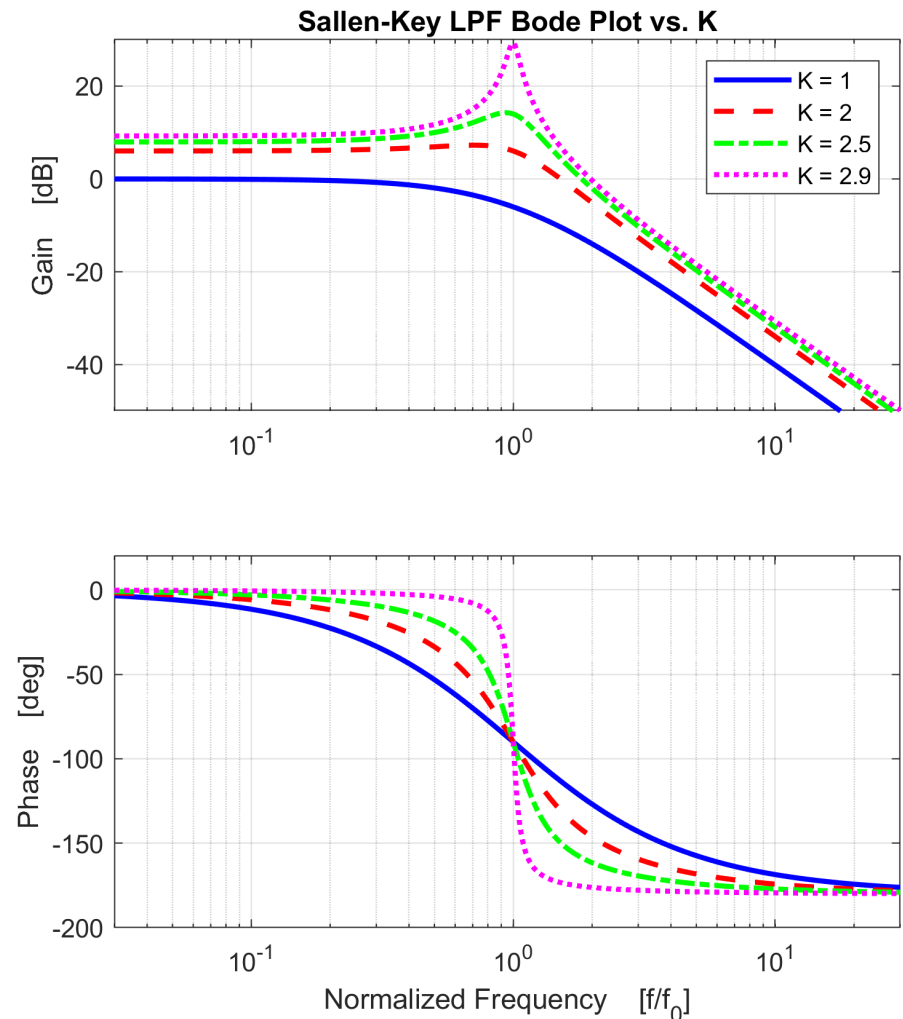- Note dependence of Q and K
 - ▣ Both set by feedback path gain
- Q and gain are independent of ω_0
 - ▣ ω_0 set by capacitors and resistors at the input
- Second-order
 - ▣ Gain roll-off: -40 dB/dec



33

Sallen-Key High Pass Filter

Sallen-Key High Pass Filter


34

- Here, we will jump straight to the simplified circuit with equal-valued components
- Location of resistors and capacitors swapped relative to low pass filter
- High pass transfer function

$$G(s) = \frac{\frac{1}{\beta} s^2}{s^2 + \left(\frac{3 - \frac{1}{\beta}}{RC} \right) s + \frac{1}{(RC)^2}}$$

□ Again,
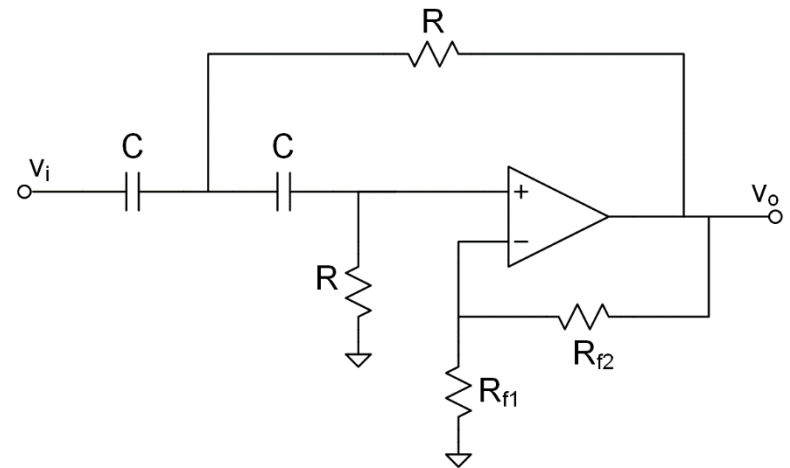
$$\omega_0 = \frac{1}{RC} \quad \text{and} \quad Q = \frac{1}{3 - \frac{1}{\beta}}$$



Sallen-Key High Pass Filter

35

- As with the low pass filter, we can write the transfer function in terms of gain, K
 - ▣ K still represents passband gain, but now it is the high-frequency gain, not the DC gain

$$G(s) = \frac{Ks^2}{s^2 + \left(\frac{3-K}{RC}\right)s + \frac{1}{(RC)^2}}$$

- ω_0 and Q are the same as for the low pass filter:


$$\omega_0 = \frac{1}{RC} \quad \text{and} \quad Q = \frac{1}{3-K}$$

- Same dependence between passband gain, resonant frequency, and Q

Sallen-Key High Pass Filter

36

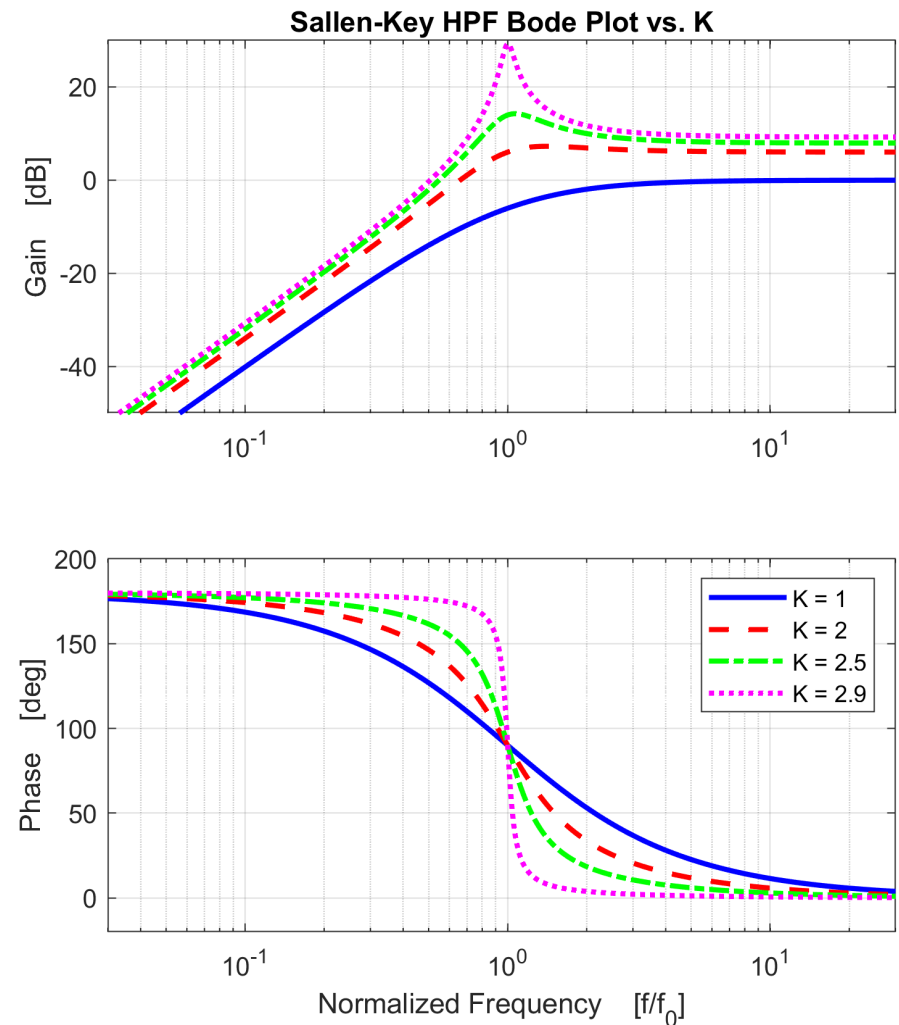- Note dependence of Q and K
 - ▣ Both set by feedback path gain
- Q and gain are independent of ω_0
 - ▣ ω_0 set by capacitors and resistors at the input
- Second-order
 - ▣ Gain roll-off: -40 dB/dec



Sallen-Key Filter – Stability

37

- Sallen-Key filter has **two feedback paths**:

- **Negative** feedback

- Generally **stabilizing**

- **Positive** feedback

- Generally **destabilizing**


- Relative amount of negative and positive feedback determines stability

- **Net negative feedback: circuit is stable**

- Behaves as a linear filter/amplifier

- **Net positive feedback: circuit is unstable**

- Will oscillate or saturate

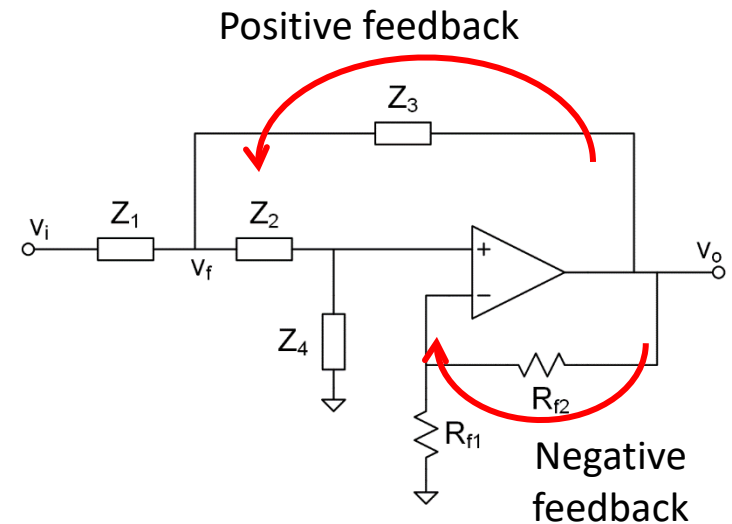


Sallen-Key Filter – Stability

38

- Overall net feedback must remain negative
 - ▣ But, we can vary just how negative by varying β
- Varying β allows us to vary Q :

$$Q = \frac{1}{3 - \frac{1}{\beta}} = \frac{1}{3 - K}$$

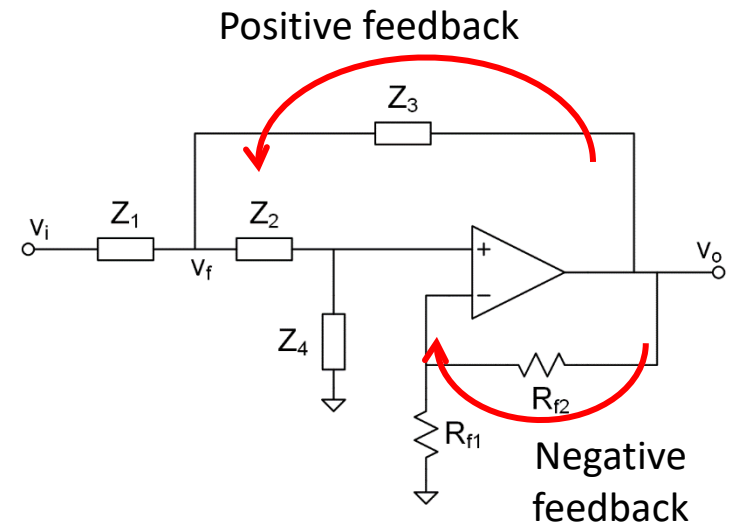- As β increases:
 - ▣ Negative feedback increases
 - ▣ Overall feedback becomes more negative
 - ▣ Quality factor, Q , decreases
 - ▣ Damping ratio, ζ , increases
 - ▣ Pass band gain, K , decreases




Sallen-Key Filter – Stability

39

- As β decreases:
 - ▣ Negative feedback decreases
 - ▣ Overall feedback becomes less negative
 - ▣ Quality factor, Q , increases
 - ▣ Damping ratio, ζ , decreases
 - ▣ Pass band gain, K , increases

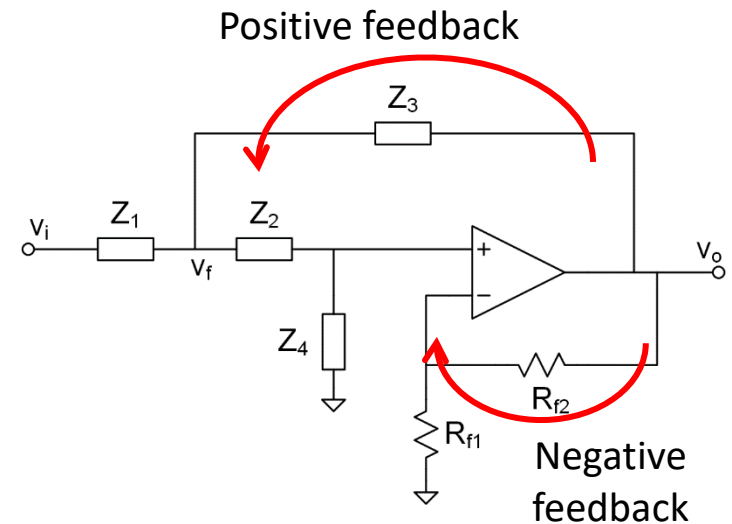- There is an upper limit on K :
 - ▣ For $K = 3$, $Q = \infty$ and $\zeta = 0$
 - ▣ An un-damped circuit
 - ▣ Negative and positive feedback cancel
 - ▣ The border between stability and instability
 - ▣ **For stability:** $K \leq 3$



40

Filter Families

Filter Families

41


- Higher-order filters of all types can be designed with transfer functions that fit into one of several ***families of filters***
 - ▣ Butterworth
 - ▣ Chebyshev
 - ▣ Elliptic
 - ▣ Bessel

- Each filter family defined by the nature of its ***characteristic polynomial***

- Equivalently, each defined by ***pole locations***, e.g.,
 - ▣ Butterworth poles lie evenly spaced on a circle in the left half of the complex plane

Filter Families – Frequency Response


42

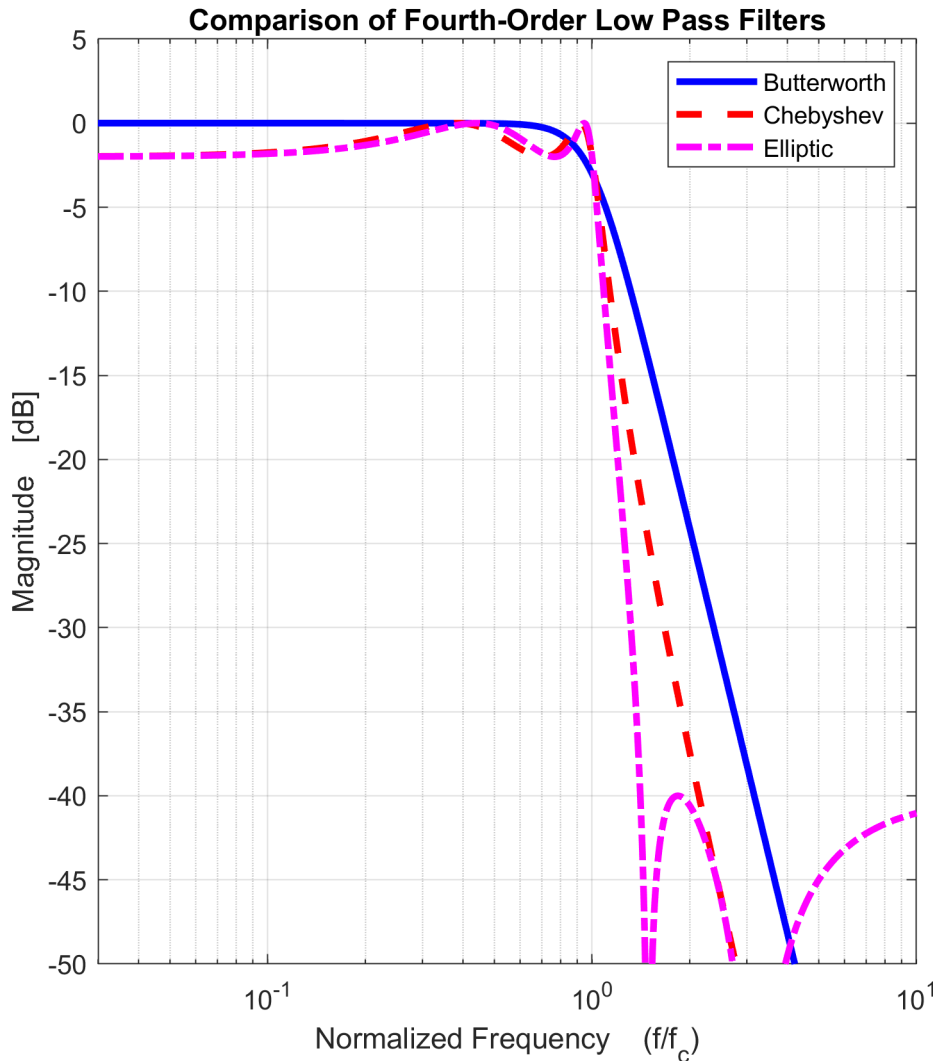

- Butterworth
 - ▣ Maximally-flat pass band
 - ▣ Slow roll off
- Chebyshev
 - ▣ Steeper roll off
 - ▣ Pass band ripple
- Elliptic
 - ▣ Very steep roll off
 - ▣ Pass band ripple
 - ▣ Stop band ripple
- As always, all about trade offs

Filter Families – System Poles

43

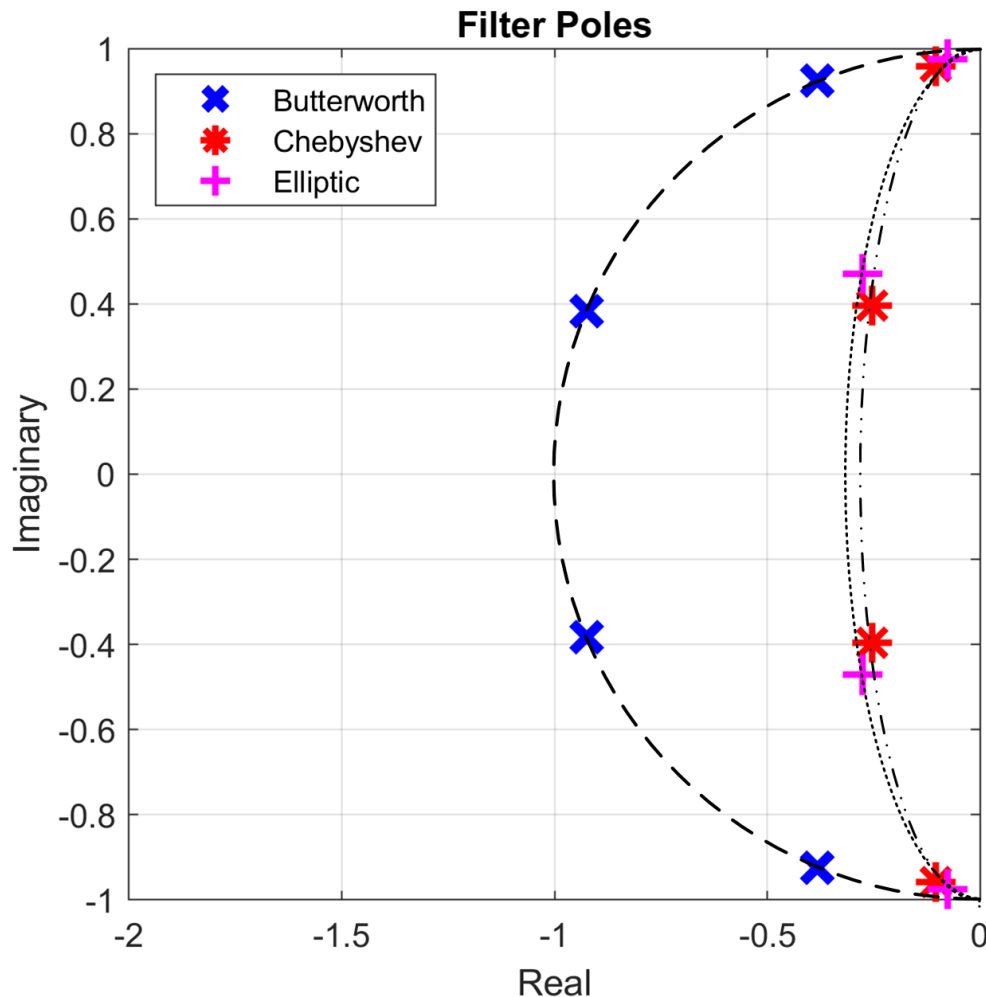

□ **Butterworth**

- Poles lie on a semi-circle in the LHP
- Equally spaced
- Equal magnitude, ω_0

□ **Chebyshev/elliptic**

- Poles lie on semi-ellipses in the LHP
- Varying magnitudes


Butterworth Poles

44

- Butterworth poles:
 - ▣ Magnitude: ω_0
 - ▣ Order: N
 - ▣ Separation angles: $180^\circ/N$
 - ▣ Poles for $k = 1 \dots N$

$$s_k = \omega_0 \left[-\sin \left[\frac{\pi(2k-1)}{2N} \right] + j \cos \left[\frac{\pi(2k-1)}{2N} \right] \right]$$

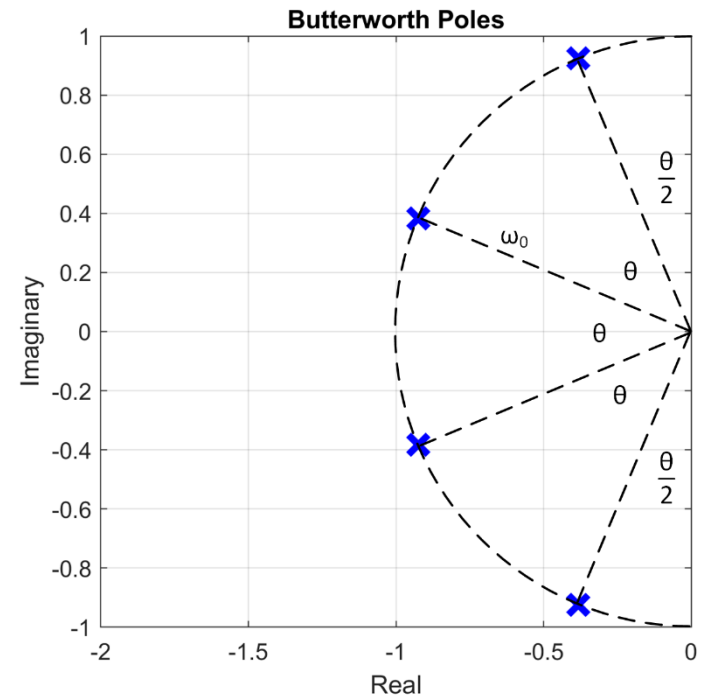- Each complex conjugate pair are the poles of a single second-order Sallen-Key stage
 - ▣ All with equal ω_0
 - ▣ Each with different ζ



45

Filter Synthesis

Filter Synthesis Procedure

46

1. Determine filter order, N , and cutoff frequency, ω_c
2. Determine ω_0 and Q or ζ for each stage by utilizing either
 - a) Design tables, or
 - b) MATLAB
3. For each stage, select R and C to yield the required ω_0

$$\omega_0 = \frac{1}{RC}$$

4. For each stage, select R_{f1} and R_{f2} to set gain, K , to provide the required Q

$$K = 3 - \frac{1}{Q}$$

Filter Design Tables

47

- ***Design tables*** exist for different filters of different orders from different filter families
 - Pole locations, ω_0 , and Q given for each second- and first-order stage for a given filter order, N
 - Only second-order stages for even N
 - Second-order plus one first-order stage for odd N
 - Frequencies are normalized
 - Multiply ω_0 by the cutoff frequency, ω_c
 - Multiply σ and ω_d by ω_c

Butterworth Design Table

48

Order, N	Section	Poles		ω_0	Q	K
		σ	ω_d			
2	1	0.7071	0.7071	1.00	0.7071	1.5858
3	1	0.5000	0.8660	1.00	1.0000	1.0000
	2	1.0000	-	1.00	-	-
4	1	0.9239	0.3827	1.00	0.5412	1.1522
	2	0.3827	0.9239	1.00	1.3065	2.2346
5	1	0.8090	0.5878	1.00	0.6180	1.382
	2	0.3090	0.9511	1.00	1.6182	2.382
	3	1.0000	-	1.00	-	-
6	1	0.9659	0.2588	1.00	0.5176	1.0681
	2	0.7071	0.7071	1.00	0.7071	1.5858
	3	0.2588	0.9659	1.00	1.9319	2.4824

Chebyshev Design Table – 0.5 dB ripple

49

Order, N	Section	Poles		ω_0	Q	K
		σ	ω_d			
2	1	0.71281	1.004	1.2313	0.8638	1.8422
3	1	0.3123	1.0219	1.0689	1.7062	2.4139
	2	0.6265	-	0.6265	-	-
4	1	0.4233	0.4210	0.5970	0.7051	1.5818
	2	0.1754	1.0163	1.0313	2.9406	2.6599
5	1	0.2931	0.6252	0.6905	1.1778	2.1510
	2	0.1120	1.0116	1.0177	4.5450	2.7800
	3	0.3623	-	0.3623	-	
6	1	0.2898	0.2702	0.3962	0.6836	1.5372
	2	0.2121	0.7382	0.7681	1.8104	2.4476
	3	0.0777	1.0085	1.0114	6.5128	2.8465

Chebyshev Design Table – 1.0 dB ripple

50

Order, N	Section	Poles		ω_0	Q	K
		σ	ω_d			
2	1	0.5489	0.8951	1.0500	0.9565	1.9545
3	1	0.2471	0.9660	0.9771	2.0177	2.5044
	2	0.4942	-	0.4942	-	-
4	1	0.3369	0.4073	0.5286	0.7846	1.7254
	2	0.1395	0.9834	0.9932	3.5590	2.7190
5	1	0.2342	0.6119	0.6552	1.3988	2.2851
	2	0.0895	0.9901	0.9941	5.5564	2.8200
	3	0.2895	-	0.2895	-	-
6	1	0.2321	0.2662	0.3531	0.7609	1.6857
	2	0.1699	0.7272	0.7468	2.1980	2.5450
	3	0.0622	0.9934	0.9954	8.0037	2.8751

Chebyshev Design Table – 3.0 dB ripple

51

Order, N	Section	Poles		ω_0	Q	K
		σ	ω_d			
2	1	0.3225	0.7772	0.8414	1.3047	202335
3	1	0.1493	0.9038	0.9161	3.0677	2.6740
	2	0.2986	-	0.2986	-	-
4	1	0.2056	0.3921	0.4427	1.0765	2.0711
	2	0.0852	0.9465	0.9503	5.5789	2.8208
5	1	0.1436	0.5970	0.6140	2.1375	2.5322
	2	0.0549	0.9659	0.9675	8.8178	2.8866
	3	0.1775	-	0.1775	-	-
6	1	0.1427	0.2616	0.2980	1.0443	2.0425
	2	0.1044	0.7148	0.7224	3.4581	2.7108
	3	0.0382	0.9764	0.9772	12.7800	2.9218

Filter synthesis in MATLAB

52

- MATLAB has built-in filter design functions, e.g.,
 - ▣ butter.m
 - ▣ cheby1.m
 - ▣ ellip.m

- Design procedure:
 1. Use functions to get transfer function coefficients for given filter specifications
 2. Create MATLAB transfer function object
 3. Determine filter poles, ω_0 , and Q from transfer function – *place low- Q stages first*
 4. Determine component values from ω_0 and Q

Butterworth Filter – `butter (...)`

53

```
[b, a] = butter(N, wn, ftype, 's')
```

□ Inputs:

- N: filter order
- wn: cutoff frequency [rad/sec]
- ftype: filter type: 'low', 'bandpass', 'high', 'stop' – optional – default: 'low'
- 's': specifies *analog* filter

□ Outputs:

- b: coefficients of the transfer function's numerator polynomial
- a: coefficients of the transfer function's denominator polynomial

Chebyshev Filter – `cheby1 (...)`

54

```
[b, a] = cheby1 (N, R, wn, ftype, 's')
```

□ Inputs:

- N: filter order
- R: pass band ripple [dB]
- wn: cutoff frequency [rad/sec]
- ftype: filter type: 'low', 'bandpass', 'high', 'stop' – optional – default: 'low'
- 's': specifies *analog* filter

□ Outputs:

- b: coefficients of the transfer function's numerator polynomial
- a: coefficients of the transfer function's denominator polynomial

Elliptic Filter – `ellip (...)`

55

```
[b, a] = cheby1 (N, Rp, Rs, wn, ftype, 's')
```

□ Inputs:

- N: filter order
- Rp: pass band ripple [dB]
- Rs: stop band attenuation [dB]
- wn: cutoff frequency [rad/sec]
- ftype: filter type: 'low', 'bandpass', 'high', 'stop' – optional – default: 'low'
- 's': specifies *analog* filter

□ Outputs:

- b: coefficients of the transfer function's numerator polynomial
- a: coefficients of the transfer function's denominator polynomial

Transfer Function Model – tf (...)

56

$$\text{sys} = \text{tf}(\mathbf{b}, \mathbf{a})$$

- ▣ \mathbf{b} : vector of numerator polynomial coefficients
 - ▣ \mathbf{a} : vector of denominator polynomial coefficients
 - ▣ sys : transfer function model object
- ▣ Transfer function is assumed to be of the form

$$G(s) = \frac{b_1 s^r + b_2 s^{r-1} + \dots + b_r s + b_{r+1}}{a_1 s^n + a_2 s^{n-1} + \dots + a_n s + a_{n+1}}$$

- ▣ Inputs to $\text{tf}(\dots)$ are
- ▣ $\text{Num} = [b_1, b_2, \dots, b_{r+1}]$;
 - ▣ $\text{Den} = [a_1, a_2, \dots, a_{n+1}]$;

Getting ω_0 and Q – damp (...)

57

```
[wn, zeta, p] = damp(sys)
```

- ▣ `sys`: transfer function system model object
 - ▣ `wn`: vector of natural frequencies (magnitudes) of poles
 - ▣ `zeta`: vector of damping ratios, ζ , of poles
 - ▣ `p`: vector of poles
-
- Use `wn` values for ω_0 of each filter stage
 - Calculate Q of each stage from ζ values

$$Q = \frac{1}{2\zeta}$$

58

Filter Design Example

Sallen-Key Filter – Example


59

- Design a Butterworth (maximally-flat) low pass active filter to satisfy the following specifications:
 - ▣ **Corner frequency:** $f_c = 1\text{MHz}$
 - ▣ **Frequency response roll off** beyond f_c : 80dB/dec
 - ▣ **Pass band (DC) gain:** 12dB (4)
- Roll off spec of 80 dB/dec tells us we need a fourth-order filter – cascade two Sallen-Key stages
- Add a constant gain stage if necessary to meet gain specification

Sallen-Key Filter – Example

60

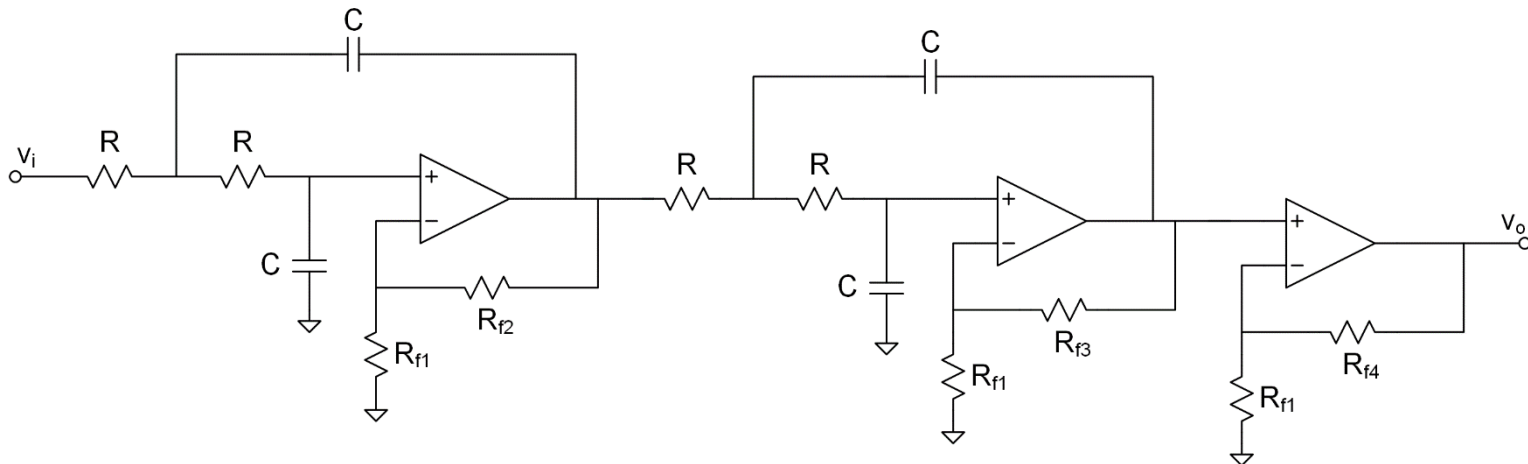
- Fourth-order filter
 - ▣ Cascade two second-order Sallen-Key stages
- Additional gain stage necessary to meet gain specification
 - ▣ Non-inverting opamp amplifier



- Note that the circuit in this example has been simplified by setting R_{f1} equal in each stage
 - ▣ Not necessarily the right choice

Sallen-Key Filter – Example

61

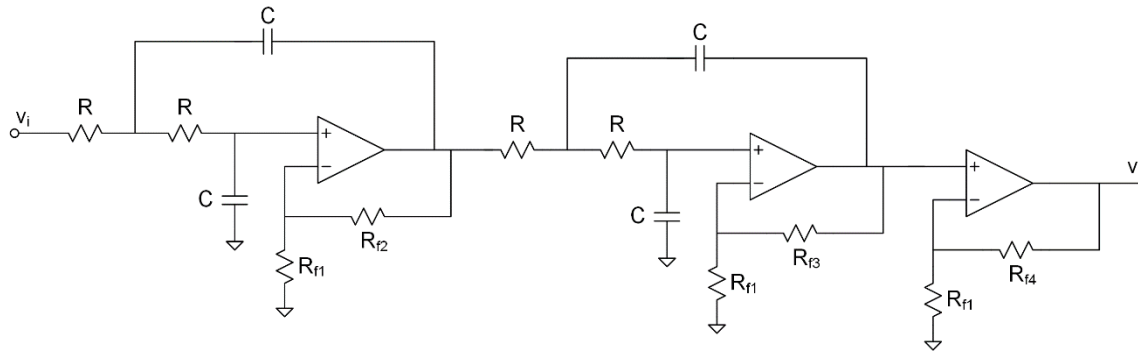

- Butterworth filter, so, for both stages,

$$\omega_0 = \omega_c = 2\pi \cdot f_c = 2\pi \cdot 1 \text{ MHz}$$

- Determine R and C for desired ω_c
 - ▣ Arbitrarily choose $C = 1 \text{ nF}$


$$R = \frac{1}{2\pi f_c C} = \frac{1}{2\pi \cdot 1 \text{ MHz} \cdot 1 \text{ nF}} = 159 \Omega$$

- ▣ If using $\pm 1\%$ resistors, 158Ω is a standard value

$R = 158 \Omega \quad \text{and} \quad C = 1 \text{ nF}$

Sallen-Key Filter – Example

62

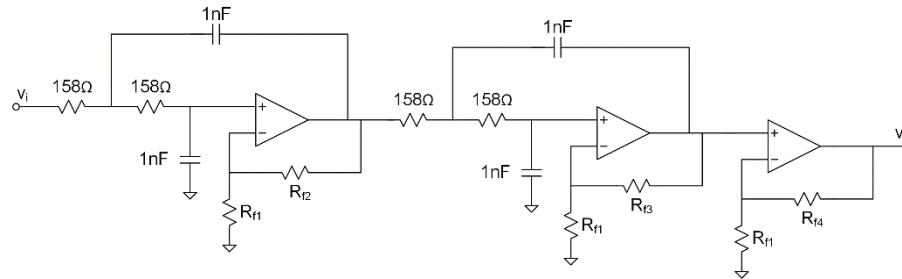

- To determine gain of each stage, consult the Butterworth design table

Order, N	Section	Poles		ω_0	Q
		σ	ω_d		
4	1	0.9239	0.3827	1.00	0.5412
	2	0.3827	0.9239	1.00	1.3065

- Calculate K for each stage from its Q

$$K_1 = 3 - \frac{1}{Q_1} = 3 - \frac{1}{0.5412} = 1.152$$

$$K_2 = 3 - \frac{1}{Q_2} = 3 - \frac{1}{1.3065} = 2.235$$

Sallen-Key Filter – Example

63

- Alternatively, use MATLAB to determine ω_0 and K values for each stage


```
5 %% filter specs
6 N = 4;
7 fc = 1e6;
8 wc = fc*(2*pi);
9
10 % design a butterworth filter
11 [num,den] = butter(N,wc,'s');
12 Gb = tf(num,den);
13
14 % get poles and corresponding magnitudes and damping
15 [w0, zeta, p] = damp(Gb);
16
17 Q = 1./(2*zeta);
18 K = 3 - 1./Q;
19
20 filt_params = table(Q, w0, K);
21
22 display(filt_params)
```

```
filt_params =
4x3 table
      Q      w0      K
-----
0.5412  6.2832e+06  1.1522
0.5412  6.2832e+06  1.1522
1.3066  6.2832e+06  2.2346
1.3066  6.2832e+06  2.2346
>>
```

- Note that we would put the low-Q stage first

Sallen-Key Filter – Example

64

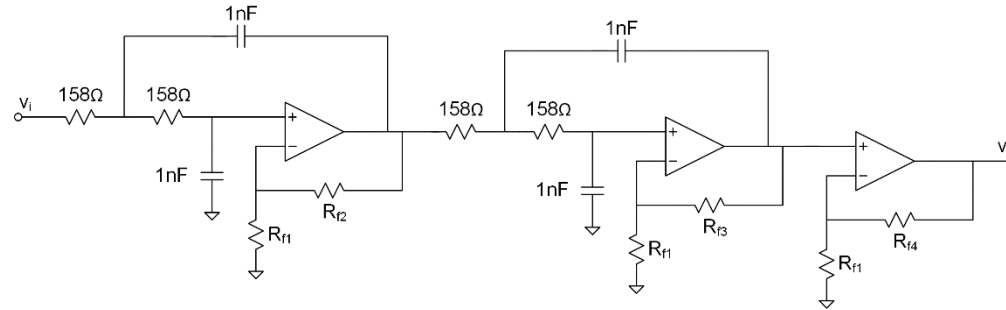

- Arbitrarily choose $R_{f1} = 5.11 \text{ k}\Omega$
- Calculate R_{f2} and R_{f3} to give the required K_1 and K_2

$$K_1 = \frac{R_{f1} + R_{f2}}{R_{f1}} \rightarrow R_{f2} = R_{f1}(K_1 - 1) = 5.11 \text{ k}\Omega \cdot 0.152 = 778 \Omega$$


$$K_2 = \frac{R_{f1} + R_{f3}}{R_{f1}} \rightarrow R_{f3} = R_{f1}(K_2 - 1) = 5.11 \text{ k}\Omega \cdot 1.235 = 6.31 \text{ k}\Omega$$

- Again, assuming $\pm 1\%$ resistors, we choose the closest standard values:

$$R_{f2} = 787 \Omega \quad \text{and} \quad R_{f3} = 6.34 \text{ k}\Omega$$

Sallen-Key Filter – Example

65

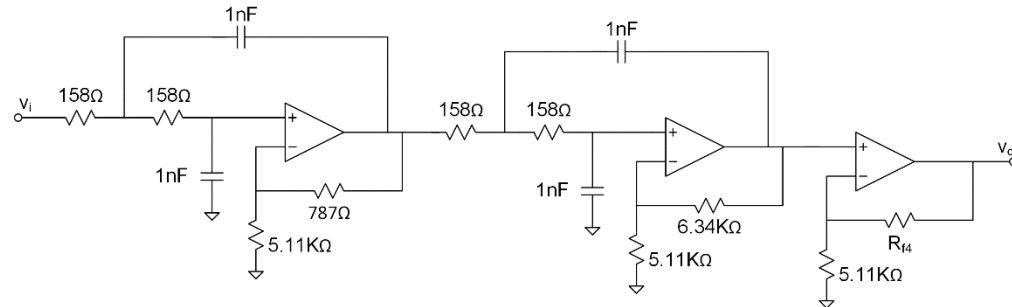

- Finally, set the gain of the third stage to satisfy the gain requirement
- Overall gain given by

$$K = K_1 K_2 K_3 = 4 \quad \rightarrow \quad K_3 = \frac{4}{K_1 K_2} = \frac{4}{1.152 \cdot 2.235} = 1.554$$

- Calculate R_{f4} to give the required K_3

$$K_3 = \frac{R_{f1} + R_{f4}}{R_{f1}} \quad \rightarrow \quad R_{f4} = R_{f1}(K_3 - 1) = 5.11 \text{ k}\Omega \cdot 0.554 = 2.83 \text{ k}\Omega$$


- Again, assuming $\pm 1\%$ resistors, we choose the closest standard value:

$$R_{f4} = 2.8 \text{ k}\Omega$$

Sallen-Key Filter – Example


66

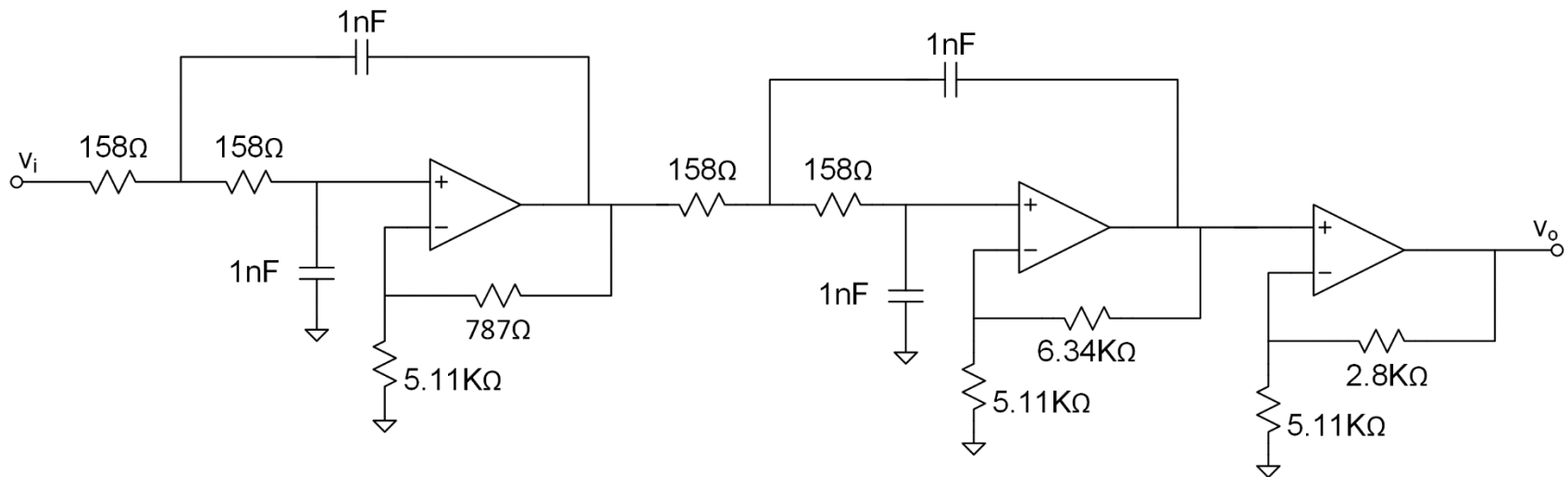The complete 4th-order Sallen-Key Butterworth low pass filter:



Sallen-Key Filter – Example

67

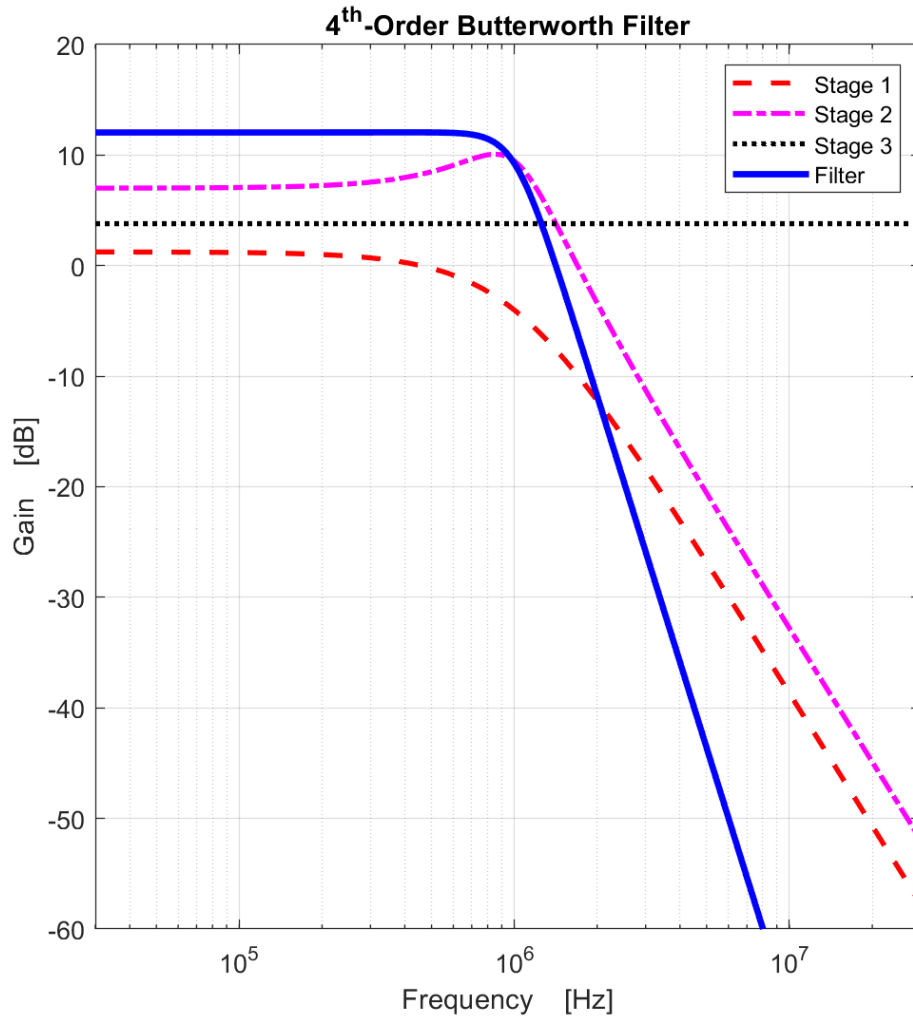

- DC gain: ~12 dB
- $f_c \approx 1 \text{ MHz}$
- Gain rolloff: -80 dB/dec
- Stage 1:
 - ▣ Low Q
 - ▣ Low gain
- Stage 2:
 - ▣ Higher Q
 - ▣ Higher gain
- Stage 3:
 - ▣ Constant gain