

SECTION 2: THREE-PHASE POWER FUNDAMENTALS

ESE 470 – Energy Distribution Systems

2

AC Circuits & Phasors

AC Electrical Signals

3

- AC electrical signals (voltages and currents) are ***sinusoidal***
 - ▣ Generated by rotating machinery
- Sinusoidal voltage (or current):

$$v(t) = V_p \cos(\omega t + \phi) \quad (1)$$

- ▣ This is a ***time-domain*** or ***instantaneous*** form expression
- Characterized by three parameters
 - ▣ ***Amplitude***
 - ▣ ***Frequency***
 - ▣ ***Phase***

Amplitude

4

$$v(t) = V_p \cos(\omega t + \phi)$$

- V_p in the above expression is **amplitude** or **peak voltage**
- We typically characterize power-system voltages and currents in terms of their **root-mean-square** (rms) values

$$V_{rms} = \left(\frac{1}{T} \int_0^T v(t)^2 dt \right)^{\frac{1}{2}} \quad (2)$$

- A signal delivers the same power to a resistive load as a DC signal equal to its rms value
- For **sinusoids**:

$$V_{rms} = \frac{V_p}{\sqrt{2}} \quad (3)$$

Euler's Identity

5

- Euler's identity allows us to express sinusoidal signals as complex exponentials

$$e^{j\omega t} = \cos(\omega t) + j \sin(\omega t) \quad (4)$$

so

$$e^{j(\omega t + \phi)} = \cos(\omega t + \phi) + j \sin(\omega t + \phi) \quad (5)$$

and

$$V_p \cos(\omega t + \phi) = V_p \operatorname{Re}\{e^{j(\omega t + \phi)}\}$$

$$V_p \cos(\omega t + \phi) = \sqrt{2} V_{rms} \operatorname{Re}\{e^{j(\omega t + \phi)}\} \quad (6)$$

Phasor Representation

6

- **Phasor representation** simplifies circuit analysis when dealing with sinusoidal signals
 - Drop the time-harmonic (oscillatory) portion of the signal representation
 - Known and constant
 - Represent with **rms amplitude** and **phase** only
- For example, consider the time-domain voltage expression

$$v(t) = \sqrt{2} V_{rms} \cos(\omega t + \phi)$$

- The phasor representation, in **exponential** form, is

$$\mathbf{V} = V_{rms} e^{j\phi}$$

- Can also express in **polar** or **Cartesian** form


$$\mathbf{V} = V_{rms} \angle \phi = V_{rms} \cos(\phi) + jV_{rms} \sin(\phi)$$

- In these notes **bold** type will be used to distinguish phasors
- We'll always assume rms values for phasor magnitudes

Phasors

7

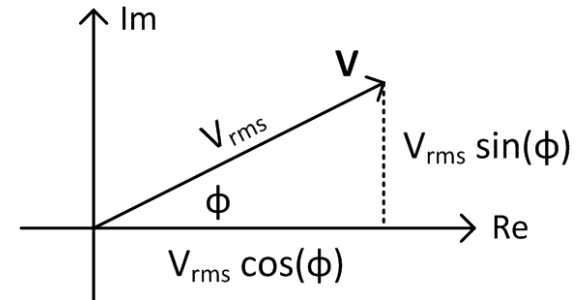- Think of a phasor as a vector in the complex plane
 - ▣ Has **magnitude** and **angle**



- Circuit analysis in the phasor domain is simplified
 - ▣ Derivative and integrals become algebraic expressions
- Consider the voltage across inductance and capacitance:

	Time Domain	Phasor Domain
Capacitor	$v(t) = \frac{1}{C} \int i(t) dt$	$V = \frac{1}{j\omega C} I$
Inductor	$v(t) = L \frac{di}{dt}$	$V = j\omega L I$
Resistor	$v(t) = i(t)R$	$V = IR$

Phasors

- In general, in the phasor domain

$$\mathbf{V} = \mathbf{I}Z \quad (7)$$

and

$$\mathbf{I} = \frac{\mathbf{V}}{Z}$$

- Ohm's law
- Z is a complex impedance
 - ▣ Not a phasor, but also expressed in exponential, polar, or Cartesian form

Phasors - Example

9

- Determine $i(t)$ and $v_L(t)$ for the following circuit, driven by a $120 V_{rms}$, $60 Hz$ source

- At $60 Hz$ the inductor impedance is

$$jX_L = j\omega L = j2\pi \cdot 60 Hz \cdot 5 mH = j1.88 \Omega$$

- The total impedance seen by the source is

$$Z = R + jX_L = 2 + j1.88 \Omega$$


- Converting to polar form

$$Z = |Z| \angle \theta$$

$$|Z| = \sqrt{R^2 + X^2} = 2.74 \Omega$$

$$\theta = \tan^{-1} \left(\frac{X}{R} \right) = 43^\circ$$

$$Z = 2.74 \angle 43^\circ \Omega$$

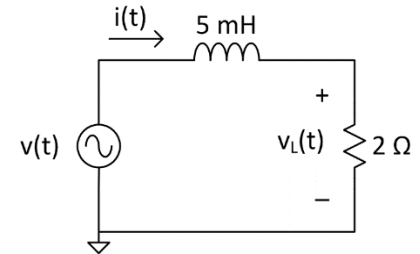

Phasors – Example

10

- The source voltage is

$$v(t) = \sqrt{2} \cdot 120V \cos(2\pi \cdot 60\text{Hz} \cdot t)$$

- The source voltage phasor is

$$V = 120 \angle 0^\circ V$$

- The current phasor is

$$I = \frac{V}{Z} = \frac{120 \angle 0^\circ V}{2.74 \angle 43^\circ \Omega} = 43.7 \angle -43^\circ A$$

- We can use the current phasor to determine the phasor for the voltage across the resistor

$$V_L = IR = (43.7 \angle -43^\circ) \cdot 2\Omega$$

$$V_L = 87.4 \angle -43^\circ V$$

Phasors – Example

11

- We have ***phasor*** representations for desired quantities

$$\mathbf{I} = 43.7 \angle -43^\circ \text{ A}$$

$$\mathbf{V}_L = 87.4 \angle -43^\circ \text{ V}$$

- We can now convert these to their time-domain expressions

$$i(t) = \sqrt{2} \cdot 43.7 \text{ A} \cdot \cos(2\pi \cdot 60\text{Hz} \cdot t - 43^\circ)$$

$$v(t) = \sqrt{2} \cdot 87.4 \text{ V} \cdot \cos(2\pi \cdot 60\text{Hz} \cdot t - 43^\circ)$$

12

Phasor Diagrams


Phasor Diagrams

13

- Phasors are complex values
 - ▣ Magnitude and phase
 - ▣ Vectors in the complex plane
 - ▣ Can represent graphically
- ***Phasor diagram***
 - ▣ Graphical representation of phasors in a circuit
 - ▣ KVL and Ohm's law expressed graphically

Phasor Diagram – Example 1

14

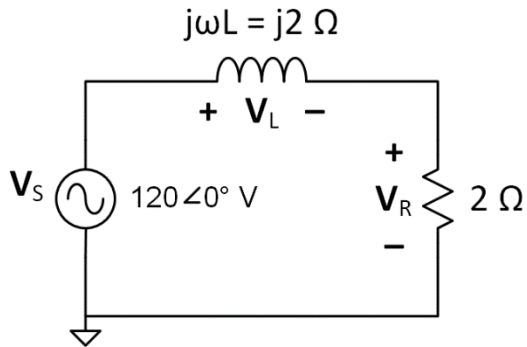

- Source voltage is the reference phasor

$$V_S = 120\angle 0^\circ \text{ V}$$


- ▣ Its phasor diagram:



- Ohm's law gives the current


$$I = \frac{V_S}{2 + j2 \Omega} = 42.2\angle -45^\circ \text{ A}$$

- ▣ Adding to the phasor diagram:

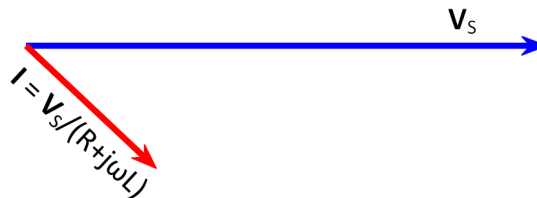

Phasor Diagram – Example 1

15

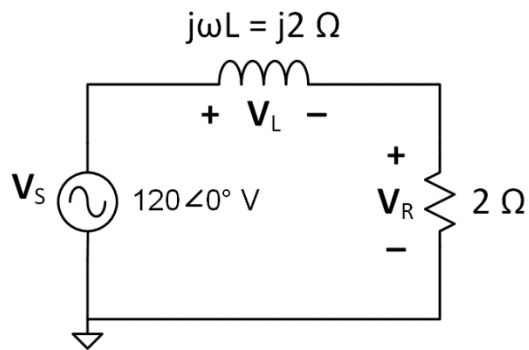

- Ohm's law gives the inductor voltage

$$V_L = I \cdot j\omega L = (42.2\angle -45^\circ \text{ A}) \cdot j2 \Omega$$


$$V_L = 85\angle 45^\circ \text{ V}$$

- Finally, KVL gives V_R

$$V_R = V_S - V_L$$


$$V_R = 120\angle 0^\circ \text{ V} - 85\angle 45^\circ \text{ V}$$

$$V_R = 85\angle -45^\circ \text{ V}$$

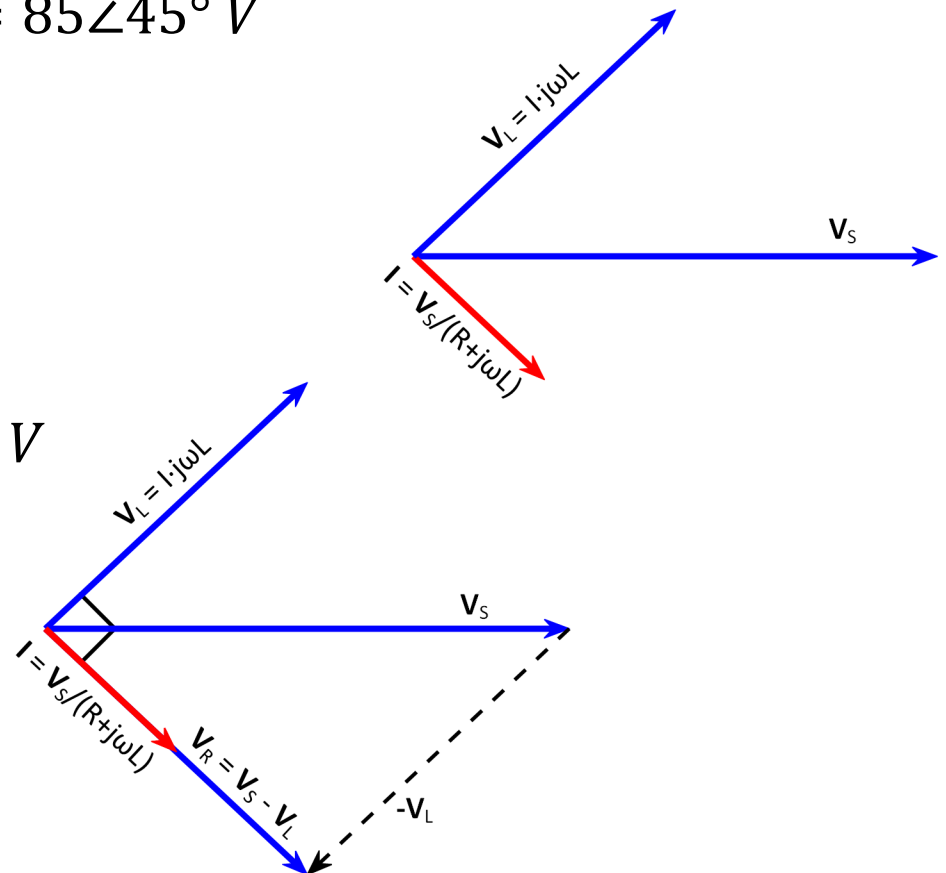

Phasor Diagram – Example 2

16

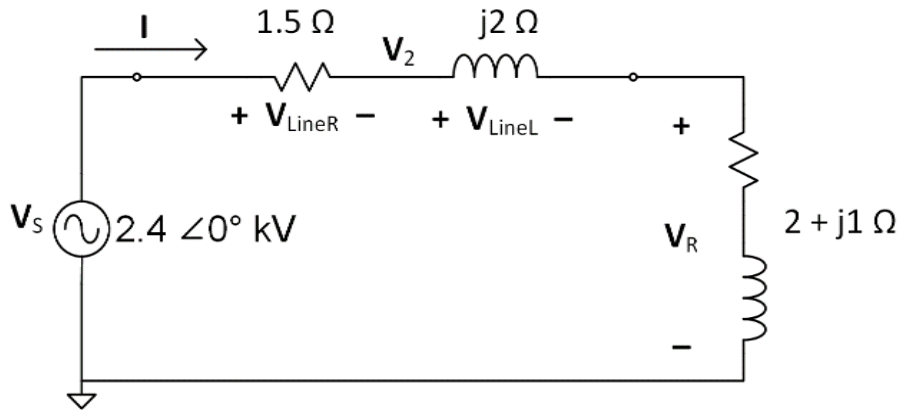

- Source voltage is the reference phasor

$$V_S = 2.4 \angle 0^\circ \text{ kV}$$




- Ohm's law gives the current

$$I = \frac{V_S}{3.5 + j3 \Omega} = 521 \angle -41^\circ \text{ A}$$



Phasor Diagram – Example 2

17

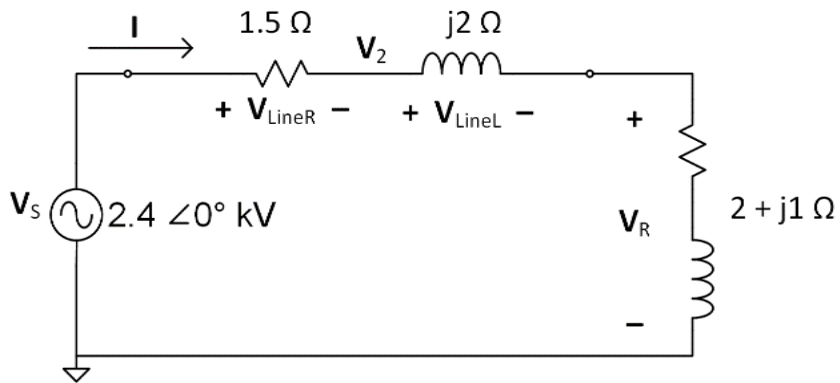

- Ohm's law gives the resistor voltage

$$V_{LineR} = I \cdot R$$

$$V_{LineR} = (521 \angle -41^\circ A) \cdot 1.5 \Omega$$

$$V_{LineR} = 781 \angle -41^\circ V$$




- KVL gives V_2

$$V_2 = V_S - V_{LineR}$$


$$V_2 = 2.4 \angle 0^\circ kV - 781 \angle -41^\circ V$$

$$V_2 = 1.88 \angle 15.7^\circ kV$$

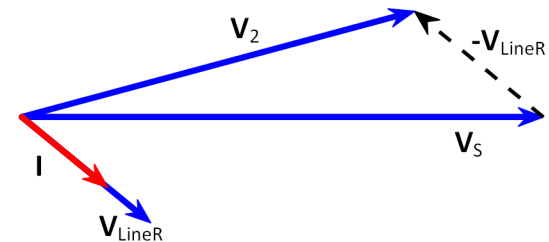

Phasor Diagram – Example 2


18

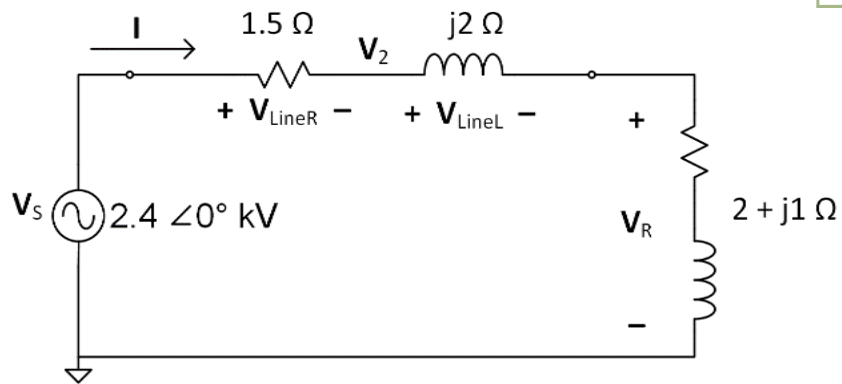

□ Drop across the inductor:

$$V_{LineL} = (521 \angle -41^\circ \text{ A}) \cdot j2 \Omega$$
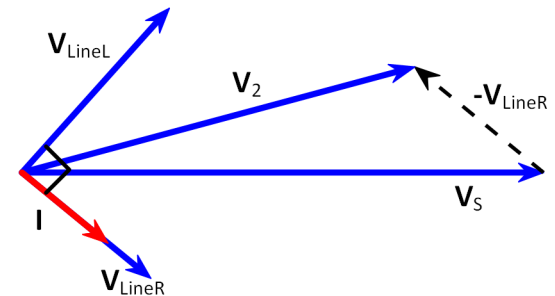
$$V_{LineL} = 1.04 \angle 49^\circ \text{ kV}$$




□ KVL gives the voltage across the load

$$V_R = V_2 - V_{LineL}$$


$$V_R = 1.88 \angle 15.7^\circ \text{ kV} - 1.04 \angle 49^\circ \text{ kV}$$
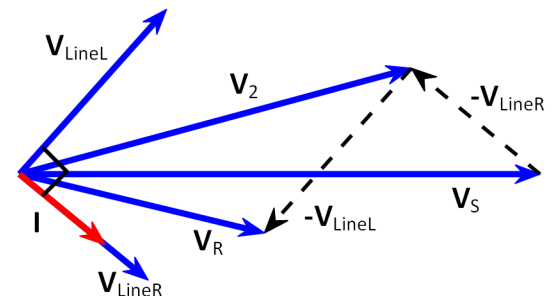
$$V_R = 1.16 \angle -14^\circ \text{ kV}$$



Phasor Diagram – Example 2

19

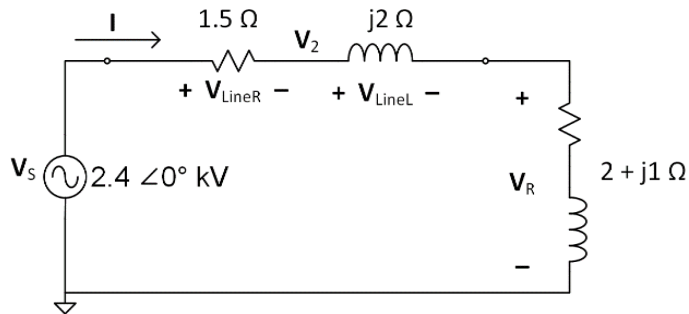


- Alternatively, treat the line as a single impedance

$$V_{Line} = I \cdot Z_{Line}$$

$$V_{Line} = (521 \angle -41^\circ A) \cdot (1.5 + j2 \Omega)$$

$$V_{LineL} = 1.3 \angle 12.5^\circ kV$$

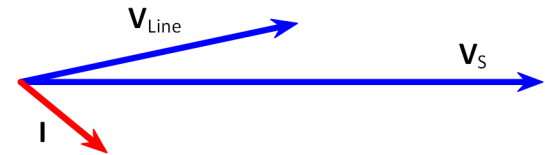


- KVL gives the voltage across the load

$$V_R = V_S - V_{Line}$$

$$V_R = 2.4 \angle 0^\circ kV - 1.3 \angle 12.5^\circ kV$$

$$V_R = 1.16 \angle -14^\circ kV$$

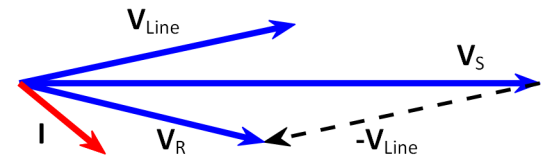

20

Power – Real Power & Power Factor

Power

21


- The overall goal of a power distribution network is to transfer power from a source to loads
- **Instantaneous power:**
 - ▣ Power supplied by a source or absorbed by a load or network element as a function of time

$$p(t) = v(t) \cdot i(t) \quad (8)$$

- The nature of this instantaneous power flow is determined by the impedance of the load
- Next, we'll look at the instantaneous power delivered to loads of different impedances

Instantaneous Power – Resistive Load

22

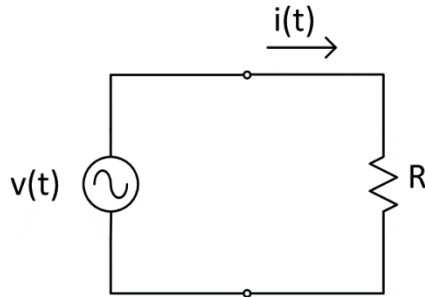

- The voltage across the resistive load is

$$v(t) = V_p \cos(\omega t + \delta)$$

- Current through the resistor is

$$i(t) = \frac{V_p}{R} \cos(\omega t + \delta)$$

- The instantaneous power absorbed by the resistor is

$$p_R(t) = v(t) \cdot i(t) = V_p \cos(\omega t + \delta) \cdot \frac{V_p}{R} \cos(\omega t + \delta)$$

$$p_R(t) = \frac{V_p^2}{R} \cos^2(\omega t + \delta) = \frac{V_p^2}{R} \frac{1}{2} [1 + \cos(2\omega t + 2\delta)]$$

Instantaneous Power – Resistive Load

23

$$p_R(t) = \frac{V_p^2}{2R} [1 + \cos(2\omega t + 2\delta)]$$

- Making use of the rms voltage

$$p_R(t) = \frac{(\sqrt{2} V_{rms})^2}{2R} [1 + \cos(2\omega t + 2\delta)]$$


$$p_R(t) = \frac{V_{rms}^2}{R} [1 + \cos(2\omega t + 2\delta)] \quad (9)$$

- The instantaneous power absorbed by the resistor has a non-zero average value and a double-frequency component

Instantaneous Power – Resistive Load

24

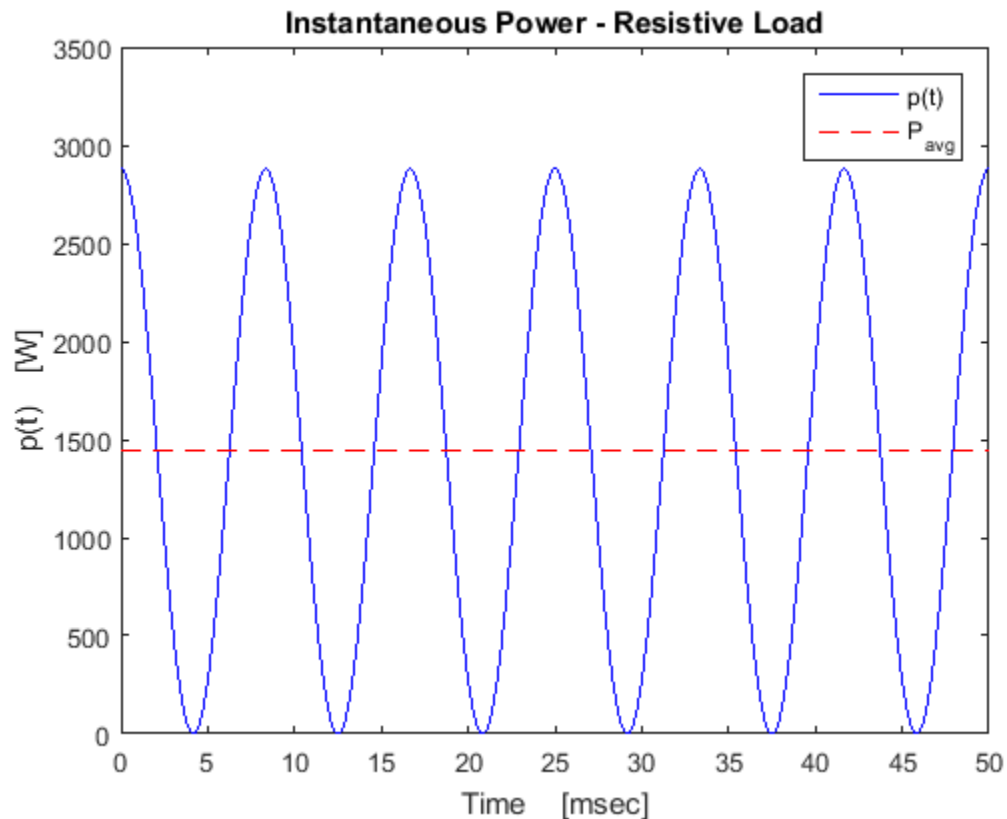- Power delivered to the resistive load has a non-zero average value and a double-frequency component



Instantaneous Power – Capacitive Load

25

- Now consider the power absorbed by a purely capacitive load

- ▣ Again, $v(t) = V_p \cos(\omega t + \delta)$

- The current flowing to the load is

$$i(t) = I_p \cos(\omega t + \delta + 90^\circ)$$


where

$$I_p = \frac{V_p}{X_C} = \frac{V_p}{1/\omega C} = \omega C V_p$$

- The instantaneous power delivered to the capacitive load is

$$p_C(t) = v(t) \cdot i(t)$$
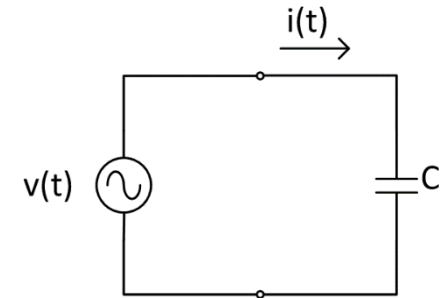
$$p_C(t) = V_p \cos(\omega t + \delta) \cdot \omega C V_p \cos(\omega t + \delta + 90^\circ)$$



Instantaneous Power – Capacitive Load

26

$$p_C(t) = \omega C V_p^2 \frac{1}{2} [\cos(-90^\circ) + \cos(2\omega t + 2\delta + 90^\circ)]$$


$$p_C(t) = \omega C \frac{V_p^2}{2} \cdot \cos(2\omega t + 2\delta + 90^\circ)$$

- In terms of rms voltage

$$p_C(t) = \omega C V_{rms}^2 \cdot \cos(2\omega t + 2\delta + 90^\circ)$$

- This is a double frequency sinusoid, but, unlike for the resistive load, the average value is zero

(10)

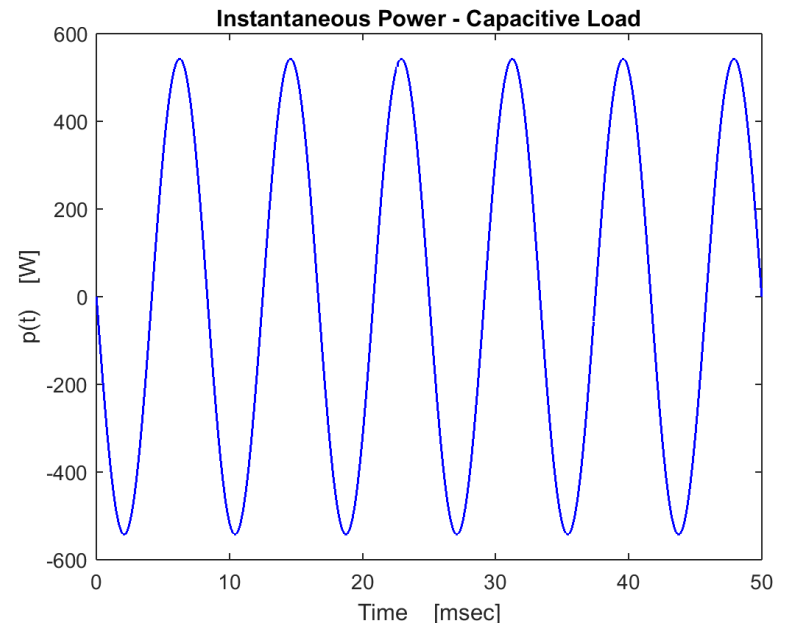

Instantaneous Power – Inductive Load


27

- Now consider the power absorbed by a purely inductive load
- Now the load current *lags* by 90°

$$i(t) = I_p \cos(\omega t + \delta - 90^\circ)$$

where
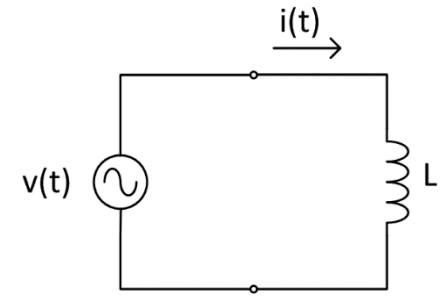
$$I_p = \frac{V_p}{X_L} = \frac{V_p}{\omega L}$$



- The instantaneous power delivered to the inductive load is

$$p_L(t) = v(t) \cdot i(t)$$

$$p_L(t) = V_p \cos(\omega t + \delta) \cdot \frac{V_p}{\omega L} \cos(\omega t + \delta - 90^\circ)$$

Instantaneous Power – Inductive Load

28

$$p_L(t) = \frac{V_p^2}{\omega L} \frac{1}{2} [\cos(90^\circ) + \cos(2\omega t + 2\delta - 90^\circ)]$$


$$p_L(t) = \frac{V_p^2}{2\omega L} \cdot \cos(2\omega t + 2\delta - 90^\circ)$$

- In terms of rms voltage

$$p_L(t) = \frac{V_{rms}^2}{\omega L} \cdot \cos(2\omega t + 2\delta - 90^\circ)$$

- As for the capacitive load, this is a double frequency sinusoid with an average value of zero

(11)

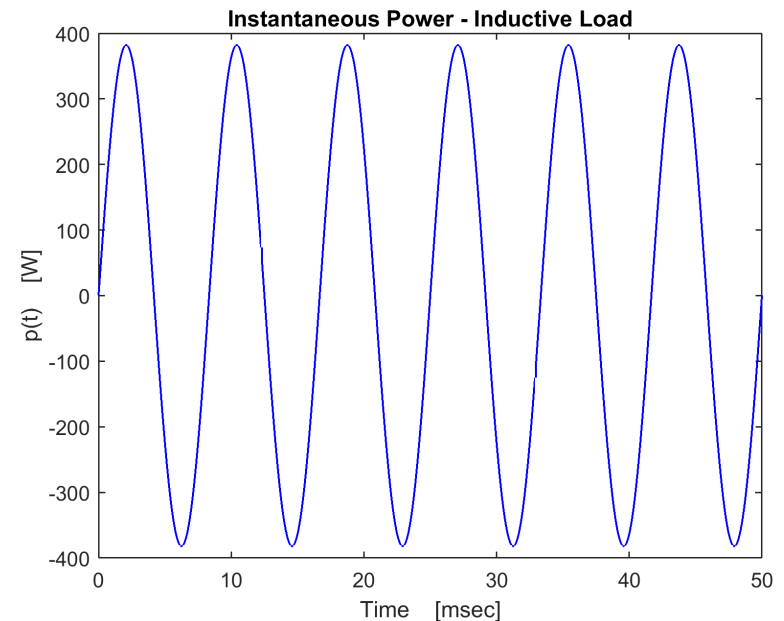

Instantaneous Power – General Impedance

29

- Finally, consider the instantaneous power absorbed by a general RLC load
- Phase angle of the current is determined by the angle of the impedance


$$i(t) = I_p \cos(\omega t + \beta)$$

- The instantaneous power is

$$p(t) = V_p \cos(\omega t + \delta) \cdot I_p \cos(\omega t + \beta)$$

$$p(t) = \frac{V_p I_p}{2} [\cos(\delta - \beta) + \cos(2\omega t + \delta + \beta)]$$
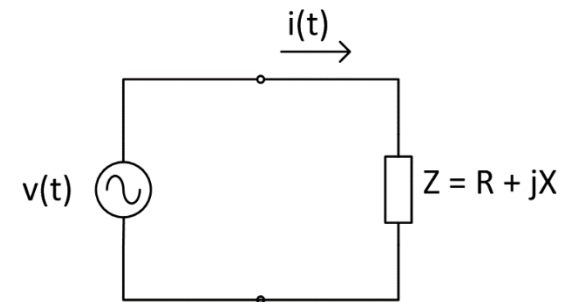
$$p(t) = V_{rms} I_{rms} [\cos(\delta - \beta) + \cos(2\omega t + 2\delta - (\delta - \beta))]$$



Instantaneous Power – General Impedance

30

- Using the following trig identity

$$\cos(A - B) = \cos(A) \cos(B) + \sin(A) \sin(B)$$

we get

$$p(t) = V_{rms} I_{rms} [\cos(\delta - \beta) + \cos(\delta - \beta) \cos(2\omega t + 2\delta) + \sin(\delta - \beta) \sin(2\omega t + 2\delta)]$$

and

$$p(t) = V_{rms} I_{rms} \cos(\delta - \beta) [1 + \cos(2\omega t + 2\delta)] + V_{rms} I_{rms} \sin(\delta - \beta) \sin(2\omega t + 2\delta)$$

Instantaneous Power – General Impedance

31

- Letting

$$I_R = I_{rms} \cos(\delta - \beta) \quad \text{and} \quad I_X = I_{rms} \sin(\delta - \beta)$$

we have

$$\begin{aligned} p(t) = & V_{rms} I_R [1 + \cos(2\omega t + 2\delta)] \\ & + V_{rms} I_X \sin(2\omega t + 2\delta) \end{aligned} \quad (12)$$

- There are two components to the power:

$$p_R(t) = V_{rms} I_R [1 + \cos(2\omega t + 2\delta)] \quad (13)$$

is the power absorbed by the resistive component of the load, and

$$p_X(t) = V_{rms} I_X \sin(2\omega t + 2\delta) \quad (14)$$

is the power absorbed by the reactive component of the load

Real Power

32

- According to (9) and (13), power delivered to a resistance has a non-zero average value
 - ▣ Purely resistive load or a load with a resistive component
- This is ***real power, average power, or active power***

$$P = V_{rms} I_R$$

$$P = V_{rms} I_{rms} \cos(\delta - \beta) \quad (15)$$

- Real power has units of ***watts*** (W)
- Real power is power that results in work (or heat dissipation)

Power Factor

33

- The phase angle ($\delta - \beta$) represents the phase difference between the voltage and the current
 - ▣ This is the **power factor angle**
 - ▣ The angle of the load impedance
- Note that the *real power* is a function of the *cosine of the power factor angle*

$$P = V_{rms} I_{rms} \cos(\delta - \beta)$$

- This is the **power factor**

$$p.f. = \cos(\delta - \beta) \tag{16}$$

- For a purely resistive load, voltage and current are in phase

$$p.f. = \cos(\delta - \beta) = \cos(0^\circ) = 1$$

$$P = V_{rms} I_{rms}$$

Power Factor

34

- For a purely capacitive load, current leads the voltage by 90°

$$p.f. = \cos(\delta - \beta) = \cos(-90^\circ) = 0$$

$$P = 0$$

- ▣ This is referred to as a ***leading power factor***
- ▣ Power factor is *leading* for loads with *capacitive* reactance
- For a purely inductive load, current lags the voltage by 90°

$$p.f. = \cos(\delta - \beta) = \cos(90^\circ) = 0$$

$$P = 0$$

- ▣ Loads with inductive reactance have *lagging* power factors
- Note that power factor is defined to always be ***positive***

$$0 \leq p.f. \leq 1$$

35

Reactive & Complex Power

Reactive Power

36

- The other part of instantaneous power, as given by (12), is the power delivered to the reactive component of the load

$$p_X(t) = V_{rms}I_{rms} \sin(\delta - \beta) \sin(2\omega t + 2\delta)$$

- Unlike real power, this component of power has zero average value
- The *amplitude* is the **reactive power**

$$Q = V_{rms}I_{rms} \sin(\delta - \beta) \text{ var}$$

- Units are **volts-amperes reactive**, or **var**
- Power that flows to and from the load reactance
 - ▣ Does not result in work or heat dissipation

Complex Power

37

- **Complex power** is defined as the product of the rms voltage phasor and *conjugate* rms current phasor

$$\boxed{\mathbf{S} = \mathbf{V}\mathbf{I}^*} \quad (18)$$

where the voltage has phase angle δ

$$\mathbf{V} = V_{rms} \angle \delta$$

and the current has phase angle β

$$\mathbf{I} = I_{rms} \angle \beta \quad \rightarrow \quad \mathbf{I}^* = I_{rms} \angle -\beta$$

- The complex power is

$$\mathbf{S} = \mathbf{V}\mathbf{I}^* = (V_{rms} \angle \delta)(I_{rms} \angle -\beta)$$

$$\mathbf{S} = V_{rms} I_{rms} \angle (\delta - \beta) \quad (19)$$

Complex Power

38

- Complex power has units of ***volts-amperes*** (VA)
- The *magnitude* of complex power is ***apparent power***

$$S = V_{rms} I_{rms} \text{ VA}$$

(20)

- Apparent power also has units of volts-amperes
- Complex power is the vector sum of real power (in phase with V) and reactive power ($\pm 90^\circ$ out of phase with V)

$$S = P + jQ$$

(21)

Complex Power

39

- **Real power** can be expressed in terms of complex power

$$P = \operatorname{Re}\{\mathbf{S}\}$$

or in terms of **apparent power**

$$P = S \cdot \cos(\delta - \beta) = S \cdot p.f.$$

- Similarly, **reactive power**, is the imaginary part of complex power

$$Q = \operatorname{Im}\{\mathbf{S}\}$$

and can also be related to **apparent power**

$$Q = S \cdot \sin(\delta - \beta)$$

- And, **power factor** is the **ratio** between **real power** and **apparent power**

$$p.f. = \cos(\delta - \beta) = \frac{P}{S}$$


40

Passive Sign Convention

Power Convention – Load Convention

41

- Applying a consistent sign convention allows us to easily determine whether network elements supply or absorb real and reactive power
- ***Passive sign convention*** or ***load convention***
 - Positive current defined to enter the positive voltage terminal of an element
- If $P > 0$ or $Q > 0$, then real or reactive power is ***absorbed*** by the element
- If $P < 0$ or $Q < 0$, then real or reactive power is ***supplied*** by the element

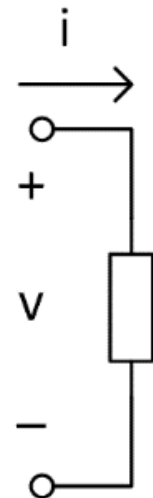

Power Absorbed by Passive Elements

42

- Complex power absorbed by a **resistor**

$$\mathbf{S}_R = \mathbf{V}\mathbf{I}_R^* = (V\angle\delta) \left(\frac{V}{R} \angle -\delta \right)$$

$$\mathbf{S}_R = \frac{V^2}{R}$$

- Positive and purely real
 - Resistors **absorb real** power
 - **Reactive** power is **zero**
- Complex power absorbed by a **capacitor**

$$\mathbf{S}_C = \mathbf{V}\mathbf{I}_C^* = (V\angle\delta)(-j\omega CV\angle -\delta)$$

$$\mathbf{S}_C = -j\omega CV^2$$

- Negative and purely imaginary
 - Capacitors **supply reactive** power
 - **Real** power is **zero**

Power Absorbed by Passive Elements

43

- Complex power absorbed by an **inductor**

$$\mathbf{S}_L = \mathbf{V}\mathbf{I}_L^* = (V\angle\delta) \left(\frac{V}{-j\omega L} \angle -\delta \right)$$

$$\mathbf{S}_L = j \frac{V^2}{\omega L}$$

- Positive and purely imaginary
 - Inductors **absorb reactive** power
 - **Real** power is **zero**
-
- In summary:
 - Resistors absorb real power, zero reactive power
 - Capacitors supply reactive power, zero real power
 - Inductors absorb reactive power, zero real power

44

Power Triangle


Power Triangle

45

- Complex power is the vector sum of real power (in phase with V) and reactive power ($\pm 90^\circ$ out of phase with V)


$$S = P + jQ$$

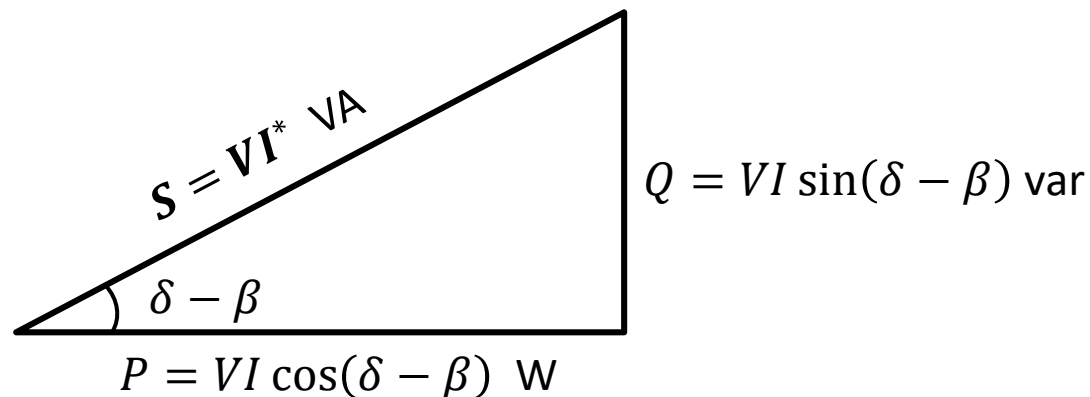- Complex, real, and reactive powers can be represented graphically, as a **power triangle**



Power Triangle

46

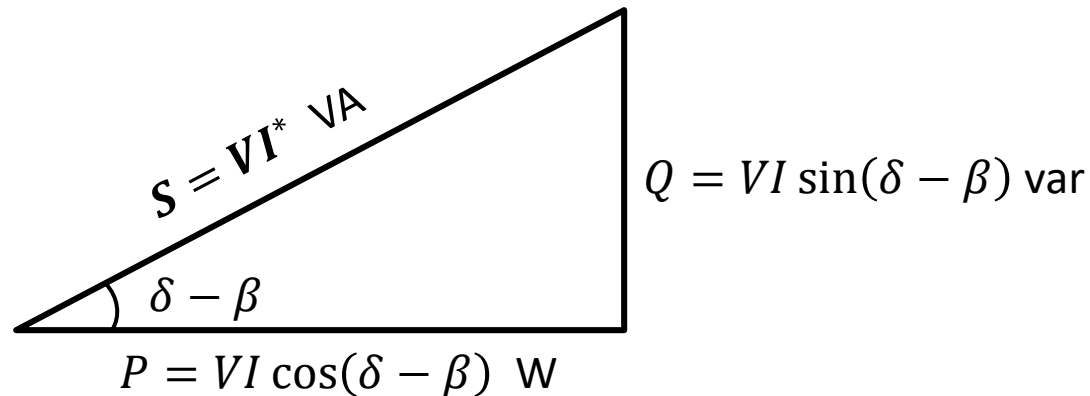


- Quickly and graphically provides power information
 - ▣ **Power factor** and power factor angle
 - ▣ **Leading** or **lagging** power factor
 - ▣ Reactive nature of the load – **capacitive** or **inductive**

Lagging Power Factor

47

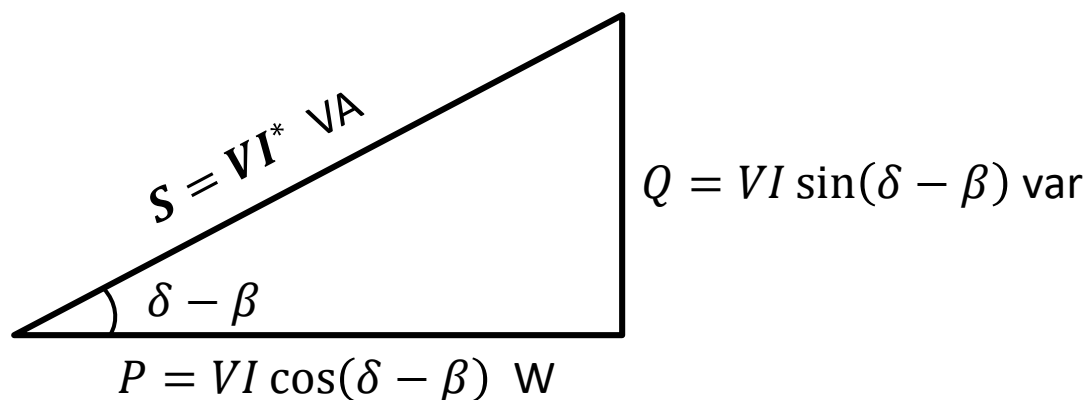- For loads with **inductive** reactance
 - Impedance angle is positive
 - Power factor angle is positive
 - Power factor is **lagging**




- Q is positive
 - The load **absorbs** reactive power

Leading Power Factor

48

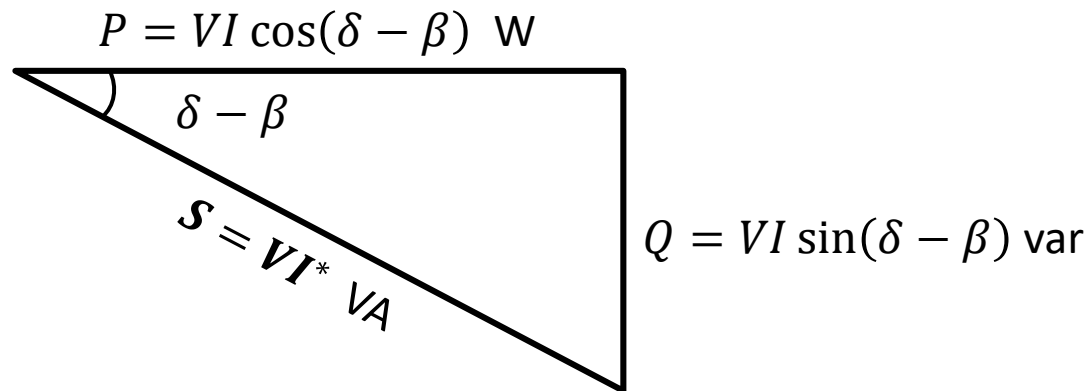- For loads with **capacitive** reactance
 - Impedance angle is negative
 - Power factor angle is negative
 - Power factor is **leading**



- Q is negative
 - The load **supplies** reactive power

49

Power Factor Correction

Power Factor Correction


50

- The overall goal of power distribution is to supply power to do work
 - ▣ *Real* power
- Reactive power does not perform work, but
 - ▣ Must be supplied by the source
 - ▣ Still flows over the lines
- For a given amount of real power consumed by a load, we'd like to
 - ▣ Reduce reactive power, Q
 - ▣ Reduce S relative to P , that is
 - ▣ Reduce the p.f. angle, and
 - ▣ Increase the p.f.
- ***Power factor correction***

Power Factor Correction – Example

51

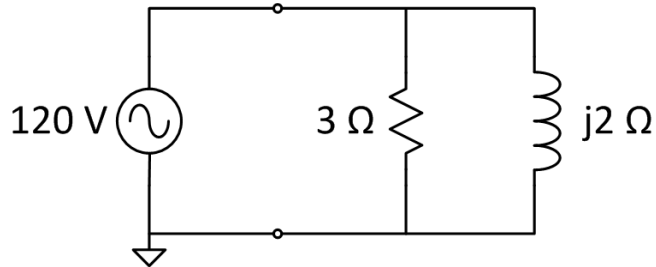- Consider a source driving an inductive load



- Determine:
 - ▣ Real power absorbed by the load
 - ▣ Reactive power absorbed by the load
 - ▣ p.f. angle and p.f.
- Draw the power triangle

- Current through the resistance is

$$I_R = \frac{120 V}{3 \Omega} = 40 A$$

- Current through the inductance is

$$I_L = \frac{120 V}{j2 \Omega} = 60 \angle -90^\circ A$$

- The total load current is

$$I = I_R + I_L = (40 - j60)A = 72.1 \angle -56.3^\circ A$$

Power Factor Correction – Example

52

- The power factor angle is

$$\theta = (\delta - \beta) = 0^\circ - (-56.3^\circ)$$

$$\theta = 56.3^\circ$$

- The power factor is

$$p.f. = \cos(\theta) = \cos(56.3^\circ)$$

$$p.f. = 0.55 \text{ lagging}$$

- Real power absorbed by the load is

$$P = VI \cos(\theta) = 120 \text{ V} \cdot 72.1 \text{ A} \cdot 0.55$$

$$P = 4.8 \text{ kW}$$

- Alternatively, recognizing that real power is power absorbed by the resistance

$$P = VI_R = 120 \text{ V} \cdot 40 \text{ A} = 4.8 \text{ kW}$$

Power Factor Correction – Example

53

- Reactive power absorbed by the load is

$$Q = VI \sin(\theta) = 120 V \cdot 72.1 A \cdot 0.832$$

$$Q = 7.2 \text{ kvar}$$

- This is also the power absorbed by the load inductance

$$Q = VI_L = 120 V \cdot 60 A = 7.2 \text{ kvar}$$

- Apparent power is

$$S = VI = 120 V \cdot 72.1 A = 8.65 \text{ kVA}$$

- Or, alternatively


$$S = \sqrt{P^2 + Q^2}$$

$$S = \sqrt{(4.8 \text{ kW})^2 + (7.2 \text{ kvar})^2} = 8.65 \text{ kVA}$$

Power Factor Correction – Example

54

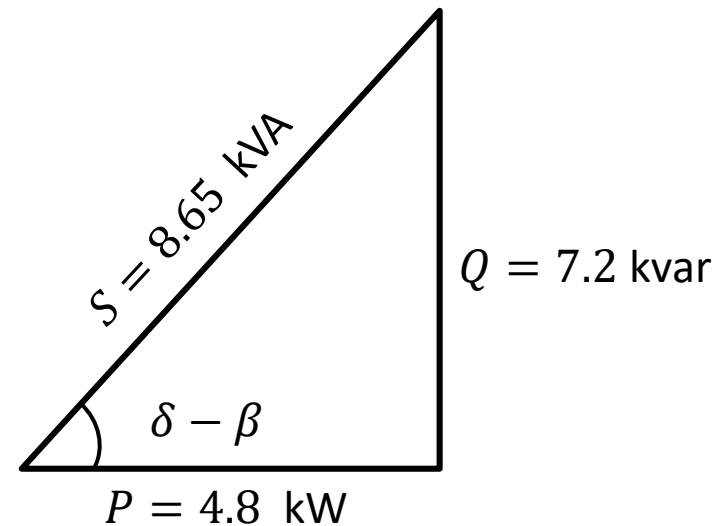- The ***power triangle***:
- Here, the source is supplying 4.8 kW at a power factor of 0.55 lagging
- Let's say we want to reduce the apparent power supplied by the source
 - Deliver 4.8 kW at a p.f. of 0.9 lagging
- Add ***power factor correction***
- Add capacitors to *supply* reactive power




Power Factor Correction – Example


55

- For $p.f. = 0.9$, we need a power factor angle of
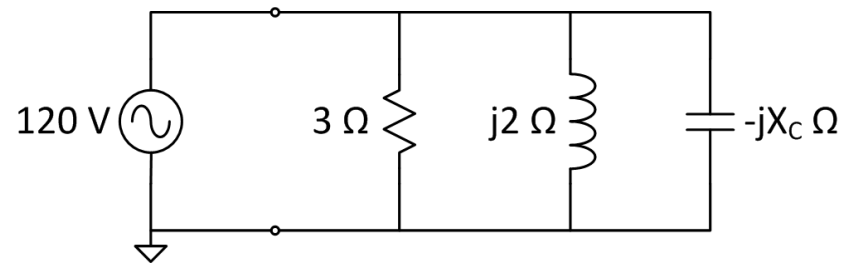
$$\theta' = \cos^{-1}(0.9) = 25.8^\circ$$



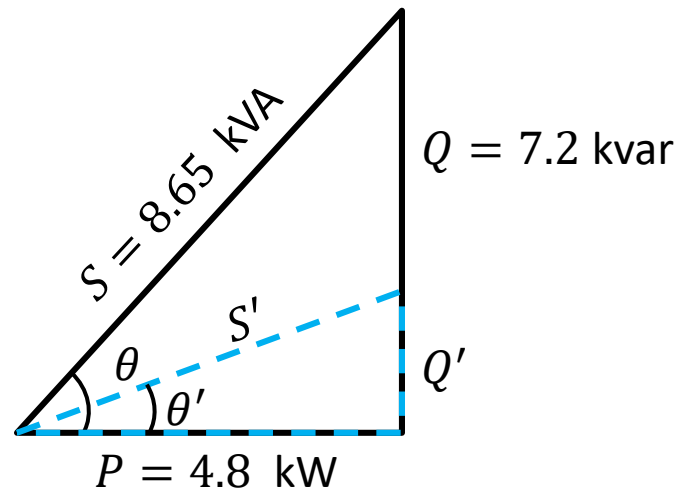- Power factor correction will help flatten the power triangle:



Power Factor Correction – Example


56

- Reactive power to the power-factor-corrected load is reduced from Q to Q'

$$Q' = P \tan(\theta')$$

$$Q' = 4.8 \text{ kW} \cdot \tan(25.8^\circ)$$

$$Q' = 2.32 \text{ kvar}$$

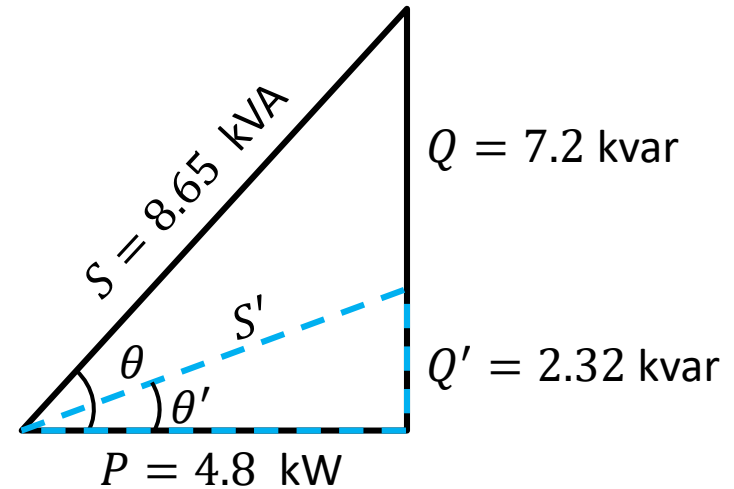

- The required reactive power *absorbed* (negative, so it is *supplied*) by the capacitors is

$$Q_C = Q' - Q = 2.32 \text{ kvar} - 7.2 \text{ kvar}$$

$$Q_C = -4.88 \text{ kvar}$$

Power Factor Correction – Example

57


- Reactive power absorbed by the capacitor is

$$Q_C = \frac{V^2}{X_C}$$

- So the required capacitive reactance is

$$X_C = \frac{V^2}{Q_C} = \frac{(120 \text{ V})^2}{-4.88 \text{ kvar}} = -2.95 \Omega$$

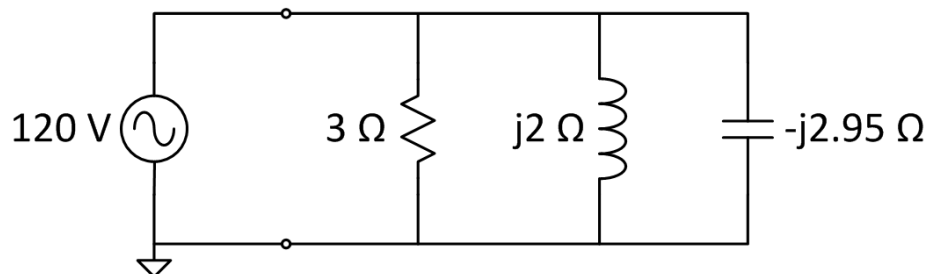- The addition of $-j2.95 \Omega$ provides the desired power factor correction




58

Example Problems

The source voltage in the circuit is

$$v(t) = \sqrt{2} \cdot 120V \cos(2\pi \cdot 60\text{Hz} \cdot t).$$

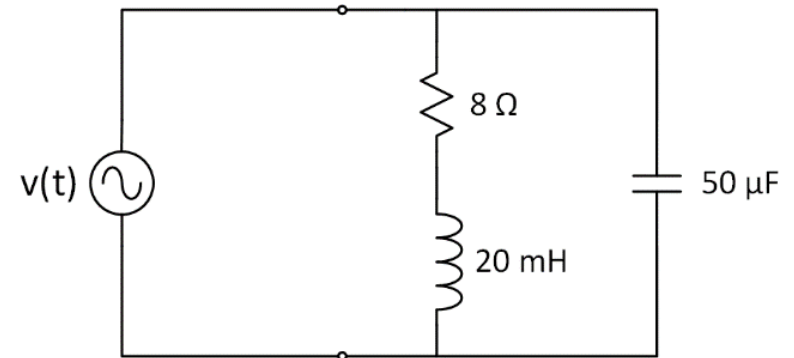Determine the complex power delivered to the load.



Two three-phase load are connected in parallel:

- ▣ 50 kVA at a power factor of 0.9, leading
- ▣ 125 kW at a power factor of 0.85, lagging.


Draw the power triangle and determine the combined power factor.

Power is delivered to a single-phase load with an impedance of $Z_L = 3 + j2 \Omega$ at 120 V. Add power factor correction in parallel with the load to yield a power factor of 0.95, lagging.

Determine the reactive power and impedance of the power factor correction component.

Draw a phasor diagram for the following circuit.

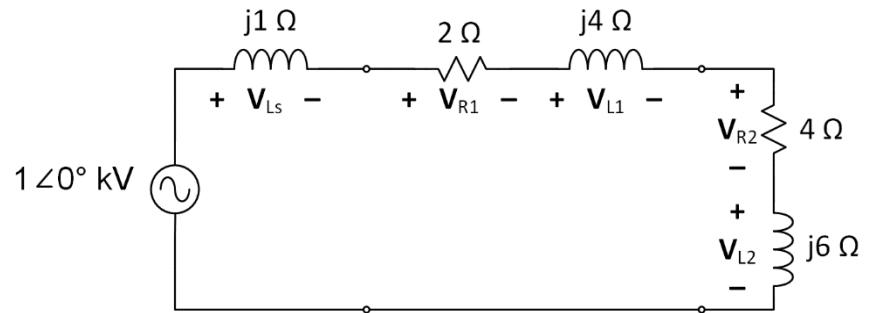- Draw a phasor for the voltage across each component and for the current
- Apply KVL graphically. That is, add the individual component phasors together graphically to show that the result is equal to the source voltage phasor.




67

Balanced Three-Phase Networks

Balanced Three-Phase Networks

68

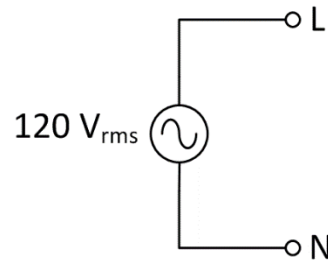- We are accustomed to **single-phase** power in our homes and offices
 - ▣ A single **line** voltage referenced to a **neutral**




- Electrical power is generated, transmitted, and largely consumed (by industrial customers) as **three-phase power**
 - ▣ Three individual line voltages and (possibly) a neutral
 - ▣ Line voltages all differ in phase by $\pm 120^\circ$

Δ - and Y-Connected Networks


69

- Two possible three-phase configurations
 - ▣ Applies to both *sources* and *loads*

Y-Connected Source

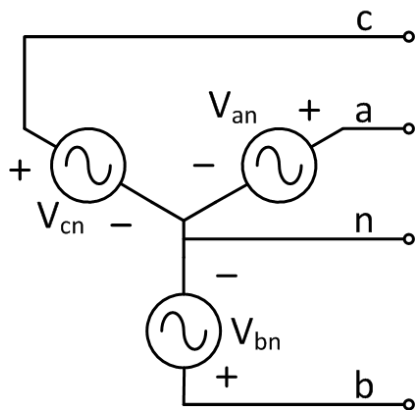

Δ -Connected Source

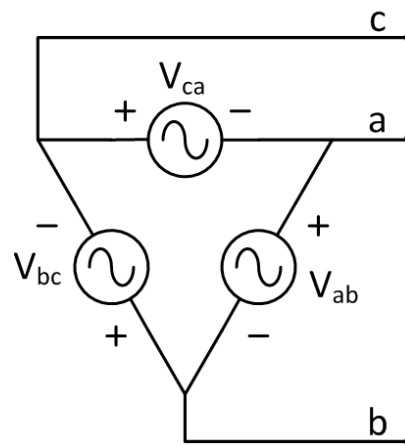


- Y-connected network has a neutral node
- Δ -connected network has no neutral

Line-to-Neutral Voltages

70

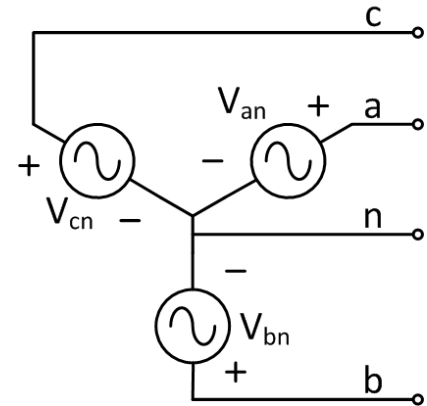- In the Y network, voltages V_{an} , V_{bn} , and V_{cn} are **line-to-neutral voltages**
- A three-phase source is **balanced** if
 - ▣ Line-to-neutral voltages have equal magnitudes
 - ▣ Line-to-neutral voltages are each 120° out of phase with one another
- A three-phase network is balanced if
 - ▣ Sources are balanced
 - ▣ The impedances connected to each phase are equal



Line-to-Neutral Voltages

71


- The line-to-neutral voltages are

$$V_{an} = V_{LN} \angle 0^\circ$$


$$V_{bn} = V_{LN} \angle -120^\circ$$

$$V_{cn} = V_{LN} \angle -240^\circ = V_{LN} \angle +120^\circ$$

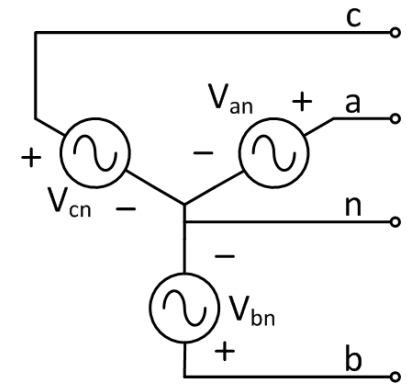- This is a **positive-sequence** or **abc-sequence** source
 - V_{an} leads V_{bn} , which leads V_{cn}
- Can also have a **negative-** or **acb-sequence** source
 - V_{an} leads V_{cn} , which leads V_{bn}
- We'll always assume **positive-sequence** sources



Positive-Sequence Phasor Diagram:

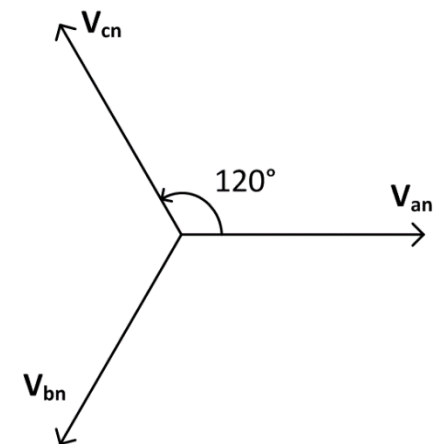

Line-to-Line Voltages

72

- The voltages between the three phases are **line-to-line voltages**
- Apply KVL to relate line-to-line voltages to line-to-neutral voltages

$$V_{ab} - V_{an} + V_{bn} = 0$$

$$V_{ab} = V_{an} - V_{bn}$$

- We know that

$$V_{an} = V_{LN} \angle 0^\circ$$

and


$$V_{bn} = V_{LN} \angle -120^\circ$$

so

$$V_{ab} = V_{LN} \angle 0^\circ - V_{LN} \angle -120^\circ = V_{LN} (1 \angle 0^\circ - 1 \angle -120^\circ)$$

$$V_{ab} = V_{LN} \left[1 - \left(-\frac{1}{2} - j\frac{\sqrt{3}}{2} \right) \right] = V_{LN} \left[\frac{3}{2} + j\frac{\sqrt{3}}{2} \right]$$
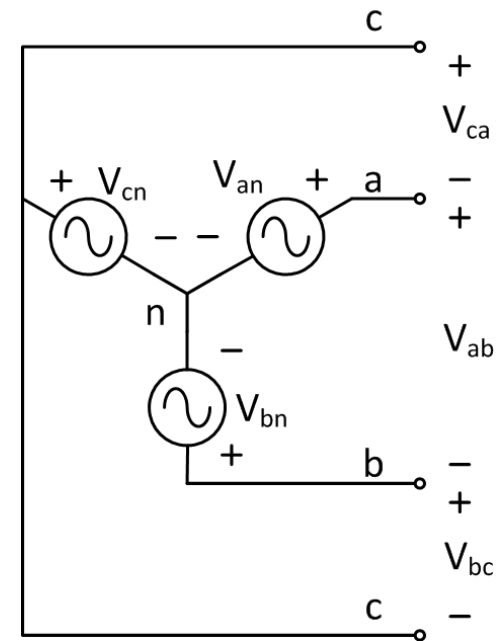
$$V_{ab} = \sqrt{3} V_{LN} \angle 30^\circ$$



Line-to-Line Voltages

73

- Again applying KVL, we can find V_{bc}

$$V_{bc} = V_{bn} - V_{cn}$$

$$V_{bc} = V_{LN} \angle -120^\circ - V_{LN} \angle 120^\circ$$


$$V_{bc} = V_{LN} \left[\left(-\frac{1}{2} - j\frac{\sqrt{3}}{2} \right) - \left(-\frac{1}{2} + j\frac{\sqrt{3}}{2} \right) \right]$$

$$V_{bc} = V_{LN} (-j\sqrt{3})$$

$$V_{bc} = \sqrt{3}V_{LN} \angle -90^\circ$$

- Similarly,
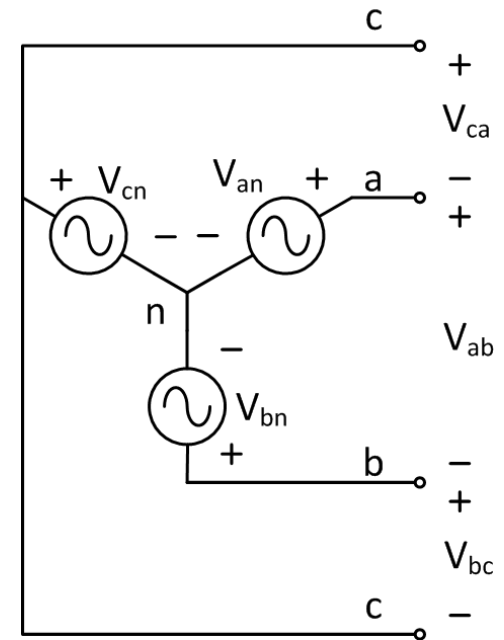
$$V_{ca} = \sqrt{3}V_{LN} \angle 150^\circ$$



Line-to-Line Voltages

74

- The line-to-line voltages, with V_{an} as the reference:

$$V_{ab} = \sqrt{3}V_{LN} \angle 30^\circ$$

$$V_{bc} = \sqrt{3}V_{LN} \angle -90^\circ$$


$$V_{ca} = \sqrt{3}V_{LN} \angle 150^\circ$$

- Line-to-line voltages are $\sqrt{3}$ times the line-to-neutral voltage
- Can also express in terms of individual line-to-neutral voltages:

$$V_{ab} = \sqrt{3}V_{an} \angle 30^\circ$$

$$V_{bc} = \sqrt{3}V_{bn} \angle 30^\circ$$
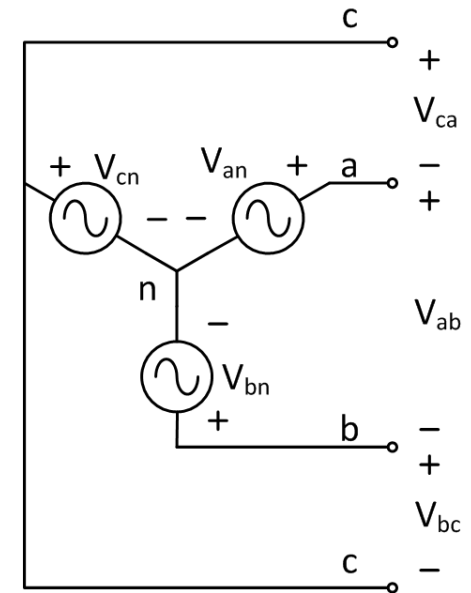
$$V_{ca} = \sqrt{3}V_{cn} \angle 30^\circ$$




75

Currents in Three-Phase Networks

Line Currents in Balanced 3 ϕ Networks

76

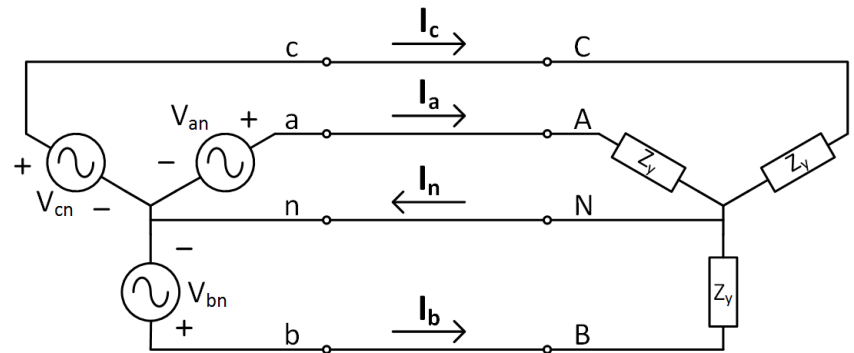- We can use the line-to-neutral voltages to determine the line currents
 - ▣ Y-connected source and load
 - ▣ Balanced load – all impedances are equal: Z_Y



$$\begin{aligned} I_a &= \frac{V_{AN}}{Z_Y} = \frac{V_{LN} \angle 0^\circ}{Z_Y} \\ I_b &= \frac{V_{BN}}{Z_Y} = \frac{V_{LN} \angle -120^\circ}{Z_Y} \\ I_c &= \frac{V_{CN}}{Z_Y} = \frac{V_{LN} \angle +120^\circ}{Z_Y} \end{aligned}$$

- Line currents are balanced as long as the source and load are balanced

Neutral Current in Balanced 3 ϕ Networks

77

- Apply KCL to determine the neutral current


$$I_n = I_a + I_b + I_c$$

$$I_n = \frac{V_{LN}}{Z_Y} [1\angle 0^\circ + 1\angle -120^\circ + 1\angle 120^\circ]$$

$$I_n = \frac{V_{LN}}{Z_Y} \left[1 + \left(-\frac{1}{2} - j\frac{\sqrt{3}}{2} \right) + \left(-\frac{1}{2} + j\frac{\sqrt{3}}{2} \right) \right]$$

$$I_n = 0$$

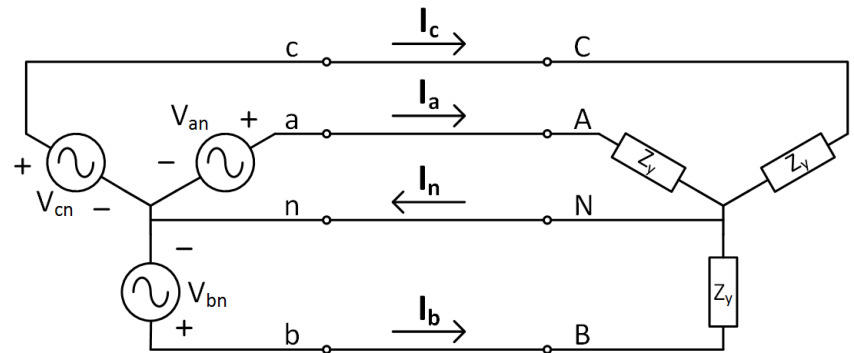- The neutral conductor carries no current in a balanced three-phase network



78


Y- and Δ -connected Loads

Three-Phase Load Configurations


79

- As for sources, three-phase loads can also be connected in two different configurations

Y-Connected Load

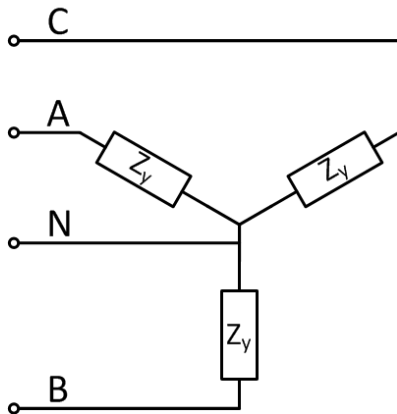

Δ -Connected Load

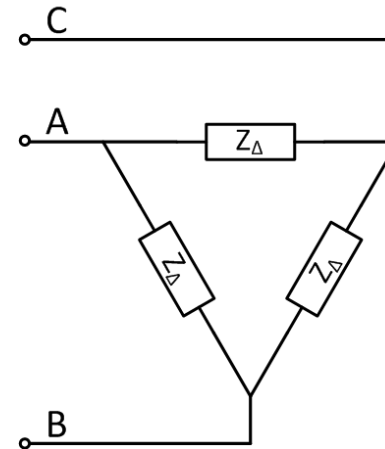


- The Y load has a neutral connection, but the Δ load does not
- Currents in a Y-connected load are the line currents we just determined
- Next, we'll look at currents in a Δ -connected load

Balanced Δ -Connected Loads

80

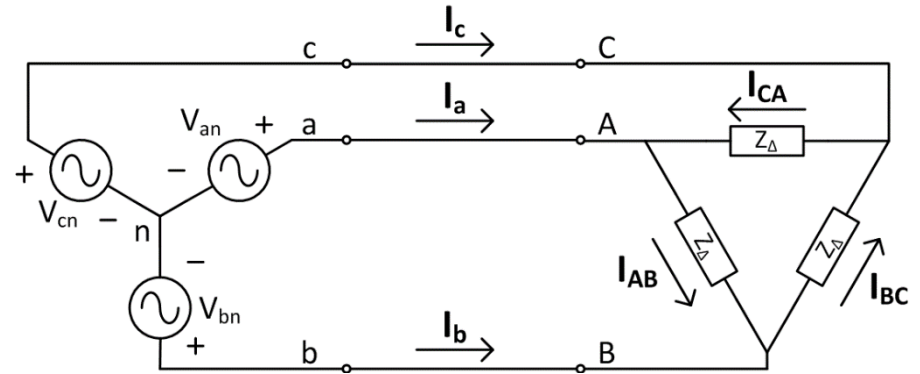- We can use line-to-line voltages to determine the currents in Δ -connected loads



$$I_{AB} = \frac{V_{AB}}{Z_{\Delta}} = \frac{\sqrt{3}V_{AN}\angle 30^{\circ}}{Z_{\Delta}} = \frac{\sqrt{3}V_{LN}\angle 30^{\circ}}{Z_{\Delta}}$$

$$I_{BC} = \frac{V_{BC}}{Z_{\Delta}} = \frac{\sqrt{3}V_{BN}\angle 30^{\circ}}{Z_{\Delta}} = \frac{\sqrt{3}V_{LN}\angle -90^{\circ}}{Z_{\Delta}}$$

$$I_{CA} = \frac{V_{CA}}{Z_{\Delta}} = \frac{\sqrt{3}V_{CN}\angle 30^{\circ}}{Z_{\Delta}} = \frac{\sqrt{3}V_{LN}\angle 150^{\circ}}{Z_{\Delta}}$$

Balanced Δ -Connected Loads


81

- Applying KCL, we can determine the line currents

$$I_a = I_{AB} - I_{CA}$$

$$I_a = \frac{\sqrt{3}V_{LN}}{Z_{\Delta}} [1\angle 30^\circ - 1\angle 150^\circ]$$
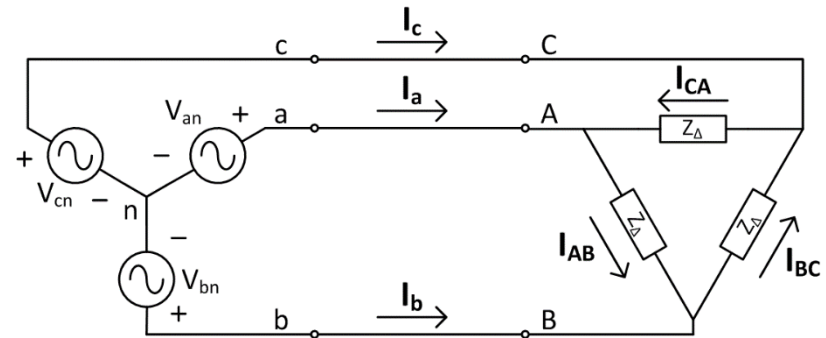
$$I_a = \frac{\sqrt{3}V_{LN}}{Z_{\Delta}} \left[\left(\frac{\sqrt{3}}{2} + j\frac{1}{2} \right) - \left(-\frac{\sqrt{3}}{2} + j\frac{1}{2} \right) \right] = \frac{\sqrt{3}V_{LN}}{Z_{\Delta}} [\sqrt{3}] = \frac{3V_{LN}}{Z_{\Delta}}$$



- The other line currents can be found similarly:

$$I_a = \frac{3V_{LN}\angle 0^\circ}{Z_{\Delta}} = \sqrt{3}I_{AB}\angle -30^\circ$$

$$I_b = \frac{3V_{LN}\angle -120^\circ}{Z_{\Delta}} = \sqrt{3}I_{BC}\angle -30^\circ$$

$$I_c = \frac{3V_{LN}\angle 120^\circ}{Z_{\Delta}} = \sqrt{3}I_{CA}\angle -30^\circ$$


82

Δ -Y Conversion

Δ – Y Conversion

83

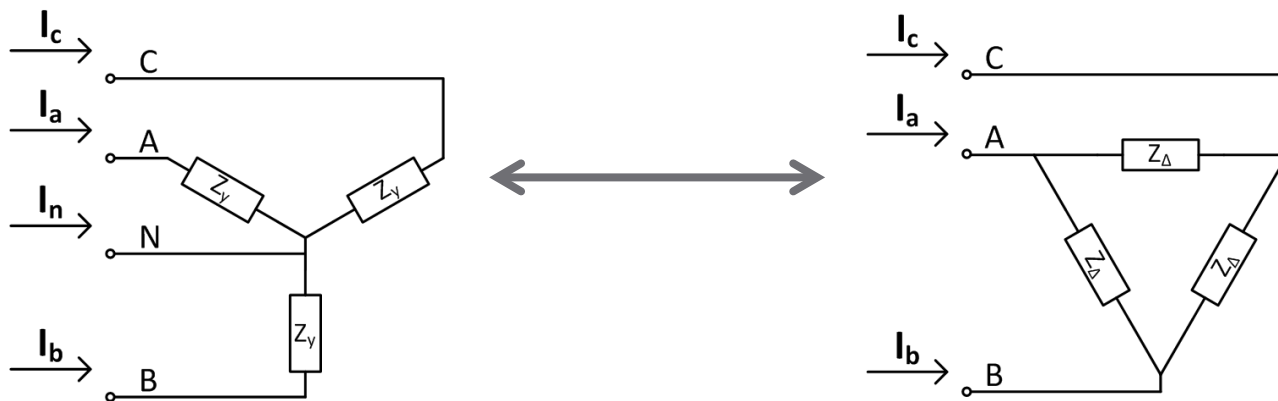- Analysis is often simpler when dealing with Y -connected loads
 - ▣ Would like a way to convert Δ loads to Y loads (and vice versa)



- For a Y load and a Δ load to be equivalent, they must result in equal line currents

$\Delta - Y$ Conversion

- Line currents for a Y -connected load:

$$I_a = \frac{V_{LN} \angle 0^\circ}{Z_Y}$$

$$I_b = \frac{V_{LN} \angle -120^\circ}{Z_Y}$$

$$I_c = \frac{V_{LN} \angle 120^\circ}{Z_Y}$$

- For a Δ -connected load:

$$I_a = \frac{3V_{LN} \angle 0^\circ}{Z_\Delta}$$

$$I_b = \frac{3V_{LN} \angle -120^\circ}{Z_\Delta}$$

$$I_c = \frac{3V_{LN} \angle 120^\circ}{Z_\Delta}$$

$\Delta - Y$ Conversion

85


- Equating any of the three line currents, we can determine the impedance relationship

$$\frac{V_{LN} \angle 0^\circ}{Z_Y} = \frac{3V_{LN} \angle 0^\circ}{Z_\Delta}$$

$$Z_Y = \frac{Z_\Delta}{3}$$

and

$$Z_\Delta = 3Z_Y$$

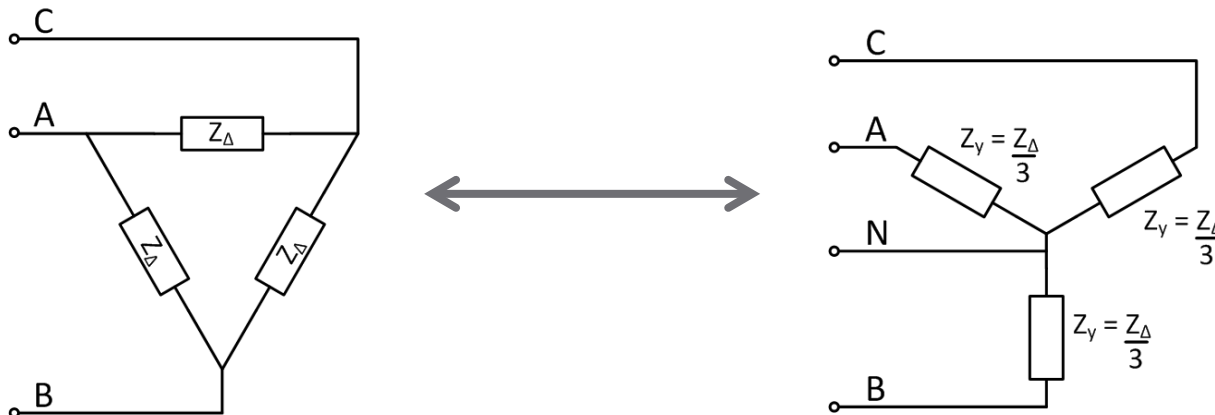


86

Per-Phase Analysis

Line-to-Neutral Schematics

87

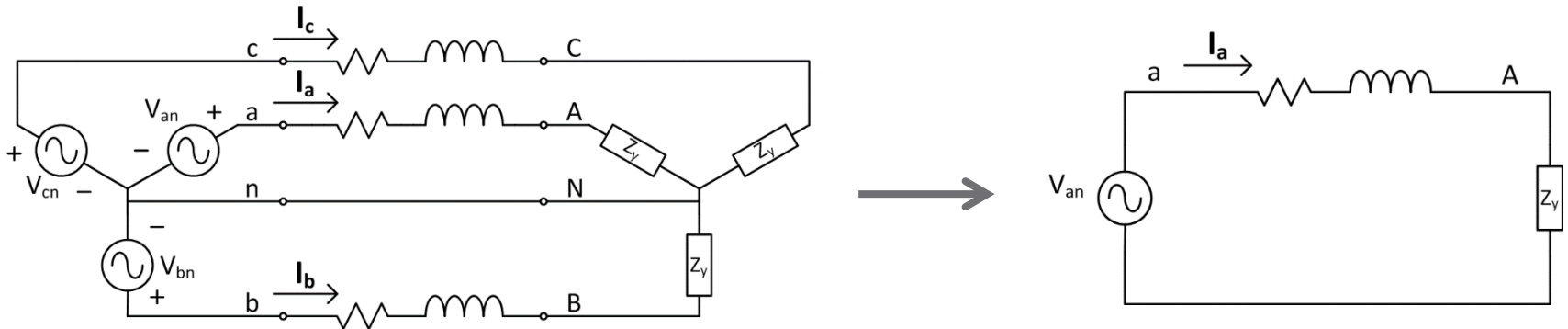
- For balanced networks, we can simplify our analysis by considering only a single phase
 - ▣ A ***per-phase analysis***
 - ▣ Other phases are simply shifted by $\pm 120^\circ$
- For example, a balanced Y - Y circuit:



One-Line Diagrams

88

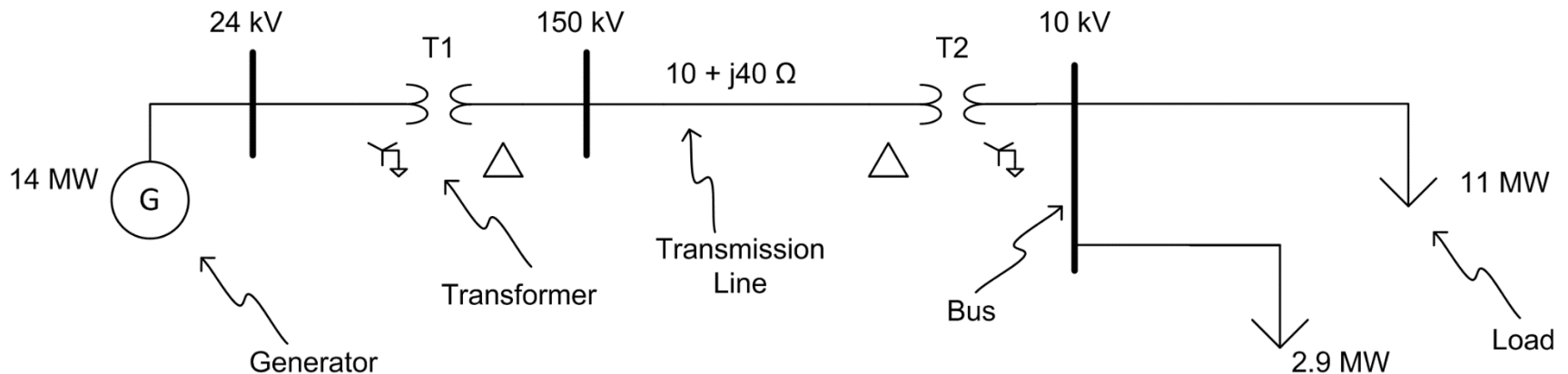- Power systems are often depicted using ***one-line diagrams*** or ***single-line diagrams***
 - ▣ Not a schematic – not all wiring is shown
- For example:



89

Example Problems

- Given the following balanced 3- ϕ quantities:

$$\mathbf{V}_{BC} = 480\angle 15^\circ \text{ and } \mathbf{I}_B = 21\angle -28^\circ$$

- Find:

1) \mathbf{V}_{AB}


2) \mathbf{V}_{AN}

3) \mathbf{I}_A

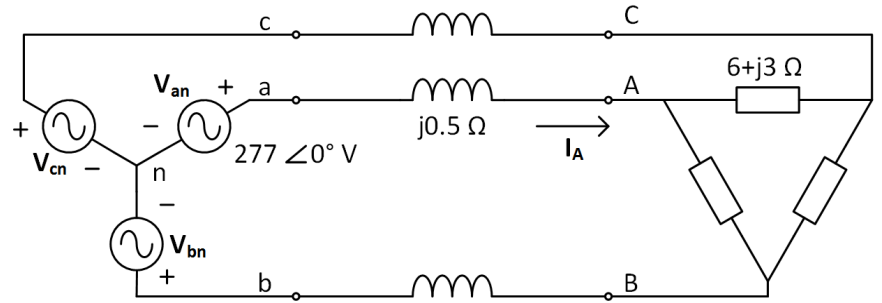4) \mathbf{I}_C


Find:

- ▣ Per-phase circuit
- ▣ Line current, I_A
- ▣ Load voltage



Find:

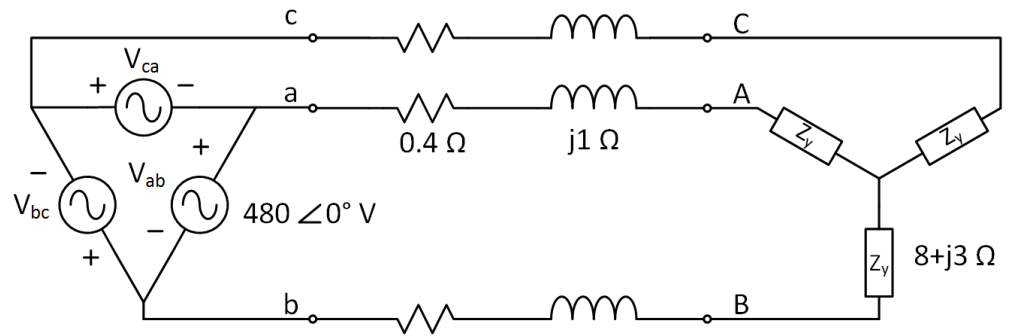- ▣ Per-phase circuit
- ▣ Line current, \mathbf{I}_A
- ▣ L-L and L-N load voltages




95

Power in Balanced 3ϕ Networks

Instantaneous Power

96

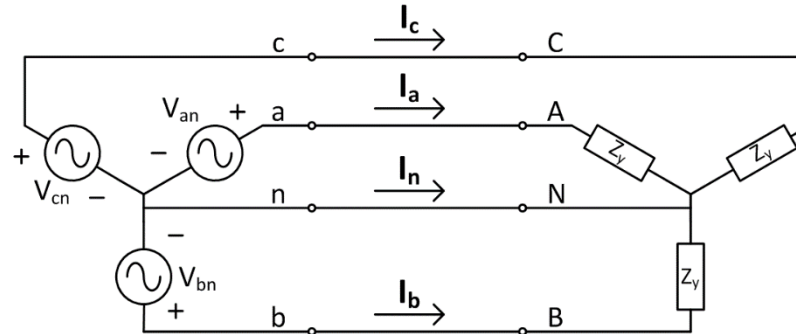

- We'll first determine the instantaneous power supplied by the source
 - ▣ Neglecting line impedance, this is also the power absorbed by the load
- The phase a line-to-neutral voltage is

$$v_{an}(t) = \sqrt{2}V_{LN} \cos(\omega t + \delta)$$

- The phase a current is

$$i_a(t) = \sqrt{2}I_L \cos(\omega t + \beta)$$

where β depends on the load impedance

Instantaneous Power

- The instantaneous power delivered out of phase a of the source is

$$p_a(t) = v_{an}(t)i_a(t)$$

$$p_a(t) = 2V_{LN}I_L \cos(\omega t + \delta) \cos(\omega t + \beta)$$

$$p_a(t) = V_{LN}I_L \cos(\delta - \beta) + V_{LN}I_L \cos(2\omega t + \delta + \beta)$$

- The b and c phases are shifted by $\pm 120^\circ$
 - ▣ Power from each of these phases is

$$p_b(t) = V_{LN}I_L \cos(\delta - \beta) + V_{LN}I_L \cos(2\omega t + \delta + \beta - 240^\circ)$$

$$p_c(t) = V_{LN}I_L \cos(\delta - \beta) + V_{LN}I_L \cos(2\omega t + \delta + \beta + 240^\circ)$$

Instantaneous Power

- The *total* power delivered by the source is the sum of the power from each phase

$$p_{3\phi}(t) = p_a(t) + p_b(t) + p_c(t)$$

$$p_{3\phi}(t) = 3V_{LN}I_L \cos(\delta - \beta) \\ + V_{LN}I_L [\cos(2\omega t + \delta + \beta) \\ + \cos(2\omega t + \delta + \beta - 240^\circ) \\ + \cos(2\omega t + \delta + \beta + 240^\circ)]$$

- Everything in the square brackets cancels, leaving

$$p_{3\phi}(t) = 3V_{LN}I_L \cos(\delta - \beta) = P_{3\phi}$$

- **Power in a balanced 3 ϕ network is constant**
- In terms of line-to-line voltages, the power is

$$P_{3\phi} = \sqrt{3}V_{LL}I_L \cos(\delta - \beta)$$

Complex Power

99

- The **complex power** delivered by phase a is

$$\mathbf{S}_a = \mathbf{V}_{an}\mathbf{I}_a^* = V_{LN}\angle\delta(I_L\angle\beta)^*$$

$$\mathbf{S}_a = V_{LN}I_L\angle(\delta - \beta)$$

$$\mathbf{S}_a = V_{LN}I_L \cos(\delta - \beta) + jV_{LN}I_L \sin(\delta - \beta)$$

- For phase b , complex power is

$$\mathbf{S}_b = \mathbf{V}_{bn}\mathbf{I}_b^* = V_{LN}\angle(\delta - 120^\circ)(I_L\angle(\beta - 120^\circ))^*$$

$$\mathbf{S}_b = V_{LN}I_L\angle(\delta - \beta)$$

$$\mathbf{S}_b = V_{LN}I_L \cos(\delta - \beta) + jV_{LN}I_L \sin(\delta - \beta)$$

- This is equal to \mathbf{S}_a and also to phase \mathbf{S}_c

Complex Power

100

- The ***total complex power*** is

$$S_{3\phi} = S_a + S_b + S_c$$

$$S_{3\phi} = 3V_{LN}I_L \angle(\delta - \beta)$$

$$S_{3\phi} = 3V_{LN}I_L \cos(\delta - \beta) + j3V_{LN}I_L \sin(\delta - \beta)$$

- The ***apparent power*** is the magnitude of the complex power

$$S_{3\phi} = 3V_{LN}I_L$$

Complex Power

101

- Complex power can be expressed in terms of the real and reactive power

$$\mathbf{S}_{3\phi} = P_{3\phi} + jQ_{3\phi}$$

- The **real power**, as we've already seen is

$$P_{3\phi} = 3V_{LN}I_L \cos(\delta - \beta)$$

- The **reactive power** is

$$Q_{3\phi} = 3V_{LN}I_L \sin(\delta - \beta)$$


Advantages of Three-Phase Power

102

- Advantages of three-phase power:
 - For a given amount of power, ***half the amount of wire required*** compared to single-phase
 - No return current on neutral conductor
 - ***Constant real power***
 - Constant motor torque
 - Less noise and vibration of machinery

Three-Phase Power – Example

103

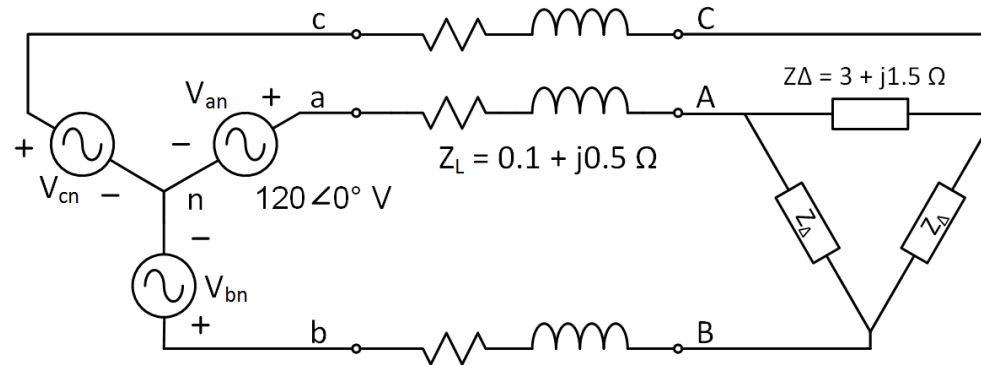

- Determine
 - ▣ Load voltage, V_{AB}
 - ▣ Power triangle for the load
 - ▣ Power factor at the load


- We'll do a per-phase analysis, so first convert the Δ load to a Y load

$$Z_Y = \frac{Z_{\Delta}}{3} = 1 + j0.5 \Omega$$

Three-Phase Power – Example

104

- The per-phase circuit:

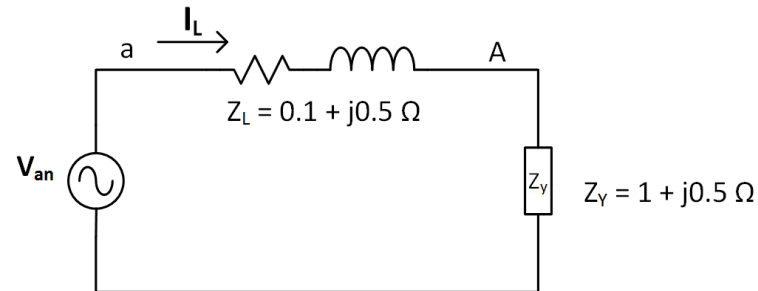

- The line current is

$$I_L = \frac{V_{an}}{Z_L + Z_Y} = \frac{120 \angle 0^\circ V}{1.1 + j1 \Omega} = \frac{120 \angle 0^\circ V}{1.45 \angle 42.3^\circ \Omega}$$

$$I_L = 80.7 \angle -42.3^\circ A$$

- The line-to-neutral voltage at the load is

$$V_{AN} = I_L Z_Y = (80.7 \angle -42.3^\circ A)(1 + j0.5 \Omega)$$

$$V_{AN} = (80.7 \angle -42.3^\circ A)(1.12 \angle 26.6^\circ \Omega)$$

$$V_{AN} = 90.25 \angle -15.71^\circ V$$

Three-Phase Power – Example

105

- The line-to-line load voltage is

$$V_{AB} = \sqrt{3}V_{AN}\angle 30^\circ$$

$$V_{AB} = 156\angle 14.3^\circ V$$

- Alternatively, we could calculate line-to-line voltage from phase A and phase B line-to-neutral voltages

$$V_{AB} = V_{AN} - V_{BN}$$

$$V_{AB} = 90.25\angle -15.71^\circ V - 90.25\angle -135.71^\circ V$$

$$V_{AB} = 156\angle 14.3^\circ V$$

Three-Phase Power – Example

106

- The complex power absorbed by the load is

$$\mathbf{S}_{3\phi} = 3\mathbf{S}_A = 3V_{AN}I_L^*$$

$$\mathbf{S}_{3\phi} = 3(90.25\angle -15.71^\circ V)(80.7\angle -42.3^\circ A)^*$$

$$\mathbf{S}_{3\phi} = 21.85 \angle 26.6^\circ \text{ kVA}$$

$$\mathbf{S}_{3\phi} = 19.53 + j9.78 \text{ kVA}$$

- The apparent power:

$$S_{3\phi} = 21.85 \text{ kVA}$$

- Real power:

$$P = 19.53 \text{ kW}$$


- Reactive power:

$$Q = 9.78 \text{ kvar}$$

Three-Phase Power – Example

107

- The power triangle at the load:

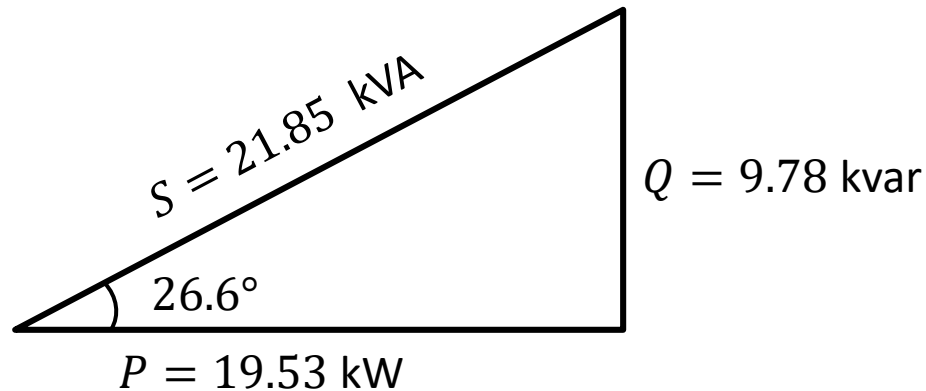

- The power factor at the load is

$$p.f. = \cos(26.6^\circ) = \frac{P}{S} = \frac{19.53 \text{ kW}}{21.85 \text{ kVA}}$$


$$p.f. = 0.89 \text{ lagging}$$

108

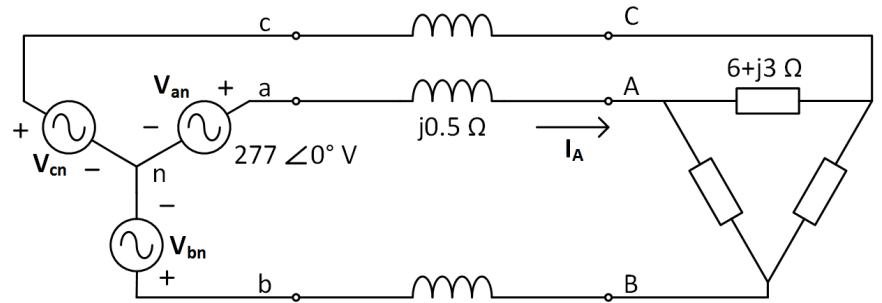Example Problems

Find:

- ▣ Source power
- ▣ Source power factor
- ▣ Load power
- ▣ Load power factor



Find:

- ▣ Source power
- ▣ Load power
- ▣ Power *lost* in lines

