

# SECTION 3: POWER TRANSFORMERS

ESE 470 – Energy Distribution Systems


# Power Transformers

2

- Transformers are used throughout the electrical grid
  - Step voltages up and down for transmission, distribution, and consumption
  - Located at power stations, substations, along distribution feeders, and at industrial customers



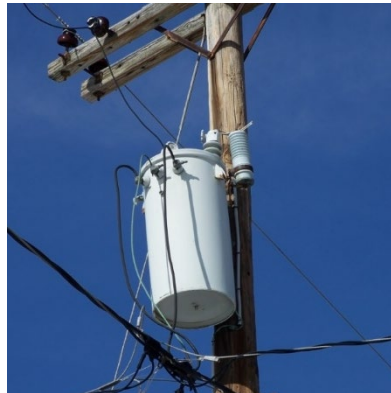[www.exportersindia.com](http://www.exportersindia.com)



- We'll first review the fundamentals of ideal transformers, then look at how we can model real transformers for analysis within the electrical grid


3

# Ideal Transformers
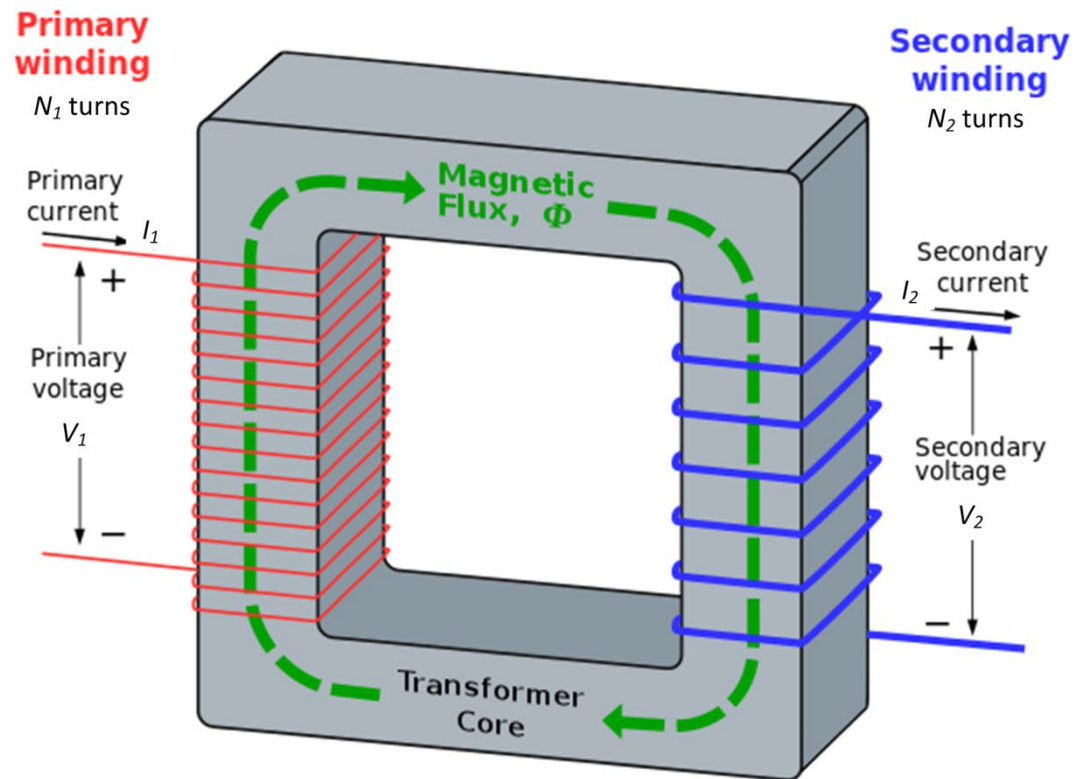
# Ideal Transformers

4

- A single-phase transformer consists of two coils of wire wound around a magnetic core
- Used for **stepping voltages up or down**
  - ▣ Stepped up for transmission
  - ▣ Stepped down for distribution and consumption
- To understand transformers, we must review two laws of electromagnetics
  - ▣ Ampere's law
  - ▣ Faraday's law



# Ampere's Law


5

- Electrical current flowing through a wire generates a magnetic field encircling that wire
- Direction of field given by right-hand rule
  - ▣ Thumb points in direction of current
  - ▣ Fingers curl in direction of field

- **Ampere's law**

$$\oint \mathbf{H} \cdot d\mathbf{l} = \frac{1}{\mu} \oint \mathbf{B} \cdot d\mathbf{l} = I \quad (1)$$

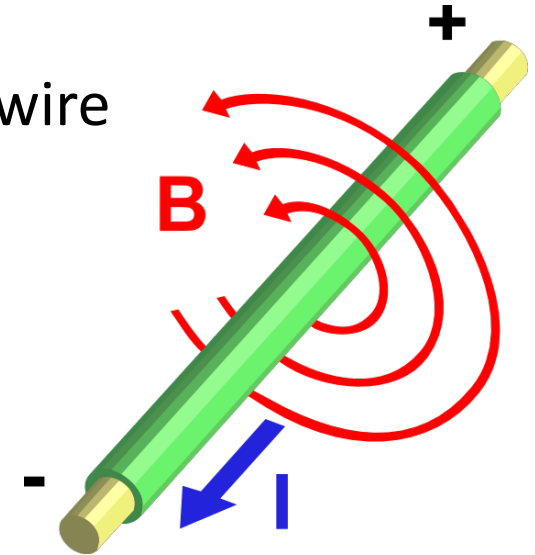- ▣  $\mathbf{H}$  is the magnetic field intensity,  $\mathbf{B}$  is the magnetic flux density,  $\mu$  is permeability, and  $I$  is current
- Ampere's law says:
  - ▣ *Integrating the magnetic field around a closed contour gives the total current enclosed by that contour*



# Faraday's Law

6


- A time-varying magnetic flux through a loop or coil of wire will produce a voltage across that loop or coil
- **Faraday's law** gives the voltage produced across an  $N$ -turn coil

$$v(t) = -N \frac{d\phi}{dt} \quad (2)$$

- $\phi$  is the magnetic flux penetrating the coil:

$$\phi = B \cdot A \quad (3)$$

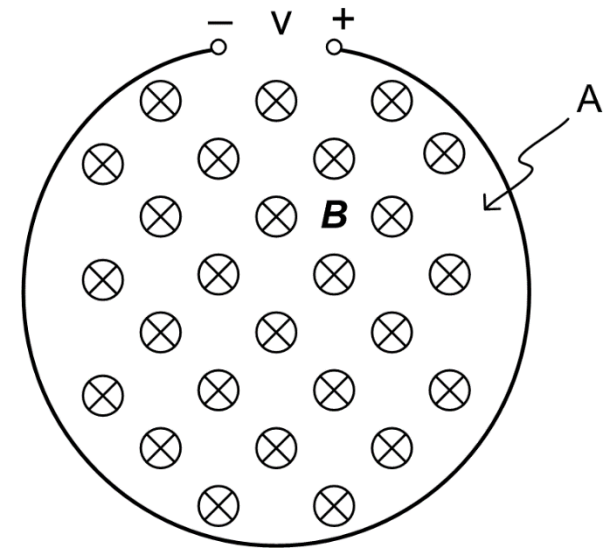where  $A$  is the cross-sectional area of the coil




# Lenz's Law

7

$$v(t) = -N \frac{d\phi}{dt}$$

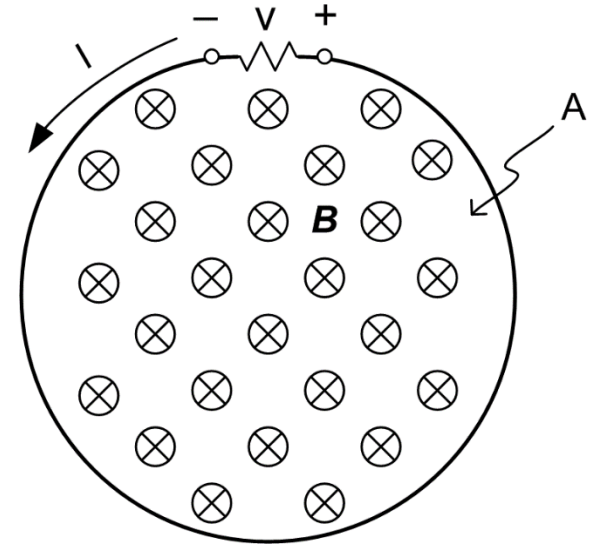
- The negative sign in Faraday's law gives the voltage polarity
  - ▣ Close the loop with an external resistance
  - ▣ Current flows and generates a magnetic field
  - ▣ Magnetic field opposes the original change in magnetic flux
  
- This is ***Lenz's law***
  
- Often see Faraday's law written without the negative sign


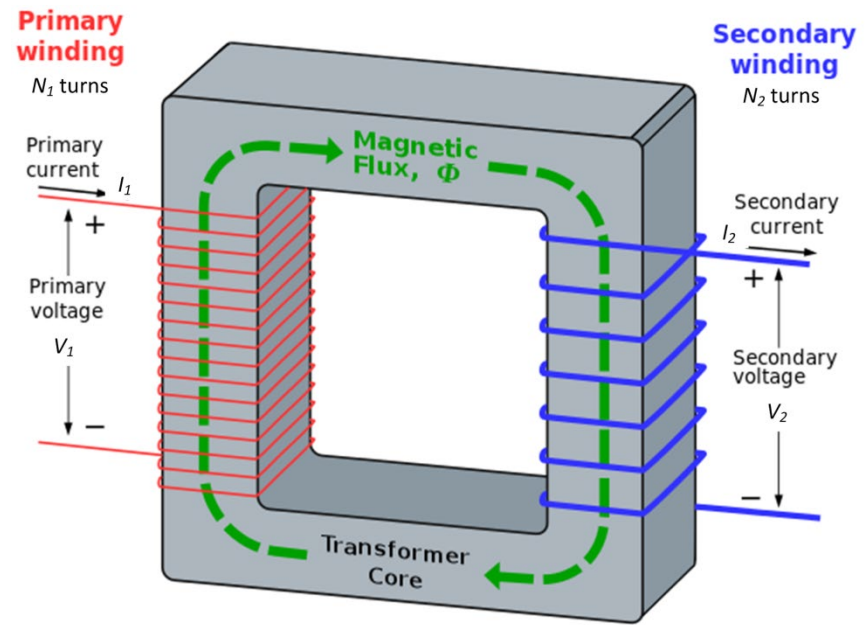
# Ideal Transformers

8

- Current flow in the primary winding generates a magnetic flux in the core
  - ▣ Ampere's law
- Flux in the core penetrates the secondary winding
- If that flux is time-varying, a voltage is induced across the secondary
  - ▣ Faraday's law





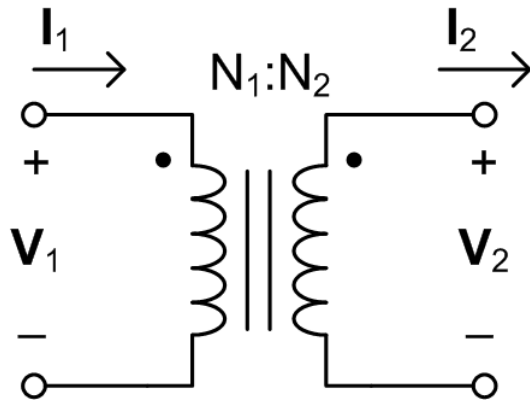
# Ideal Transformers

9

- For ***ideal transformers***, we assume the following:
  1. Windings have zero resistance – no losses in windings
  2. Permeability of the core is infinite,  $\mu = \infty$ , and the reluctance of the core is zero,  $R = 0$
  3. All flux is entirely confined to the core – no *leakage flux*
  4. No core losses – no *hysteresis* or *eddy currents*



- Dots on symbol indicate polarity
  - ▣ Current enters one dotted terminal, current leaves the other
  - ▣ Positive voltage at one dotted terminal, positive voltage at the other

10

# Transformer Current Relationships

# Ideal Transformers – Current Relationships

11

- Evaluate Ampere's law around a closed contour,  $C$ 
  - ▣ Through center of core
  - ▣ Length  $l$
  - ▣ Everywhere tangential to the  $H$ -field


$$\oint \mathbf{H} \cdot d\mathbf{l} = I$$

- The magnetic field is tangential to  $C$ , so

$$\oint \mathbf{H} \cdot d\mathbf{l} = Hl \tag{4}$$

- Contour encloses  $N_1$  turns of the primary winding and  $N_2$  turns of the secondary in the opposite direction
  - ▣ Total enclosed current:

$$I = N_1 I_1 - N_2 I_2 \tag{5}$$

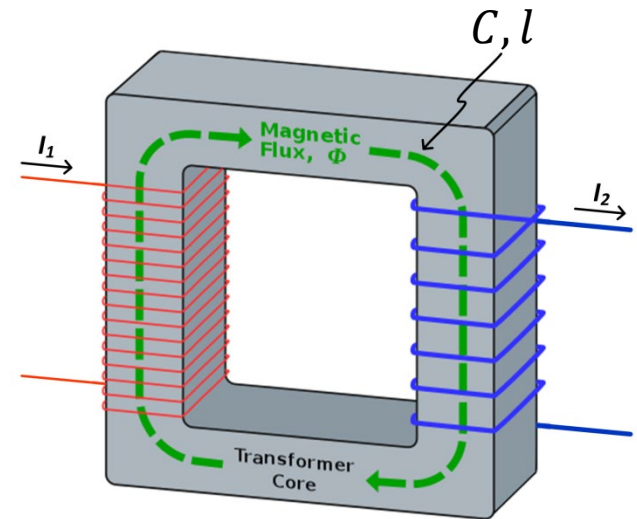

# Ideal Transformers – Current Relationships

12

- Ampere's law gives us

$$\mathbf{H}l = N_1\mathbf{I}_1 - N_2\mathbf{I}_2 \quad (6)$$

- We can relate magnetic field intensity to flux density

$$\mathbf{H} = \frac{\mathbf{B}}{\mu} \quad (7)$$

- And, multiplying by the cross-sectional area of the core, we get the flux


$$\Phi = \mathbf{B}A = \mu\mathbf{H}A \rightarrow \mathbf{H} = \frac{\Phi}{\mu A} \quad (8)$$

- Substituting (8) into (6), we have

$$\left(\frac{l}{\mu A}\right)\Phi = N_1\mathbf{I}_1 - N_2\mathbf{I}_2 \quad (9)$$

- The term in parentheses is the **reluctance** of the core
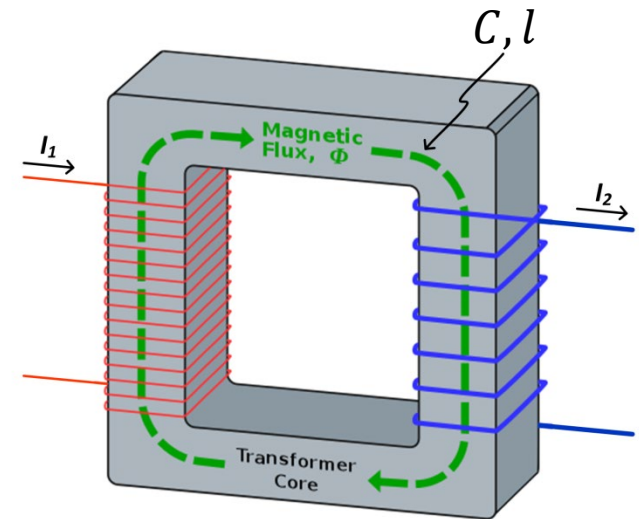
$$R = \left(\frac{l}{\mu A}\right) \quad (10)$$



# Ideal Transformers – Current Relationships

13

- Using (10) in (9) gives

$$N_1 \mathbf{I}_1 - N_2 \mathbf{I}_2 = R \Phi \quad (11)$$

- Recall that, for an ideal transformer,  $R = 0$ , so

$$N_1 \mathbf{I}_1 = N_2 \mathbf{I}_2 \quad (12)$$

or

$$\mathbf{I}_1 = \frac{N_2}{N_1} \mathbf{I}_2 \quad \text{and} \quad \mathbf{I}_2 = \frac{N_1}{N_2} \mathbf{I}_1 \quad (13)$$

- We define the **turns ratio** as the ratio of the number of turns on the primary winding to the number of turns on the secondary winding

$$a_t = \frac{N_1}{N_2} \quad (14)$$

- Using the turns ratio, the current relationships are

$$\mathbf{I}_1 = \frac{1}{a_t} \mathbf{I}_2 \quad \text{and} \quad \mathbf{I}_2 = a_t \mathbf{I}_1 \quad (15)$$

14

# Transformer Voltage Relationships

# Ideal Transformers – Voltage Relationships

15

- Faraday's law relates the voltage at each winding to the flux through that winding

$$V_1 = -N_1 \frac{d\Phi}{dt} \quad \text{and} \quad V_2 = -N_2 \frac{d\Phi}{dt} \quad (16, 17)$$

- Dividing the (16) by (17) gives

$$\frac{V_1}{V_2} = \frac{N_1}{N_2}$$

So,

$$V_1 = a_t V_2 \quad \text{and} \quad V_2 = \frac{1}{a_t} V_1 \quad (18)$$

# Ideal Transformers

16

- To summarize current and voltage relationships:

$$I_2 = a_t I_1 \quad (15)$$

$$V_2 = \frac{1}{a_t} V_1 \quad (18)$$

- ***Step-up transformer***

- $a_t < 1, N_1 < N_2$
- Voltage increases from primary to secondary
- Current decreases

- ***Step-down transformer***

- $a_t > 1, N_1 > N_2$
- Voltage decreases from primary to secondary
- Current increases



17

# Transformer Power & Impedance

# Ideal Transformers - Power

18

- The complex power entering the primary side of the transformer is

$$\mathbf{S}_1 = \mathbf{V}_1 \mathbf{I}_1^* \quad (19)$$

- And, the complex power delivered out of the secondary side is

$$\mathbf{S}_2 = \mathbf{V}_2 \mathbf{I}_2^* \quad (20)$$

- Using the transformer voltage and current relationships, (19) becomes

$$\mathbf{S}_1 = a_t \mathbf{V}_2 \frac{1}{a_t} \mathbf{I}_2^* = \mathbf{V}_2 \mathbf{I}_2^* = \mathbf{S}_2$$


- We see that power is conserved in an ideal transformer
  - ▣ As expected, since we've assumed there are no losses

# Ideal Transformers - Impedance

19

- By definition, the impedance seen looking into the primary side of a transformer is

$$Z_{in} = \frac{V_1}{I_1} \quad (21)$$

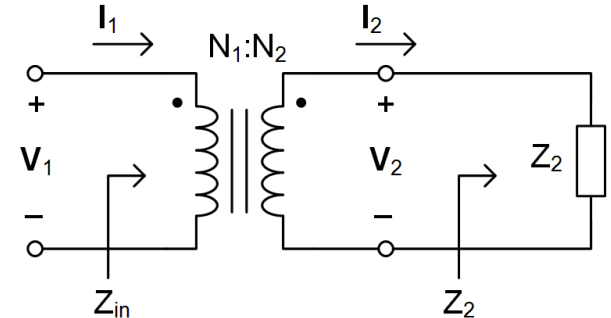

- An impedance  $Z_2$ , connected to the secondary side dictates

$$Z_2 = \frac{V_2}{I_2} \quad (22)$$

- Using the  $I/V$  relationships, we get

$$Z_{in} = \frac{a_t V_2}{1/a_t I_2} = a_t^2 \frac{V_2}{I_2} = a_t^2 Z_2$$

$$\boxed{Z_{in} = a_t^2 Z_2 = Z'_2} \quad (23)$$

- The impedance seen looking into the primary side of a transformer is the impedance connected to the secondary side multiplied by the turns ratio squared
  - The **reflected load impedance**

20

# Real Transformer Models

# Real Transformers


21

- In practice, transformers are not ideal
  - ▣ Winding losses
  - ▣ Leakage flux
  - ▣ Finite core permeability – non-zero reluctance
  - ▣ Core losses
  
- Need an ***equivalent circuit model*** to account for these non-idealities
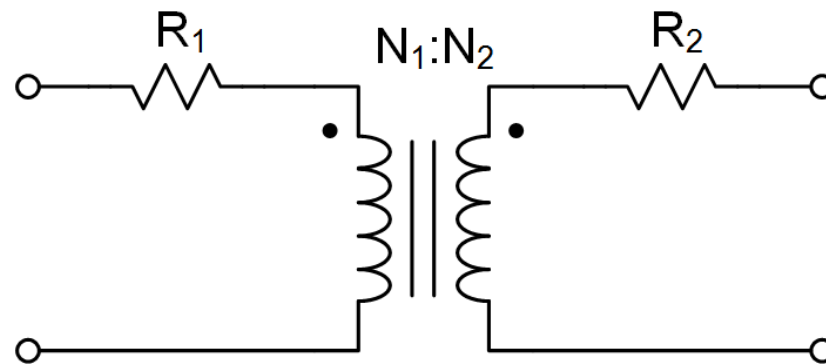
# Winding Losses

22


- Wires of the primary and secondary windings have non-zero resistance
  - ▣ Results in losses in the windings
  - ▣ Add series resistance to each side of the ideal transformer model


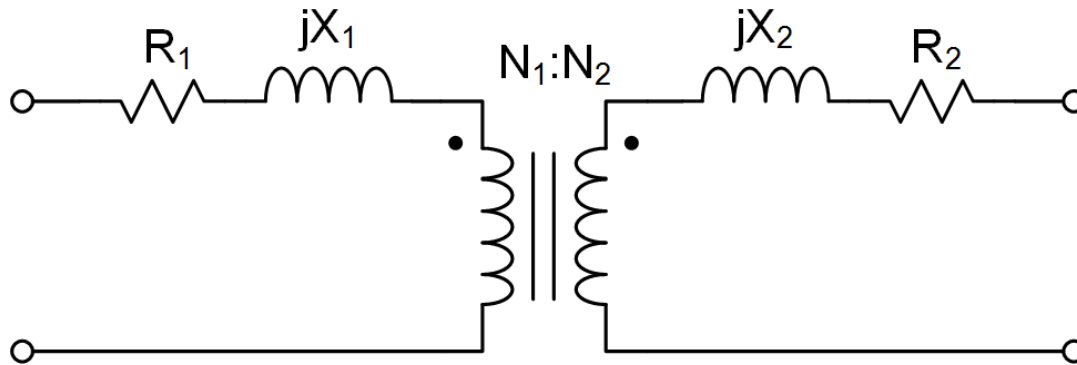
# Leakage Flux

23

- Not all flux generated by the primary side links the secondary winding
  - ▣ **Leakage flux**
- Results in a voltage drop that leads the current by  $90^\circ$ 
  - ▣ Winding inductance



# Finite Core Permeability

24

- Going back to (11), we have

$$N_1 \mathbf{I}_1 - N_2 \mathbf{I}_2 = R \Phi \quad (11)$$

where we'll now account for non-zero reluctance

- Faraday's law in phasor form tells us

$$\mathbf{V} = N j \omega \Phi$$

so

$$\Phi = \frac{\mathbf{V}}{N j \omega} \quad (23)$$

- Substituting (23) into (11) we have

$$N_1 \mathbf{I}_1 - N_2 \mathbf{I}_2 = -j R \frac{\mathbf{V}_1}{N_1 \omega}$$

$$\mathbf{I}_1 - \frac{N_2}{N_1} \mathbf{I}_2 = -j \frac{R}{N_1^2 \omega} \mathbf{V}_1$$




# Finite Core Permeability

25

$$I_1 - \frac{N_2}{N_1} I_2 = -j \frac{R}{N_1^2 \omega} V_1 \quad (24)$$

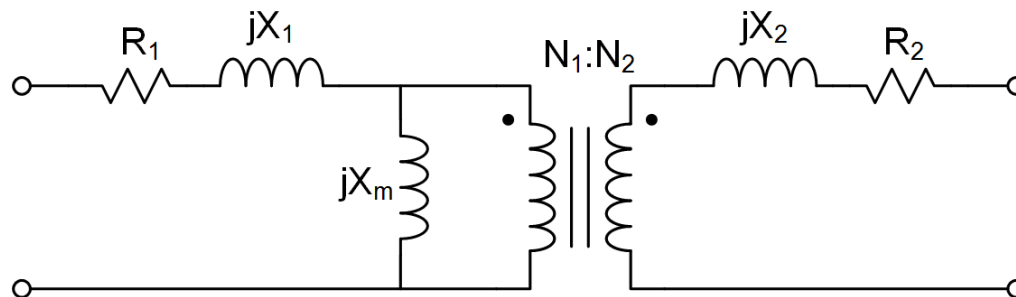
- These are all *currents*
- The term on the right-hand side is the ***magnetizing current***
  - ▣ Due to non-zero reluctance
  - ▣ *Lags*  $V_1$  by  $90^\circ$
  - ▣ Model as a ***shunt inductor***


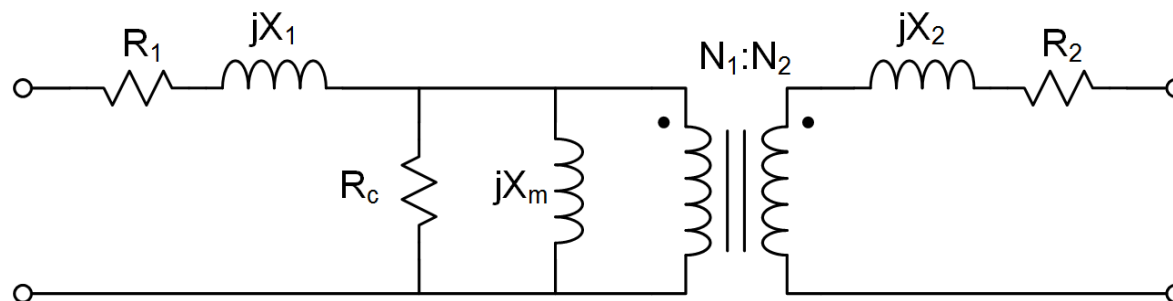
# Core Losses

26

- In addition to losses in the windings, real transformers have losses in the core
  - ▣ Hysteresis in the  $B/H$  relationship
  - ▣ Eddy currents
- Modeled as ***shunt resistance*** on the primary side,  $R_m$




- ***Laminated cores*** are used to limit eddy current losses

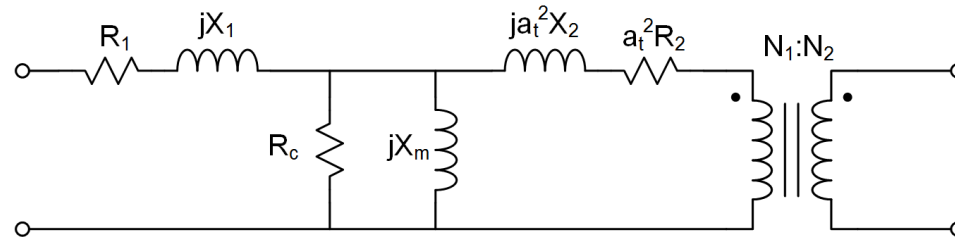
# Real Transformer Model

27

- The model can be simplified by referring the secondary-side impedances to the primary side



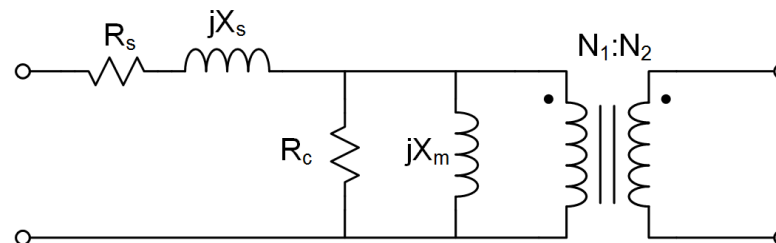- We can make a further simplifying approximation by combining series impedances



- The transformers themselves in these models are *ideal*


28

# Identifying Model Parameters
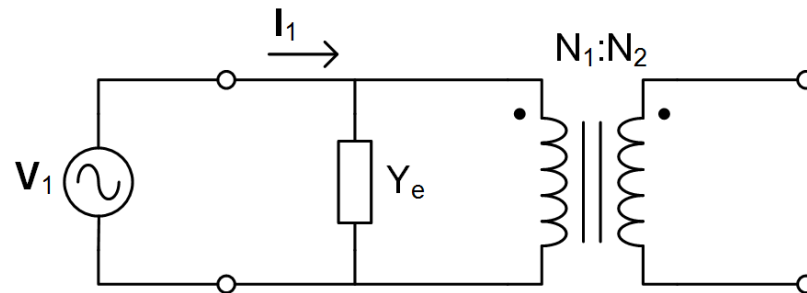
# Identifying Model Parameters

29

- Open-circuit test
  - ▣ Rated voltage applied to the primary
  - ▣ Secondary is open – no load
  - ▣ Measure current and power loss at the primary
  - ▣ Neglect series impedances



- Here,  $Y_e$  is the excitation current admittance

$$Y_e = \frac{1}{R_c} + \frac{1}{jX_m} = G_c - jB_m$$

# Open-Circuit Test

30

- Measuring the primary-side voltage and current allows for calculation of the *magnitude* of the excitation admittance

$$|Y_e| = \frac{I_{1,oc}}{V_{1,oc}} = |G_c - jB_m|$$

- Measured power loss allows for calculation of  $G_c$

$$G_c = \frac{P_{oc}}{V_{1,oc}^2}$$


- Finally, calculate  $B_m$  from  $|Y_e|$  and  $G_c$

$$B_m = \sqrt{|Y_e|^2 - G_c^2}$$
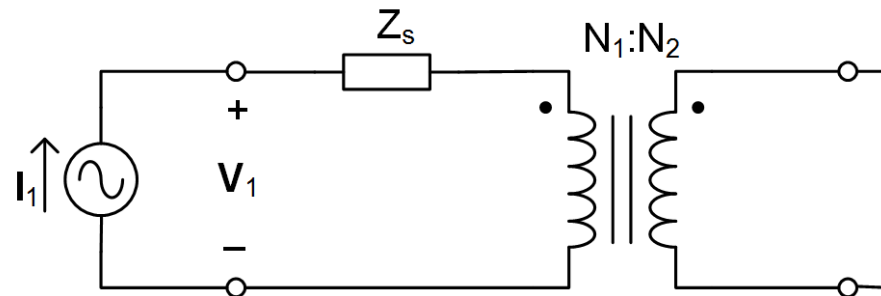
# Short-Circuit Test

31

- Short-circuit test
  - ▣ Rated *current* applied at the primary side
  - ▣ Secondary side is shorted
  - ▣ Measure voltage and power loss at the primary side
  - ▣ Neglect shunt admittance



- Here,  $Z_s$  is the equivalent *series* impedance

$$Z_s = R_s + jX_s$$

# Short-Circuit Test

32

- Determine  $|Z_s|$  from the measured primary-side voltage and current

$$|Z_s| = \frac{V_{1,sc}}{I_{1,sc}} = |R_s + jX_s|$$

- Use the power loss measurement to determine  $R_s$

$$R_s = \frac{P_{sc}}{I_{1,sc}^2}$$


- Finally, calculate  $X_s$  from  $|Z_s|$  and  $R_s$

$$X_s = \sqrt{|Z_s|^2 - R_s^2}$$



# Transformer Model – Example


33

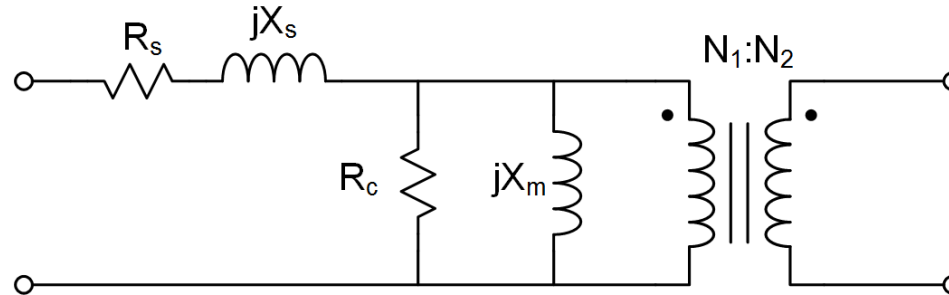

- A single-phase, 100 kVA, 480/120 V transformer is subjected to short-circuit and open-circuit tests to determine model parameters
- The results:
  - Open circuit:  $I_{1,oc} = 0.05 \text{ A}$  ,  $P_{oc} = 0.1 \text{ W}$
  - Short circuit:  $V_{1,sc} = 80 \text{ V}$  ,  $P_{sc} = 10 \text{ kW}$
- Determine model parameters:  $R_s$ ,  $X_s$ ,  $R_c$ , and  $X_m$

# Transformer Model – Example

34

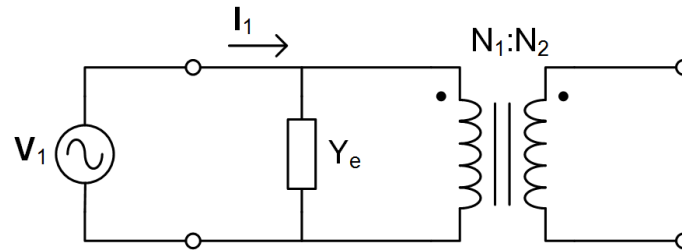

- From the open-circuit test:

$$|Y_e| = \frac{I_{1,oc}}{V_{1,oc}} = \frac{0.05 \text{ A}}{480 \text{ V}} = 104 \mu\text{S}$$

$$G_c = \frac{P_{oc}}{V_{1,oc}^2} = \frac{0.1 \text{ W}}{(480 \text{ V})^2} = 434 \text{ nS}$$

$$B_m = \sqrt{|Y_e|^2 - G_c^2} = 104 \mu\text{S}$$


$$R_c = \frac{1}{G_c} = 2.3 \text{ M}\Omega$$

and

$$X_m = \frac{1}{B_m} = 9.62 \text{ k}\Omega$$

# Transformer Model – Example

35

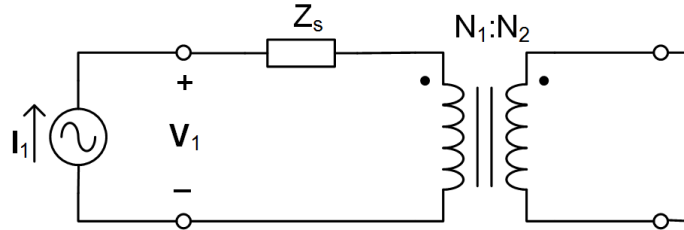

- From the short-circuit test:

$$|Z_s| = \frac{V_{1,sc}}{I_{1,sc}} = \frac{V_{1,sc}}{I_{1,rated}}$$

- Here, the applied current is the *rated current*
  - ▣ Determine from the nameplate power rating

$$I_{1,rated} = \frac{S_{rated}}{V_{1,rated}} = \frac{100 \text{ kVA}}{480 \text{ V}} = 208.3 \text{ A}$$

- The magnitude of the series impedance is

$$|Z_s| = \frac{80 \text{ V}}{208.3 \text{ A}} = 384 \text{ m}\Omega$$

# Transformer Model – Example

36


- Using the measured power and primary-side current, we can calculate series resistance

$$R_s = \frac{P_{1,sc}}{I_{1,sc}^2} = \frac{10 \text{ kW}}{(208 \text{ A})^2} = 230 \text{ m}\Omega$$

- The equivalent series reactance is

$$X_s = \sqrt{|Z_s|^2 - R_s^2} = 307 \text{ m}\Omega$$

- The equivalent circuit model is:

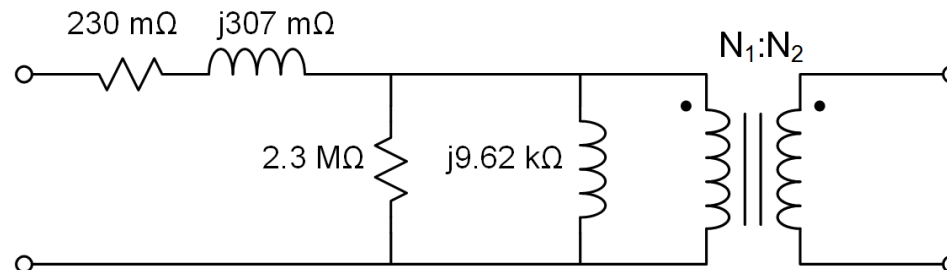

37

# The Per-Unit System

# The Per-Unit System

38

- Power systems contain many, many transformers
- System analysis would require always referring impedances from one side of transformers to the other
  - ▣ Tedious and error prone
- Instead, we use a system of normalized voltages, currents, power, and impedance
  - ▣ The ***per-unit system***
- In per-unit, all quantities are normalized by base values – for example:


$$V_{pu} = \frac{V}{V_{base}} \quad (1)$$

- The selected base values are all related by transformer turns ratios
  - ▣ ***Transformers are eliminated*** from the per-unit schematic

# The Per-Unit System - Preview

39


□ Initial schematic:

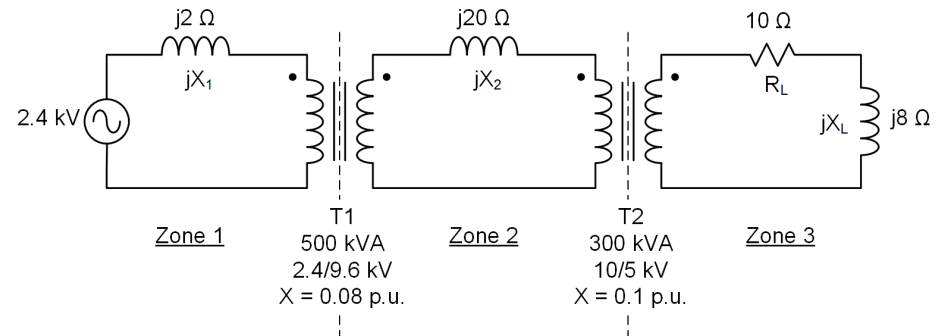

□ Per-unit schematic:

■ Transformers have been eliminated

■ All values are in per-unit (p.u.)

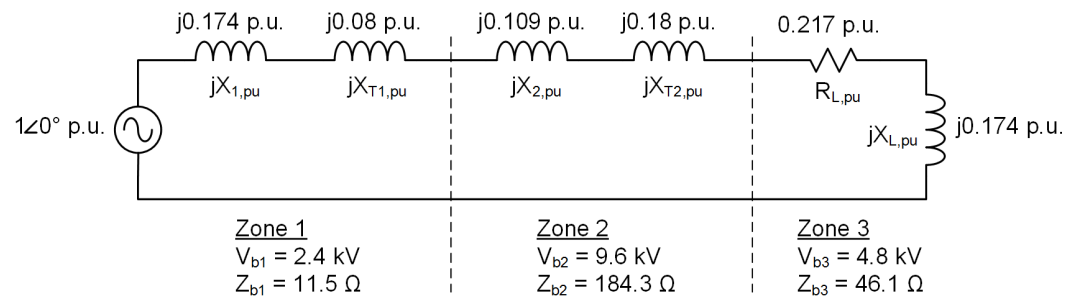

□ To understand how to interpret per-unit schematics, we'll see how to convert both single- and three-phase circuits to per-unit

# Per-Unit Conversion – Single-Phase

40

- To convert a single-phase circuit to per-unit:
  1. Re-draw the circuit
    - Eliminate all transformers
    - Clearly delineate voltage zones, as defined by the transformers
    - Do not label any numerical voltage, current, impedance, or power values
  2. Select a single power base value,  $S_b = P_b = Q_b$
  3. Select a voltage base,  $V_b$ , for each voltage level
    - Must be related by transformer turns ratios
  4. Calculate the impedance base at each voltage level

$$Z_b = \frac{V_b^2}{S_b} = R_b = X_b \quad (2)$$

5. Calculate the current base at each voltage level

$$I_b = \frac{V_b}{Z_b} = \frac{S_b}{V_b} \quad (3)$$

6. Convert all actual values to per-unit values




# Transformer Base Impedance

41

- Transformer impedances are typically specified in per-unit or as percent of base impedance values

- For example:

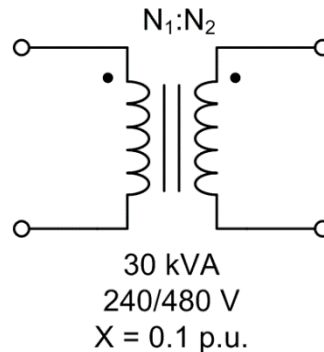

- Here, the reactance accounting for leakage flux (series inductance) is specified
  - 10% of base impedance value for the transformer
- Base impedance given by nameplate voltage and power ratings
- At the primary side

$$Z_{b1} = \frac{V_{b1}^2}{S_b} = \frac{(240 \text{ V})^2}{30 \text{ kVA}} = 1.92 \Omega$$

# Transformer Impedance

42

- Per-unit reactance is calculated from actual reactance as

$$X_{pu} = \frac{X}{Z_b}$$

- So the actual leakage reactance is

$$X = X_{pu} \cdot Z_b = 0.1 \cdot 1.92 \Omega = 192 \text{ m}\Omega$$

- The per-unit leakage reactance is specified on the base dictated by the transformer's nameplate ratings
  - System base voltages and impedances at primary and secondary side may differ from the intrinsic transformer base
  - Per-unit reactance can be **converted to a new base** when necessary

# Per-Unit Base Conversion

43

- Convert an old per-unit reactance,  $X_{pu,old}$ , to a per-unit reactance on a new base,  $X_{pu,new}$

$$X_{pu,new} = \frac{X}{Z_{b,new}} = X \frac{S_{b,new}}{V_{b,new}^2} \quad (4)$$

- We know we can express the actual reactance as

$$X = X_{pu,old} \cdot Z_{b,old} = X_{pu,old} \left( \frac{V_{b,old}^2}{S_{b,old}} \right) \quad (5)$$

- Substituting (5) into (4)


$$X_{pu,new} = X_{pu,old} \left( \frac{V_{b,old}^2}{S_{b,old}} \right) \left( \frac{S_{b,new}}{V_{b,new}^2} \right)$$

- This provides a general formula for converting from one base to another

$$Z_{pu,new} = Z_{pu,old} \left( \frac{V_{b,old}^2}{S_{b,old}} \right) \left( \frac{S_{b,new}}{V_{b,new}^2} \right) \quad (6)$$

# Single-Phase Per-Unit Conversion – Example

44

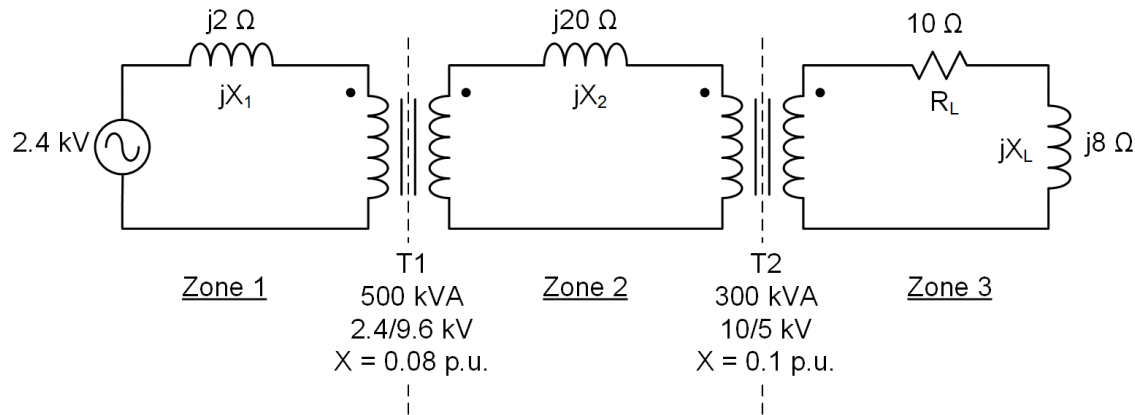


- Convert the circuit above to a per-unit circuit
  - Note that transformer reactances are already specified as per-unit values
  - Three zones – three voltage bases
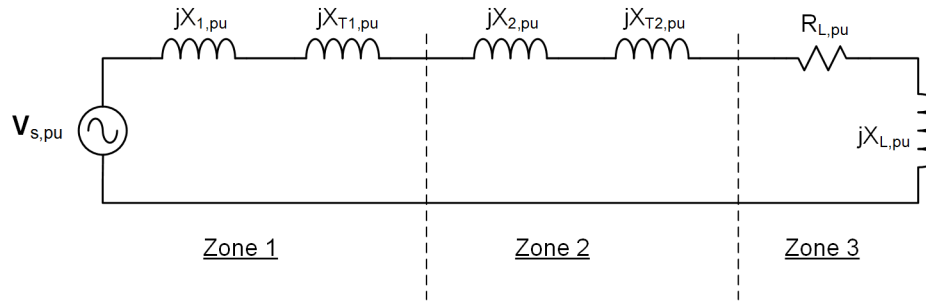
# Single-Phase Per-Unit Conversion – Example

45

- First, re-draw the schematic in per-unit form



- We'll fill in the various per-unit values as we calculate them
- Next, arbitrarily select a single power base for the network

$$S_b = 500 \text{ kVA}$$

# Single-Phase Per-Unit Conversion – Example

46

- Next, select a voltage base and calculate impedance and current base values for each voltage level

- ▣ Zone 1:

$$V_{b1} = 2.4 \text{ kV}$$

$$Z_{b1} = \frac{V_{b1}^2}{S_b} = \frac{(2.4 \text{ kV})^2}{500 \text{ kVA}} = 11.5 \Omega$$

$$I_{b1} = \frac{V_{b1}}{Z_{b1}} = \frac{2.4 \text{ kV}}{11.5 \Omega} = 208.3 \text{ A}$$

- ▣ Zone 2:

$$V_{b2} = 9.6 \text{ kV}$$

$$Z_{b2} = \frac{V_{b2}^2}{S_b} = \frac{(9.6 \text{ kV})^2}{500 \text{ kVA}} = 184.3 \Omega$$

$$I_{b2} = \frac{V_{b2}}{Z_{b2}} = \frac{9.6 \text{ kV}}{184.3 \Omega} = 52.1 \text{ A}$$

# Single-Phase Per-Unit Conversion – Example

47

- ▣ Zone 3:

$$V_{b3} = 4.8 \text{ kV}$$

$$Z_{b3} = \frac{V_{b3}^2}{S_b} = \frac{(4.8 \text{ kV})^2}{500 \text{ kVA}} = 46.1 \Omega$$

$$I_{b3} = \frac{V_{b3}}{Z_{b3}} = \frac{4.8 \text{ kV}}{46.1 \Omega} = 104.1 \text{ A}$$

- Next, calculate the per-unit circuit impedances, starting with zone 1:

$$X_{1,pu} = \frac{X_1}{Z_{b1}} = \frac{2 \Omega}{11.5 \Omega} = 0.174 \text{ p.u.}$$

- For transformer T1, the base voltages are the same as the nameplate rating for the transformer
  - ▣ Per-unit leakage reactance is the same as the nameplate value

$$X_{T1,pu} = 0.08 \text{ p.u.}$$

# Single-Phase Per-Unit Conversion – Example

48

- In zone 2:

$$X_{2,pu} = \frac{20 \Omega}{184.3 \Omega} = 0.109 \text{ p.u.}$$

- For transformer T2, the base voltages differ from the rated nameplate values
  - ▣  $X_{T2,pu}$  must be converted to the system base

$$X_{T2,pu} = X_{T2,pu,old} \left( \frac{V_{b,old}^2}{S_{b,old}} \right) \left( \frac{S_b}{V_b^2} \right)$$

$$X_{T2,pu} = 0.1 \text{ p.u.} \left( \frac{(10 \text{ kV})^2}{300 \text{ kVA}} \right) \left( \frac{500 \text{ kVA}}{(9.6 \text{ kV})^2} \right)$$

$$X_{T2,pu} = 0.18 \text{ p.u.}$$



# Single-Phase Per-Unit Conversion – Example

49


- In zone 3, at the load:

$$R_{L,pu} = \frac{10 \Omega}{46.1 \Omega} = 0.217 \text{ p.u.}$$

and

$$X_{L,pu} = \frac{8 \Omega}{46.1 \Omega} = 0.174 \text{ p.u.}$$


- The resulting per-unit circuit:

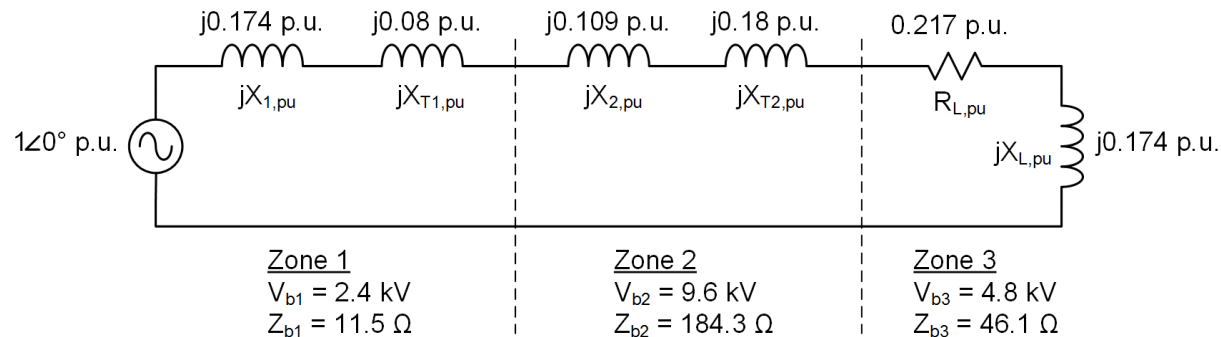

- Note that there are no ideal transformers in the per-unit circuit

# Per-Unit Circuit Analysis – Example

50

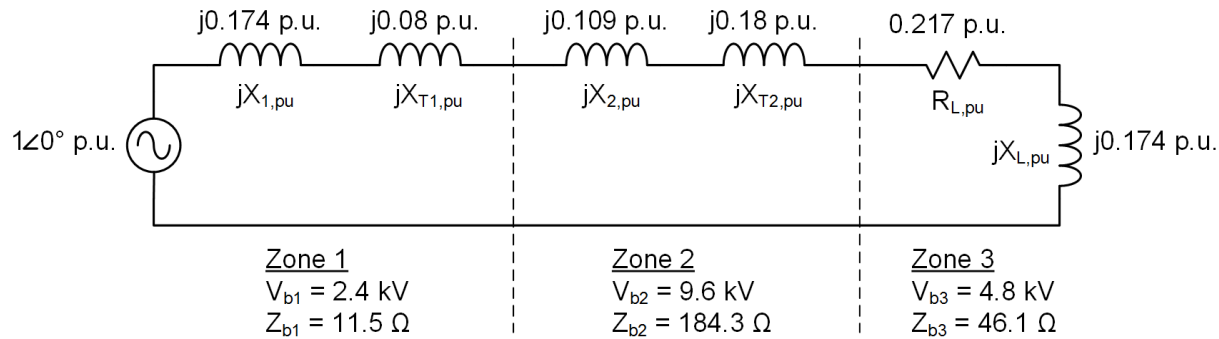

- For the circuit from the previous example, determine the per-unit and actual load current
- Very simple when using the per-unit circuit


$$I_{L,pu} = \frac{V_{s,pu}}{R_L + j(X_{1,pu} + X_{T1,pu} + X_{2,pu} + X_{T2,pu} + X_{L,pu})}$$

$$I_{L,pu} = \frac{1\angle 0^\circ}{0.217 + j0.717 \text{ p.u.}} = 1.33\angle -73.2^\circ \text{ p.u.}$$

$$I_{L,pu} = 1.33\angle -73.2^\circ \text{ p.u.}$$

# Per-Unit Circuit Analysis – Example

51

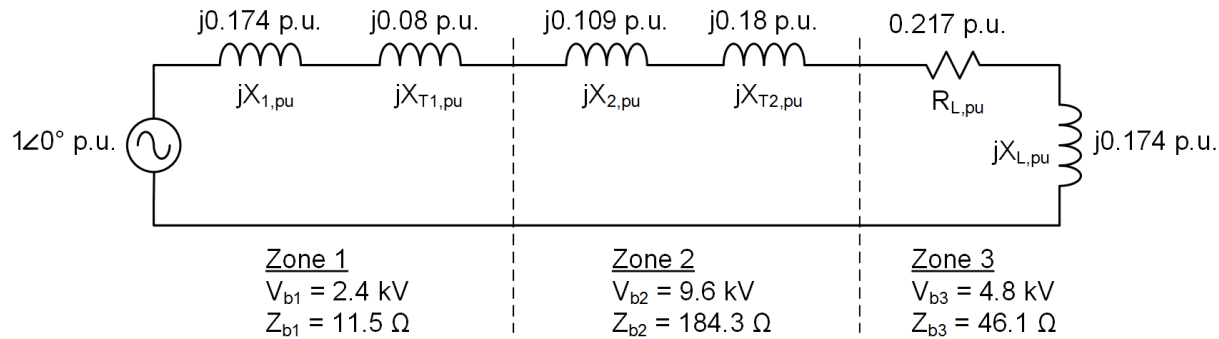

- The current base at the load is

$$I_{b3} = \frac{V_{b3}}{Z_{b3}} = \frac{4.8\text{ kV}}{46.1\ \Omega} = 104.1\text{ A}$$

- So, the actual load current is

$$I_L = I_{L,pu} \cdot I_{b3} = 104.1\text{ A} \cdot 1.33 \angle -73.2^\circ$$


$$I_L = 139 \angle -73.2^\circ\text{ A}$$

52

# Example Problems


Find:

- ▣ Load voltage
- ▣ Load power

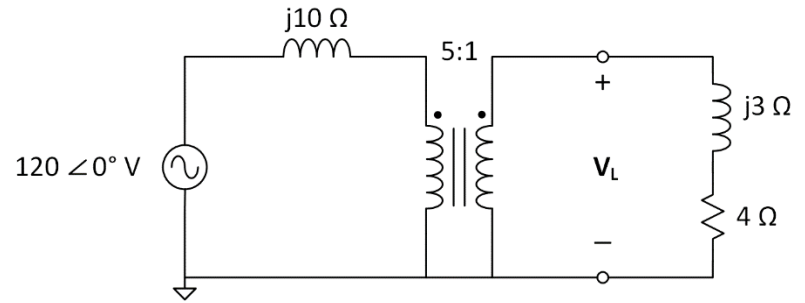



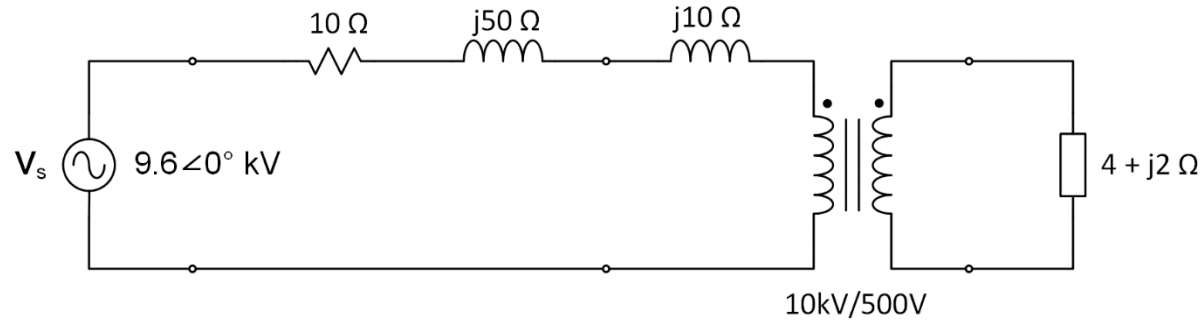Draw a per-unit schematic for the following circuit, and determine the load voltage and power in both per-unit and actual values. Use a power base of 200 kVA.









58

# Three-Phase Per-Unit System

# Three-Phase Per-Unit Circuits

59

- Balanced three-phase circuits can be represented in per-unit as well
    - Use a  $3\text{-}\phi$  power base
    - Use line-to-line voltages
- 
- Procedure for conversion to per-unit:
    1. Re-draw the circuit
      - Eliminate all transformers
      - Clearly delineate voltage zones, as defined by the transformers
      - Do not label any numerical voltage, current, impedance, or power values
    2. Select a single  $3\text{-}\phi$  power base,  $S_{b3\phi}$
    3. Select line-to-line voltage bases,  $V_{b,LL}$  for each voltage level
      - Must be related by transformer turns ratios

# Three-Phase Per-Unit Circuits

60

4. Calculate the impedance base at each voltage level

$$Z_b = \frac{V_{b,LL}^2}{S_{b3\phi}} = \frac{(\sqrt{3}V_{b,LN})^2}{3S_{b1\phi}} = \frac{V_{b,LN}^2}{S_{b1\phi}} \quad (7)$$

- Note that this is identical to (2), the single-phase impedance base

5. Calculate the current base at each voltage level

$$I_b = \frac{S_{b3\phi}}{\sqrt{3}V_{b,LL}} = \frac{3S_{b1\phi}}{\sqrt{3}\sqrt{3}V_{b,LN}} = \frac{S_{b1\phi}}{V_{b,LN}} \quad (8)$$

or

$$I_b = \frac{V_{b,LL}}{\sqrt{3}Z_b} = \frac{V_{b,LN}}{Z_b}$$


- Again, identical to the single-phase impedance base, (3)

6. Convert all actual values to per-unit values
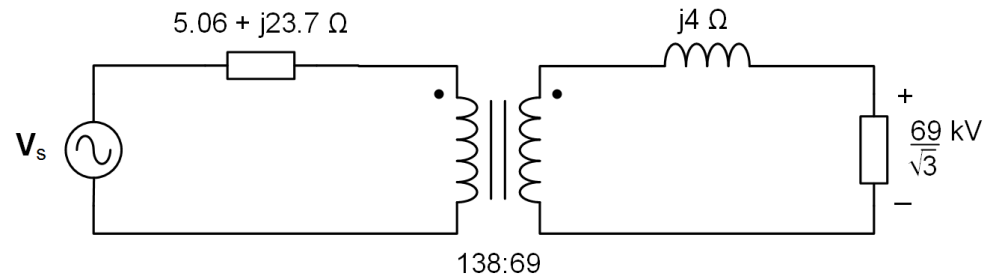
# Three-Phase Per-Unit Analysis - Example

61

- The following is a per-phase schematic for a balanced three-phase circuit



- The power delivered to the load is

$$S_L = 100 + j50 \text{ MVA}$$

- The line-to-line voltage at the load is

$$V_{L,LL} = 69 \angle 0^\circ \text{ kV}$$


- Determine:

- ▣ Supply current
- ▣ Complex power delivered from the supply
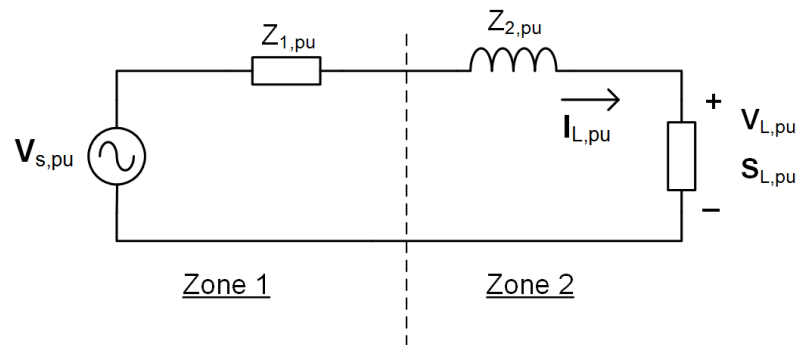
# Three-Phase Per-Unit Analysis - Example

62

- We'll first convert the circuit to a per-unit circuit
- Begin by drawing the per-unit circuit
  - ▣ Eliminate ideal transformers
  - ▣ Don't yet know the per-unit values



- Next, arbitrarily select a ***three-phase power base***

$$S_{b3\phi} = 150 \text{ MVA}$$

# Three-Phase Per-Unit Analysis - Example

63

- Select ***line-to-line voltage bases*** for each voltage level
  - ▣ At the source:  $V_{b,LL1} = 138 \text{ kV}$
  - ▣ At the load:  $V_{b,LL2} = 69 \text{ kV}$
  
- Use the power and voltage bases to calculate the ***impedance base*** at each voltage level

$$Z_{b1} = \frac{V_{b,LL1}^2}{S_{b3\phi}} = \frac{(138 \text{ kV})^2}{150 \text{ MVA}} = 126.96 \Omega$$

$$Z_{b2} = \frac{V_{b,LL2}^2}{S_{b3\phi}} = \frac{(69 \text{ kV})^2}{150 \text{ MVA}} = 31.74 \Omega$$

# Three-Phase Per-Unit Analysis - Example

64

- Calculate the current base at each voltage level

$$I_{b1} = \frac{V_{b,LL1}}{\sqrt{3}Z_{b1}} = \frac{138 \text{ kV}}{\sqrt{3} \cdot 126.96 \Omega} = 627.6 \text{ A}$$

$$I_{b2} = \frac{V_{b,LL2}}{\sqrt{3}Z_{b2}} = \frac{69 \text{ kV}}{\sqrt{3} \cdot 31.74 \Omega} = 1255 \text{ A}$$

- Next, convert the circuit impedances to per-unit

- At the source:

$$Z_{1,pu} = \frac{5.06 + j23.7 \Omega}{126.96 \Omega} = 0.19 \angle 77.9^\circ \text{ p.u.}$$

- At the load side:

$$Z_{2,pu} = \frac{4 \angle 90^\circ \Omega}{31.74 \Omega} = 0.126 \angle 90^\circ \text{ p.u.}$$



# Three-Phase Per-Unit Analysis - Example


65

- The per-unit, three-phase power to the load is

$$S_{L,pu} = \frac{100 + j50 \text{ MVA}}{S_{b3\phi}} = \frac{111.8 \angle 26.6^\circ \text{ MVA}}{150 \text{ MVA}}$$

$$S_{L,pu} = 0.745 \angle 26.6^\circ \text{ p.u.}$$

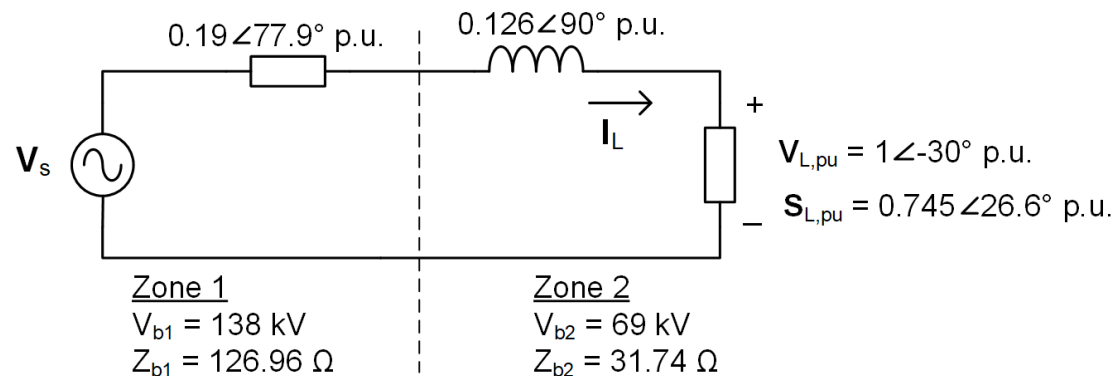- We can now complete the per-unit, per-phase circuit:




- Note that that, even though we are using a L-L voltage base, voltages in the per-phase circuit are still L-N
  - ▣ Load voltage phase agrees with line-to-line  $0^\circ$  phase reference
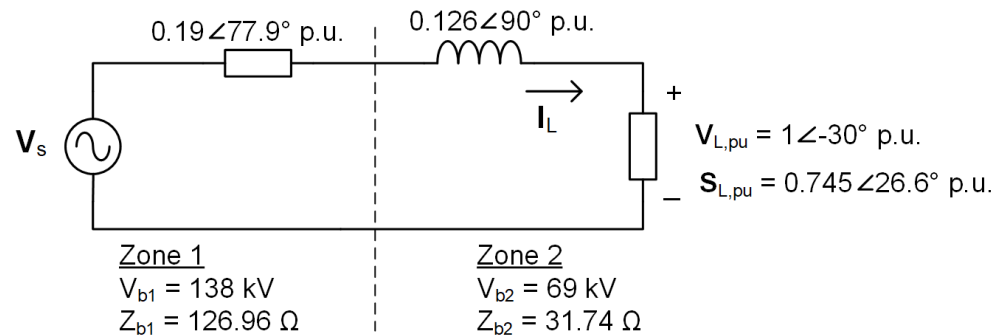
# Three-Phase Per-Unit Analysis - Example

66

- Now, use the per-unit circuit to determine the per-unit load current



$$I_{L,pu} = \left( \frac{S_{L,pu}}{V_{L,pu}} \right)^* = \left( \frac{0.745 \angle 26.6^\circ}{1 \angle -30^\circ} \right)^*$$

$$I_{L,pu} = 0.745 \angle -56.6^\circ \text{ p.u.} = I_{s,pu}$$

- The source voltage is

$$V_{s,pu} = 1 \angle -30^\circ + I_{L,pu} (0.19 \angle 77.9^\circ + 0.126 \angle 90^\circ)$$

$$V_{s,pu} = 1.147 \angle -20.24^\circ$$

# Three-Phase Per-Unit Analysis - Example

67

- The per-unit source power is

$$S_{s,pu} = V_{s,pu} I_{s,pu}^* = 1.147 \angle -20.24^\circ \cdot 0.745 \angle 56.6^\circ$$

$$S_{s,pu} = 0.855 \angle 36.4^\circ$$

- We can now use the per-unit values to determine actual quantities
- The actual supply voltage is (note the  $+30^\circ$  phase shift due to conversion to L-L)

$$V_s = V_{s,pu} \cdot V_{b1} \cdot 1 \angle 30^\circ = 1.147 \angle -20.24^\circ \cdot 138 \text{ kV} \cdot 1 \angle 30^\circ$$

$$V_s = 158.3 \angle 9.76 \text{ kV}$$

- The actual supply current is

$$I_s = I_{s,pu} \cdot I_{b1} = 0.745 \angle -26.6^\circ \cdot 627.6 \text{ A}$$

$$I_s = 467.6 \angle -26.6^\circ \text{ A}$$

- And, the actual supply power is

$$S_s = S_{s,pu} \cdot S_{b3\phi} = 0.855 \angle 36.4^\circ \cdot 150 \text{ MVA}$$

$$S_s = 128.18 \angle 36.4^\circ \text{ MVA} = 103.2 + j76.1 \text{ MVA}$$

68

# 3- $\phi$ Transformers – Y/Y, $\Delta/\Delta$


# Three-Phase Transformers

69

- Three-phase transformers are constructed from banks of single-phase transformers
- Primary and secondary sides can each be connected as a Y or a  $\Delta$  configuration
- Four Possible configurations:
  - Y-Y
  - $\Delta$ - $\Delta$
  - Y- $\Delta$
  - $\Delta$ -Y


# Y-Y Transformer

70

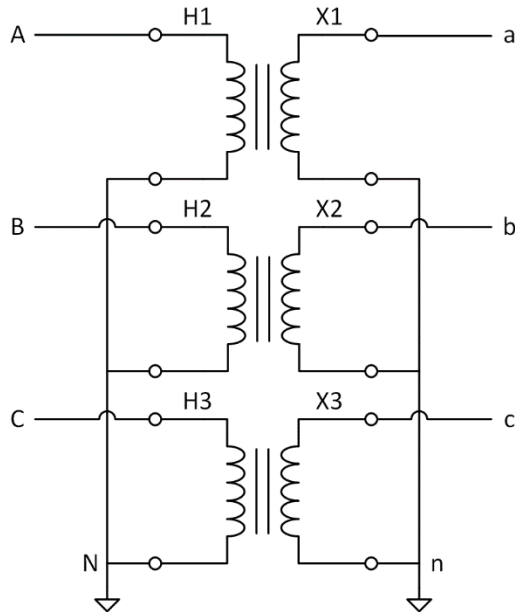


- Note nomenclature:
  - High-voltage terminals:  $H_1, H_2, H_3$
  - Low-voltage terminals:  $X_1, X_2, X_3$
  - Terminal labels serve as dots
  - High-voltage phases: A, B, C
  - Low-voltage phases: a, b, c

## One-line diagram:

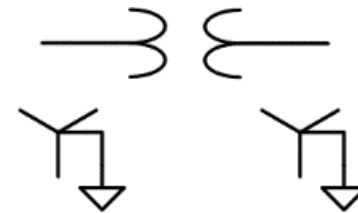


## Phasor diagram:

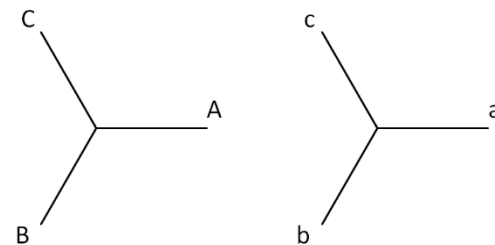

- No phase shift through the transformer


# $\Delta$ - $\Delta$ Transformer

71

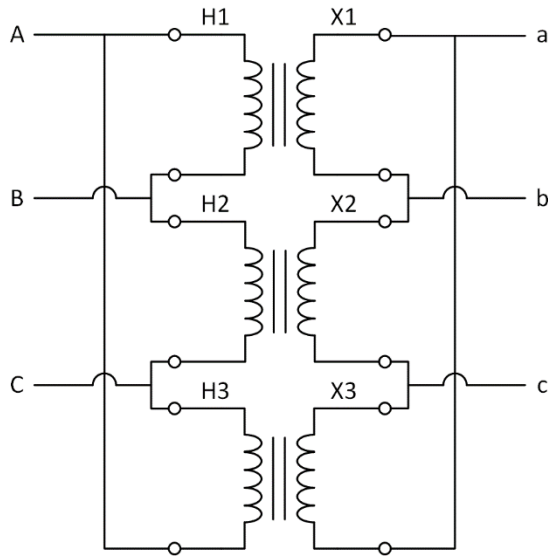


- Voltages across windings are line-to-line voltages
- No phase shift through the transformer

One-line diagram:

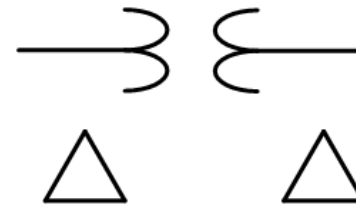

Phasor diagram:

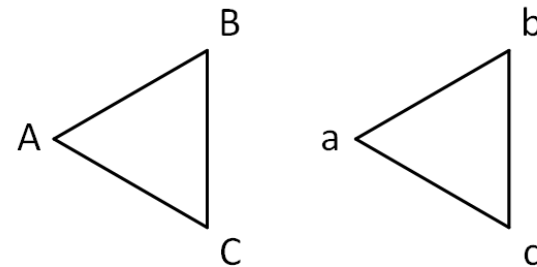


72

# 3- $\phi$ Transformers – Y/ $\Delta$ , $\Delta$ /Y




# Y- $\Delta$ (or $\Delta$ -Y) Transformer

73

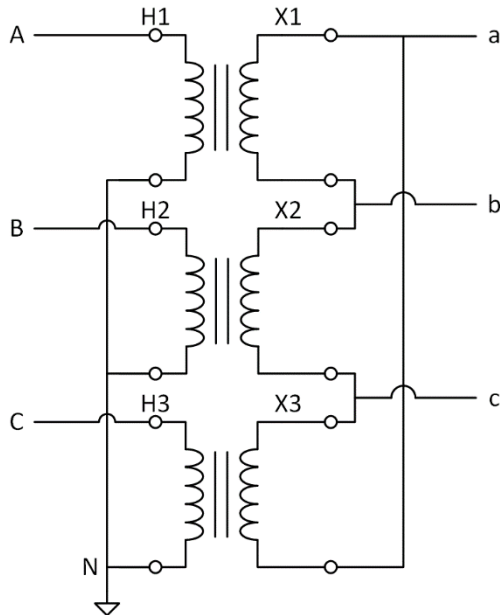

Input Phasor diagram:

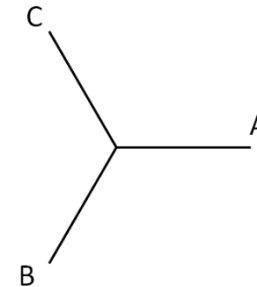


- Here the phase relationships are a bit more complicated
- Each primary voltage is in phase with its corresponding secondary voltage
  - $V_{AN}$  is in phase with  $V_{ab}$
  - $V_{BN}$  is in phase with  $V_{bc}$
  - $V_{CN}$  is in phase with  $V_{ca}$

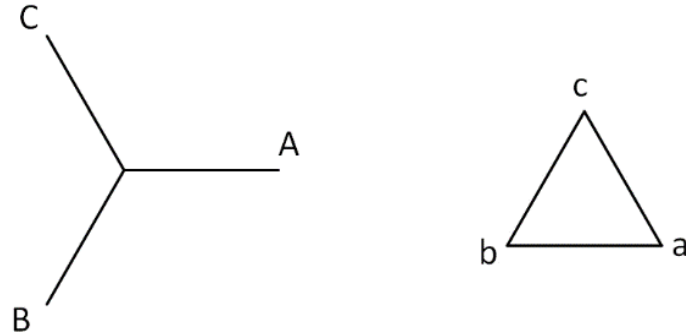
# Y- $\Delta$ ( $\Delta$ -Y) Transformer

74

- The Y- and  $\Delta$ -side phasor diagrams:



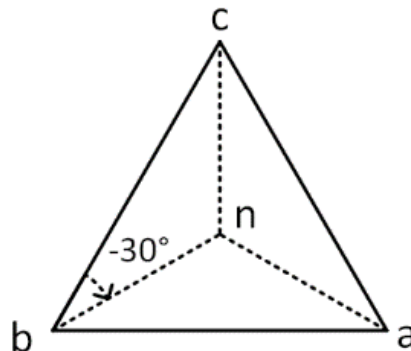- Note that there is a phase shift of  $-30^\circ$  between line-to-neutral voltages on the Y side and line-to-neutral voltages on the  $\Delta$  side



# Y- $\Delta$ ( $\Delta$ -Y) Transformer – Voltage Relationship

75

- Transformer turns ratio,  $a_t$ , relates line-to-neutral voltage on the Y side to line-to-line voltage on the  $\Delta$  side

$$V_{ab} = \frac{1}{a_t} V_{AN}$$

- On the  $\Delta$  side

$$V_{ab} = \sqrt{3} V_{an} \angle 30^\circ$$

so

$$V_{an} = \frac{1}{\sqrt{3} a_t} V_{AN} \angle -30^\circ$$

- The turns ratio is effectively increased by a factor of  $\sqrt{3}$  and there is a phase shift of  $-30^\circ$

# Y- $\Delta$ ( $\Delta$ -Y) Transformer – Current Relationship

76

- For current, we have

$$\mathbf{I}_{ab} = a_t \mathbf{I}_A$$

- On the  $\Delta$  side, we know

$$\mathbf{I}_a = \sqrt{3} \mathbf{I}_{ab} \angle -30^\circ$$

or

$$\mathbf{I}_{ab} = \frac{\mathbf{I}_a}{\sqrt{3}} \angle 30^\circ$$

- So the current relationship is

$$\mathbf{I}_a = \sqrt{3} a_t \mathbf{I}_A \angle -30^\circ$$

- Again, this shows that the effective turns ratio is

$$\sqrt{3} a_t$$

- ▣ And, there is a phase shift through the transformer of  $-30^\circ$


77

# Per-Phase, Per-Unit Models

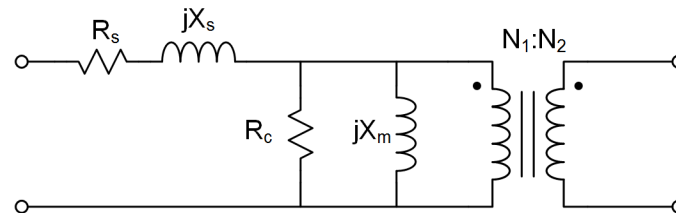
# Per-Phase, Per-Unit Transformer Models

78

- Each of the three single-phase transformers in the three-phase bank can be modeled as



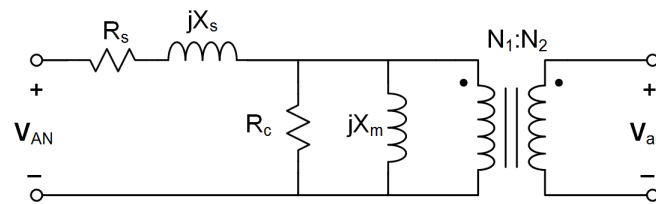
- In the per-phase model, we need the equivalent line-to-neutral impedances
  - ▣ Unchanged for Y connections
  - ▣ Divided by 3 for  $\Delta$  connections
- The Y-Y or  $\Delta$ - $\Delta$  equivalent **per-phase** circuit is the same as above:



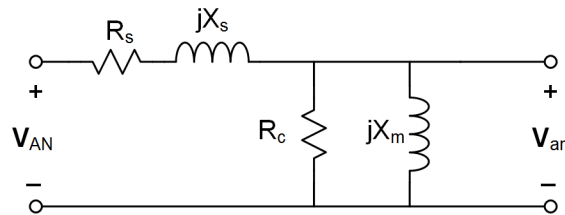
# Per-Phase, Per-Unit Transformer Models

79


- The transformer disappears from the **per-unit** equivalent circuit:



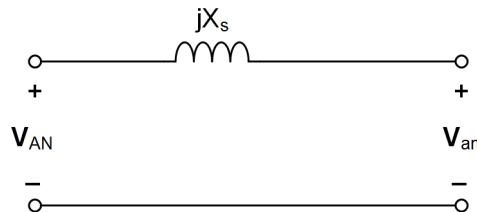- It is common to neglect the exciting current and winding losses and account only for leakage flux



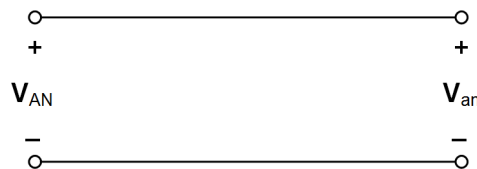
- For an ideal Y-Y or  $\Delta$ - $\Delta$  transformer, the per-unit circuit is



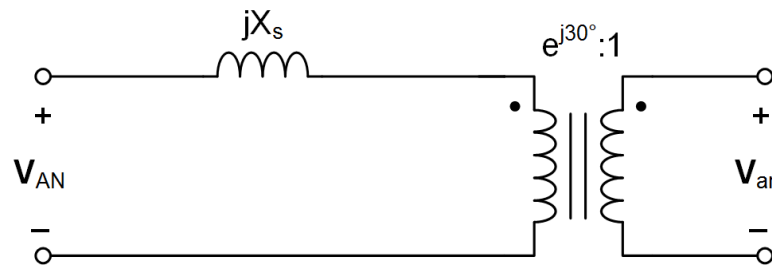
# Per-Phase, Per-Unit Transformer Models

80

- For the Y- $\Delta$  or  $\Delta$ -Y transformer, we must account for the phase shift
  - Per-unit includes a conceptual phase-shifting transformer
  - Voltage bases must be related by the effective turns ratio – must include the  $\sqrt{3}$  factor
- Simplified Y- $\Delta$  per-unit circuit:



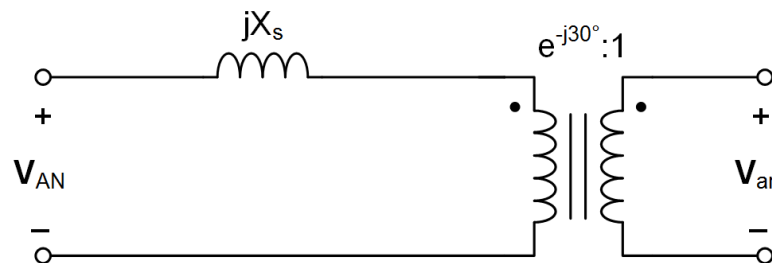- Simplified  $\Delta$ -Y per-unit circuit:





81

# Power Transformer Miscellany

# Transformer Uses



82

- $\Delta$  connection advantages:
    - Third harmonic current confined to the core
      - Due to non-linear B-H characteristics of the core
  - Y connection advantages
    - Neutral point simplifies grounding
    - Reduced insulation requirement
- 
- **$\Delta$ -Y transformers**
    - Most common type of transformers
    - Step-up/step-down with Y connection at high-voltage side to reduce insulation requirements
    - $\Delta$  winding confines third harmonic currents
  - **$\Delta$ - $\Delta$  transformers**
    - Attractive from repair/maintenance standpoint
      - Can remove one transformer and still deliver (reduced)  $3\phi$  power
  - **Y-Y transformers**
    - Not commonly used due to problems with third harmonic currents
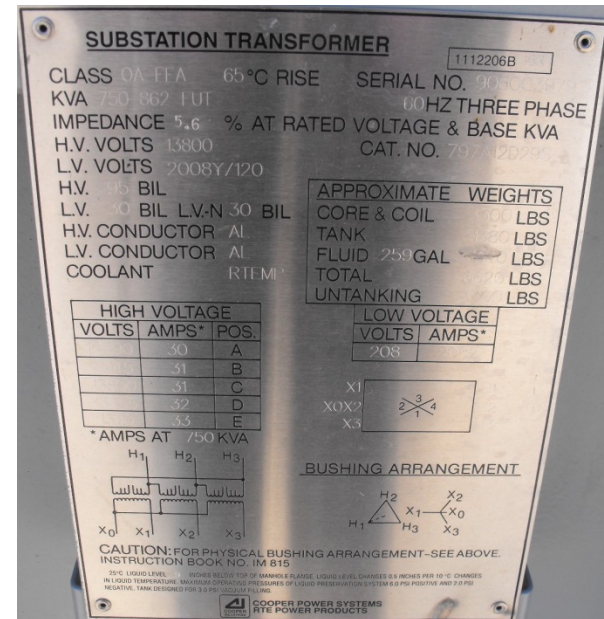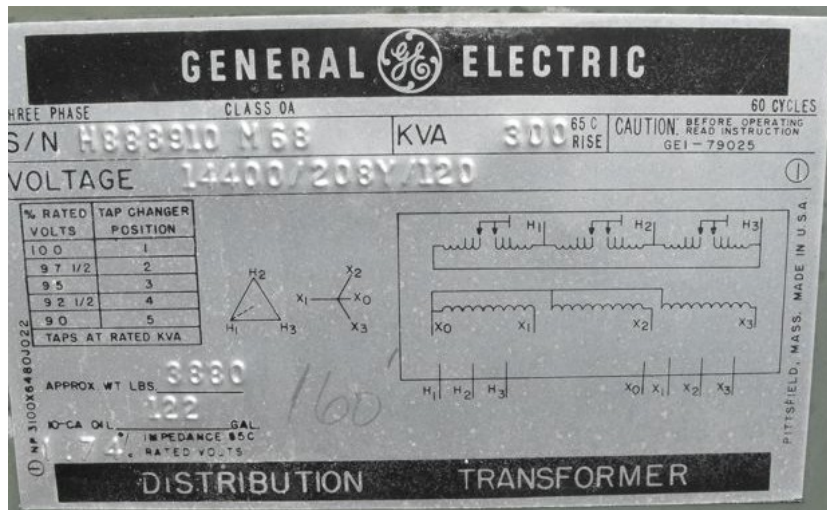
# Transformer Nameplate Ratings

83

- Transformer properties and ratings are specified on the transformer **nameplate**:



- Includes, among other specs:
  - Power rating
  - Voltage ratings – turns ratio
  - Configuration – delta or Y
  - Impedance

# Transformer Impedance

84

- Impedance specified on the nameplate as a percentage
  - ▣ Per-unit value multiplied by 100%
  - ▣ Typically stamped on the nameplate – determined through testing
  - ▣ Assume this is **series impedance magnitude**

□ For example:

- ▣  $S_{rated} = 750 \text{ kVA}$
- ▣  $V_{rated} = 13.8 \text{ kV}$
- ▣  $\%Z = 5.6\%$  or  $0.056 \text{ p.u.}$


□ The impedance base at the primary:

$$Z_b = \frac{V_{rated}^2}{S_{rated}} = \frac{(13.8 \text{ kV})^2}{750 \text{ kVA}} = 253.9 \Omega$$

□ The actual impedance magnitude is

$$Z_s = \%Z \cdot Z_b = 0.056 \cdot 253.9 \Omega$$

$$Z_s = 14.2 \Omega$$

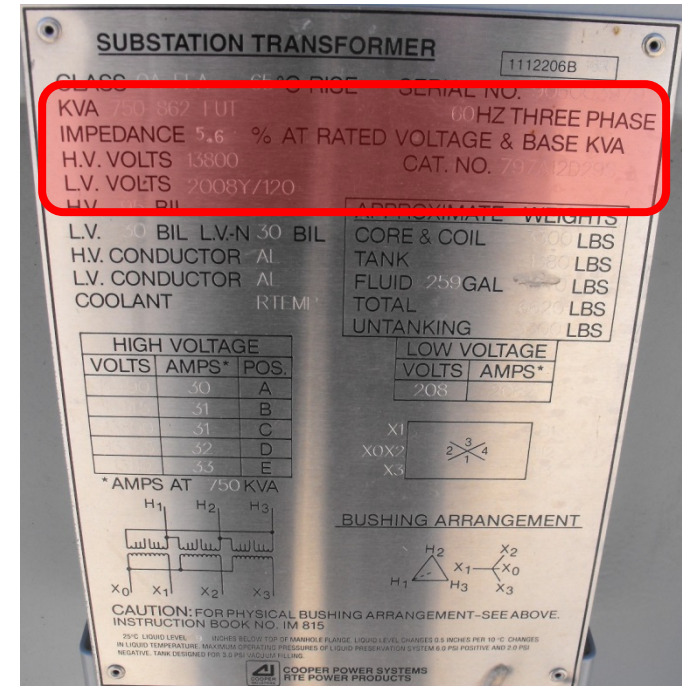

# Transformer Impedance

- Another way to understand transformer impedance:
  - ▣ ***Voltage drop at the rated load due to transformer impedance, expressed as a percentage of the rated voltage***
- For the previous example, the rated current is

$$I_{rated} = \frac{S_{rated}}{V_{rated}} = \frac{750 \text{ kVA}}{13.8 \text{ kV}} = 54.3 \text{ A}$$

- We determined that the actual impedance was  $14.2 \Omega$ , so

$$V_{drop} = I_{rated} \cdot Z_s = 54.3 \text{ A} \cdot 14.2 \Omega = 771.7 \text{ V}$$

- Expressed as a percentage of the rated voltage, we have

$$\%Z = \frac{V_{drop}}{V_{rated}} \cdot 100\% = \frac{771.7 \text{ V}}{13.8 \text{ kV}} \cdot 100\% = 5.6\%$$

# Distribution Transformers

86


- Neighborhoods are typically in the range of 7.2 kV, line-to-neutral
- Pole-mounted ***distribution transformers*** step voltage down
  - ▣ Single phase 120/240 V
- ***Pad-mounted*** or ***vault*** (underground) distribution transformers are also common


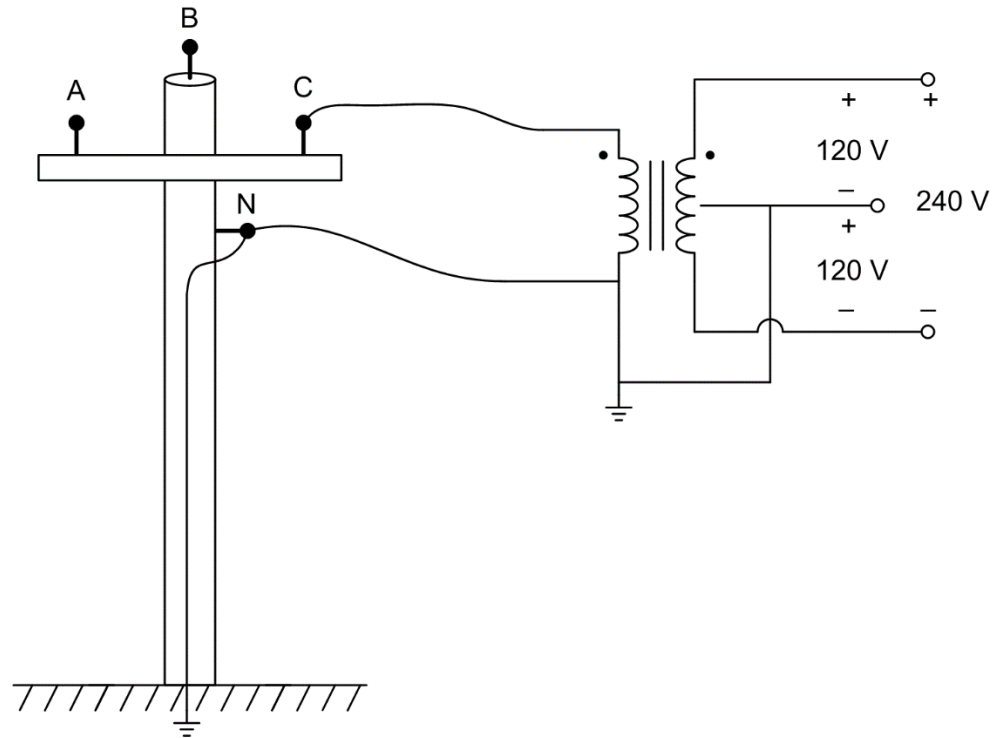
# Distribution Transformers

87

- Single-phase distribution transformers tap off of a single phase
- Neutral center tap on secondary
- Single-phase 120 V and 240 V service to homes and businesses




88
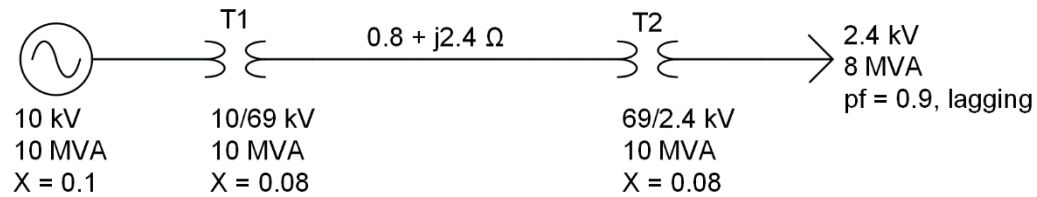
# Example Problems



Using the *single-phase* per-unit conversion procedure,

- Draw a per-phase, per-unit schematic
- Determine the generator voltage in per-unit and in volts
- Determine the power delivered by the generator in p.u. and VA











Using the **three-phase** per-unit conversion procedure,

- Draw a per-phase, per-unit schematic
- Determine the generator voltage in per-unit and in volts
- Determine the power delivered by the generator in p.u. and VA

