

SECTION 6: HIGH-VOLTAGE DC TRANSMISSION

ESE 470 – Energy Distribution Systems

2

Introduction

High-Voltage AC Transmission

3

- Power is transmitted at ***high voltage***
 - ▣ Lower current
 - ▣ Lower I^2R line losses

- Most power transmitted as ***high-voltage AC***
 - ▣ Transformers step voltages up for transmission, down at loads
 - ▣ Transformers only work for AC

- Advancement of ***power electronics*** has enabled high-voltage DC (HVDC) transmission
 - ▣ Power electronic converters can generate DC voltages of 100s of kV

HVAC Transmission – Disadvantages

4

- HVAC Transmission has disadvantages:
 - Reactive power consumed by transmission lines
 - Losses
 - Skin effect
 - AC current crowds toward outer surface of cables
 - AC resistance greater than DC resistance
 - Losses
 - Grid stability is a concern
 - Power transmission must be limited to maintain grid stability
 - Can't arbitrarily connect large sections of grid without considering stability
 - AC power transfer between asynchronous networks is not possible

High-Voltage DC Transmission

5

- Advantages of HVDC transmission:
 - ▣ ***Lower transmission loss***
 - No reactive power transfer
 - No skin effect
 - Less conductor required
 - ▣ ***Power flow control***
 - Independent control of real and reactive power direction and magnitude (for some HVDC architectures)
 - ▣ ***Smaller right of way (RoW) required***
 - Fewer conductors
 - Fewer towers
 - ▣ ***Less costly than AC transmission***
 - For longer lines exceeding some breakeven distance

HVDC Applications

6

- Long-distance bulk power transmission
 - ▣ Lower loss
 - ▣ Lower cost
 - ▣ Smaller RoW

- Power transfer between asynchronous AC grids
 - ▣ Back-to-back HVDC
 - ▣ Improves stability of each grid
 - ▣ Cascading failures will not propagate across the HVDC link

- Stabilizing AC grids
 - ▣ Power transfer within an AC network to improve stability

HVDC Applications

7

- Undersea/underground cables
 - ▣ No charging current
 - ▣ Lower loss than AC

- Integration of renewable generation sources
 - ▣ Solar/wind farms
 - ▣ Possibly distant from load centers
 - ▣ Offshore wind farms
 - ▣ Asynchronous generation

8

HVDC Link Configurations


HVDC System Overview

9

- HVDC links exist within and between 3- ϕ AC power grids
- The components of an HVDC system:
 - ▣ ***Converter stations***
 - Conversion between AC and DC
 - One at either end of a DC link
 - Collocated for back-to-back links
 - Rectifier: AC-to-DC conversion
 - Inverter: DC-to-AC conversion
 - ▣ ***Transmission lines/cables***
 - Overhead lines and towers
 - Undersea/underground cables
 - ▣ ***Electrodes***
 - Provide grounding for earth or sea return currents

HVDC System Overview

10

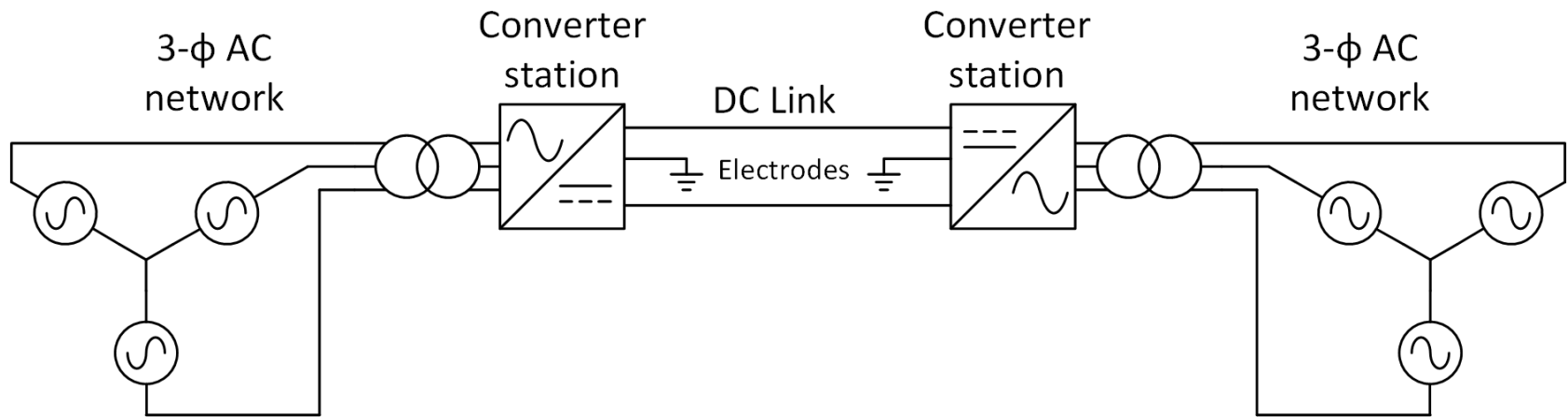

HVDC Link Configurations


11

- HVDC configurations differ in:
 - Number of DC poles
 - Monopolar: single DC voltage (e.g. +500 kV)
 - Bipolar: positive and negative DC voltages (e.g. ± 500 kV)
 - Return current path
 - Metallic
 - Ground/sea
 - None (bipolar configurations)

HVDC Link Configurations

12

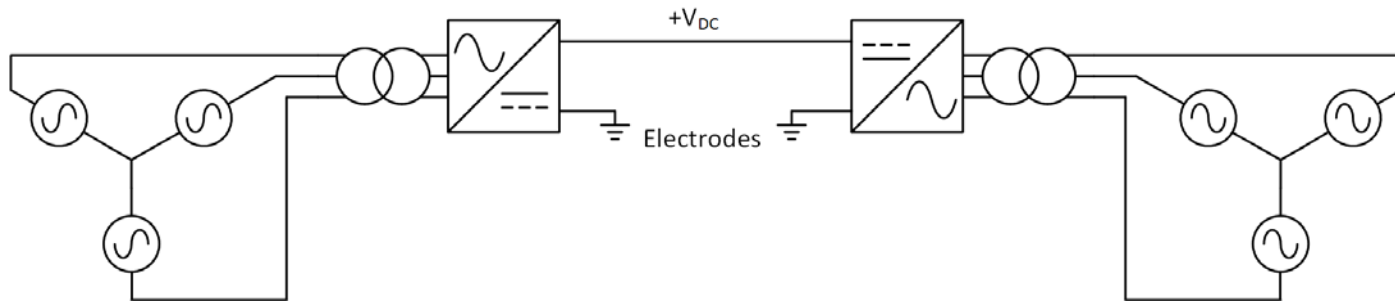□ ***Monopolar with ground/sea return path:***




- Single HVDC line
- Return currents flow through the earth or sea at low voltage
- Simplest configuration
 - Electrode design is non-trivial
- Common configuration for undersea links

HVDC Link Configurations

13

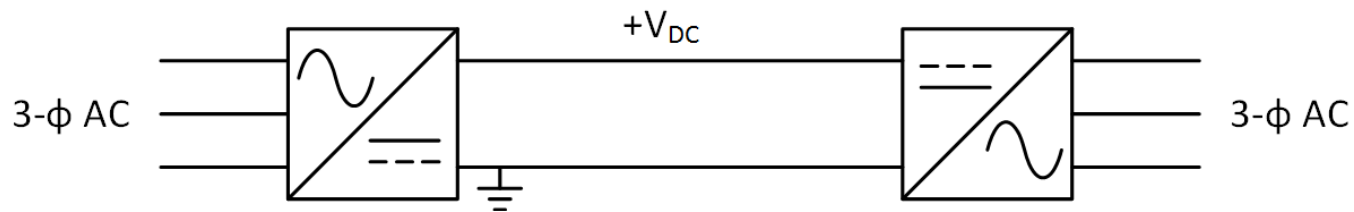□ ***Monopolar with metallic return path:***




- Dedicated metallic cable for return currents
- When grounding electrodes and ground return current are not an option
 - Environmental concerns
 - Real estate restrictions


HVDC Link Configurations

14

□ ***Bipolar with ground return path:***

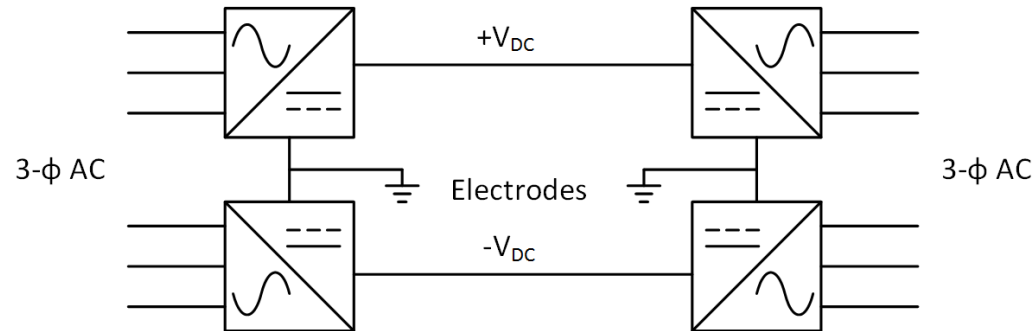

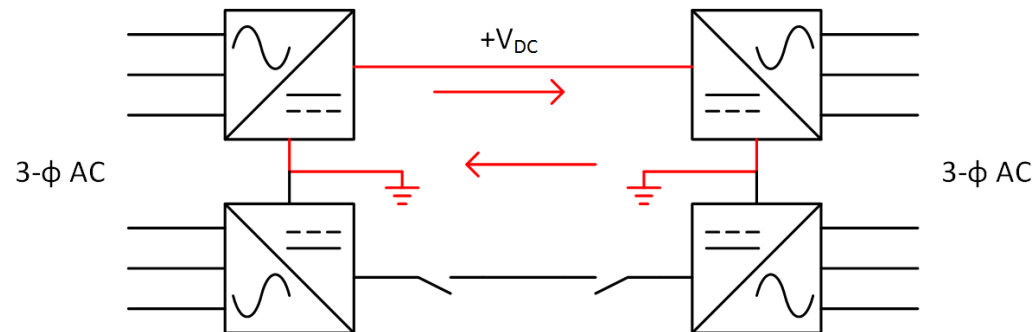
- Positive and negative DC voltages
- Little to no current through ground path under normal operation
- In case of a single-pole fault, return current can flow on the ground path:



HVDC Link Configurations

15

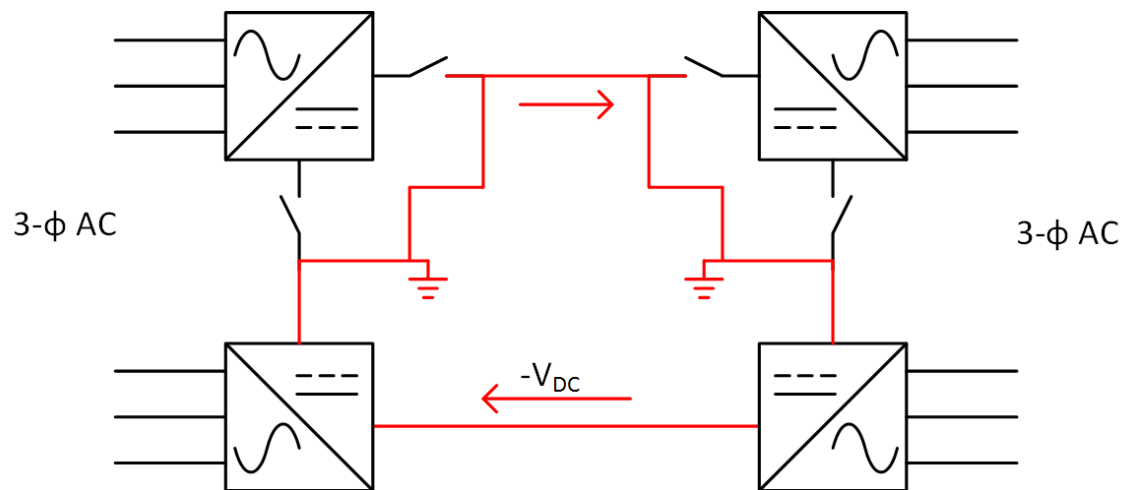
- ***Bipolar with ground return path*** (cont'd):
 - ▣ In the event of a failure involving the transformer/converters of a single pole
 - Failed pole's conductors can be used as a low-voltage return path



HVDC Link Configurations

16

□ *Bipolar with metallic return path:*

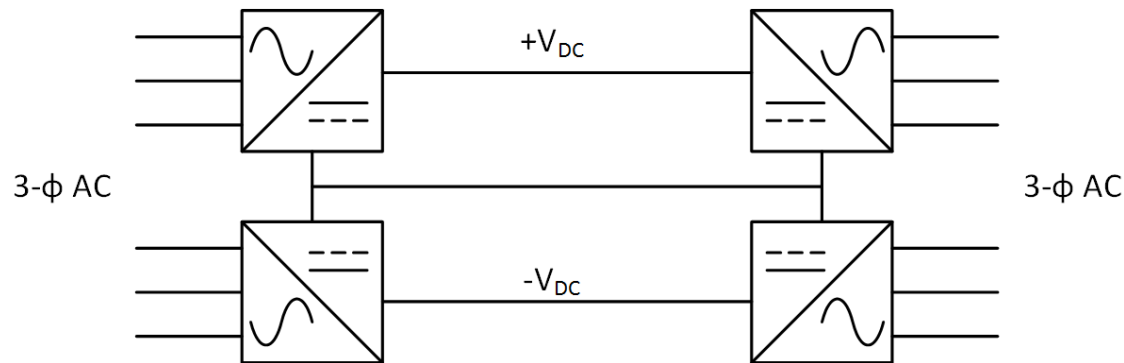


- Dedicated metallic cable for return currents
- When electrodes are not a viable option
- Little to no current in return cable under normal operation
- Same backup mode options as bipolar w/ ground return

HVDC Link Configurations

17

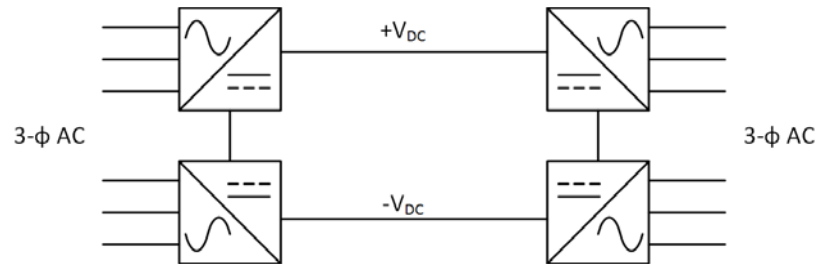□ ***Bipolar with no dedicated return path:***



- Least expensive bipolar configuration
 - Cable fault on either pole removes entire link from service
 - Monopolar operation is an option in the event of a single-pole converter/transformer failure
- ## □ ***Back-to-back converter:***
- Rectifier and inverter in the same location
 - No transmission line
 - Lower voltage than for long-distance links
 - For power transfer between asynchronous AC networks


18

HVDC vs. AC Cost Comparison

HVDC vs. AC Cost Comparison

19

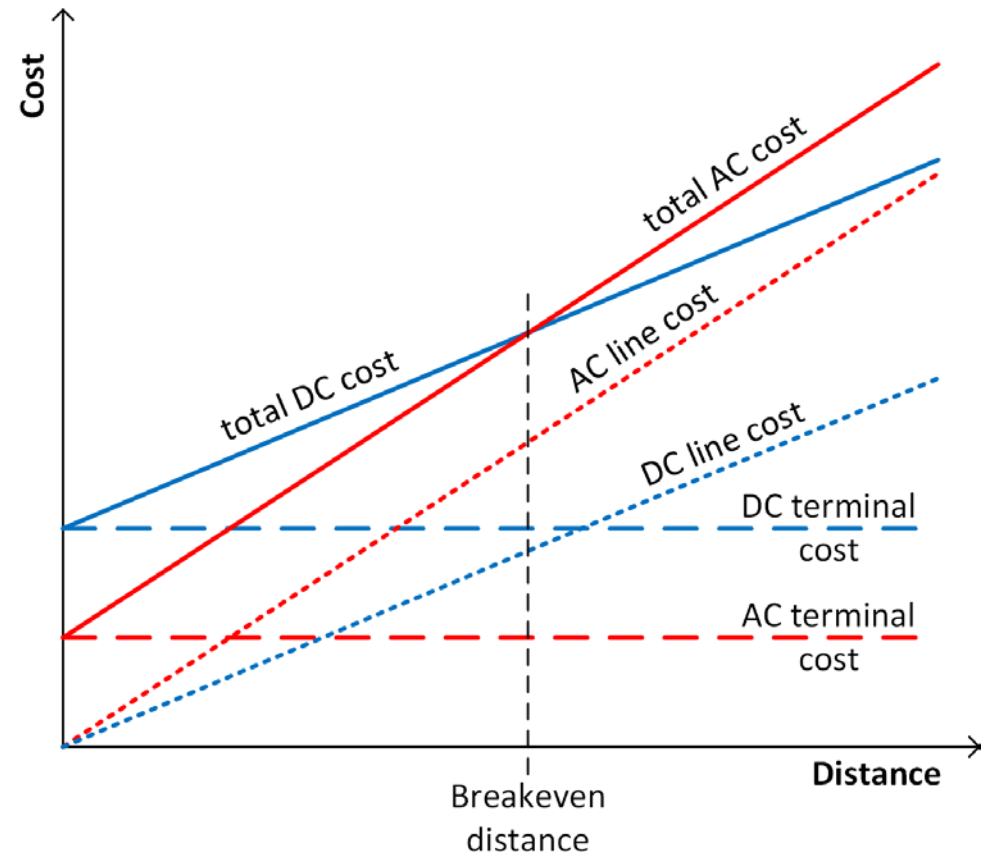- For the same amount of power and loss, HVDC requires less conductor
 - Lower cost per km
- Fixed terminal station cost
 - HVDC far more costly
- Beyond some **breakeven distance**, HVDC is more economical
 - ~600 – 800 km for overhead lines
 - ~50 km for undersea cables



20

HVDC System Types

HVDC System Types


21

- Two basic categories of HVDC systems
 - ▣ ***Line-commutated converters***
 - Current-source converters (CSC)
 - ▣ ***Forced-commutated (or self-commutated) converters***
 - Voltage-source converters (VSC)
- Difference is in the switching devices employed and how those switches are controlled
 - ▣ Specifically, how the switches are turned off

Line-Commutated Converters

22


- Current-source converters (CSC)
 - Converter looks like a **current source** to the AC grid
- **Switching devices:** thyristors
 - Previously mercury arc valves
 - Turn-on time is controlled
 - Turn-off occurs when voltage across thyristors changes polarity (goes negative)
 - Operation requires active generation in AC grid
- Typical loss: <1% per converter station
- **Power flow**
 - Converters consume reactive power
 - Real power flow along DC link in one direction only

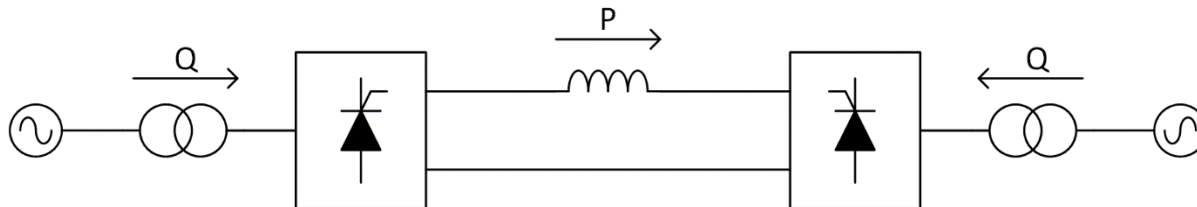

Self-Commutated Converters

23

- Voltage-source converters (VSC)
 - ▣ Converter looks like a **voltage source** to the AC grid
- **Switching devices:** typically insulated gate bipolar transistors (IGBTs)
 - ▣ Turn-on and turn-off is controlled by a control signal
 - ▣ Capable of operating connected to AC grid with only passive loads
 - ▣ Can provide black start capability
- Typical loss: 1% - 3% per converter (varies with topology)
- **Power flow**
 - ▣ Independent control of real and reactive power

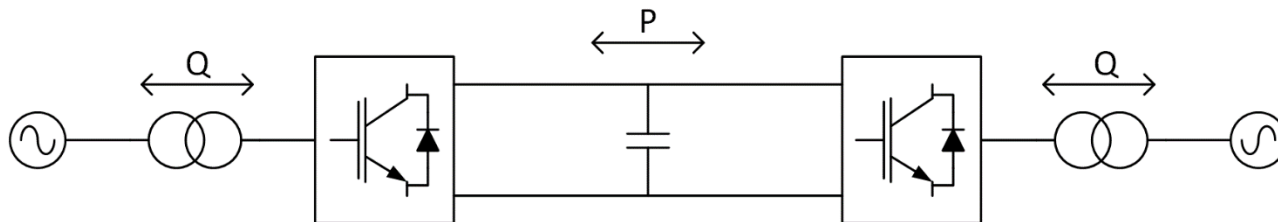

24


Line-Commutated Converters

Line-Commutated Converters

25

- Line-commutated converters
 - ▣ Most common type of HVDC system currently in operation
 - ▣ Converters use thyristors as switching elements

- ***Thyristor***


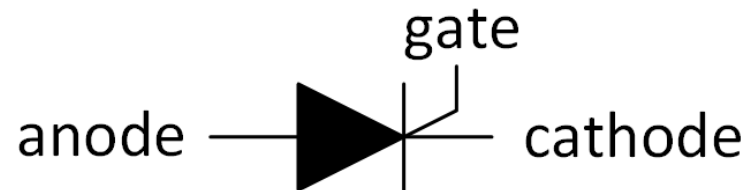


- ▣ Like diodes, thyristors block current in the reverse (cathode-to-anode) direction
- ▣ Unlike diodes, thyristors also block forward current until turned on with a control signal applied to the gate terminal



Thyristors

26

□ Diode half-wave rectifier

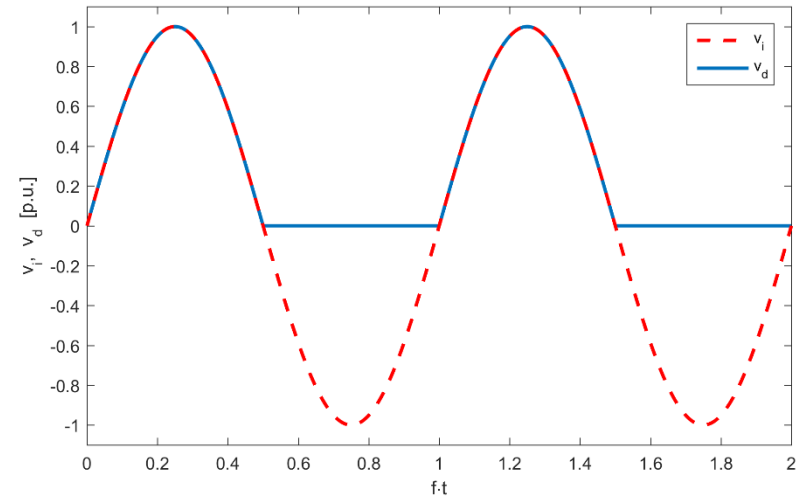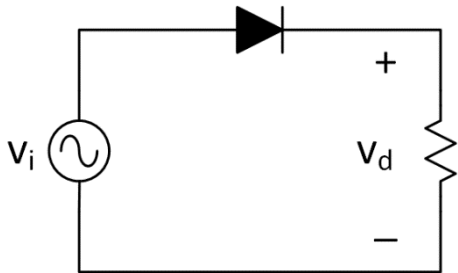



□ Thyristor half-wave rectifier

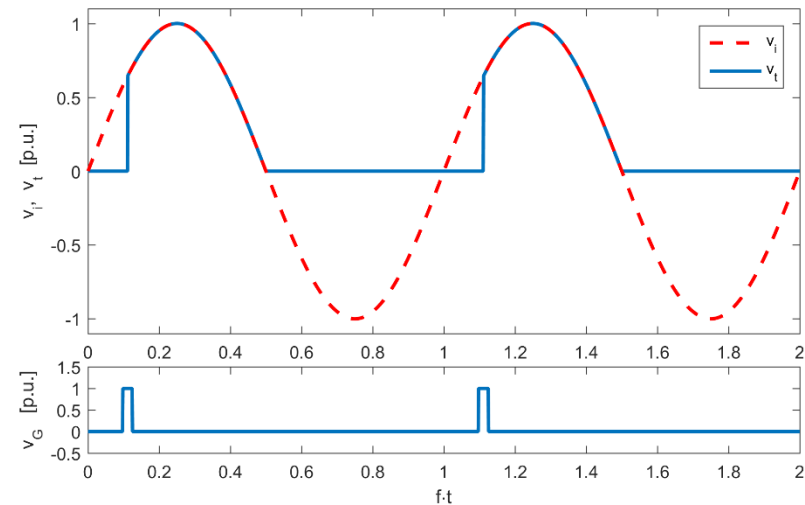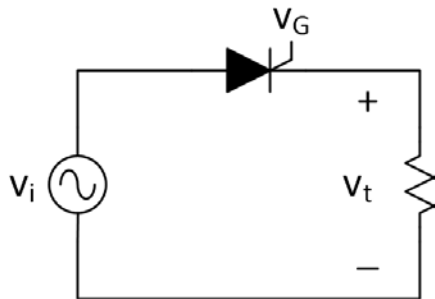

Delay Angle

27

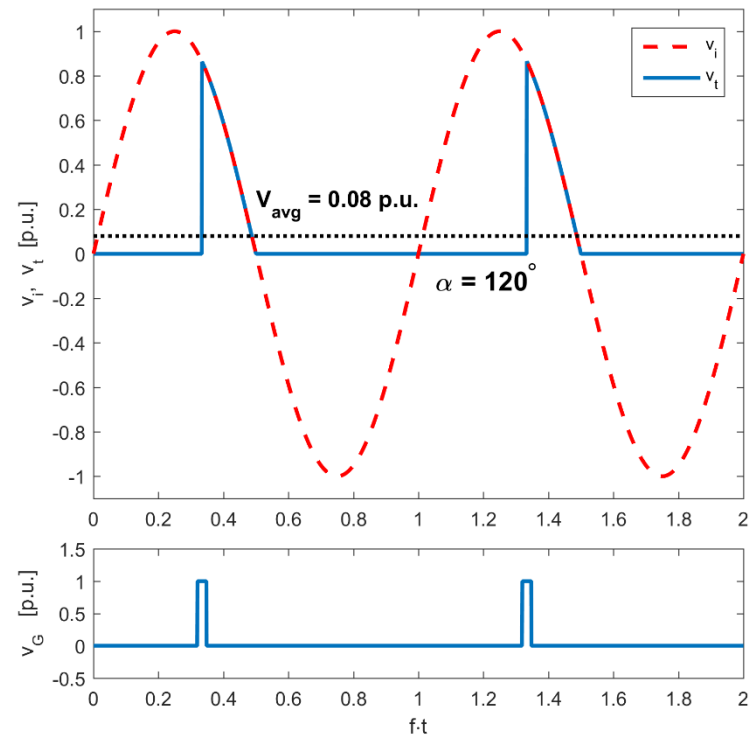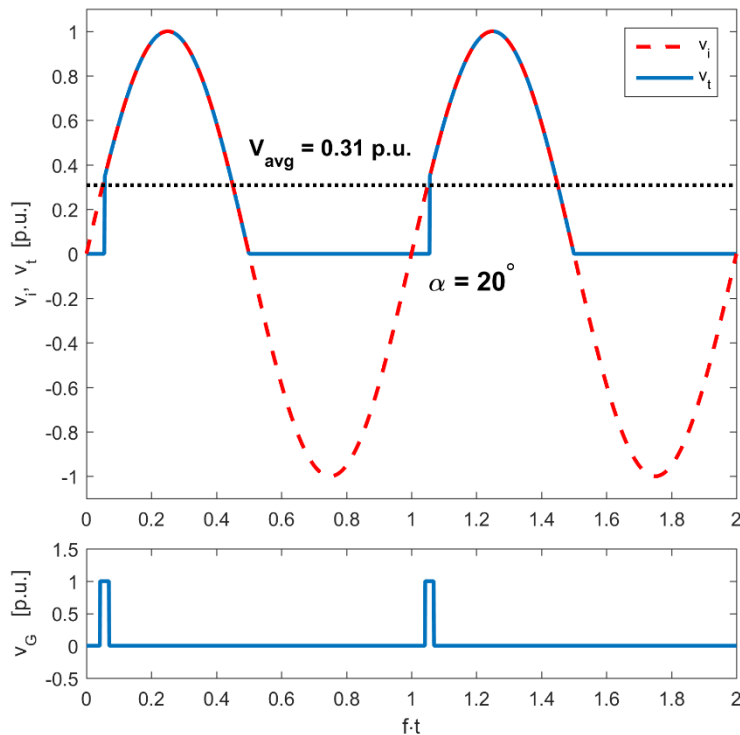- Thyristor turn on time can be delayed past the point of natural conduction by a **delay angle**, α
 - ▣ Average output voltage controlled by α




Three-Phase Full-Bridge Converters

28

- Converter stations use thyristors arranged in full-bridge configurations
- ***Six-pulse thyristor converter:***
 - ▣ Commutation occurs every 60°
 - ▣ Thyristors numbered in order of conduction
 - ▣ DC output voltage:

$$v_d = v_{Pn} - v_{Nn}$$


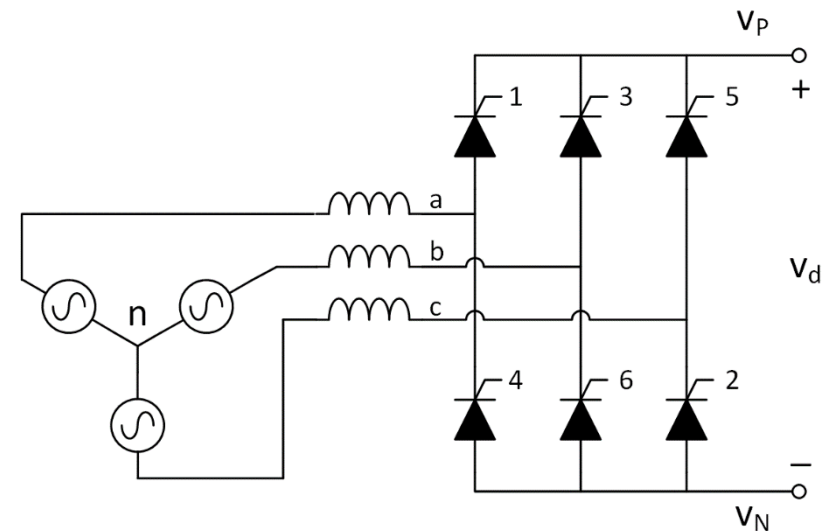


Six-Pulse Converter

29



- Turn-on time delayed by **delay angle**, α , past the point of natural commutation

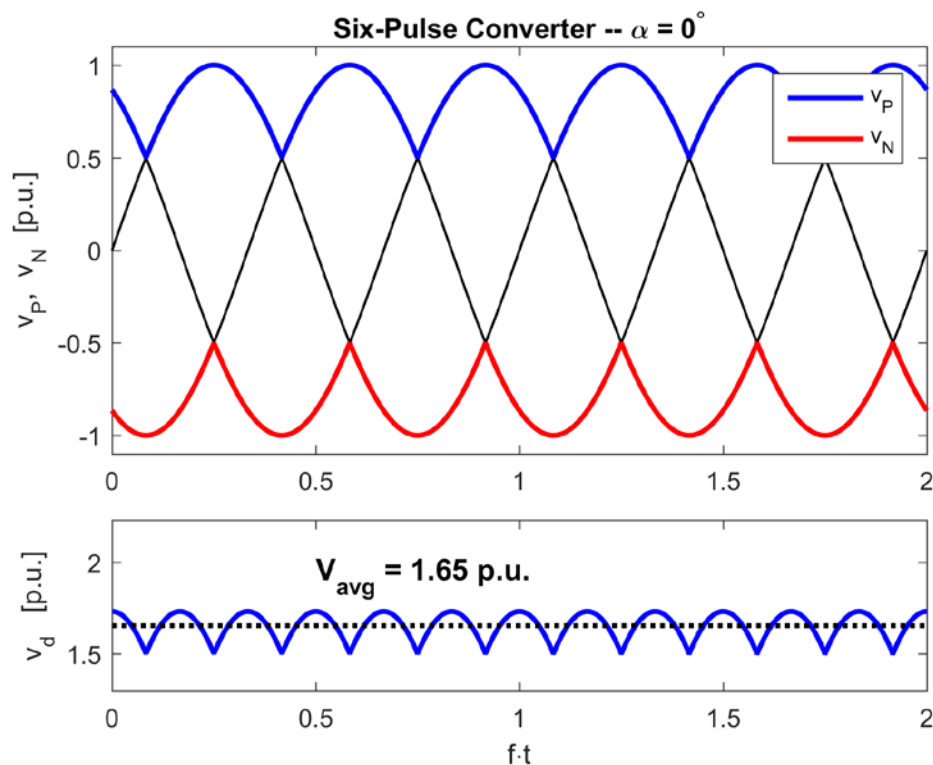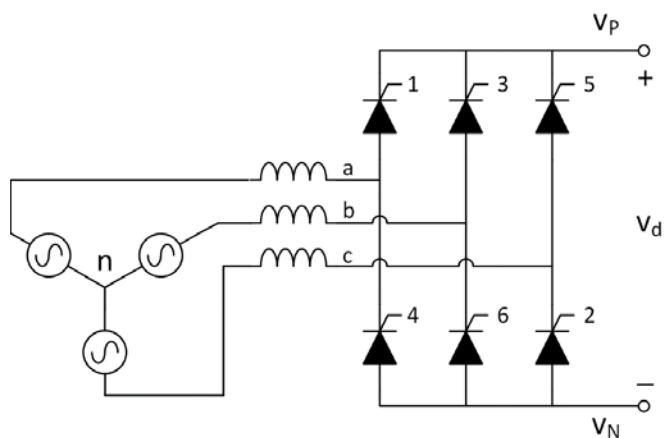- Maximum average DC output for $\alpha = 0^\circ$
- Average DC output is negative for $\alpha > 90^\circ$



Six-Pulse Converter


30

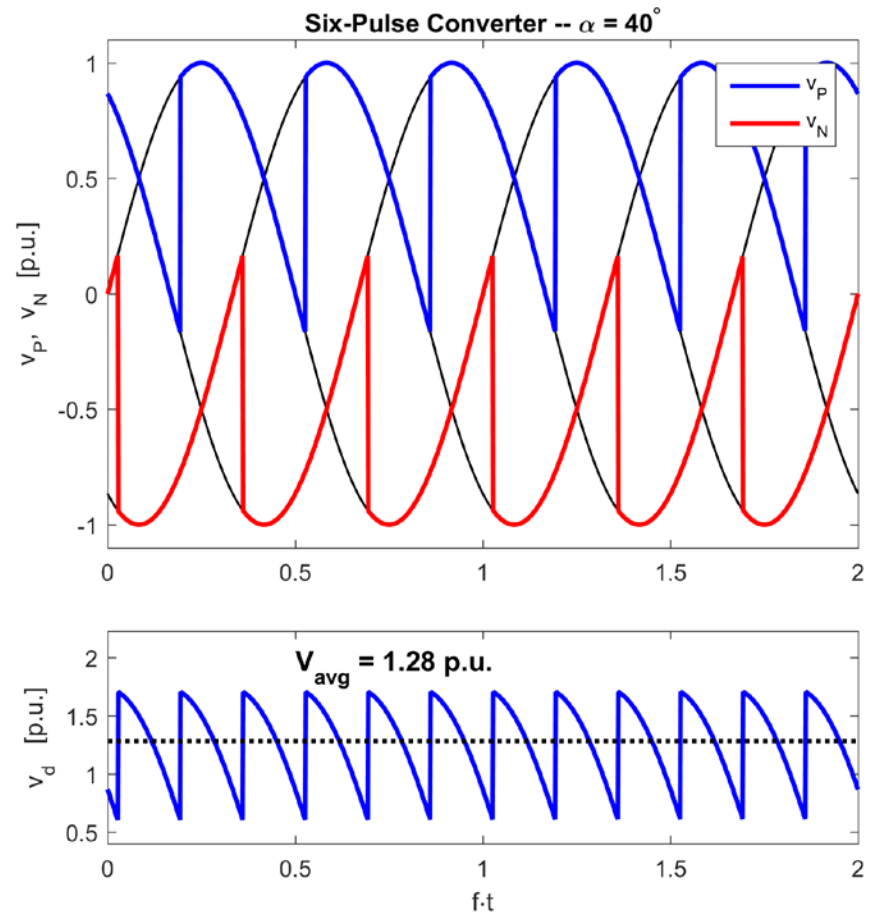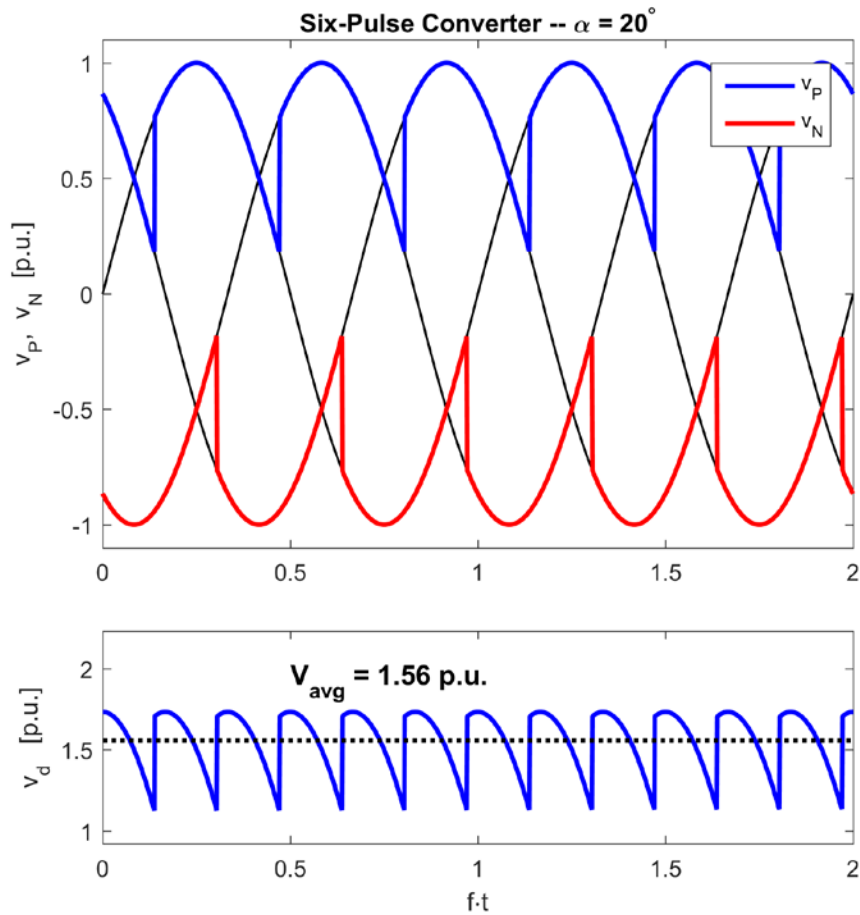

Six-Pulse Converter

31

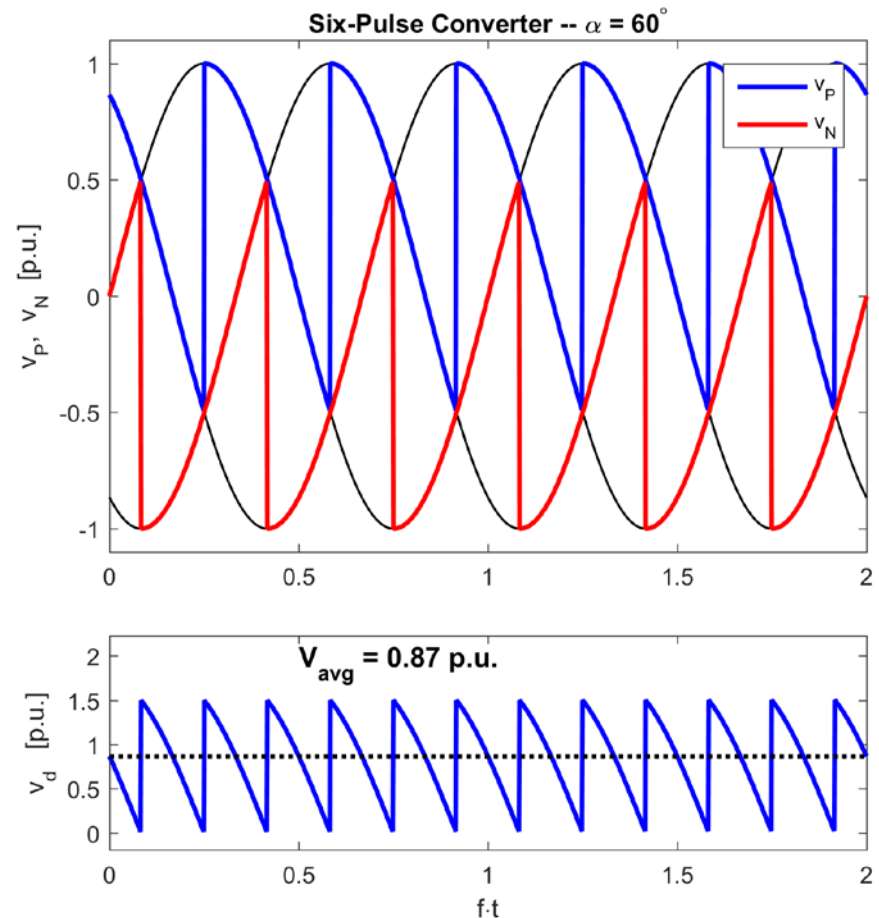
- Converter output, v_d , is clearly not pure DC
 - ▣ Six pulses per period
 - ▣ Significant *harmonics* injected onto the AC grid
 - ▣ **AC filtering** required to reduce harmonics



Twelve-Pulse Converter

32


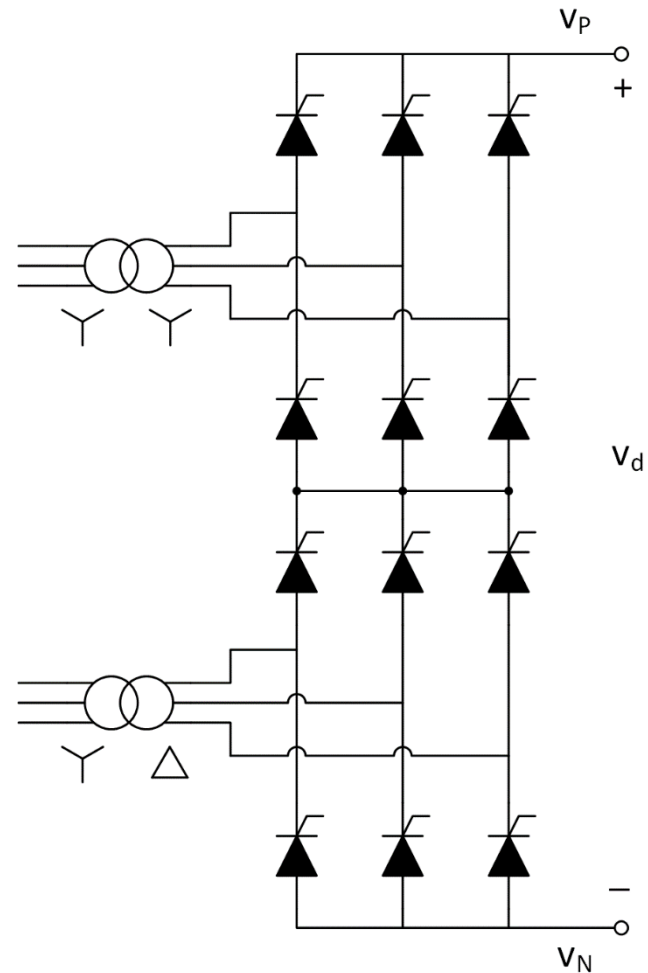
- **Twelve-pulse converter**
 - Two six-pulse bridges connected in series
 - Three-phase input to one bridge is phase shifted 30° relative to the input of the other
 - Y/Y and Y/ Δ transformers
 - Commutation occurs every 30°



Twelve-Pulse Converter



33

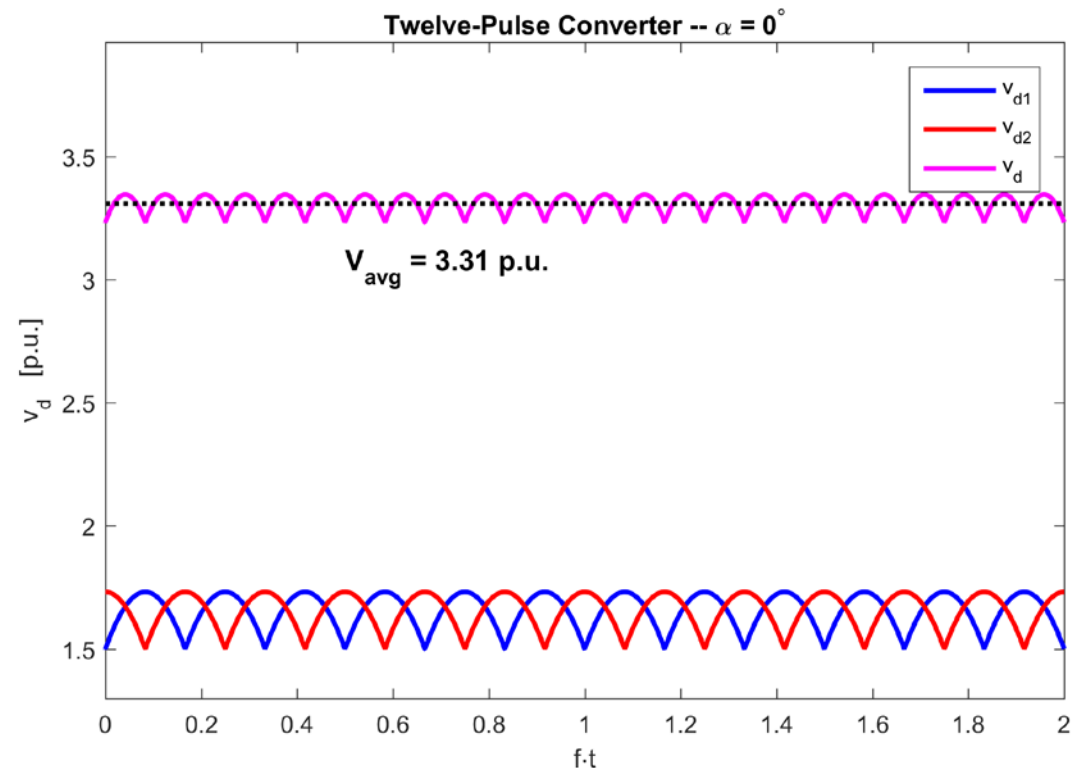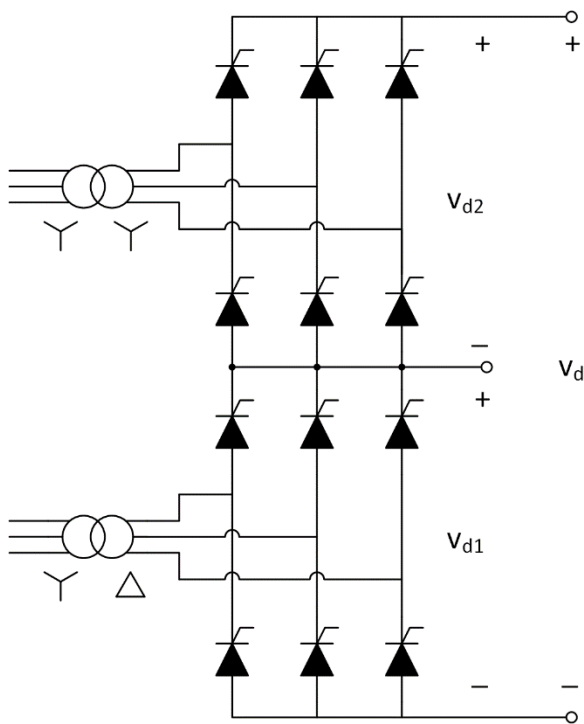- Now, 12 pulses per period
 - ▣ Harmonics are greatly reduced
 - ▣ AC filtering requirements are lessened



Twelve-Pulse Converter


34

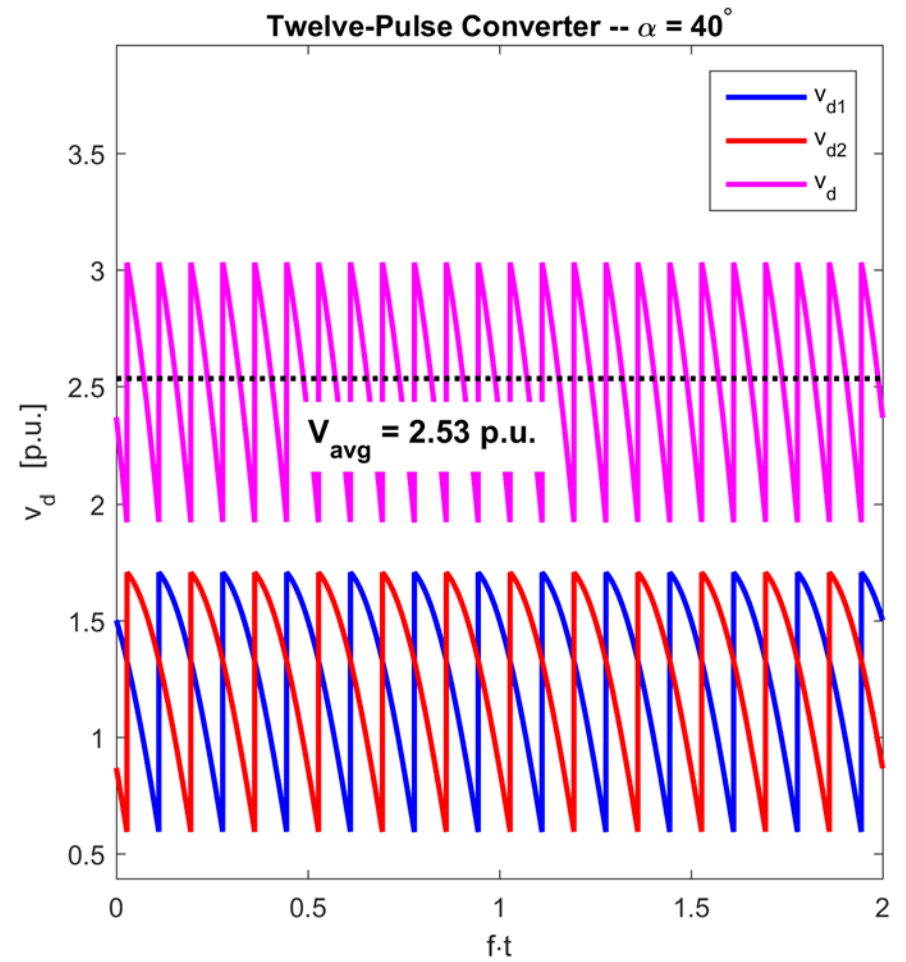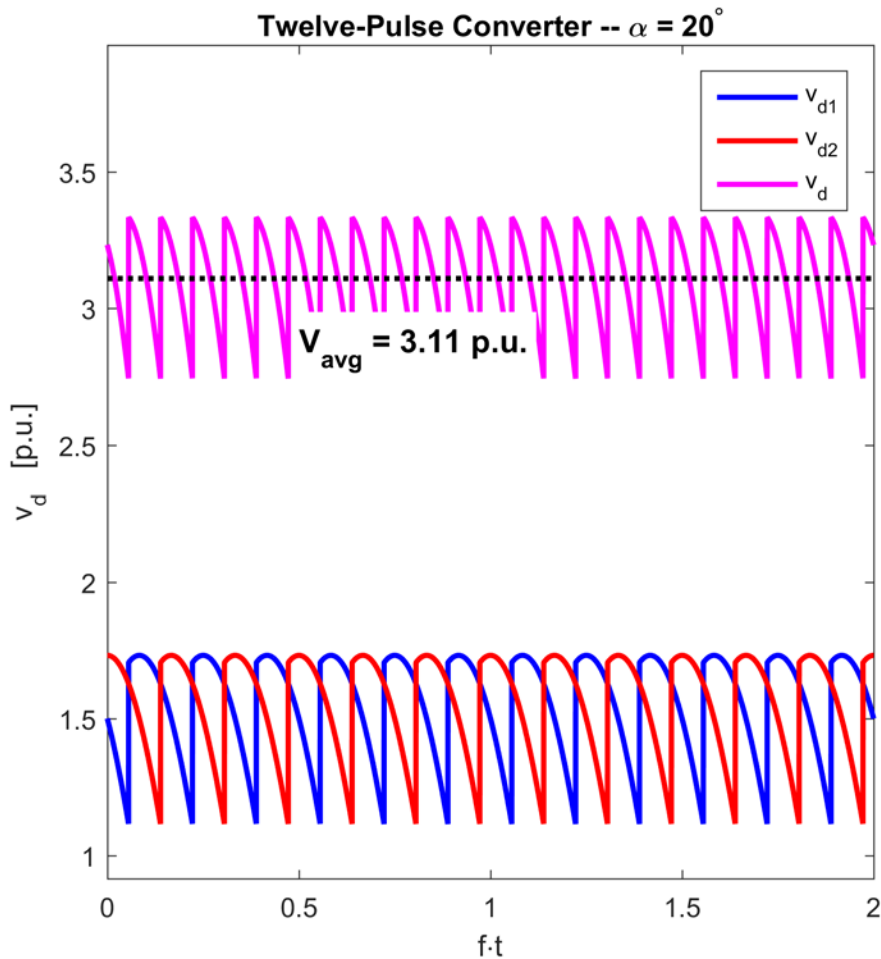

Thyristor Valves

35

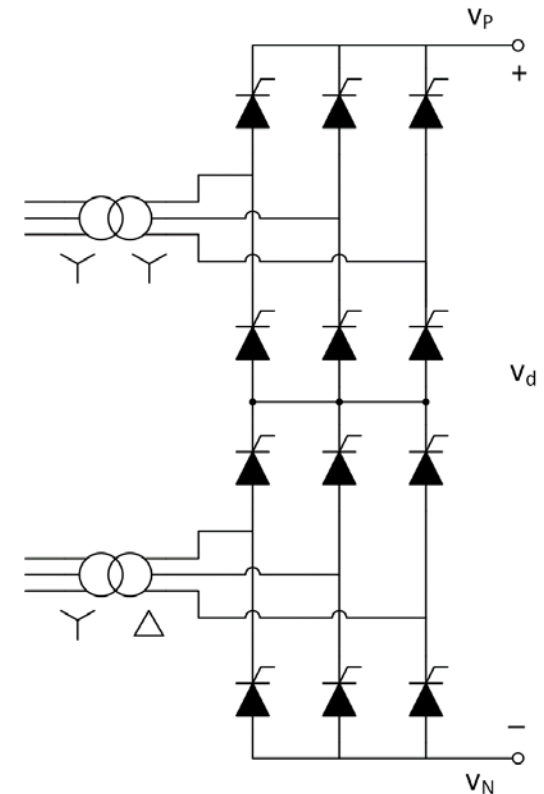- Each thyristor shown in the bridge schematics is really many series-connected thyristors
 - ▣ Necessary to withstand high voltages
 - ▣ Each group of thyristors called a **valve**



36


Voltage Source Converters

Voltage Source Converters

37

- **VSC HVDC** systems use switching devices that can be turned on and off
 - ▣ **IGBT**: insulated-gate bipolar transistor
 - ▣ **GTO**: gate-turn-off thyristor
 - ▣ **IGCT**: insulated gate commutated thyristor

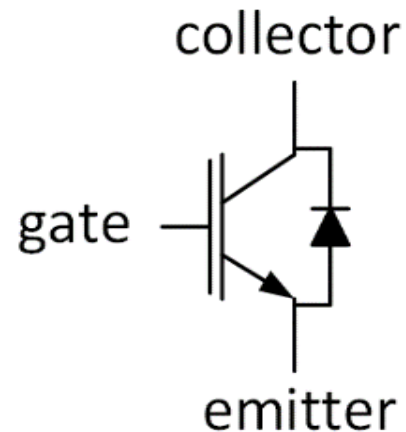- Most commonly used devices are **IGBTs** with anti-parallel free-wheeling diodes




Voltage Source Converters

38



- **VSC configurations:**
 - Two-level converter
 - Multi-level converter
 - Modular multi-level converter (MMC)

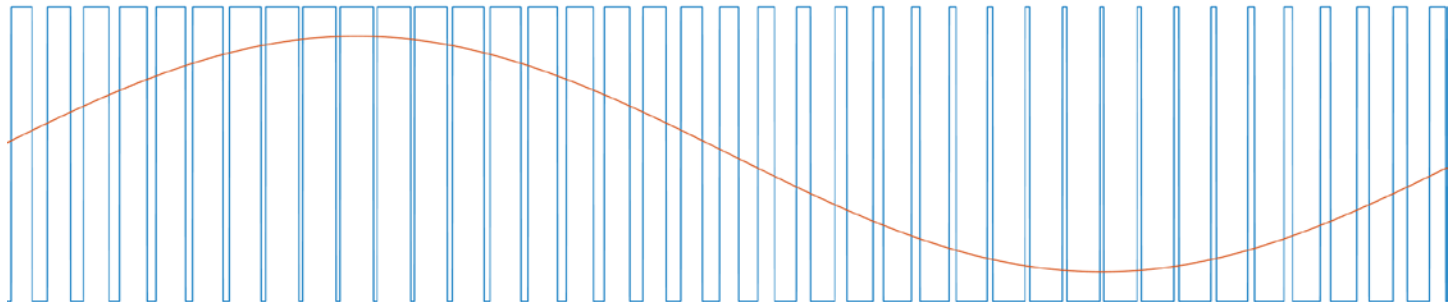- Operation of two-level and multi-level converter is based on the principle of ***pulse-width modulation (PWM)***
 - Switches open and close between three-phase AC and DC poles at a frequency well above the power line frequency
 - Duration that switches are connected to DC voltage (pulse width) is varied
 - Average output voltage approximates sinusoids at the line frequency



Two-Level Converter



39

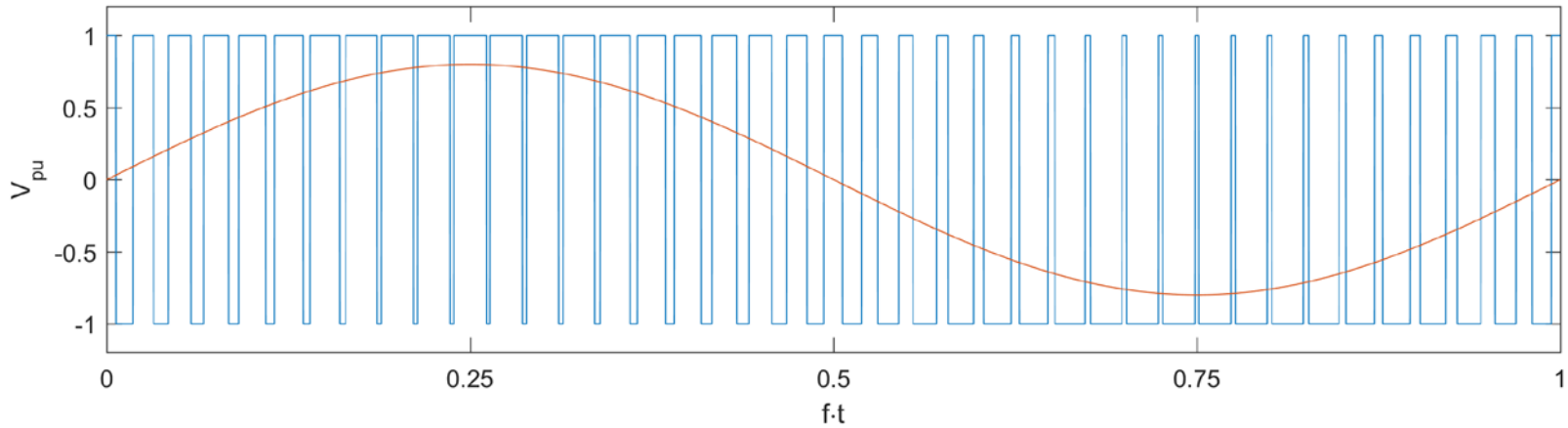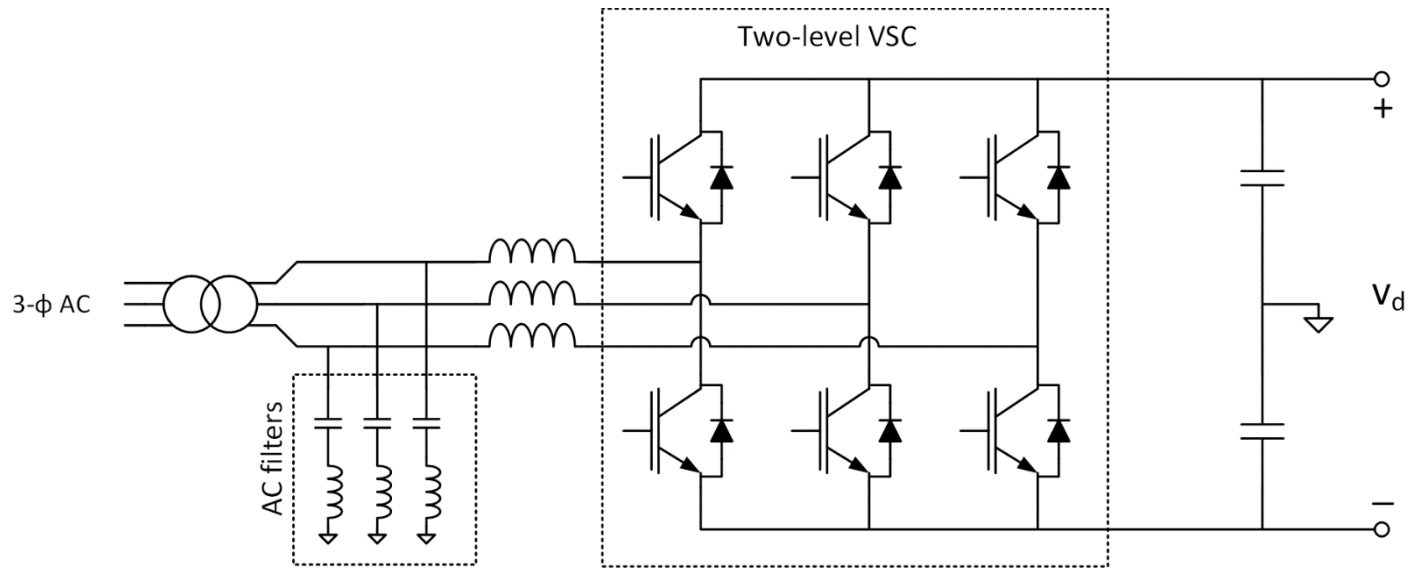

Three-Level Converter

40

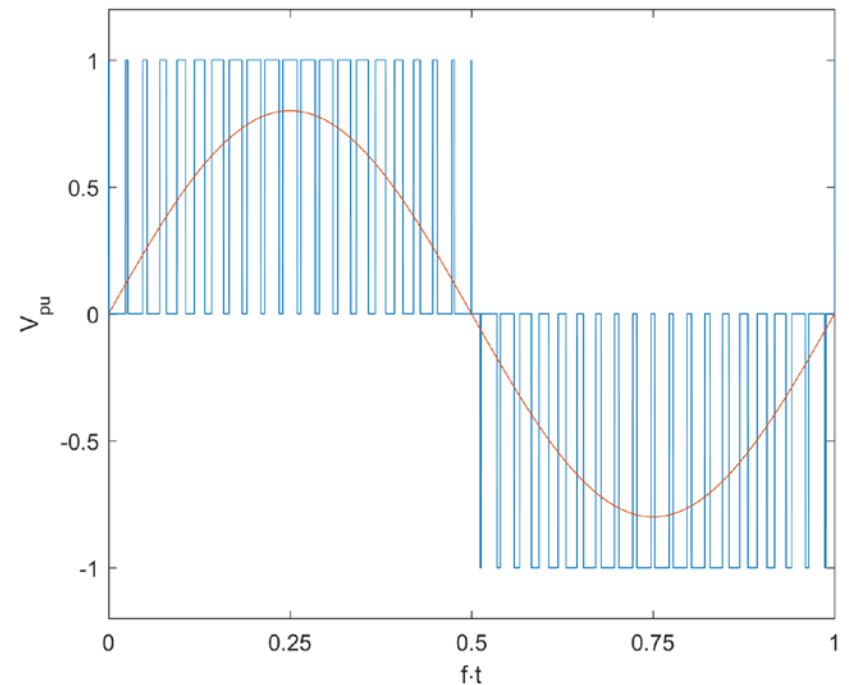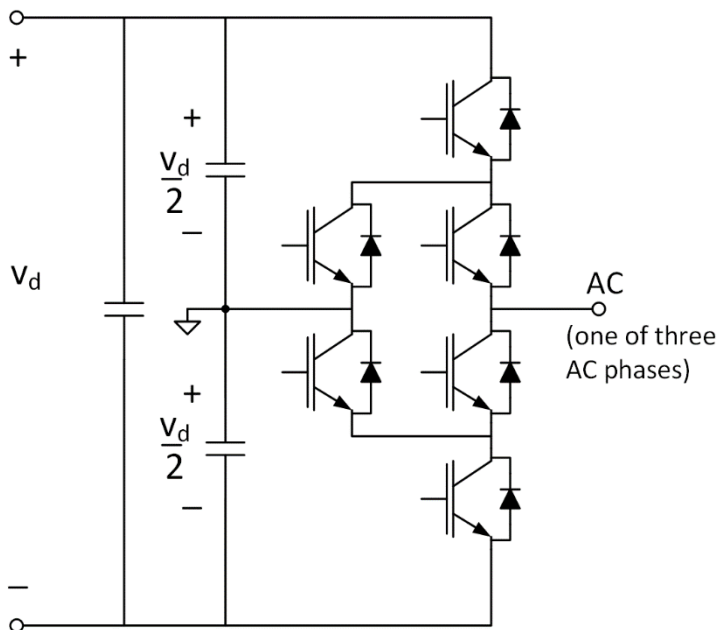- Similar to two-level VSC, but now PWM voltage switches between three levels
 - ▣ Closer approximation of a sinusoid
 - ▣ Harmonics are reduced
 - ▣ Filtering requirements are reduced



Modular Multilevel Converter



41

- ***Modular multilevel converter (MMC)***
 - Six valves, like two-level converter
 - One connecting each AC phase to each DC voltage
 - Valves act as individual voltage sources
 - Not binary switches
 - AC synthesized with many (hundreds) voltage levels
 - ***PWM is not used***
 - Lower switching losses
 - ***Very low harmonics***
 - Filtering often unnecessary
 - Much smaller converter station footprint
 - Complex control system requirements
 - Common architecture for new HVDC projects
 - E.g. Trans Bay Cable, Pittsburg to San Francisco, CA

Modular Multilevel Converter

42

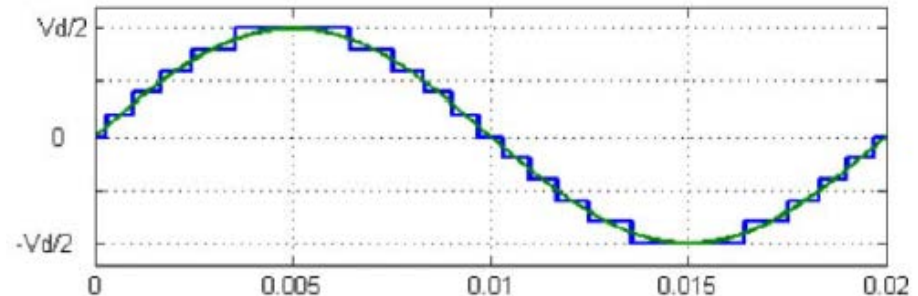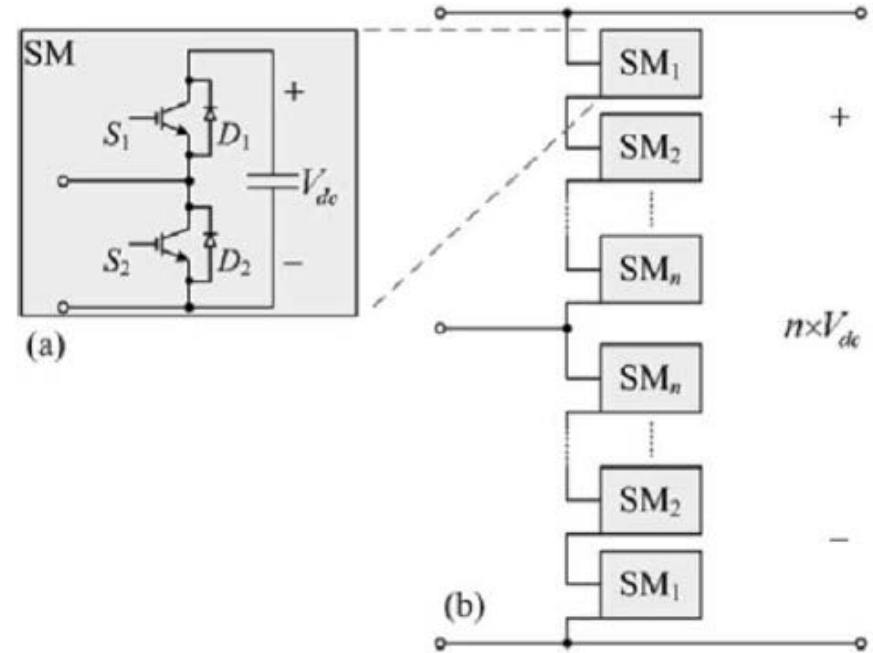- Multiple **submodules** connected in series
 - Typically hundreds
 - One for each voltage level
- Two states for each:
 - Capacitor connected in series with the output
 - Stored voltage added to the output
 - Capacitor bypassed
 - No voltage added to the output



source: *An Overview Introduction of VSC-HVDC: State-of-art and Potential Applications in Electric Power Systems*; Feng Wang, Tuan Le, Anders Mannikoff, Anders Bergman; Cigrè International Symposium, Bologna, Italy, Sept. 2011.

43

HVDC Converter Stations

Valve Hall

44

- Thyristor valve units
 - Installed indoors – ***valve hall***
 - Valves are suspended from the ceiling
 - Lower voltage near the ceiling
 - Highest voltages at the bottom
 - Air insulated
 - Water cooled



Converter Transformers

45


- Converter transformers are located outside
 - ▣ Large wall bushings bring AC power into the valve hall



Converter Station

46

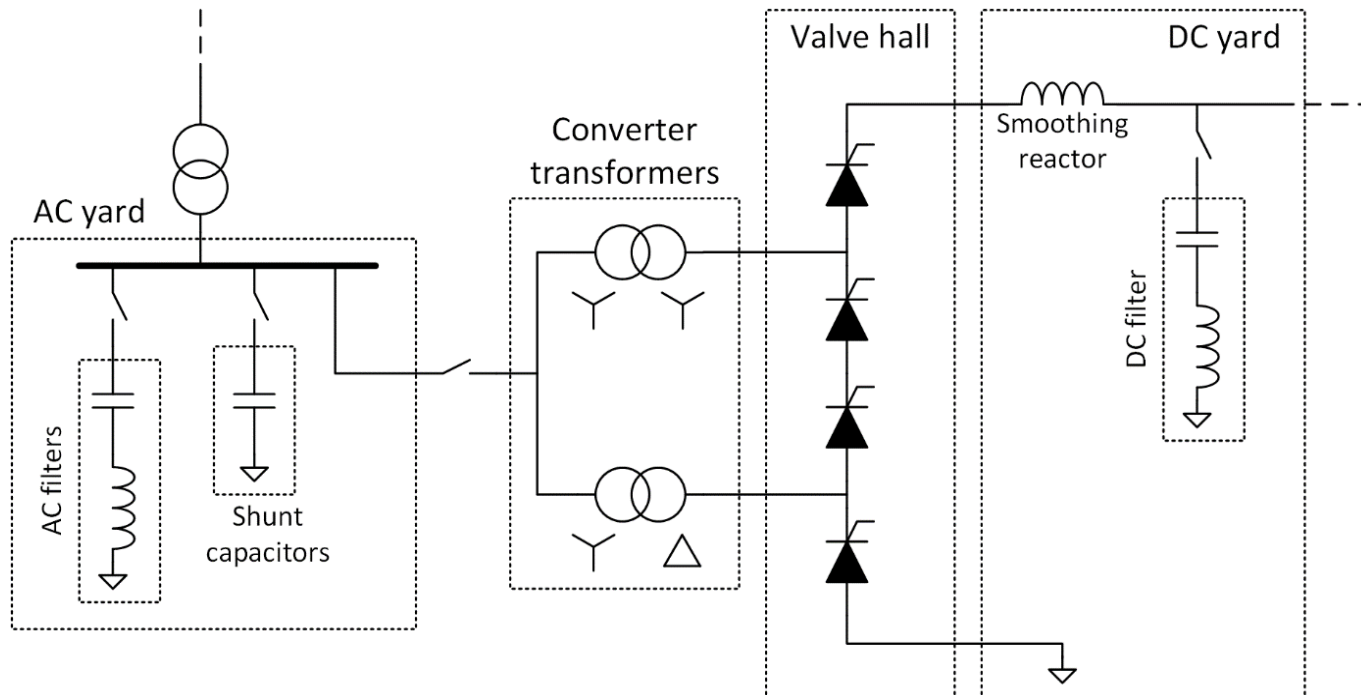
- Simplified converter station one-line for single HVDC pole:



- Replicated for bipolar configuration

Converter Station


47

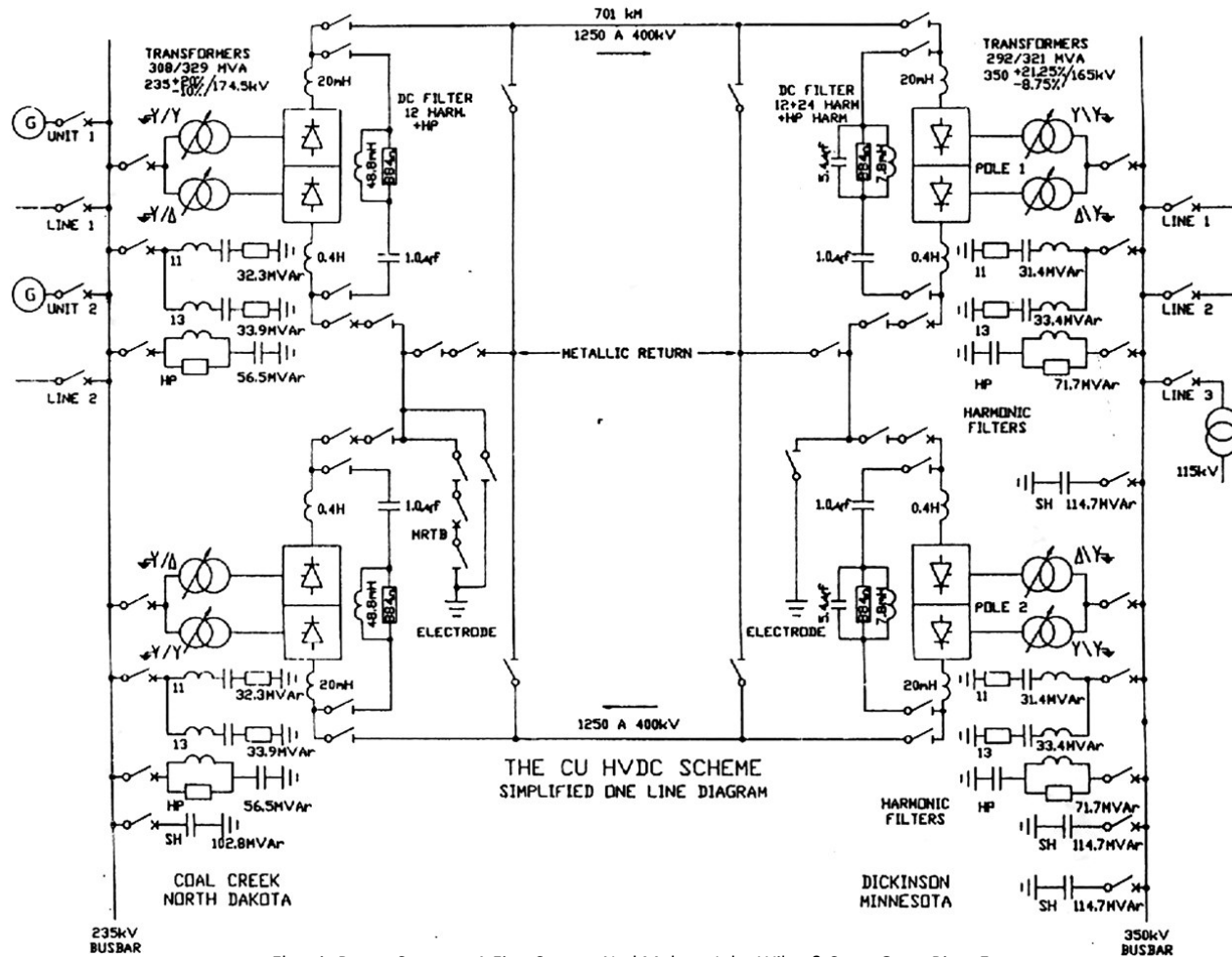

source: Electric Power Systems, A First Course; Ned Mohan; John Wiley & Sons; Great River Energy

Station Layout – Single DC Pole

48

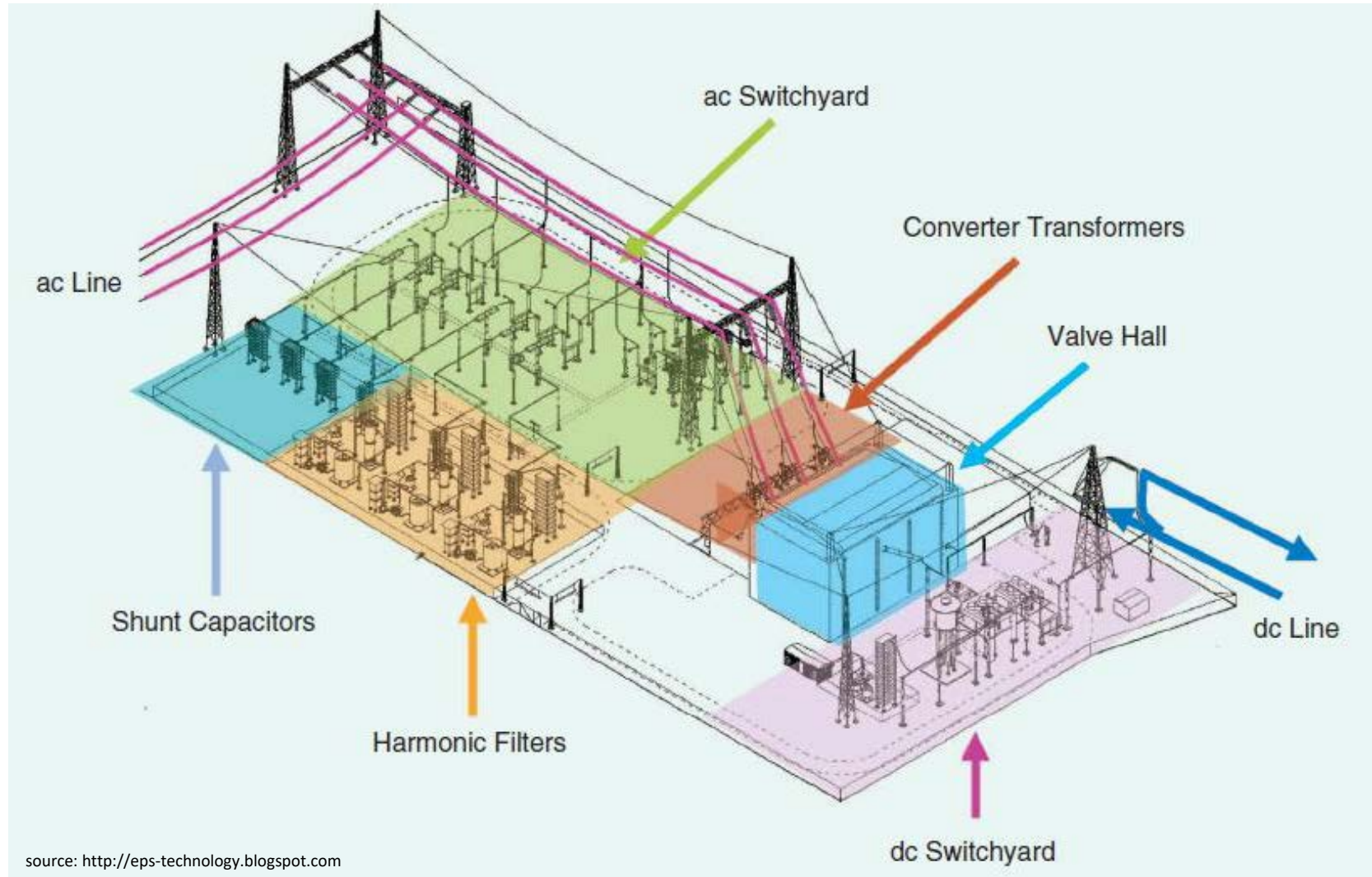

49

Example HVDC Projects

Pacific DC Intertie

50

- The Dalles, OR to Sylmar, CA
 - ▣ Columbia River hydropower to LA
- Length: 1,362 km
- Capacity: 3100 MW
 - ▣ ~50% of LA's peak load
- Bipolar w/ ground return
 - ▣ ± 500 kV
- Twelve-pulse thyristor converters



Pacific DC Intertie

51

- Pacific DC Intertie towers south of Prineville



Rio Madeira, Brazil

52


- Amazon basin to Sao Paulo
 - ▣ Hydropower to coastal cities
- Length: 2,375 km
 - ▣ World's longest
- Capacity: 6300 MW
- Bipolar w/ ground return
 - ▣ ± 600 kV
- Twelve-pulse thyristor converters



Trans Bay Cable

53

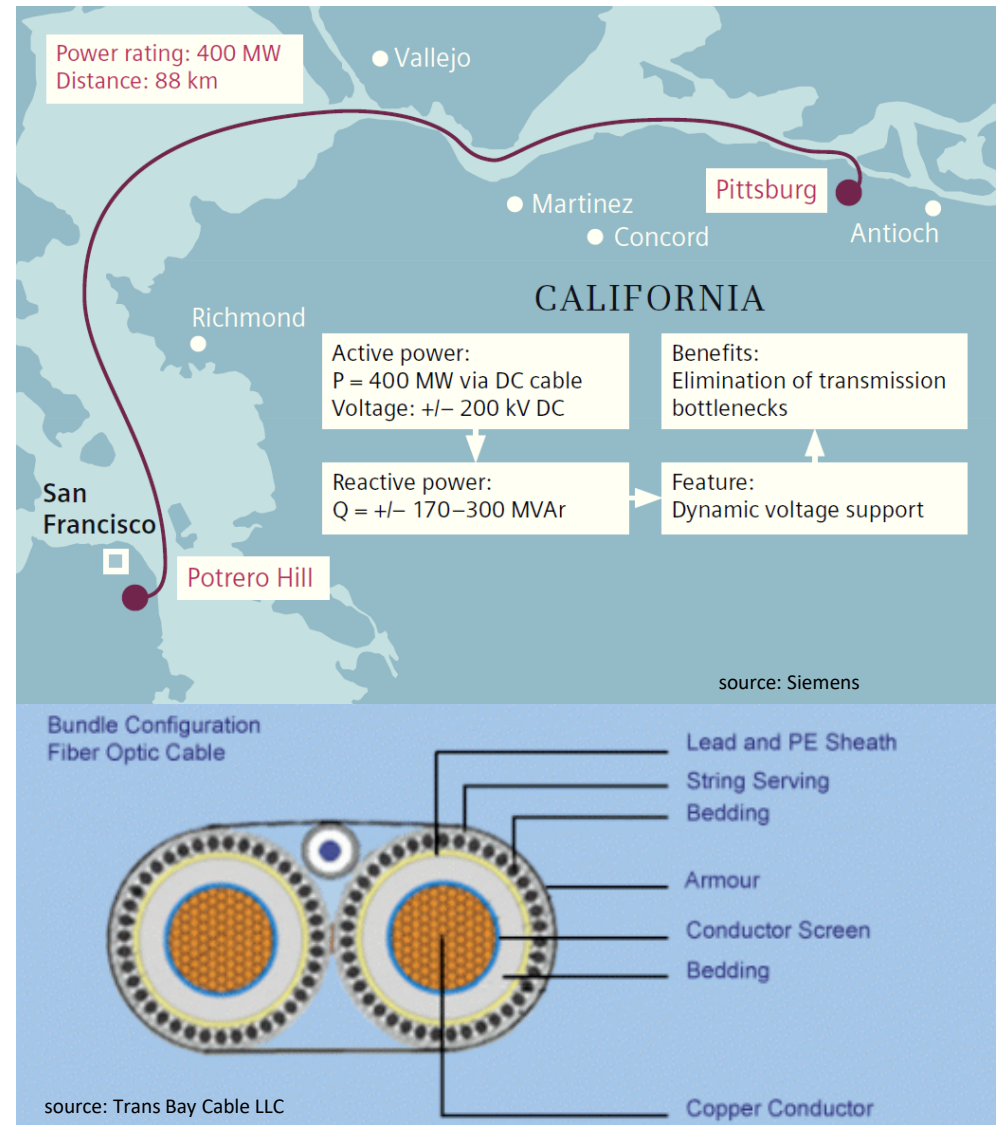
- Pittsburg, CA to San Francisco
 - ▣ Additional power to geographically-isolated San Francisco
- Length: 88 km
 - ▣ Under the SF Bay
- Capacity: 800 MW
- Bipolar with metallic return
 - ▣ ± 200 kV
- MMC VSC



Tres Amigas – B2B Converter

54

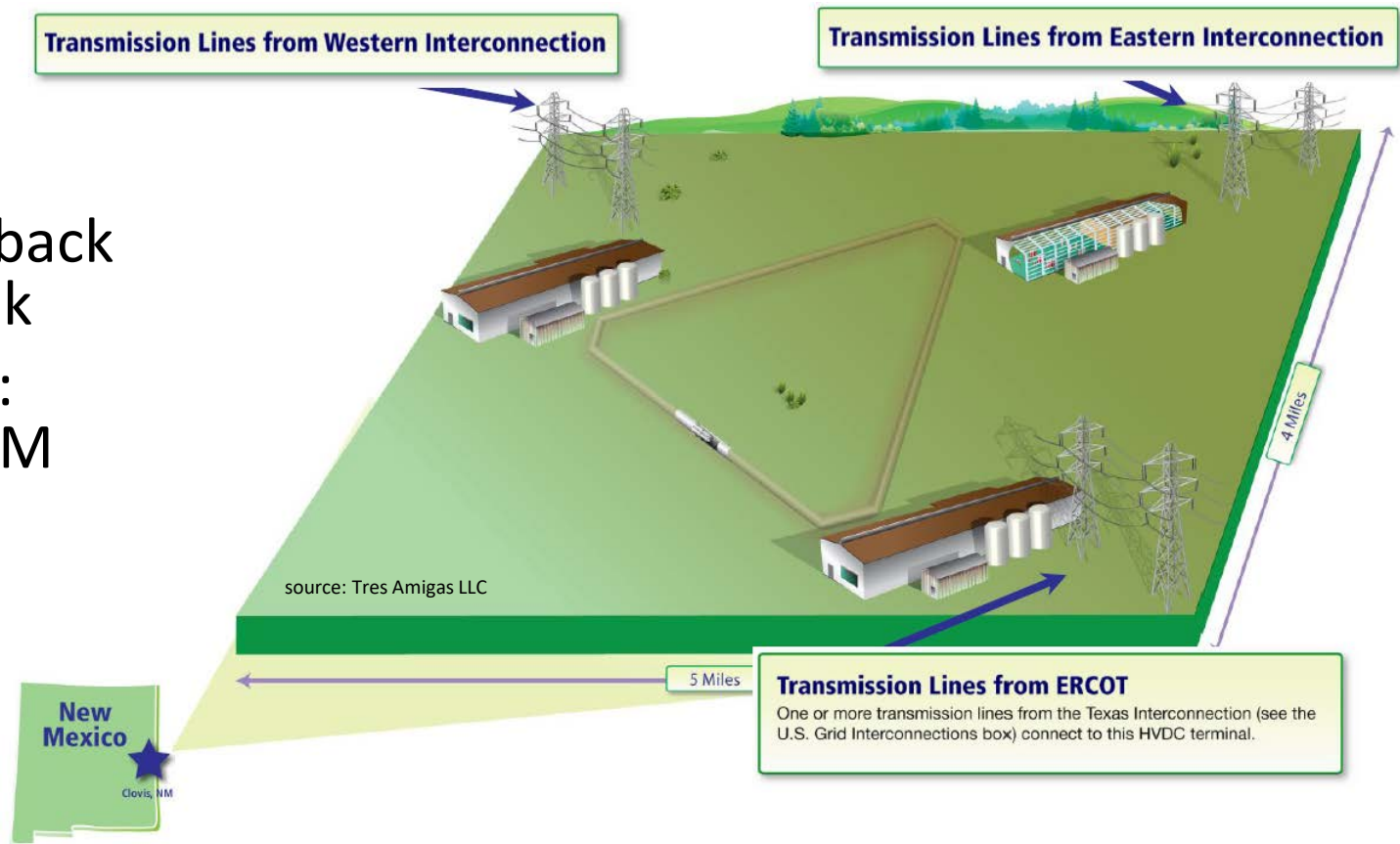- Back-to-back HVDC link
- Location: Clovis, NM



- Back-to-back converters will connect Eastern, Western, and Texas Interconnections

Tres Amigas – B2B Converter

55

- HVDC converter stations
 - ▣ Connected by three 5 GW DC links
 - ▣ Scalable to 30 GW
- High temperature superconducting DC cable
 - ▣ Underground ring configuration
- Converter station may also include 5 MW battery storage for voltage and frequency regulation
- Project still in planning phases
 - ▣ System design/timeline still uncertain