

SECTION 7: FAULT ANALYSIS

ESE 470 – Energy Distribution Systems

2

Introduction

Power System Faults

3

- **Faults** in three-phase power systems are **short circuits**
 - Line-to-ground
 - Line-to-line
- Result in the flow of excessive current
 - Damage to equipment
 - Heat – burning/melting
 - Structural damage due to large magnetic forces
- **Bolted** short circuits
 - True short circuits – i.e., zero impedance
- In general, fault impedance may be non-zero
- Faults may be **opens** as well
 - We'll focus on short circuits

Types of Faults

4

- Type of faults from most to least common:
 - ▣ Single line-to-ground faults
 - ▣ Line-to-line faults
 - ▣ Double line-to-ground faults
 - ▣ Balanced three-phase (symmetrical) faults

- We'll look first at the least common type of fault – the symmetrical fault – due to its simplicity

5 Subtransient Fault Current


Fault Current

6

- Faults occur nearly instantaneously
 - Lightning, tree fall, arcing over insulation, etc.
- Step change from steady-state behavior
 - Like throwing a switch to create the fault at $t = 0$
- Consider an unloaded synchronous generator
 - Equivalent circuit model:

- R: generator resistance
- L: generator inductance
- $i(t) = 0$ for $t < 0$

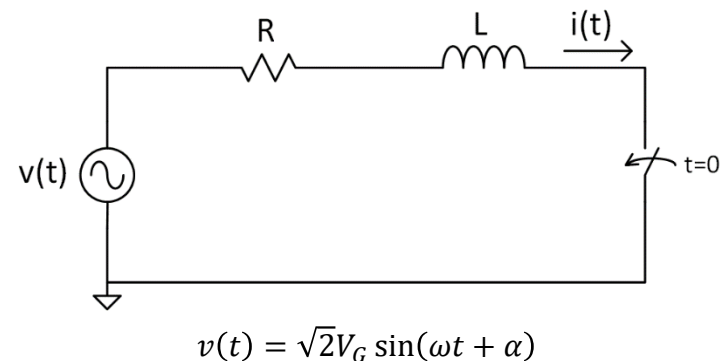- Source phase, α , determines voltage at $t = 0$
 - Short circuit can occur at any point in a 60 Hz cycle



Fault Current

7

- The governing differential equation for $t > 0$ is

$$\frac{di}{dt} + i(t) \frac{R}{L} = \frac{\sqrt{2}V_G}{L} \sin(\omega t + \alpha)$$

- The solution gives the fault current

$$i(t) = \frac{\sqrt{2}V_G}{Z} \left[\sin(\omega t + \alpha - \theta) - \sin(\alpha - \theta) e^{-t\frac{R}{L}} \right]$$

where $Z = \sqrt{R^2 + (\omega L)^2}$ and $\theta = \tan^{-1} \left(\frac{\omega L}{R} \right)$

- This total fault current is referred to as the ***asymmetrical fault current***
 - It has a ***steady-state*** component




$$i_{ac}(t) = \frac{\sqrt{2}V_G}{Z} \sin(\omega t + \alpha - \theta)$$

- And a ***transient*** component

$$i_{dc}(t) = -\frac{\sqrt{2}V_G}{Z} \sin(\alpha - \theta) e^{-t\frac{R}{L}}$$

Fault Current

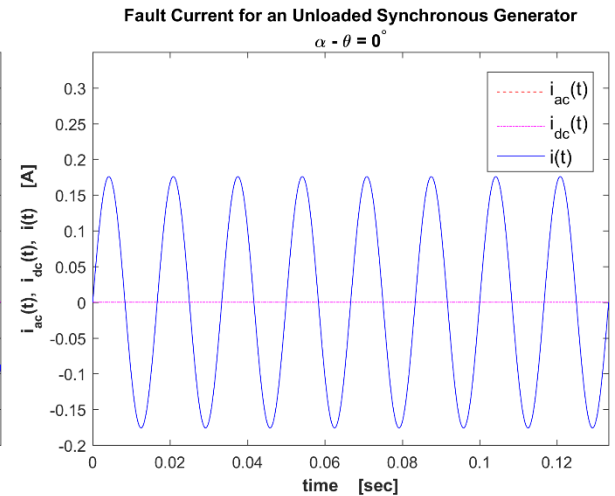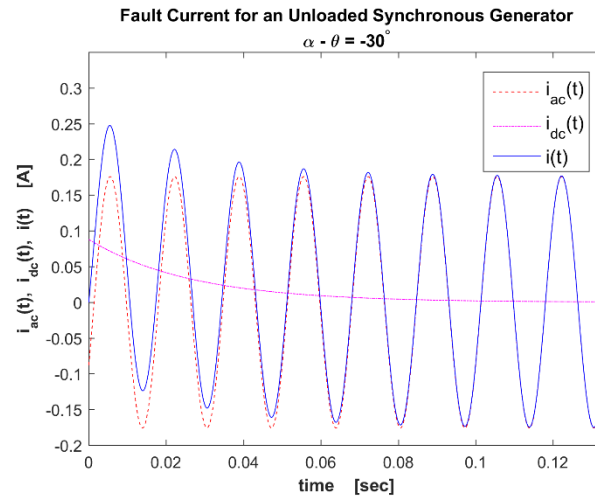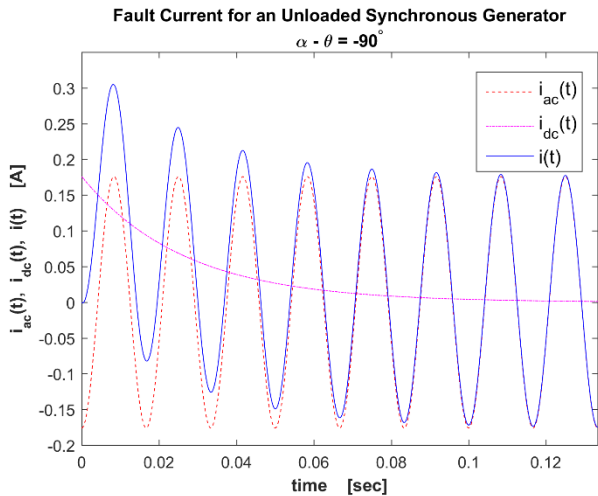- Magnitude of the transient fault current, i_{dc} , depends on α
 - $i_{dc}(0) = 0$ for $\alpha = \theta$
 - $i_{dc}(0) = \sqrt{2}I_{ac}$ for $\alpha = \theta - 90^\circ$
 - $I_{ac} = V_G/Z$ is the rms value of the steady-state fault current



- Worst-case fault current occurs for $\alpha = \theta - 90^\circ$

$$i(t) = \frac{\sqrt{2}V_G}{Z} \left[\sin\left(\omega t - \frac{\pi}{2}\right) + e^{-t\frac{R}{L}} \right]$$

Fault Current

- Important points here:
 - Total fault current has both ***steady-state*** and ***transient*** components – asymmetrical
 - Magnitude of the asymmetry (transient component) depends on the ***phase of the generator voltage*** at the time of the fault
 - In this class, we will use the ***steady-state*** current component, \mathbf{I}_{ac} , as our primary fault current metric

Generator Reactance

10

- The reactance of the generator was assumed constant in the previous example
- Physical characteristics of real generators result in a ***time-varying reactance*** following a fault
 - Time-dependence modeled with ***three reactance values***
 - X_d'' : subtransient reactance
 - X_d' : transient reactance
 - X_d : synchronous reactance
 - Reactance increases with time, such that

$$X_d'' < X_d' < X_d$$

Sub-Transient Fault Current

11

- Transition rates between reactance values are dictated by two time constants:
 - τ_d'' : short-circuit subtransient time constant
 - τ_d' : short-circuit transient time constant
- Neglecting generator resistance, i.e. assuming $\theta = 90^\circ$, the synchronous portion of the fault current is

$$i_{ac}(t) = \sqrt{2}V_G \left[\left(\frac{1}{X_d''} - \frac{1}{X_d'} \right) e^{-\frac{t}{\tau_d''}} + \left(\frac{1}{X_d'} - \frac{1}{X_d} \right) e^{-\frac{t}{\tau_d'}} + \frac{1}{X_d} \right] \sin \left(\omega t + \alpha - \frac{\pi}{2} \right)$$

- At the instant of the fault, $t = 0$, the rms synchronous fault current is

$$I_F'' = \frac{V_G}{X_d''}$$

- This is the rms **subtransient fault current**, I_F''
- This will be our primary metric for assessing fault current

12

Symmetrical Three-Phase Short Circuits

Symmetrical 3- ϕ Short Circuits


13

- Next, we'll calculate the subtransient fault current resulting from a balanced three-phase fault
- We'll make the following simplifying assumptions:
 - Transformers modeled with leakage reactance only
 - Neglect winding resistance and shunt admittances
 - Neglect Δ - Y phase shifts
 - Transmission lines modeled with series reactance only
 - Synchronous machines modeled as constant voltage sources in series with subtransient reactances
 - Generators and motors
 - Induction motors are neglected or modeled as synchronous motors
 - Non-rotating loads are neglected

Symmetrical 3- ϕ Short Circuits

14

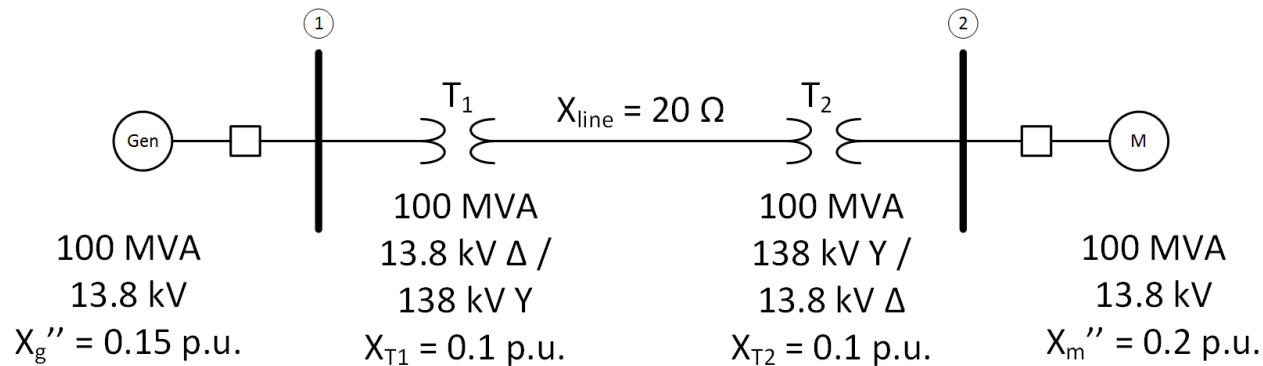- We'll apply superposition to determine three-phase subtransient fault current
- Consider the following power system:




- Assume there is a balanced three-phase short of bus 1 to ground at $t = 0$


Symmetrical 3- ϕ Short Circuits

15

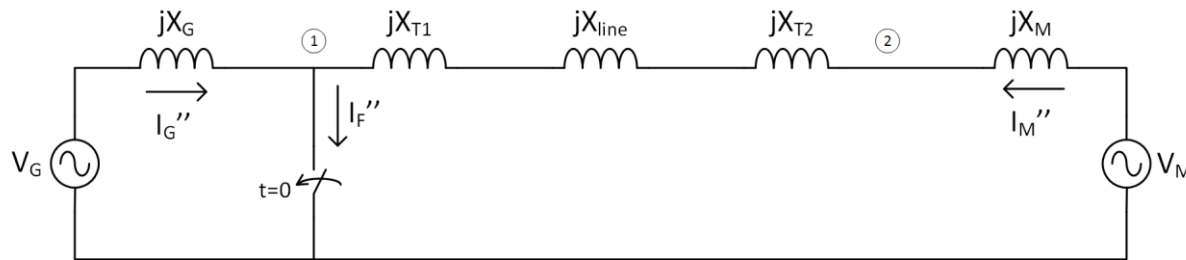- The instant of the fault can be modeled by the switch closing in the following line-to-neutral schematic




- The short circuit (closed switch) can be represented by two back-to-back voltage sources, each equal to V_F

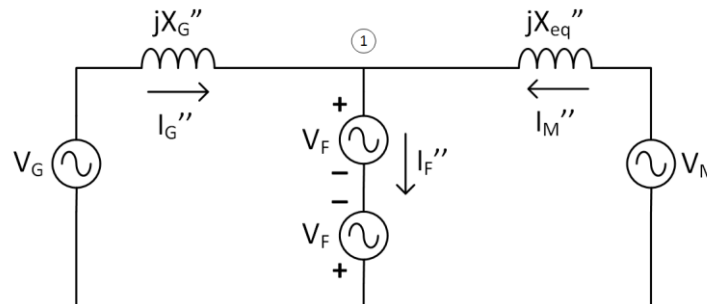


Symmetrical 3- ϕ Short Circuits

16

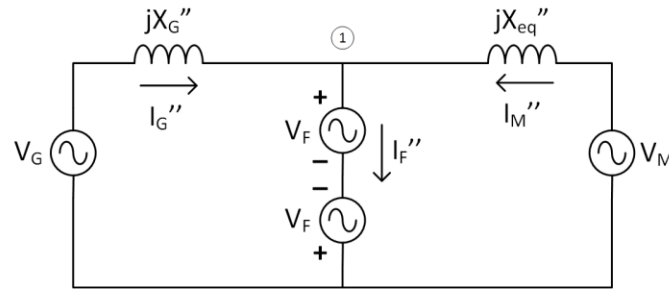


- Applying superposition, we can represent this circuit as the sum of two separate circuits:

Circuit 1

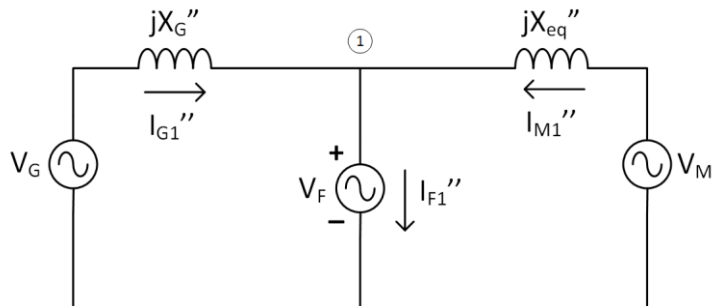

Circuit 2

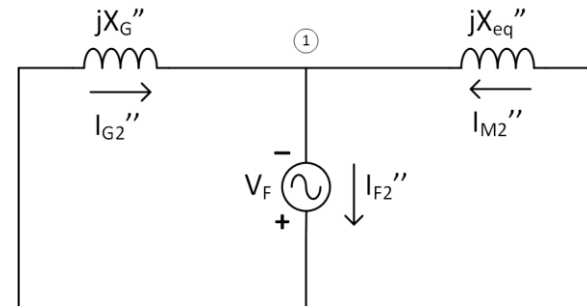

Symmetrical 3- ϕ Short Circuits


17

- Assume that the value of the fault-location source, V_F , is the **pre-fault voltage** at that location
 - ▣ Circuit 1, then, represents the **pre-fault circuit**, so


$$I''_{F1} = 0$$

- ▣ The V_F source can therefore be removed from circuit 1

Circuit 1

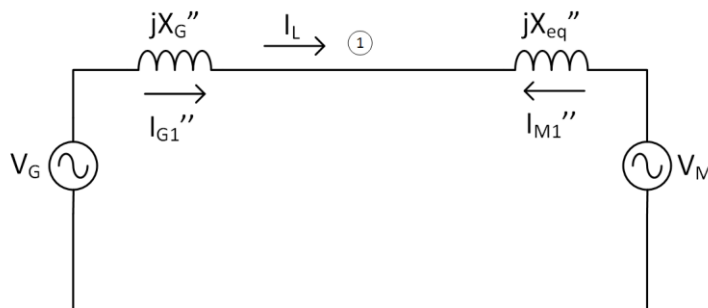

Circuit 2

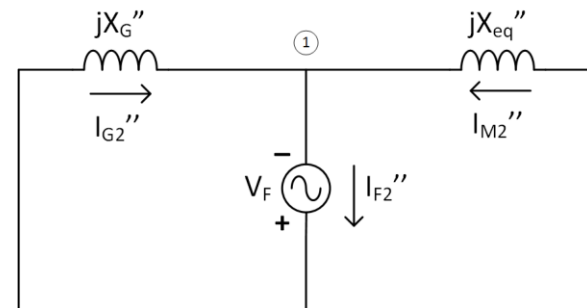

Symmetrical 3- ϕ Short Circuits

18

- The current in circuit 1, I_L , is the pre-fault line current
- Superposition gives the fault current

$$I''_F = I''_{F1} + I''_{F2} = I''_{F2}$$

- The generator fault current is

$$I''_G = I''_{G1} + I''_{G2}$$

$$I''_G = I_L + I''_{G2}$$


- The motor fault current is

$$I''_M = I''_{M1} + I''_{M2}$$

$$I''_M = -I_L + I''_{M2}$$

Symmetrical 3- ϕ Fault – Example


19

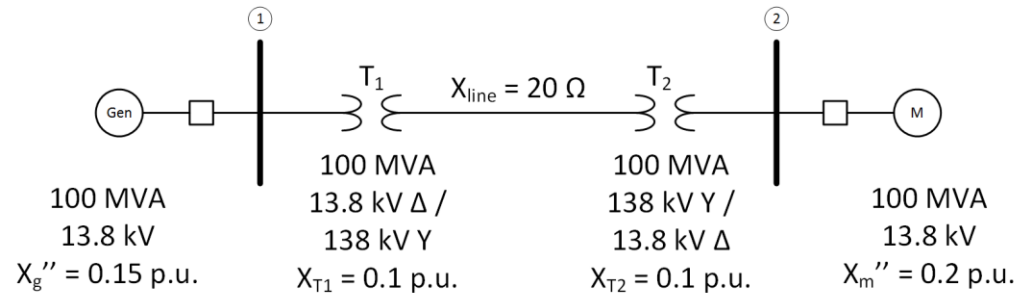

- For the simple power system above:
 - Generator is supplying rated power
 - Generator voltage is 5% above rated voltage
 - Generator power factor is 0.95 lagging
- A bolted three-phase fault occurs at bus 1
- Determine:
 - Subtransient fault current
 - Subtransient generator current
 - Subtransient motor current

Symmetrical 3- ϕ Fault – Example

20

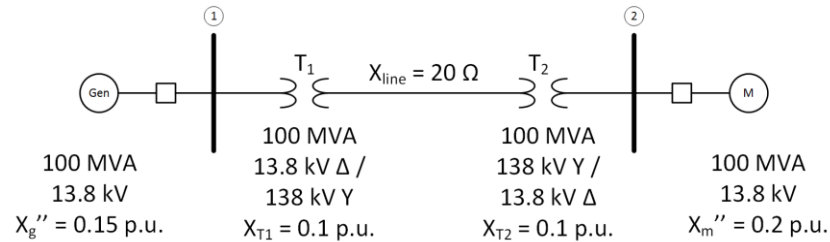

- First convert to per-unit
 - Use $S_b = 100$ MVA
- Base voltage in the transmission line zone is

$$V_{b,tl} = 138 \text{ kV}$$

- Base impedance in the transmission line zone is

$$Z_{b,tl} = \frac{V_{b,tl}^2}{S_b} = \frac{(138 \text{ kV})^2}{100 \text{ MVA}} = 190.4 \Omega$$



- The per-unit transmission line reactance is

$$X_{tl} = \frac{20 \Omega}{190.4 \Omega} = 0.105 \text{ p.u.}$$



Symmetrical 3- ϕ Fault – Example

21

- The two per-unit circuits are

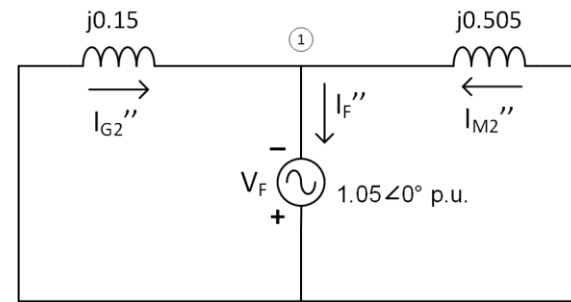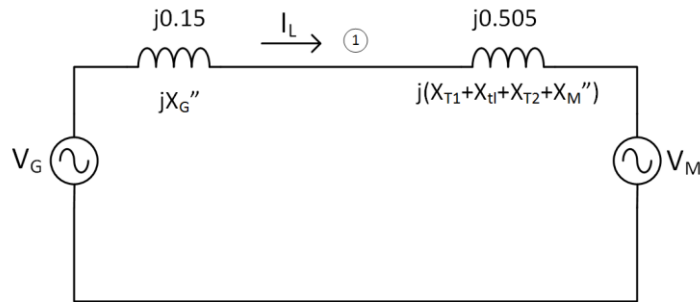

- These can be simplified by combining impedances

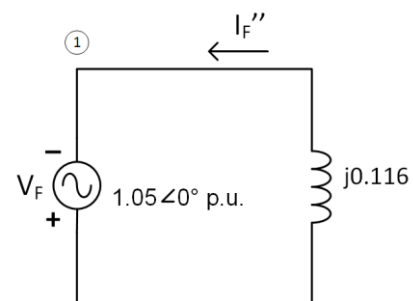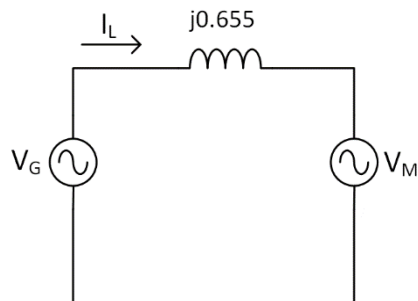

Symmetrical 3- ϕ Fault – Example

22

- Using circuit 2, we can calculate the subtransient fault current

$$\mathbf{I''_F} = \frac{1.05\angle 0^\circ}{j0.116} = 9.079\angle -90^\circ \text{ p.u.}$$

- To convert to kA, first determine the current base in the generator zone

$$I_{b,G} = \frac{S_b}{\sqrt{3}V_{b,G}} = \frac{100 \text{ MVA}}{\sqrt{3} \cdot 13.8 \text{ kV}} = 4.18 \text{ kA}$$

- The **subtransient fault current** is

$$\mathbf{I''_F} = (9.079\angle -90^\circ) \cdot 4.18 \text{ kA}$$

$$\mathbf{I''_F} = 37.98\angle -90^\circ \text{ kA}$$

Symmetrical 3- ϕ Fault – Example

23

- The **pre-fault line current** can be calculated from the pre-fault generator voltage and power

$$I_L = \left(\frac{S_G/3}{V_G''/\sqrt{3}} \right)^* = \left(\frac{S_G}{\sqrt{3}V_G''} \right)^* = \frac{(100 \angle \cos^{-1}(0.95) \text{ MVA})^*}{(\sqrt{3} \cdot 1.05 \cdot 13.8 \angle 0^\circ \text{ kV})^*}$$

$$I_L = \frac{100 \angle -18.19^\circ \text{ MVA}}{\sqrt{3} \cdot 1.05 \cdot 13.8 \angle 0^\circ \text{ kV}}$$

$$I_L = 3.98 \angle -18.19^\circ \text{ kA}$$

- Or, in per-unit:

$$I_L = \frac{3.98 \angle -18.19^\circ \text{ kA}}{4.18 \text{ kA}} = 0.952 \angle -18.19^\circ \text{ p.u.}$$

- This will be used to find the generator and motor fault currents

Symmetrical 3- ϕ Fault – Example

24

- The generator's contribution to the fault current is found by applying current division

$$I''_{G2} = I''_F \frac{0.505}{0.505 + 0.15} = 7.0 \angle -90^\circ \text{ p.u.}$$

- Adding the pre-fault line current, we have the **subtransient generator fault current**

$$I''_G = I_L + I''_{G2}$$

$$I''_G = 0.952 \angle -18.19^\circ + 7.0 \angle -90^\circ$$

$$I''_G = 7.35 \angle -82.9^\circ \text{ p.u.}$$

- Converting to kA

$$I''_G = (7.35 \angle -82.9^\circ) \cdot 4.18 \text{ kA}$$

$$I''_G = 30.74 \angle -82.9^\circ \text{ kA}$$

Symmetrical 3- ϕ Fault – Example

25

- Similarly, for the motor

$$I''_{M2} = I''_F \frac{0.15}{0.505 + 0.15} = 2.08 \angle -90^\circ \text{ p.u.}$$

- Subtracting the pre-fault line current gives the **subtransient motor fault current**

$$I''_M = -I_L + I''_{M2}$$

$$I''_M = -0.952 \angle -18.19^\circ + 2.08 \angle -90^\circ$$

$$I''_M = 2.0 \angle -116.9^\circ$$

- Converting to kA

$$I''_M = (2.0 \angle -116.9^\circ) \cdot 4.18 \text{ kA}$$

$$I''_M = 8.36 \angle -116.9^\circ \text{ kA}$$

26

Symmetrical Components

Symmetrical Components

27

- In the previous section, we saw how to calculate subtransient fault current for balanced three-phase faults
- Unsymmetrical faults are much more common
 - ▣ Analysis is more complicated
- We'll now learn a tool that will simplify the analysis of unsymmetrical faults
 - ▣ The ***method of symmetrical components***

Symmetrical Components

28


- The ***method of symmetrical components***:
 - Represent an asymmetrical set of N phasors as a sum of N sets of symmetrical component phasors
 - These N sets of phasors are called ***sequence components***
- Analogous to:
 - Decomposition of electrical signals into differential and common-mode components
 - Decomposition of forces into orthogonal components
- For a three-phase system ($N = 3$), sequence components are:
 - Zero sequence components
 - Positive sequence components
 - Negative sequence components

Sequence Components

29


□ **Zero sequence components**

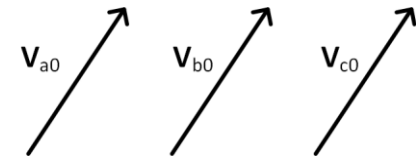- Three phasors with equal magnitude and equal phase
- V_{a0}, V_{b0}, V_{c0}




□ **Positive sequence components**

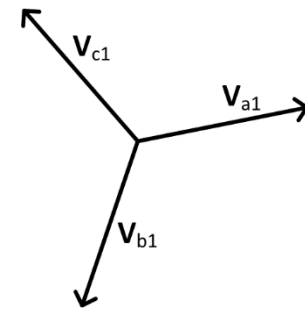- Three phasors with equal magnitude and $\pm 120^\circ$, positive-sequence phase
- V_{a1}, V_{b1}, V_{c1}



□ **Negative sequence components**

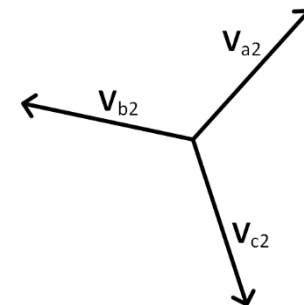- Three phasors with equal magnitude and $\pm 120^\circ$, negative-sequence phase
- V_{a2}, V_{b2}, V_{c2}



Sequence Components

- Note that the absolute phase and the magnitudes of the sequence components is not specified
 - ▣ Magnitude and phase define a unique set of sequence components
- ***Any set of phasors – balanced or unbalanced – can be represented as a sum of sequence components***

$$\begin{bmatrix} \mathbf{V}_a \\ \mathbf{V}_b \\ \mathbf{V}_c \end{bmatrix} = \begin{bmatrix} \mathbf{V}_{a0} \\ \mathbf{V}_{b0} \\ \mathbf{V}_{c0} \end{bmatrix} + \begin{bmatrix} \mathbf{V}_{a1} \\ \mathbf{V}_{b1} \\ \mathbf{V}_{c1} \end{bmatrix} + \begin{bmatrix} \mathbf{V}_{a2} \\ \mathbf{V}_{b2} \\ \mathbf{V}_{c2} \end{bmatrix} \quad (1)$$

Sequence Components

31

- The phasors of each sequence component have a fixed phase relationship
 - ▣ If we know one, we know the other two
 - ▣ Assume we know phase a – use that as the reference

- For the zero sequence components, we have

$$\mathbf{V}_0 = \mathbf{V}_{a0} = \mathbf{V}_{b0} = \mathbf{V}_{c0} \quad (2)$$

- For the positive sequence components,

$$\mathbf{V}_1 = \mathbf{V}_{a1} = (1\angle 120^\circ) \cdot \mathbf{V}_{b1} = (1\angle 240^\circ) \cdot \mathbf{V}_{c1} \quad (3)$$

- And, for the negative sequence components,

$$\mathbf{V}_2 = \mathbf{V}_{a2} = (1\angle 240^\circ) \cdot \mathbf{V}_{b2} = (1\angle 120^\circ) \cdot \mathbf{V}_{c2} \quad (4)$$

- Note that we're using phase a as our reference, so

$$\mathbf{V}_0 = \mathbf{V}_{a0}, \quad \mathbf{V}_1 = \mathbf{V}_{a1}, \quad \mathbf{V}_2 = \mathbf{V}_{a2}$$

Sequence Components

32

- Next, we define a complex number, a , that has unit magnitude and phase of 120°

$$a = 1\angle 120^\circ \quad (5)$$

- ▣ Multiplication by a results in a rotation (a phase shift) of 120°
 - ▣ Multiplication by a^2 yields a rotation of $240^\circ = -120^\circ$
- Using (5) to rewrite (3) and (4)

$$V_1 = V_{a1} = aV_{b1} = a^2V_{c1} \quad (6)$$

$$V_2 = V_{a2} = a^2V_{b2} = aV_{c2} \quad (7)$$

Sequence Components

- Using (2), (6), and (7), we can rewrite (1) in a simplified form

$$\begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} V_0 \\ V_1 \\ V_2 \end{bmatrix} \quad (8)$$

- The vector on the left is the vector of phase voltages, V_p
 - The vector on the right is the vector of (phase a) sequence components, V_s
 - We'll call the 3×3 transformation matrix A
- We can rewrite (8) as

$$V_p = AV_s \quad (9)$$

Sequence Components

- We can express the sequence voltages as a function of the phase voltages by inverting the transformation matrix

$$\mathbf{V}_s = \mathbf{A}^{-1} \mathbf{V}_p \quad (10)$$

where

$$\mathbf{A}^{-1} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \quad (11)$$

So

$$\begin{bmatrix} \mathbf{V}_0 \\ \mathbf{V}_1 \\ \mathbf{V}_2 \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} \mathbf{V}_a \\ \mathbf{V}_b \\ \mathbf{V}_c \end{bmatrix} \quad (12)$$

Sequence Components

35

- The same relationships hold for three-phase currents
- The phase currents are

$$\mathbf{I}_p = \begin{bmatrix} \mathbf{I}_a \\ \mathbf{I}_b \\ \mathbf{I}_c \end{bmatrix}$$

- And, the sequence currents are

$$\mathbf{I}_s = \begin{bmatrix} \mathbf{I}_0 \\ \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix}$$

Sequence Components

36

- The transformation matrix, \mathbf{A} , relates the phase currents to the sequence currents

$$\mathbf{I}_p = \mathbf{A}\mathbf{I}_s$$

$$\begin{bmatrix} \mathbf{I}_a \\ \mathbf{I}_b \\ \mathbf{I}_c \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} \mathbf{I}_0 \\ \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} \quad (13)$$

- And vice versa

$$\mathbf{I}_s = \mathbf{A}^{-1}\mathbf{I}_p$$

$$\begin{bmatrix} \mathbf{I}_0 \\ \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} \mathbf{I}_a \\ \mathbf{I}_b \\ \mathbf{I}_c \end{bmatrix} \quad (14)$$

Sequence Components – Balanced System

37

- Before applying sequence components to unbalanced systems, let's first look at the ***sequence components for a balanced, positive-sequence, three-phase system***
- For a ***balanced system***, we have

$$V_b = V_a \cdot 1\angle -120^\circ = a^2 V_a$$

$$V_c = V_a \cdot 1\angle 120^\circ = a V_a$$

- The sequence voltages are given by (12)
 - The ***zero sequence voltage*** is

$$V_0 = \frac{1}{3}[V_a + V_b + V_c] = \frac{1}{3}[V_a + a^2 V_a + a V_a]$$

$$V_0 = \frac{1}{3}V_a[1 + a^2 + a]$$

- Applying the identity $1 + a^2 + a = 0$, we have

$$V_0 = 0$$

Sequence Components – Balanced System

38

- The ***positive sequence component*** is given by

$$V_1 = \frac{1}{3} [V_a + aV_b + a^2V_c]$$

$$V_1 = \frac{1}{3} [V_a + a \cdot a^2V_a + a^2 \cdot aV_a]$$

$$V_1 = \frac{1}{3} [V_a + a^3V_a + a^3V_a]$$

- Since $a^3 = 1 \angle 0^\circ$, we have

$$V_1 = \frac{1}{3} [3V_a]$$

$$V_1 = V_a$$

Sequence Components – Balanced System

39

- The ***negative sequence component*** is given by

$$V_2 = \frac{1}{3} [V_a + a^2 V_b + a V_c]$$

$$V_2 = \frac{1}{3} [V_a + a^2 \cdot a^2 V_a + a \cdot a V_a]$$

$$V_2 = \frac{1}{3} [V_a + a^4 V_a + a^2 V_a]$$

- Again, using the identity $1 + a^2 + a = 0$, along with the fact that $a^4 = a$, we have

$$V_2 = 0$$

Sequence Components – Balanced System

40

- So, for a **positive-sequence, balanced**, three-phase system, the **sequence voltages** are

$$V_0 = 0, \quad V_1 = V_a, \quad V_2 = 0$$

- Similarly, the **sequence currents** are

$$I_0 = 0, \quad I_1 = I_a, \quad I_2 = 0$$

- This is as we would expect
 - ▣ No zero- or negative-sequence components for a positive-sequence balanced system
 - ▣ Zero- and negative-sequence components are only used to account for imbalance

Sequence Components

41

- We have just introduced the concept of ***symmetric components***
 - ▣ Allows for decomposition of, possibly unbalanced, three-phase phasors into ***sequence components***
- We'll now apply this concept to power system networks to develop ***sequence networks***
 - ▣ ***Decoupled networks*** for each of the sequence components
 - ▣ Sequence networks become ***coupled only at the point of imbalance***
 - ▣ Simplifies the analysis of unbalanced systems

42

Sequence Networks

Sequence Networks

43

- ***Power system components each have their own set of sequence networks***
 - Non-rotating loads
 - Transmission lines
 - Rotating machines – generators and motors
 - Transformers
- Sequence networks for overall systems are interconnections of the individual sequence network
- Sequence networks become coupled in a particular way at the fault location depending on type of fault
 - Line-to-line
 - Single line-to-ground
 - Double line-to-ground
- Fault current can be determined through simple analysis of the coupled sequence networks

44

Sequence Networks – Non-Rotating Loads

Sequence Networks – Non-Rotating Loads

45

- Consider a balanced Y-load with the neutral grounded through some non-zero impedance
- Applying KVL gives the phase-*a*-to-ground voltage

$$V_{ag} = Z_y I_a + Z_n I_n$$

$$V_{ag} = Z_y I_a + Z_n (I_a + I_b + I_c)$$

$$V_{ag} = (Z_y + Z_n) I_a + Z_n I_b + Z_n I_c \quad (15)$$


- For phase *b*:

$$V_{bg} = Z_y I_b + Z_n I_n = Z_y I_b + Z_n (I_a + I_b + I_c)$$

$$V_{bg} = Z_n I_a + (Z_y + Z_n) I_b + Z_n I_c \quad (16)$$

- Similarly, for phase *c*:
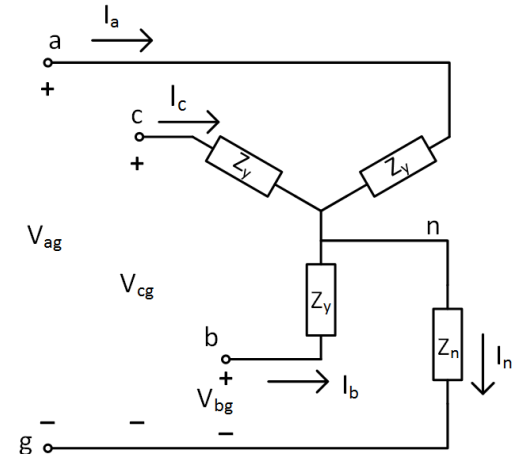
$$V_{cg} = Z_n I_a + Z_n I_b + (Z_y + Z_n) I_c \quad (17)$$



Sequence Networks – Non-Rotating Loads

46

- Putting (15) – (17) in matrix form

$$\begin{bmatrix} \mathbf{V}_{ag} \\ \mathbf{V}_{bg} \\ \mathbf{V}_{cg} \end{bmatrix} = \begin{bmatrix} (Z_y + Z_n) & Z_n & Z_n \\ Z_n & (Z_y + Z_n) & Z_n \\ Z_n & Z_n & (Z_y + Z_n) \end{bmatrix} \begin{bmatrix} \mathbf{I}_a \\ \mathbf{I}_b \\ \mathbf{I}_c \end{bmatrix}$$

or

$$\mathbf{V}_p = \mathbf{Z}_p \mathbf{I}_p \quad (18)$$

where \mathbf{V}_p and \mathbf{I}_p are the phase voltages and currents, respectively, and \mathbf{Z}_p is the **phase impedance matrix**

- We can use (9) and (13) to rewrite (18) as

$$\mathbf{A} \mathbf{V}_s = \mathbf{Z}_p \mathbf{A} \mathbf{I}_s$$

- Solving for \mathbf{V}_s

$$\mathbf{V}_s = \mathbf{A}^{-1} \mathbf{Z}_p \mathbf{A} \mathbf{I}_s$$

or

$$\mathbf{V}_s = \mathbf{Z}_s \mathbf{I}_s \quad (19)$$

Sequence Networks – Non-Rotating Loads

$$\mathbf{V}_s = \mathbf{Z}_s \mathbf{I}_s \quad (19)$$

where Z_s is the *sequence impedance matrix*

$$\mathbf{Z}_s = \mathbf{A}^{-1} \mathbf{Z}_p \mathbf{A} = \begin{bmatrix} (Z_y + 3Z_n) & 0 & 0 \\ 0 & Z_y & 0 \\ 0 & 0 & Z_y \end{bmatrix} \quad (20)$$

- Equation (19) then becomes a set of three uncoupled equations

$$\mathbf{V}_0 = (Z_y + 3Z_n) \mathbf{I}_0 = Z_0 \mathbf{I}_0 \quad (21)$$

$$\mathbf{V}_1 = Z_y \mathbf{I}_1 = Z_1 \mathbf{I}_1 \quad (22)$$


$$\mathbf{V}_2 = Z_y \mathbf{I}_2 = Z_2 \mathbf{I}_2 \quad (23)$$

Sequence Networks – Non-Rotating Loads


48

- Equations (21) – (23) describe the uncoupled ***sequence networks***


- Zero-sequence network:

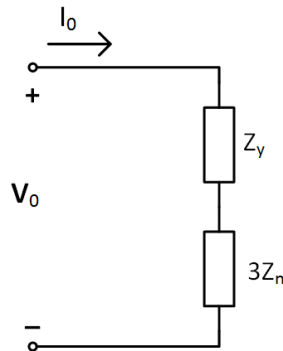

- Positive-sequence network:

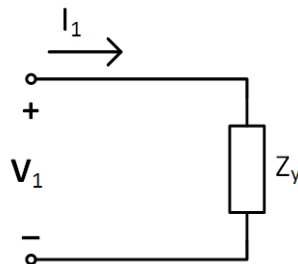

- Negative-sequence network:

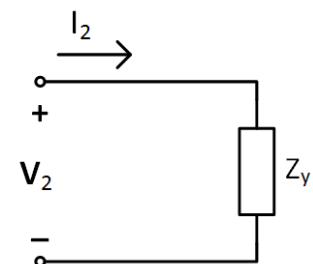


Sequence Networks – Non-Rotating Loads


49

- We can develop similar sequence networks for a balanced Δ -connected load
 - $Z_y = Z_\Delta/3$
 - There is no neutral point for the Δ -network, so $Z_n = \infty$ - an open circuit


- Zero-sequence network:

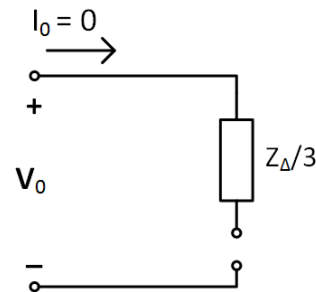

- Positive-sequence network:

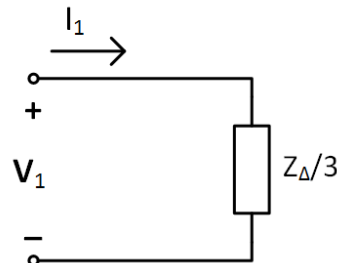

- Negative-sequence network:

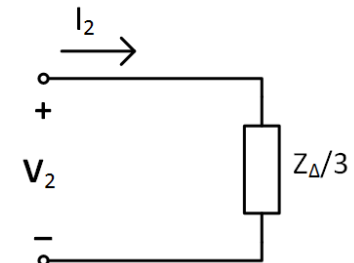


50

Sequence Networks – 3- ϕ Lines

Sequence Networks – 3- ϕ Lines

51

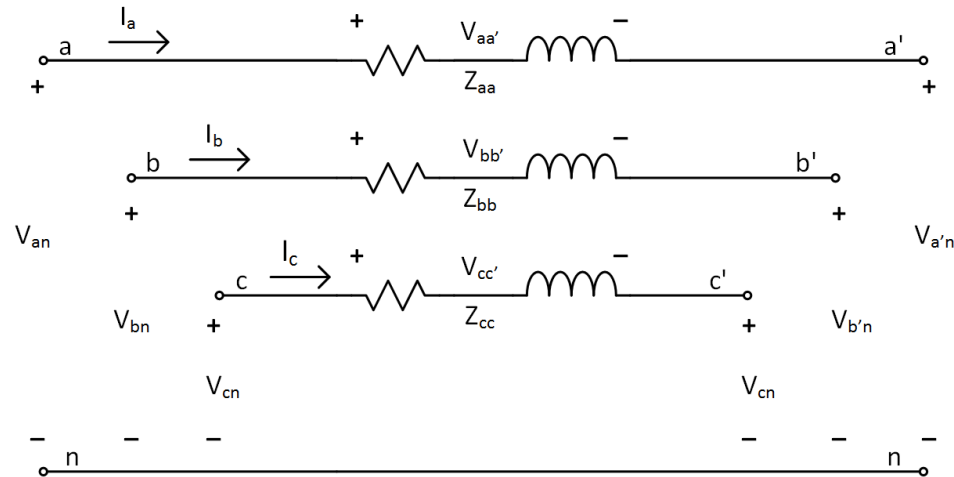- Balanced, three-phase lines can be modeled as



- The voltage drops across the lines are given by the following system of equations

$$\begin{bmatrix} V_{aa'} \\ V_{bb'} \\ V_{cc'} \end{bmatrix} = \begin{bmatrix} Z_{aa} & Z_{ab} & Z_{ac} \\ Z_{ba} & Z_{bb} & Z_{bc} \\ Z_{ca} & Z_{cb} & Z_{cc} \end{bmatrix} \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} V_{an} - V_{a'n} \\ V_{bn} - V_{b'n} \\ V_{cn} - V_{c'n} \end{bmatrix} \quad (24)$$

Sequence Networks – 3- ϕ Lines

52

- Writing (24) in compact form

$$\mathbf{V}_p - \mathbf{V}_{p'} = \mathbf{Z}_p \mathbf{I}_p \quad (25)$$

- \mathbf{Z}_p is the ***phase impedance matrix***
 - Self impedances along the diagonal
 - Mutual impedances elsewhere
 - Symmetric
 - Diagonal, if we neglect mutual impedances

Sequence Networks – 3- ϕ Lines

53

- We can rewrite (25) in terms of sequence components

$$AV_s - AV_{s'} = Z_p AI_s$$

$$V_s - V_{s'} = A^{-1} Z_p AI_s$$

$$V_s - V_{s'} = Z_s I_s \tag{26}$$

where Z_s is the sequence impedance matrix

$$Z_s = A^{-1} Z_p A \tag{27}$$

- Z_s is diagonal so long as the system impedances are balanced, i.e.
 - ▣ Self impedances are equal: $Z_{aa} = Z_{bb} = Z_{cc}$
 - ▣ Mutual impedances are equal: $Z_{ab} = Z_{ac} = Z_{bc}$

Sequence Networks – 3- ϕ Lines

54

- For balanced lines, \mathbf{Z}_S is diagonal

$$\mathbf{Z}_S = \begin{bmatrix} Z_{aa} + 2Z_{ab} & 0 & 0 \\ 0 & Z_{aa} - Z_{ab} & 0 \\ 0 & 0 & Z_{aa} - Z_{ab} \end{bmatrix} = \begin{bmatrix} Z_0 & 0 & 0 \\ 0 & Z_1 & 0 \\ 0 & 0 & Z_2 \end{bmatrix}$$

- Because Z_S is diagonal, (26) represents three uncoupled equations

$$\mathbf{V}_0 - \mathbf{V}_{0'} = Z_0 \mathbf{I}_0 \quad (28)$$

$$\mathbf{V}_1 - \mathbf{V}_{1'} = Z_1 \mathbf{I}_1 \quad (29)$$


$$\mathbf{V}_2 - \mathbf{V}_{2'} = Z_2 \mathbf{I}_2 \quad (30)$$

Sequence Networks – 3- ϕ Lines


55

- Equations (28) – (30) describe the voltage drop across three uncoupled ***sequence networks***


- Zero-sequence network:

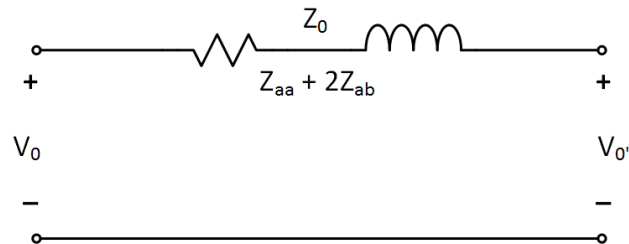

- Positive-sequence network:

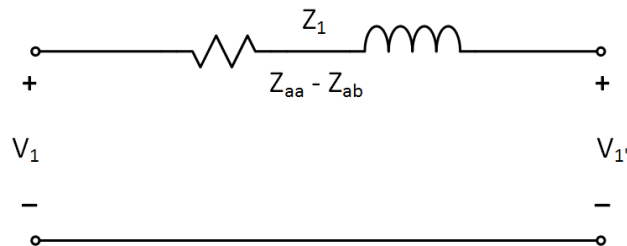

- Negative-sequence network:

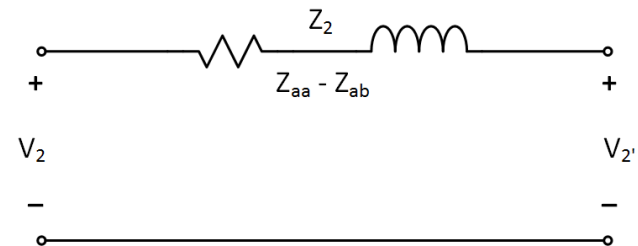


56

Sequence Networks –Rotating Machines

Sequence Networks – Rotating Machines

57

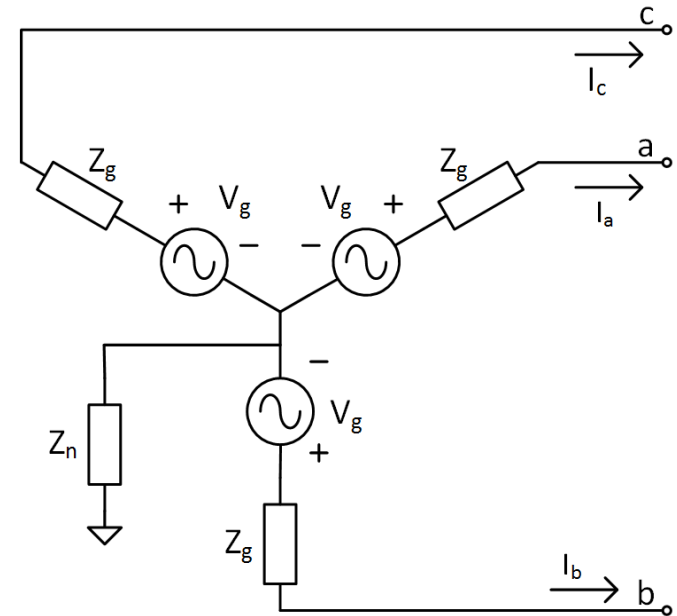- Consider the following model for a **synchronous generator**
- Similar to the Y-connected load
 - ▣ Generator includes **voltage sources** on each phase
- Voltage sources are **positive sequence**
 - ▣ Sources will appear **only in the positive-sequence network**




Sequence Networks – Synchronous Generator


58

□ Sequence networks for Y-connected synchronous generator


▣ Zero-sequence network:

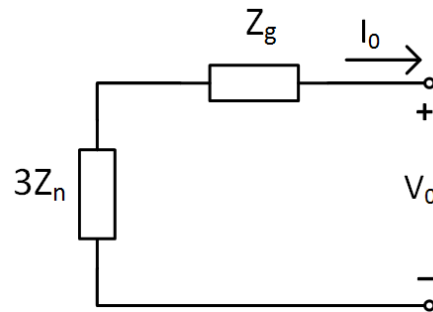

▣ Positive-sequence network:

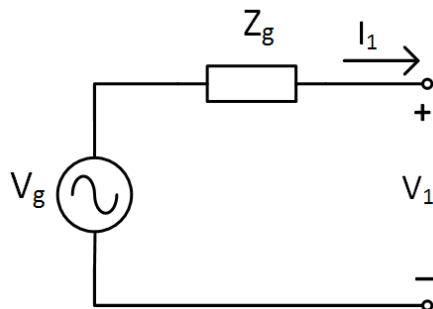

▣ Negative-sequence network:

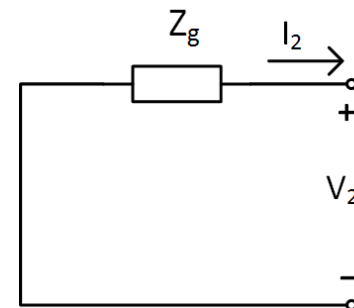

Sequence Networks – Motors

59

□ Synchronous motors

- Sequence networks identical to those for synchronous generators
- Reference current directions are reversed

□ Induction motors

- Similar sequence networks to synchronous motors, except source in the positive sequence network set to zero


60

Sequence Networks – Transformers

Sequence Networks - Y-Y Transformers

61

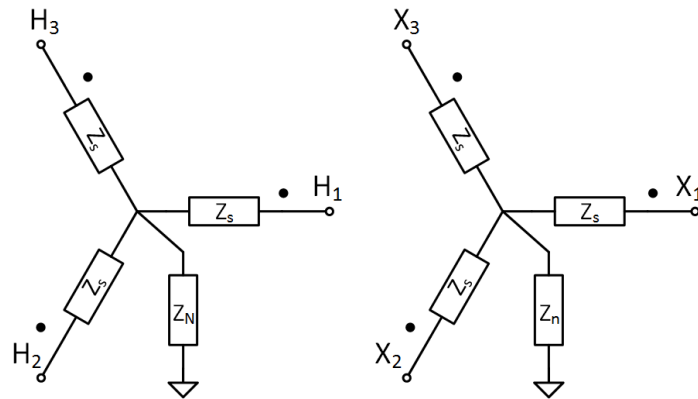- Per-unit sequence networks for transformers
 - ▣ Simplify by neglecting transformer shunt admittances
- Consider a Y-Y transformer




- Similar to the Y-connected load, the voltage drops across the neutral impedances are $3I_0Z_N$ and $3I_0Z_n$
 - ▣ $3Z_N$ and $3Z_n$ each appear in the zero-sequence network
 - ▣ Can be combined in the per-unit circuit as long as shunt impedances are neglected

Sequence Networks – Y-Y Transformers


62

- Impedance accounting for leakage flux and winding resistance for each winding can be referred to the primary
 - Add together into a single impedance, Z_s , in the per-unit model
- Y-Y transformer sequence networks


- Zero-sequence network:

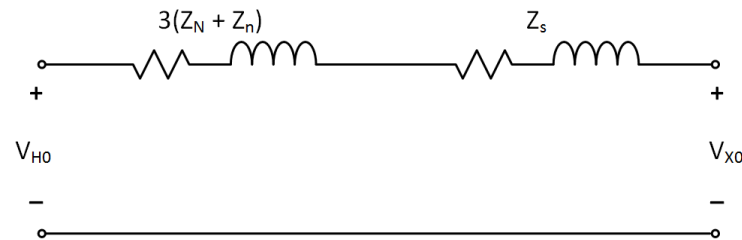

- Positive-sequence network:

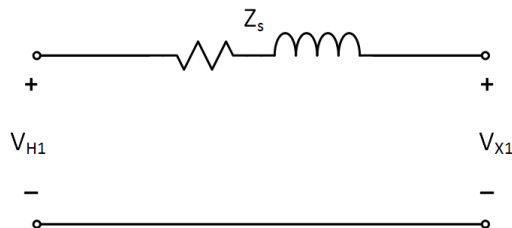


- Negative-sequence network:

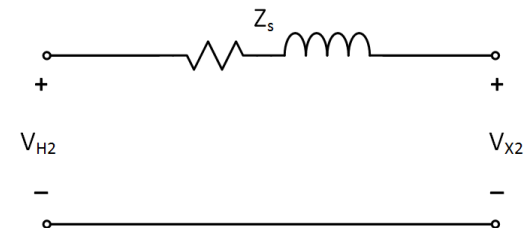

Sequence Networks – Y- Δ Transformers

63

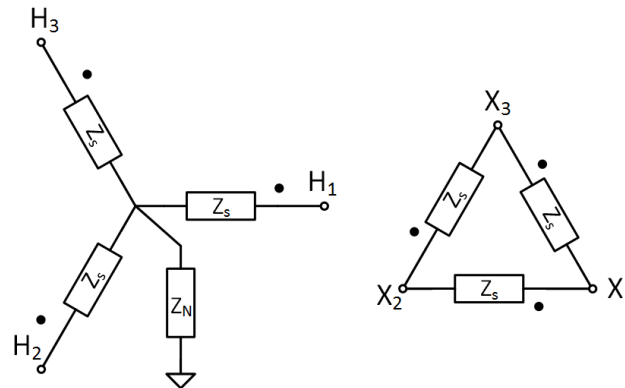- Y- Δ transformers differ in a couple of ways




- Must account for phase shift from primary to secondary
 - For positive-sequence network, Y-side voltage and current lead Δ -side voltage and current
 - For negative-sequence network, Y-side voltage and current lag Δ -side voltage and current
- No neutral connection on the Δ side
 - Zero-sequence current cannot enter or leave the Δ winding

Sequence Networks – Y-Δ Transformers


64

□ Sequence networks for Y-Δ Transformers


□ Zero-sequence network:

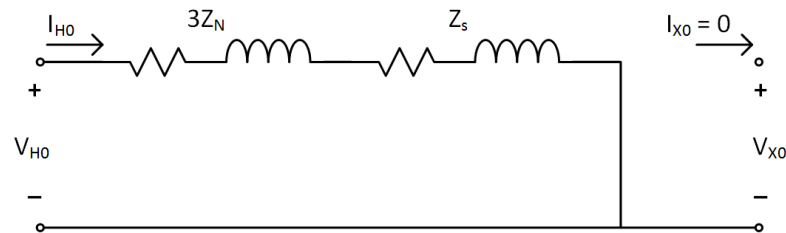

□ Positive-sequence network:

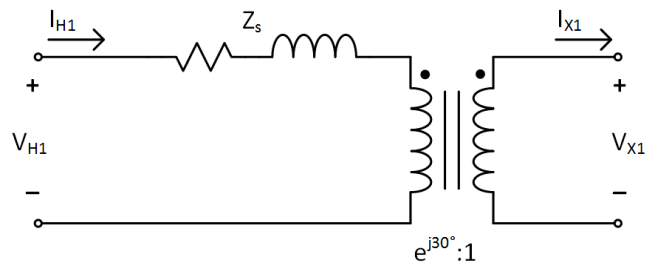



□ Negative-sequence network:

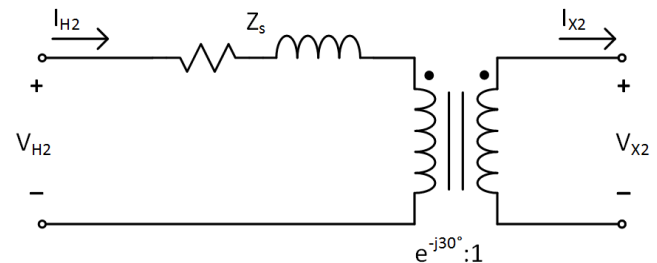

Sequence Networks – Δ - Δ Transformers

65

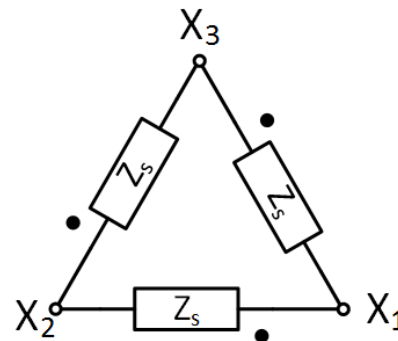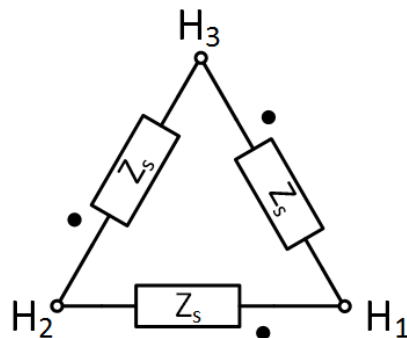- Δ - Δ transformers
 - ▣ Like Y-Y transformers, no phase shift
 - ▣ No neutral connections
 - Zero-sequence current cannot flow into or out of either winding




Sequence Networks – Δ - Δ Transformers


66

□ Sequence networks for Δ - Δ Transformers


□ Zero-sequence network:

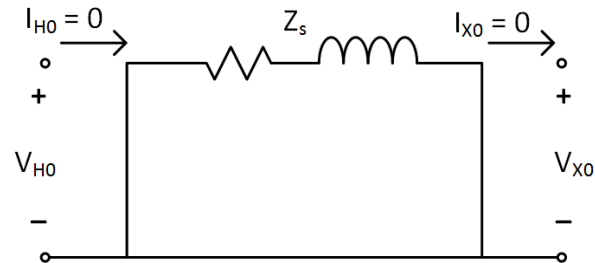

□ Positive-sequence network:

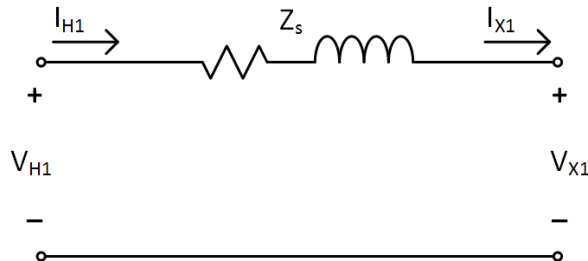

□ Negative-sequence network:

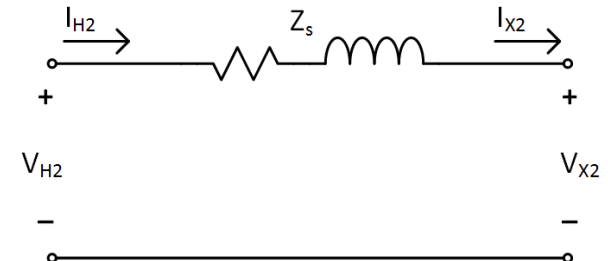

67

Power in Sequence Networks

Power in Sequence Networks

68

- We can relate the power delivered to a system's sequence networks to the three-phase power delivered to that system
- We know that the complex power delivered to a three-phase system is the sum of the power at each phase

$$S_p = V_{an}I_a^* + V_{bn}I_b^* + V_{cn}I_c^*$$

- In matrix form, this looks like

$$S_p = [V_{an} \quad V_{bn} \quad V_{cn}] \begin{bmatrix} I_a^* \\ I_b^* \\ I_c^* \end{bmatrix}$$

$$S_p = \mathbf{V}_p^T \mathbf{I}_p^* \tag{28}$$

Power in Sequence Networks

69

- Recall the following relationships

$$\mathbf{V}_p = \mathbf{A}\mathbf{V}_s \quad (9)$$

$$\mathbf{I}_p = \mathbf{A}\mathbf{I}_s \quad (13)$$

- Using (9) and (13) in (28), we have

$$\mathbf{S}_p = (\mathbf{A}\mathbf{V}_s)^T (\mathbf{A}\mathbf{I}_s)^*$$

$$\mathbf{S}_p = \mathbf{V}_s^T \mathbf{A}^T \mathbf{A}^* \mathbf{I}_s^* \quad (29)$$

- Computing the product in the middle of the right-hand side of (29), we find

$$\mathbf{A}^T \mathbf{A}^* = \begin{bmatrix} 3 & 0 & 0 \\ 0 & 3 & 0 \\ 0 & 0 & 3 \end{bmatrix} = 3\mathbf{I}_3$$

where \mathbf{I}_3 is the 3×3 identity matrix

Power in Sequence Networks

70

- Equation (29) then becomes

$$S_p = \mathbf{V}_S^T 3\mathbf{I}_3 \mathbf{I}_S^*$$

$$S_p = 3\mathbf{V}_S^T \mathbf{I}_S^*$$

$$S_p = 3[\mathbf{V}_0 \quad \mathbf{V}_1 \quad \mathbf{V}_2] \begin{bmatrix} \mathbf{I}_0^* \\ \mathbf{I}_1^* \\ \mathbf{I}_2^* \end{bmatrix}$$


$$S_p = 3(\mathbf{V}_0 \mathbf{I}_0^* + \mathbf{V}_1 \mathbf{I}_1^* + \mathbf{V}_2 \mathbf{I}_2^*)$$

- The total power delivered to a three-phase network is three times the sum of the power delivered to the three sequence networks
 - The three sequence networks represent only one of the three phases – recall, we chose to consider only phase a

71

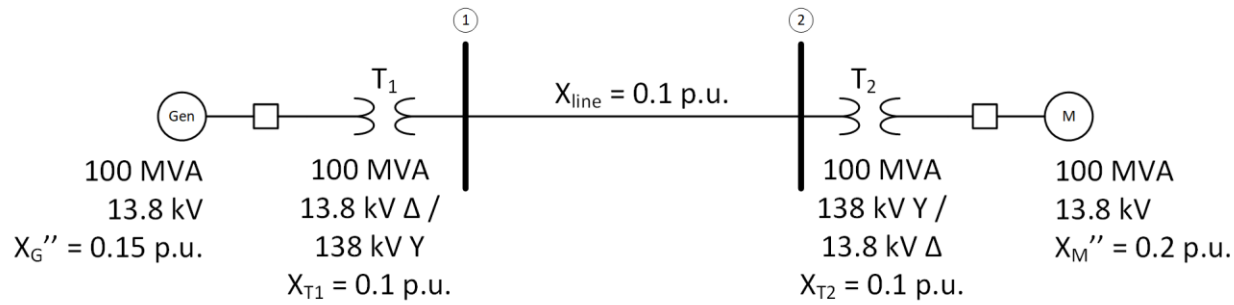Example Problems

A bolted, symmetric, three-phase fault occurs 60% of the way from bus 1 to bus 2. Determine the subtransient fault current in per-unit and in amperes. The load is consuming rated power at rated voltage and unity power factor.



Determine the sequence components for the following unbalanced set of three-phase voltage phasors:

$$\mathbf{V}_a = 1\angle 0^\circ \text{ p.u.}$$

$$\mathbf{V}_b = 0.5\angle -60^\circ \text{ p.u.}$$

$$\mathbf{V}_c = 2\angle 200^\circ \text{ p.u.}$$

Determine the phase components for the following set of sequence components:

$$\mathbf{V}_0 = 1 \angle 60^\circ \text{ p.u.}$$

$$\mathbf{V}_1 = 1 \angle 0^\circ \text{ p.u.}$$

$$\mathbf{V}_2 = 0 \text{ p.u.}$$

80

Unsymmetrical Faults

Unsymmetrical Faults

- The majority of faults that occur in three-phase power systems are unsymmetrical
 - ▣ Not balanced
 - ▣ Fault current and voltage differ for each phase
- The method of symmetrical components and sequence networks provide us with a tool to analyze these unsymmetrical faults
- We'll examine three types of unsymmetrical faults
 - ▣ Single line-to-ground (SLG) faults
 - ▣ Line-to-line (LL) faults
 - ▣ Double line-to-ground (DLG) faults

Unsymmetrical Fault Analysis - Procedure

82

- Basic procedure for fault analysis:
 1. Generate sequence networks for the system
 2. Interconnect sequence networks appropriately at the fault location
 3. Perform circuit analysis on the interconnected sequence networks

Unsymmetrical Fault Analysis


83

- To simplify our analysis, we'll make the following assumptions
 1. System is balanced before the instant of the fault
 2. Neglect pre-fault load current
 - All pre-fault machine terminal voltages and bus voltages are equal to V_F
 3. Transmission lines are modeled as series reactances only
 4. Transformers are modeled with leakage reactances only
 5. Non-rotating loads are neglected
 6. Induction motors are either neglected or modeled as synchronous motors

Unsymmetrical Fault Analysis

84

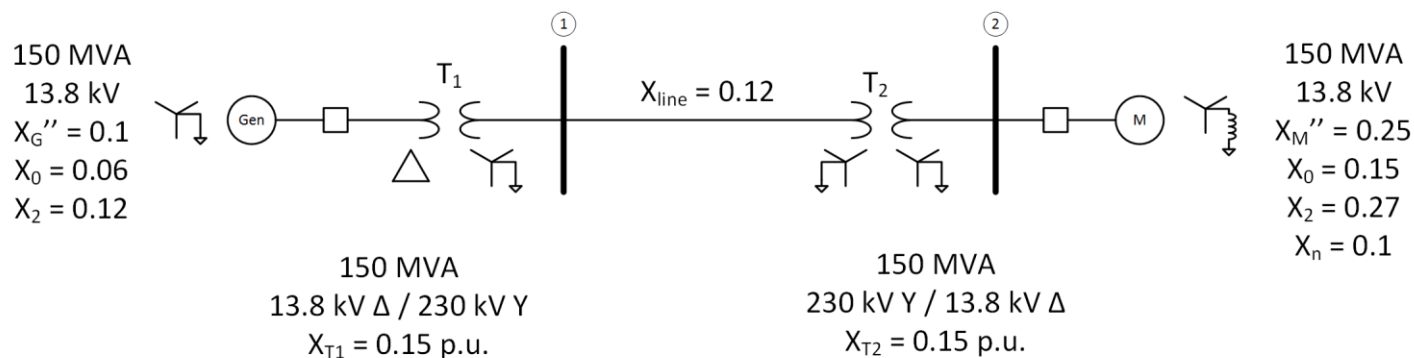
- Each sequence network includes all interconnected power-system components
 - ▣ Generators, motors, lines, and transformers
- Analysis will be simplified if we represent each sequence network as its Thévenin equivalent
 - ▣ From the perspective of the fault location
- For example, consider the following power system:




Unsymmetrical Fault Analysis – Sequence Networks

85

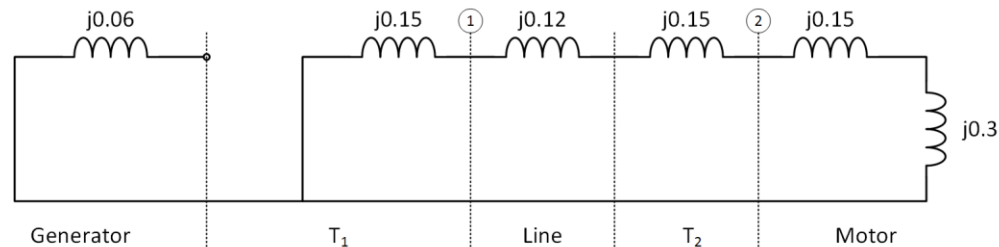- The sequence networks for the system are generated by interconnecting the sequence networks for each of the components
- The zero-sequence network:



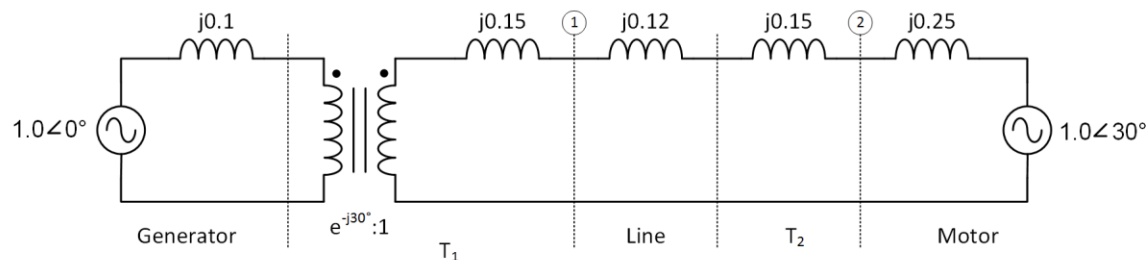
- The positive-sequence network:
 - Assuming the generator is operating at the rated voltage at the time of the fault




Unsymmetrical Fault Analysis – Sequence Networks

86

- The negative sequence network:

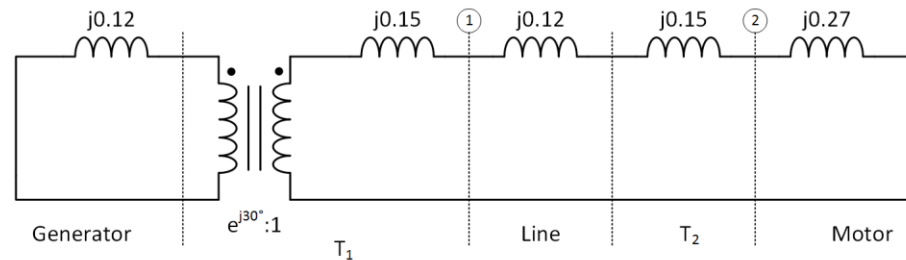

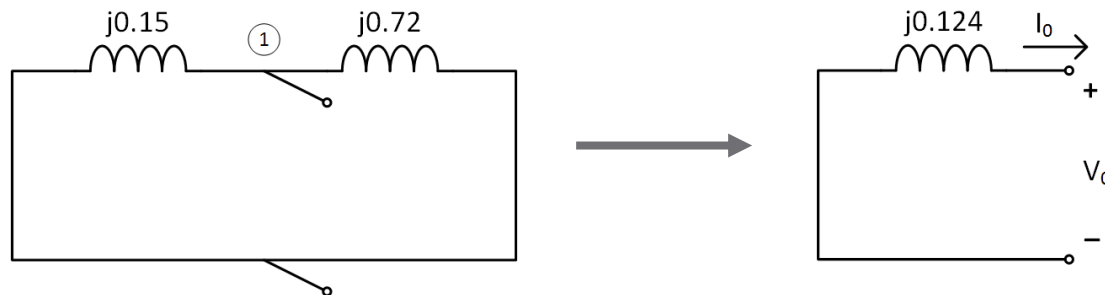
- Now, let's assume there is some sort of fault at bus 1
 - Determine the Thévenin equivalent for each sequence network from the perspective of bus 1
- Simplifying the zero-sequence network to its Thévenin equivalent




Unsymmetrical Fault Analysis – Sequence Networks

87

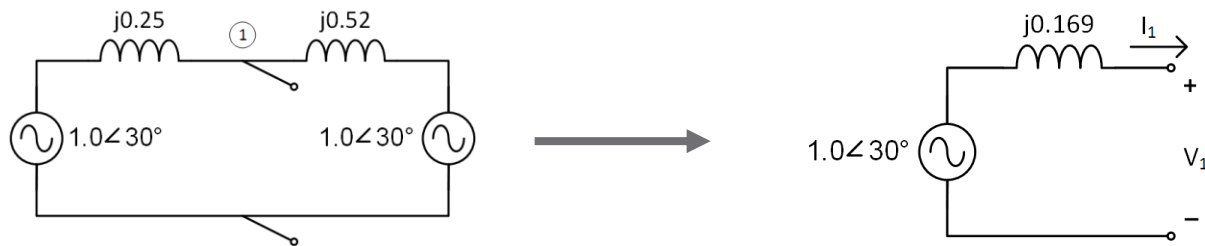- The positive-sequence network simplifies to the following circuit with the following Thévenin equivalent



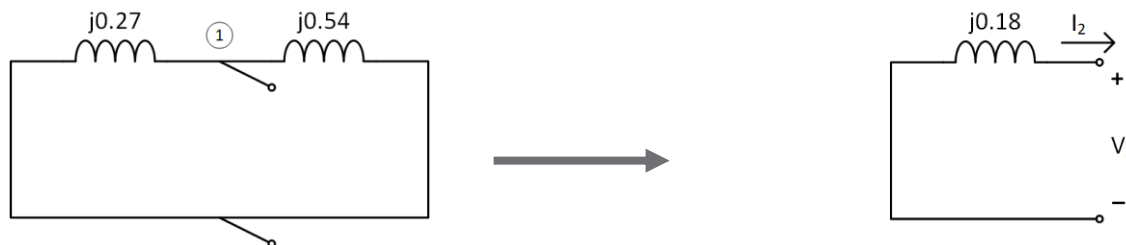- Similarly, for the negative-sequence network, we have



- Next, we'll see how to interconnect these networks to analyze different types of faults



88

Single-Line-to-Ground Fault

Unsymmetrical Fault Analysis – SLG Fault

89

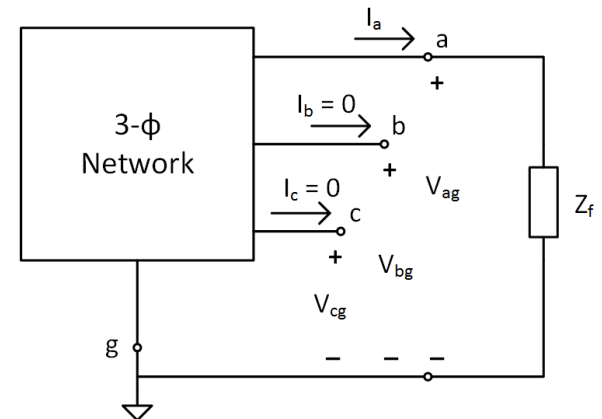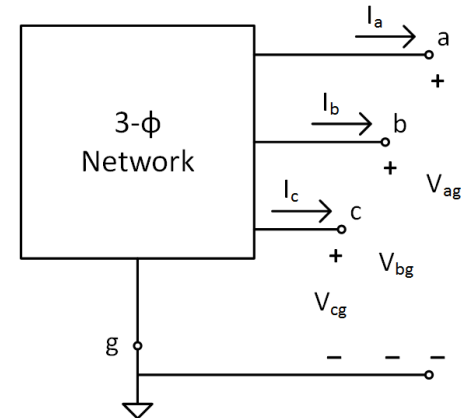- The following represents a generic three-phase network with terminals at the fault location:
- If we have a single-line-to-ground fault, where phase a is shorted through Z_f to ground, the model becomes:



Unsymmetrical Fault Analysis – SLG Fault

90

- The **phase-domain fault conditions**:

$$I_a = \frac{V_{ag}}{Z_f} \quad (1)$$


$$I_b = I_c = 0 \quad (2)$$

- Transforming these phase-domain currents to the sequence domain

$$\begin{bmatrix} I_0 \\ I_1 \\ I_2 \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} V_{ag}/Z_f \\ 0 \\ 0 \end{bmatrix} = \frac{1}{3} \begin{bmatrix} V_{ag}/Z_f \\ V_{ag}/Z_f \\ V_{ag}/Z_f \end{bmatrix} \quad (3)$$

- This gives one of our **sequence-domain fault conditions**

$$I_0 = I_1 = I_2 \quad (4)$$

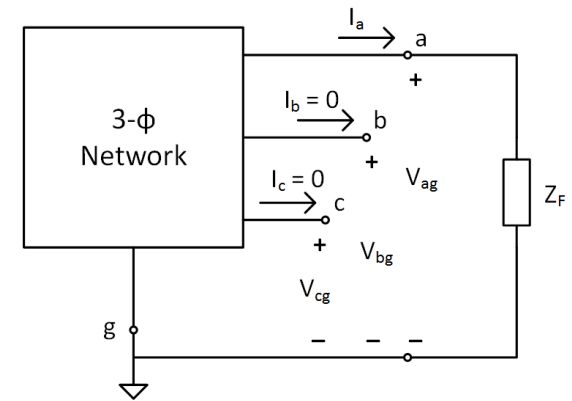

Unsymmetrical Fault Analysis – SLG Fault

91

- We know that

$$I_a = \frac{V_{ag}}{Z_f} = I_0 + I_1 + I_2 \quad (5)$$

and

$$V_{ag} = V_0 + V_1 + V_2 \quad (6)$$

- Using (5) and (6) in (1), we get

$$I_0 + I_1 + I_2 = \frac{1}{Z_f} (V_0 + V_1 + V_2)$$

- Using (4), this gives our second ***sequence-domain fault condition***

$$I_0 = I_1 = I_2 = \frac{1}{3Z_f} (V_0 + V_1 + V_2) \quad (7)$$

Unsymmetrical Fault Analysis – SLG Fault


92

- The sequence-domain fault conditions are satisfied by connecting the sequence networks in series along with three times the fault impedance
- We want to find the phase domain fault current, I_F

$$I_F = I_a = I_0 + I_1 + I_2 = 3I_1$$

$$I_1 = \frac{V_F}{Z_0 + Z_1 + Z_2 + 3Z_F}$$
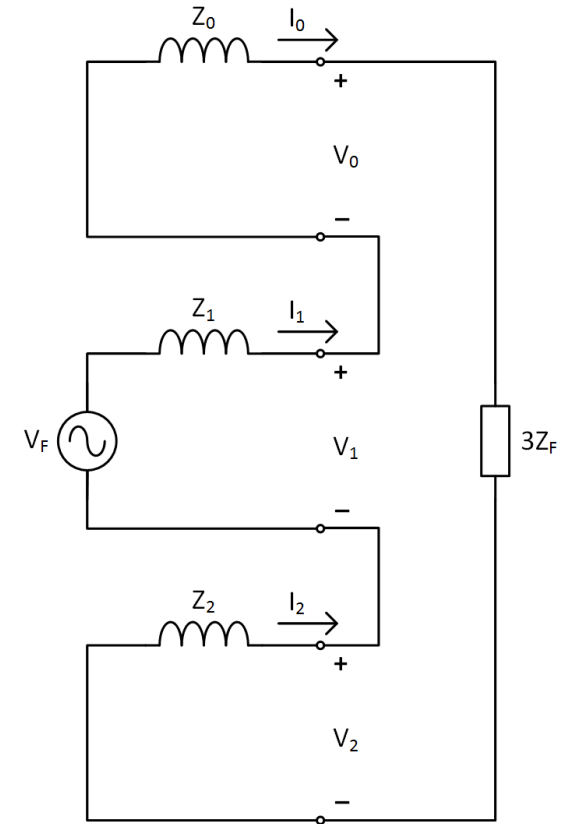
$$I_F = \frac{3V_F}{Z_0 + Z_1 + Z_2 + 3Z_F}$$




(8)


SLG Fault - Example

93

- Returning to our example power system

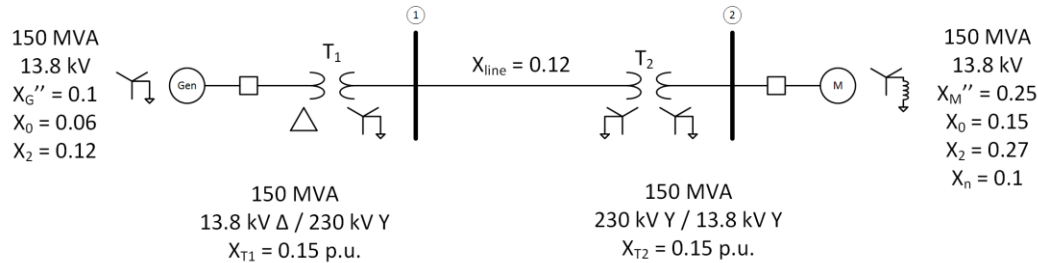

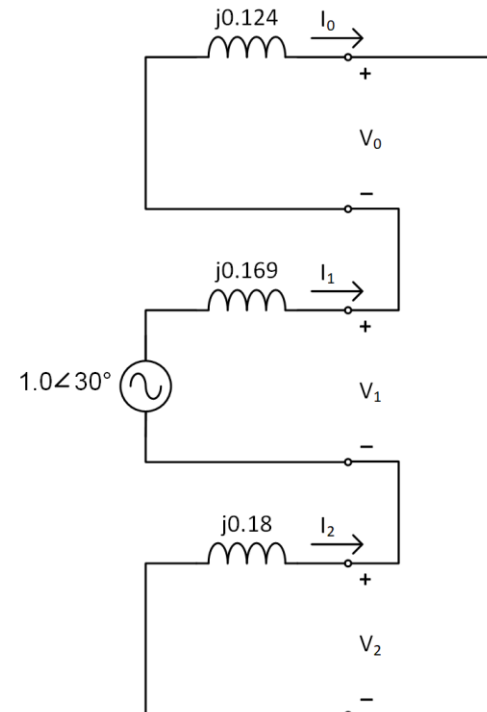- The interconnected sequence networks for a ***bolted fault*** at bus 1:



SLG Fault - Example

94

- The fault current is

$$I_F = \frac{3V_F}{Z_0 + Z_1 + Z_2 + 3Z_F}$$

$$I_F = \frac{3.0 \angle 30^\circ}{j0.473} = 6.34 \angle -60^\circ \text{ p.u.}$$

- The current base at bus 1 is

$$I_b = \frac{S_b}{\sqrt{3}V_{b1}} = \frac{150 \text{ MVA}}{\sqrt{3} 230 \text{ kV}} = 376.5 \text{ A}$$

- So the fault current in kA is

$$I_F = (6.34 \angle -60^\circ)(376.5 \text{ A})$$

$$I_F = 2.39 \angle -60^\circ \text{ kA}$$

95

Line-to-Line Fault


Unsymmetrical Fault Analysis – LL Fault

96

- Now consider a **line-to-line fault** between phase *b* and phase *c* through impedance Z_F
- Phase-domain fault conditions:

$$I_a = 0 \quad (9)$$
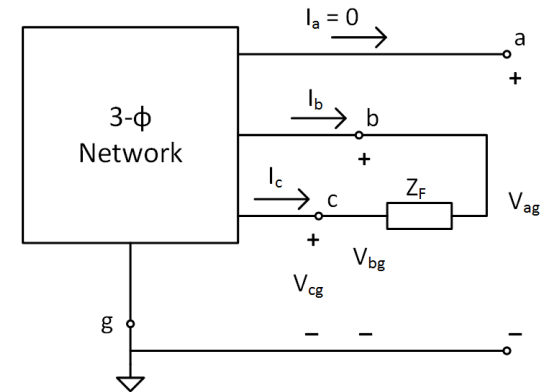
$$I_b = -I_c = \frac{V_{bg} - V_{cg}}{Z_F} \quad (10)$$



- Transforming to the sequence domain

$$\begin{bmatrix} I_0 \\ I_1 \\ I_2 \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} 0 \\ I_b \\ -I_b \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 0 \\ (a - a^2)I_b \\ (a^2 - a)I_b \end{bmatrix} \quad (11)$$

- So, the first two sequence-domain fault conditions are

$$I_0 = 0 \quad (12)$$

$$I_2 = -I_1 \quad (13)$$

Unsymmetrical Fault Analysis – LL Fault

97

- To derive the remaining sequence-domain fault condition, rearrange (10) and transform to the sequence domain

$$\mathbf{V}_{bg} - \mathbf{V}_{cg} = \mathbf{I}_b \mathbf{Z}_F$$

$$\begin{aligned} (\mathbf{V}_0 + a^2 \mathbf{V}_1 + a \mathbf{V}_2) - (\mathbf{V}_0 + a \mathbf{V}_1 + a^2 \mathbf{V}_2) \\ = (\mathbf{I}_0 + a^2 \mathbf{I}_1 + a \mathbf{I}_2) \mathbf{Z}_F \end{aligned}$$

$$a^2 \mathbf{V}_1 + a \mathbf{V}_2 - a \mathbf{V}_1 - a^2 \mathbf{V}_2 = (a^2 - a) \mathbf{I}_1 \mathbf{Z}_F$$

$$(a^2 - a) \mathbf{V}_1 - (a^2 - a) \mathbf{V}_2 = (a^2 - a) \mathbf{I}_1 \mathbf{Z}_F$$

- The last sequence-domain fault condition is

$$\mathbf{V}_1 - \mathbf{V}_2 = \mathbf{I}_1 \mathbf{Z}_F \tag{14}$$

Unsymmetrical Fault Analysis – LL Fault

98



- Sequence-domain fault conditions

$$I_0 = 0 \quad (12)$$

$$I_2 = -I_1 \quad (13)$$


$$V_1 - V_2 = I_1 Z_F \quad (14)$$

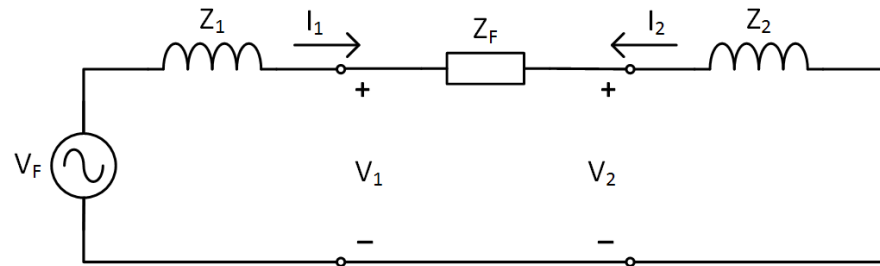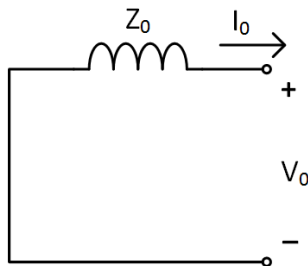- These can be satisfied by:
 - Leaving the zero-sequence network open
 - Connecting the terminals of the positive- and negative-sequence networks together through Z_F



Unsymmetrical Fault Analysis – LL Fault

99

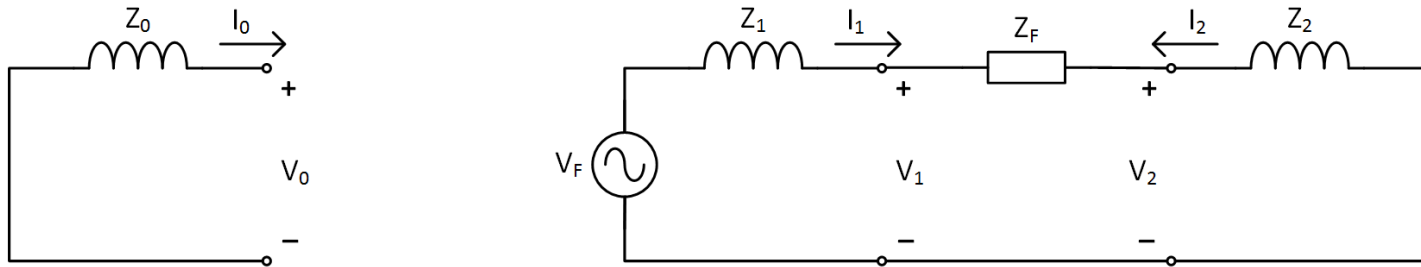

- The fault current is the phase b current, which is given by

$$I_F = I_b = I_0 + a^2 I_1 + a I_2$$

$$I_F = a^2 I_1 - a I_1$$

$$I_F = -j\sqrt{3} I_1 = \frac{-j\sqrt{3} V_F}{Z_1 + Z_2 + Z_F}$$


$$I_F = \frac{\sqrt{3} V_F \angle -90^\circ}{Z_1 + Z_2 + Z_F}$$

(15)


LL Fault - Example

100

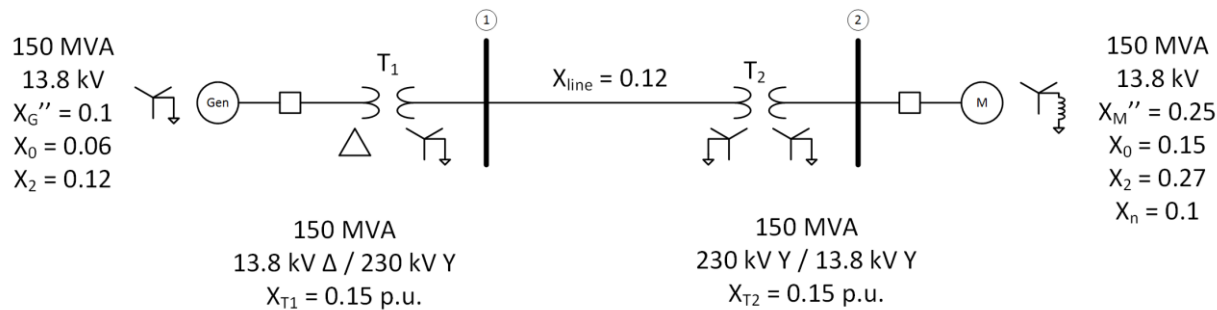- Now consider the same system with a bolted line-to-line fault at bus 1



- The sequence network:

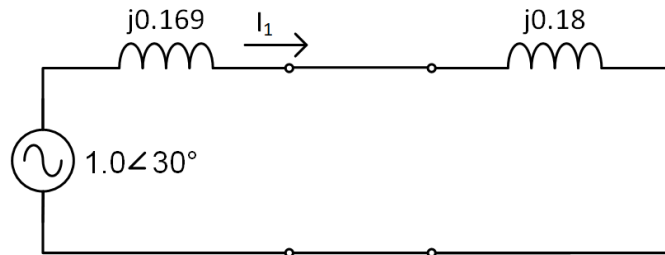

LL Fault - Example

101

$$\mathbf{I}_1 = \frac{1 \angle 30^\circ}{j0.349} = 2.87 \angle -60^\circ$$

- The subtransient fault current is given by (15) as

$$\mathbf{I}_F = (\sqrt{3} \angle -90^\circ)(2.87 \angle -60^\circ)$$

$$\mathbf{I}_F = 4.96 \angle -150^\circ \text{ p.u.}$$

- Using the previously-determined current base, we can convert the fault current to kA

$$\mathbf{I}_F = I_{b1} \cdot 4.96 \angle -150^\circ$$

$$\mathbf{I}_F = (4.96 \angle -150^\circ)(376.5A)$$

$$\mathbf{I}_F = 1.87 \angle -150^\circ \text{ kA}$$

102

Double-Line-to-Ground Fault


Unsymmetrical Fault Analysis – DLG Fault

103

- Now consider a **double line-to-ground fault**
 - ▣ Assume phases b and c are shorted to ground through Z_F
- Phase-domain fault conditions:

$$I_a = 0 \quad (16)$$
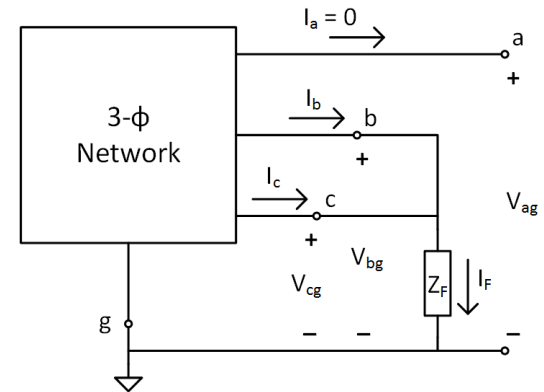
$$I_b + I_c = \frac{V_{bg}}{Z_F} = \frac{V_{cg}}{Z_F} \quad (17)$$



- It can be shown that (16) and (17) transform to the following sequence-domain fault conditions (analysis skipped here)

$$I_0 + I_1 + I_2 = 0 \quad (18)$$

$$V_1 = V_2 \quad (19)$$

$$I_0 = \frac{1}{3Z_F} (V_0 - V_1) \quad (20)$$

Unsymmetrical Fault Analysis – DLG Fault

104

- Sequence-domain fault conditions


$$\mathbf{I}_0 + \mathbf{I}_1 + \mathbf{I}_2 = 0 \quad (18)$$

$$\mathbf{V}_1 = \mathbf{V}_2 \quad (19)$$

$$\mathbf{I}_0 = \frac{1}{3Z_F} (\mathbf{V}_0 - \mathbf{V}_1) \quad (20)$$


- To satisfy these fault conditions

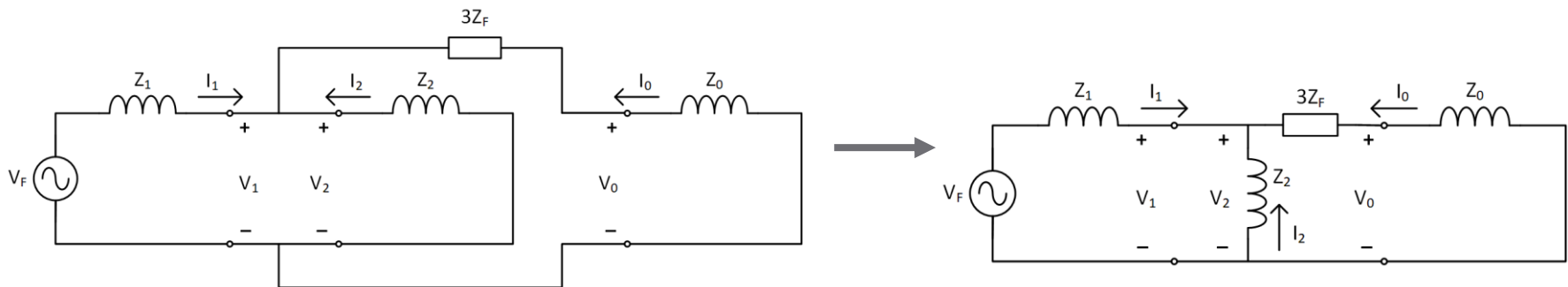- ▣ Connect the positive- and negative-sequence networks together directly
- ▣ Connect the zero- and positive-sequence networks together through $3Z_F$



Unsymmetrical Fault Analysis – DLG Fault

105

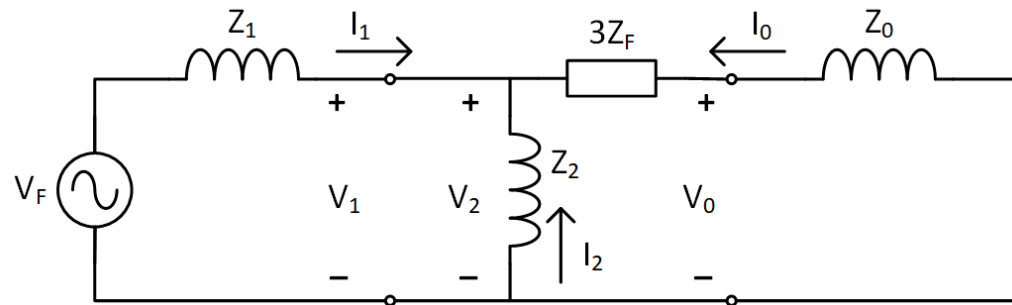

- The fault current is the sum of the phase b and phase c currents, as given by (17)
 - ▣ In the sequence domain the fault current is

$$I_F = I_b + I_c = 3I_0$$

$I_F = 3I_0$


(21)

- I_0 can be determined by a simple analysis (e.g. nodal) of the interconnected sequence networks


DLG Fault - Example

106

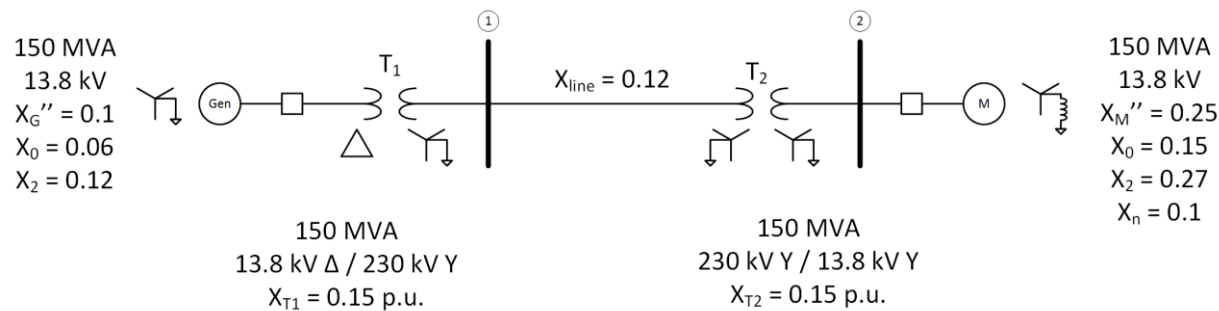- Now determine the subtransient fault current for a bolted double line-to-ground fault at bus 1




- The sequence network:

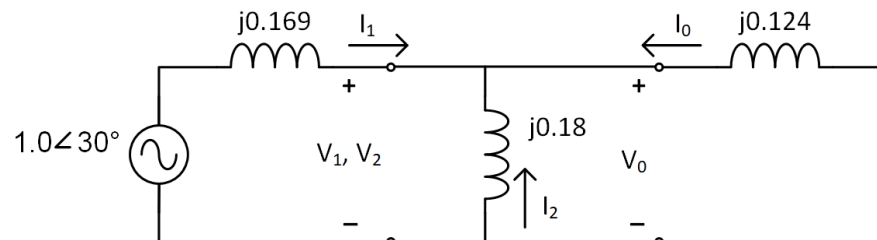

- Here, because $Z_F = 0$, $V_0 = V_1 = V_2$

DLG Fault - Example

107

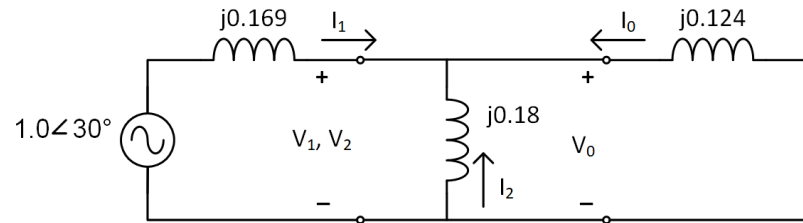

- To find I_F , we must determine I_0
- We can first find V_0 by applying voltage division

$$V_0 = V_F \frac{Z_2 || Z_0}{Z_1 + Z_2 || Z_0}$$

$$V_0 = 1.0\angle 30^\circ \frac{j0.18 || j0.124}{j0.169 + j0.18 || j0.124}$$

$$V_0 = 0.303\angle 30^\circ$$

DLG Fault - Example

108

- Next, calculate I_0

$$I_0 = \frac{-V_0}{Z_0} = \frac{-0.303 \angle 30^\circ}{j0.124} = 2.44 \angle 120^\circ \text{ p.u.}$$

- The per-unit fault current is

$$I_F = 3I_0 = 7.33 \angle 120^\circ \text{ p.u.}$$

- Using the current base to convert to kA, gives the subtransient DLG fault current


$$I_F = (7.33 \angle 120^\circ)(376.5 \text{ A})$$

$$I_F = 2.76 \angle 120^\circ \text{ kA}$$

109

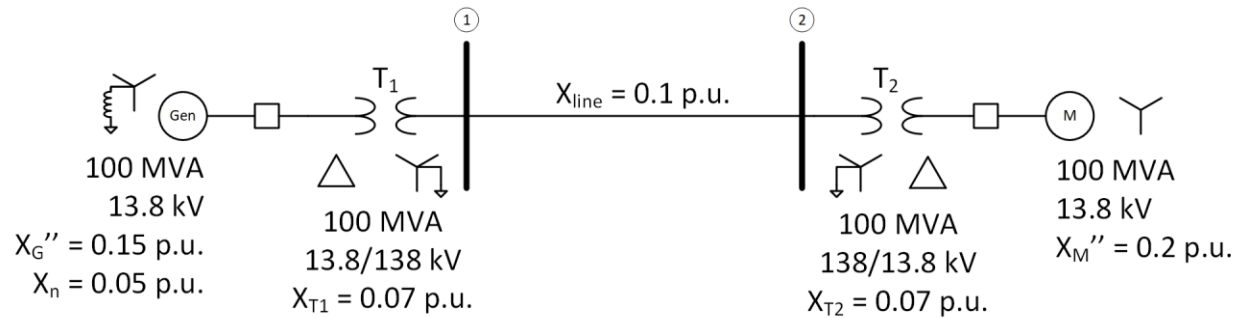Example Problems

Draw the sequence networks for the following power system.
Assume the generator is operating at rated voltage.



Reduce the sequence networks to their Thévenin equivalents for a fault occurring half of the way along the transmission line.

Determine the subtransient fault current resulting from a DLG fault, half way along the transmission line, through an impedance of $j0.2$ p.u.

