

SECTION 4: ULTRACAPACITORS

ESE 471 – Energy Storage Systems

2


Introduction

Ultracapacitors

3

- Capacitors are ***electrical energy*** storage devices
 - ▣ Energy is stored in an ***electric field***
- ***Advantages*** of capacitors for energy storage
 - ▣ High specific power
 - ▣ High efficiency
 - ▣ Equal charge and discharge rates
 - ▣ Long lifetime
- ***Disadvantages*** of capacitors for energy storage
 - ▣ Low specific energy
- ***Ultracapacitors*** (or ***supercapacitors***) are variations of traditional capacitors with significantly improved specific energy
 - ▣ Useful in high-power energy-storage applications

Ultracapacitors – Ragone Plot

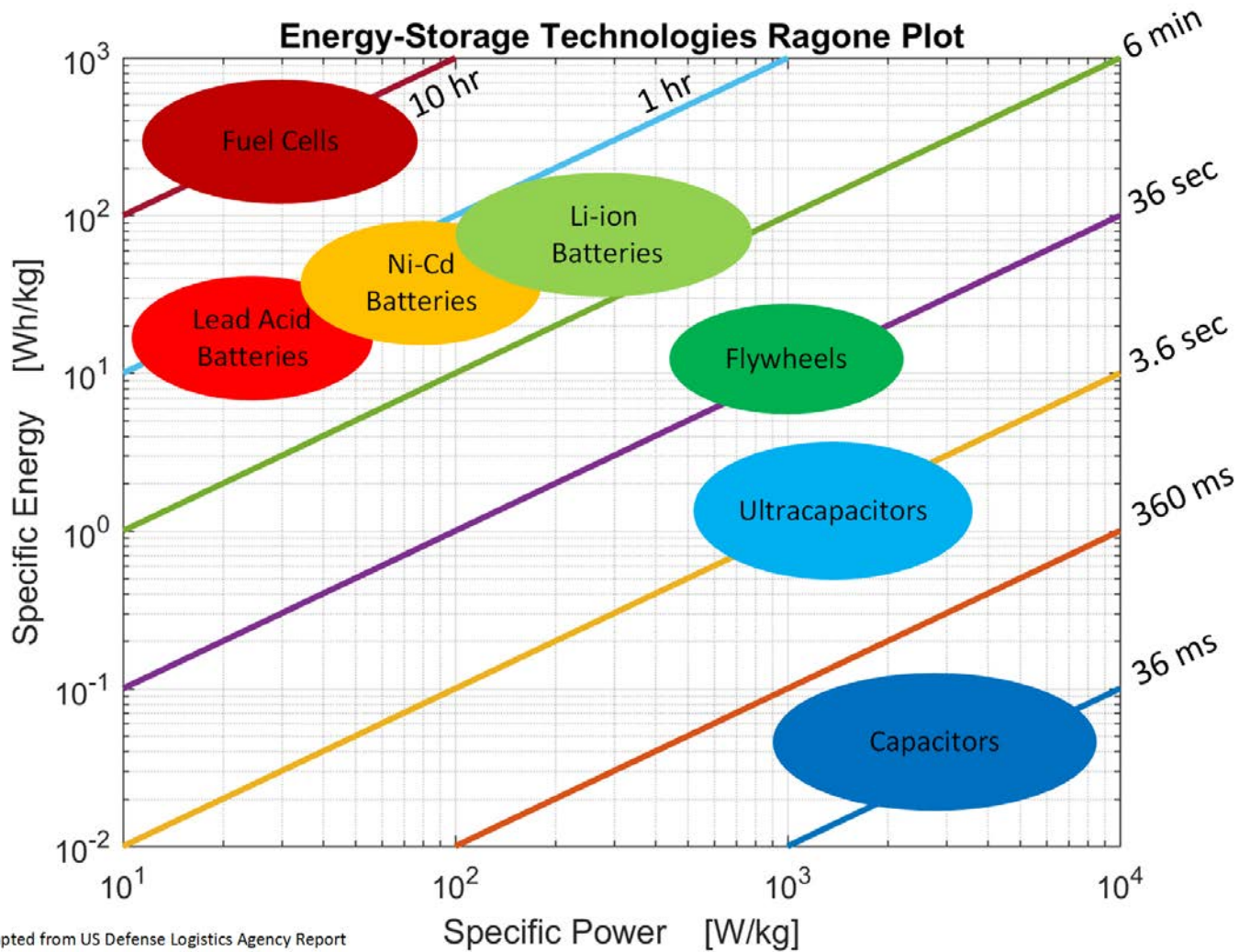

Adapted from US Defense Logistics Agency Report

Ultracapacitors - Applications

5

- Ultracapacitors are useful in relatively **high-power, low-energy** applications
 - They occupy a similar region in the Ragone plane as flywheels

- **Energy recovery** and **regenerative braking** applications
 - Cars
 - EV, HEV, ICE (e.g. Mazda 6 i-ELOOP)
 - Buses
 - Trains
 - Cranes
 - Elevators

- **Uninterruptible power supply (UPS)** applications
 - Fast-responding, short-term power until generators take over

- **Wind turbine pitch control**
 - Put turbine blades in safe position during loss of power


6

Capacitor Fundamentals

Fluid Capacitor

7

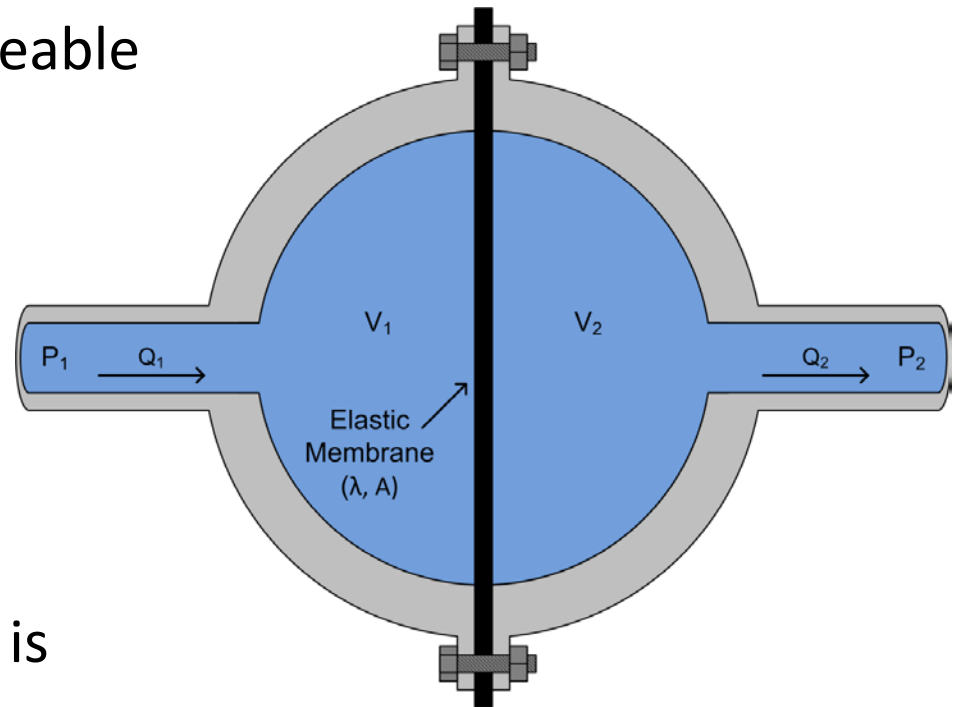- Consider the following device:
 - Two rigid hemispherical shells
 - Separated by an impermeable elastic membrane
 - Modulus of elasticity, λ
 - Area, A
 - Incompressible fluid
 - External pumps set pressure or flow rate at each port
 - Total volume inside shell is constant
 - Volume on either side of the membrane may vary



Fluid Capacitor – Equilibrium

8

- Equal pressures

$$\Delta P = P_1 - P_2 = 0$$


- No fluid flow

$$Q_1 = Q_2 = 0$$

- Membrane does not deform

- Equal volume on each side

$$V_1 = V_2 = \frac{V}{2}$$

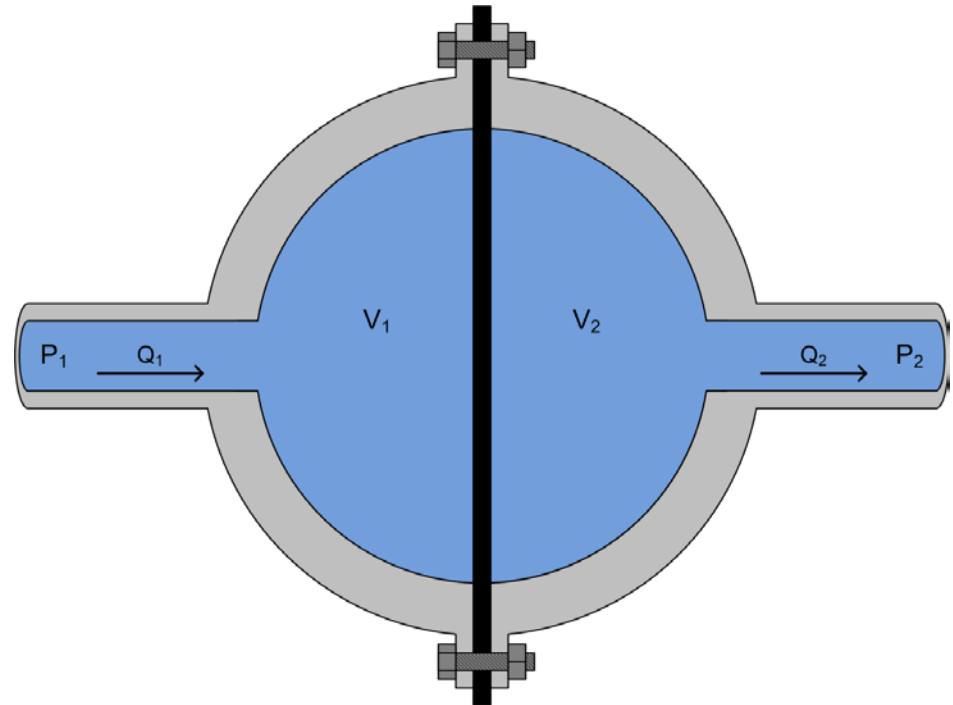

Fluid Capacitor – $P_1 > P_2$

9

- Pressure differential

$$\Delta P = P_1 - P_2 > 0$$

- Membrane deforms

- Volume differential


$$\Delta V = V_1 - V_2 > 0$$

- Transient flow as membrane stretches, but...

- No steady-state flow

- As $t \rightarrow \infty$

$$Q_1 = Q_2 = 0$$

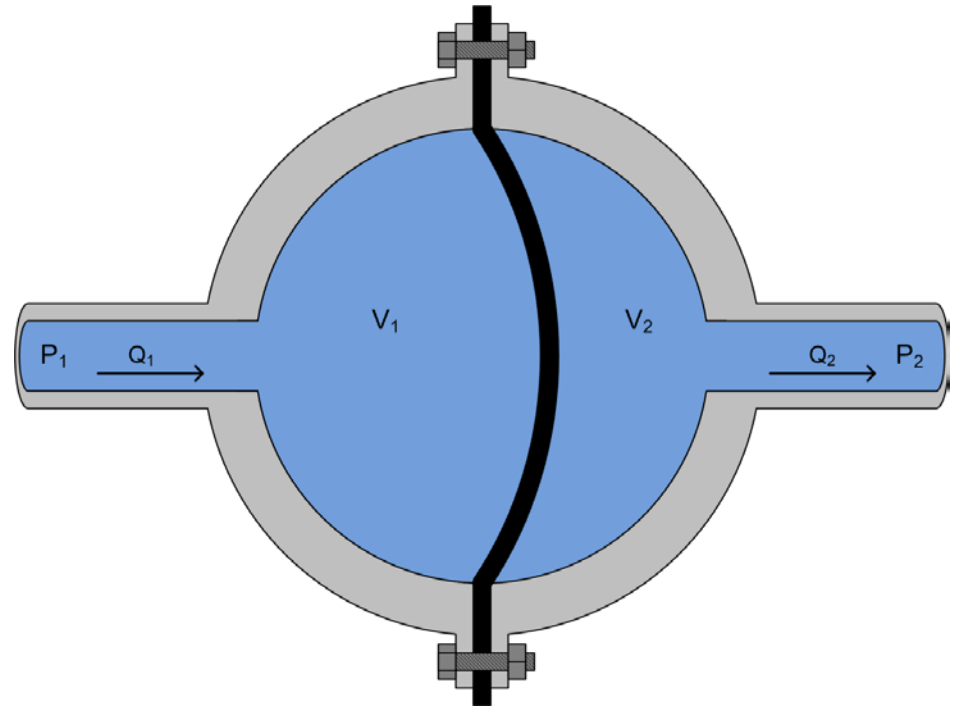

Fluid Capacitor – $P_1 < P_2$

10

- Pressure differential

$$\Delta P = P_1 - P_2 < 0$$

- Volume differential

$$\Delta V = V_1 - V_2 < 0$$


- ΔV proportional to:

- ▣ Pressure differential
- ▣ Physical properties, λ, A

- Total volume remains constant

$$V_1 + V_2 = V$$

- Again, no steady-state flow

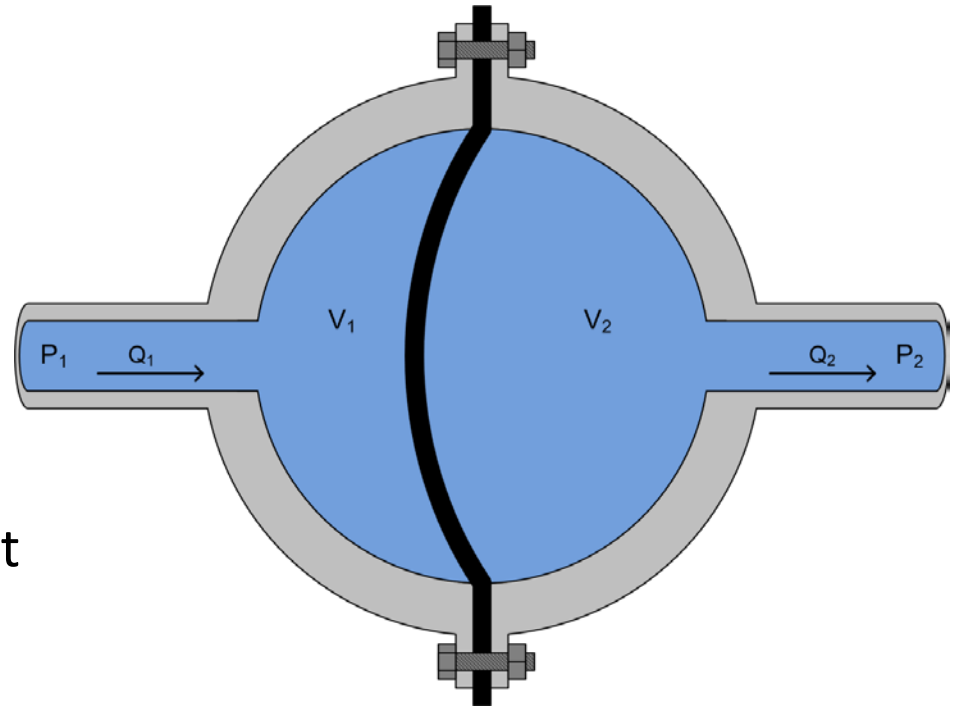

Fluid Capacitor – Constant Flow Rate

11

- Constant flow rate forced into port 1

$$Q_1 \neq 0$$

- Incompressible, so flows are equal and opposite

$$Q_1 = Q_2$$


- Volume on each side proportional to time

$$V_1 = \frac{V}{2} + Q_1 \cdot t$$

$$V_2 = \frac{V}{2} - Q_2 \cdot t = \frac{V}{2} - Q_1 \cdot t$$

- Volume differential proportional to time

$$\Delta V = V_1 - V_2 = 2Q_1 \cdot t$$

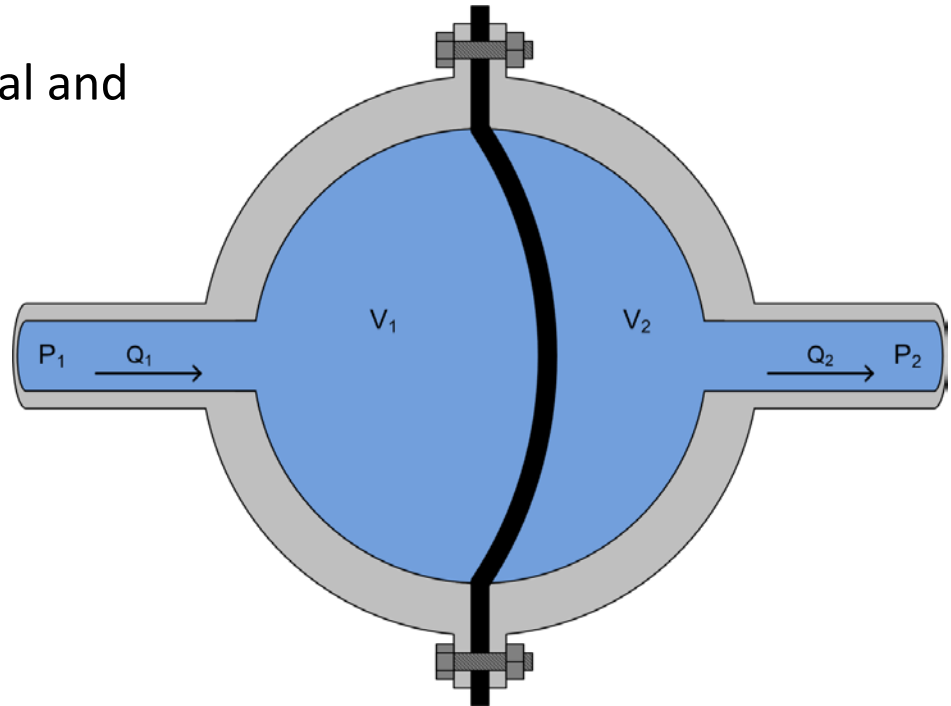

Fluid Capacitor – Capacitance


12

- Define a relationship between differential volume and pressure

- **Capacitance**

$$C = \frac{\Delta V}{\Delta P}$$

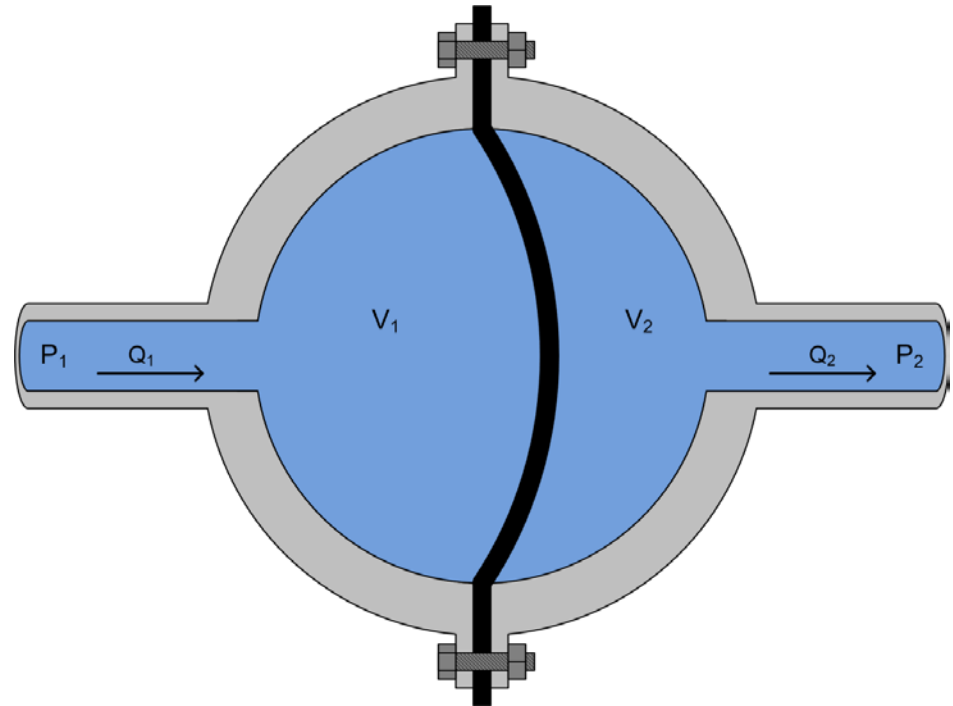- Intrinsic device property
- Determined by physical parameters:
 - ▣ Membrane area, A
 - ▣ Modulus of elasticity, λ



Fluid Capacitor – DC vs. AC

13

- In steady-state (DC), no fluid flows

$$Q_1 = Q_2 = 0$$


- Consider sinusoidal ΔP (AC):

$$\Delta P = P \sin(\omega t)$$

- Resulting flow rate is proportional to:

- ▣ Rate of change of differential pressure
- ▣ Capacitance
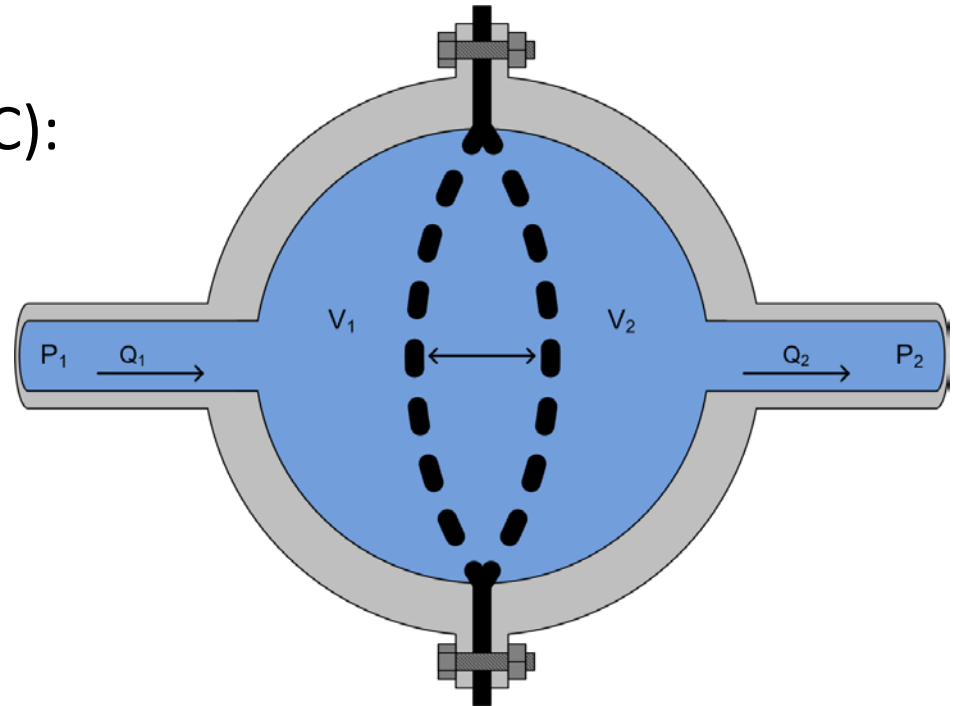
$$Q_1 = Q_2 = C \frac{dP}{dt} = \omega C P \cos(\omega t)$$



Fluid Capacitor – Time-Varying ΔP

14

- Equal and opposite flow at both ports

$$Q_1 = Q_2$$

- Not the same fluid flowing at both ports
 - ▣ Fluid cannot permeate the membrane

- ***Fluid appears to flow through the device***


- ▣ Due to the displacement of the membrane
- ▣ A ***displacement flow***

- The faster ΔP changes, the higher the flow rate

$$Q \propto \omega$$

- The larger the capacitance, the higher the flow rate


$$Q \propto C$$

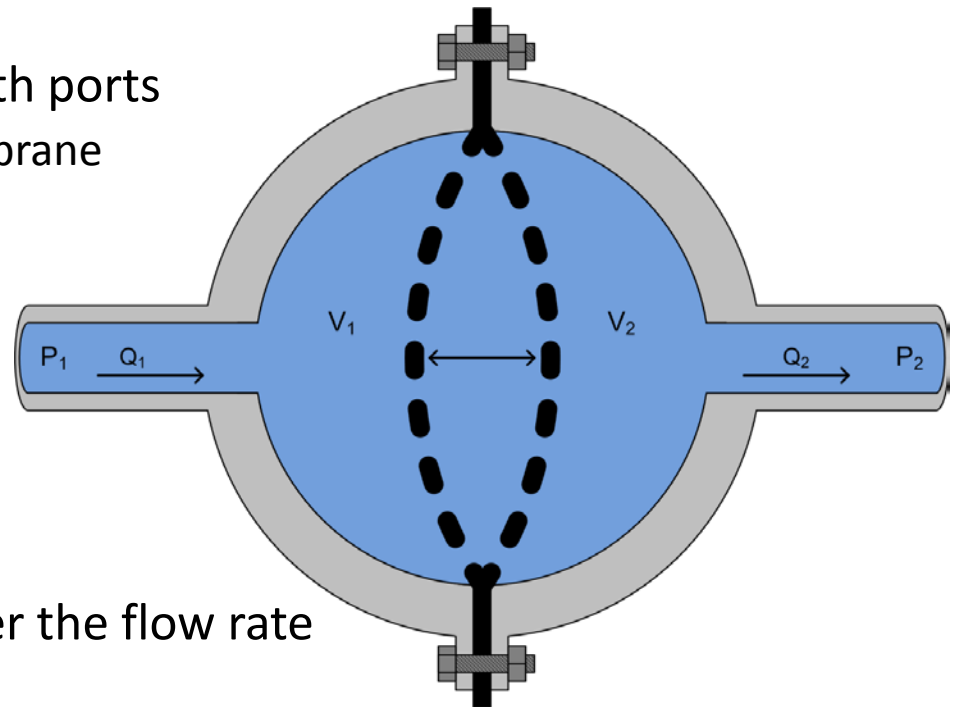

Fluid Capacitor – Changing ΔP

15

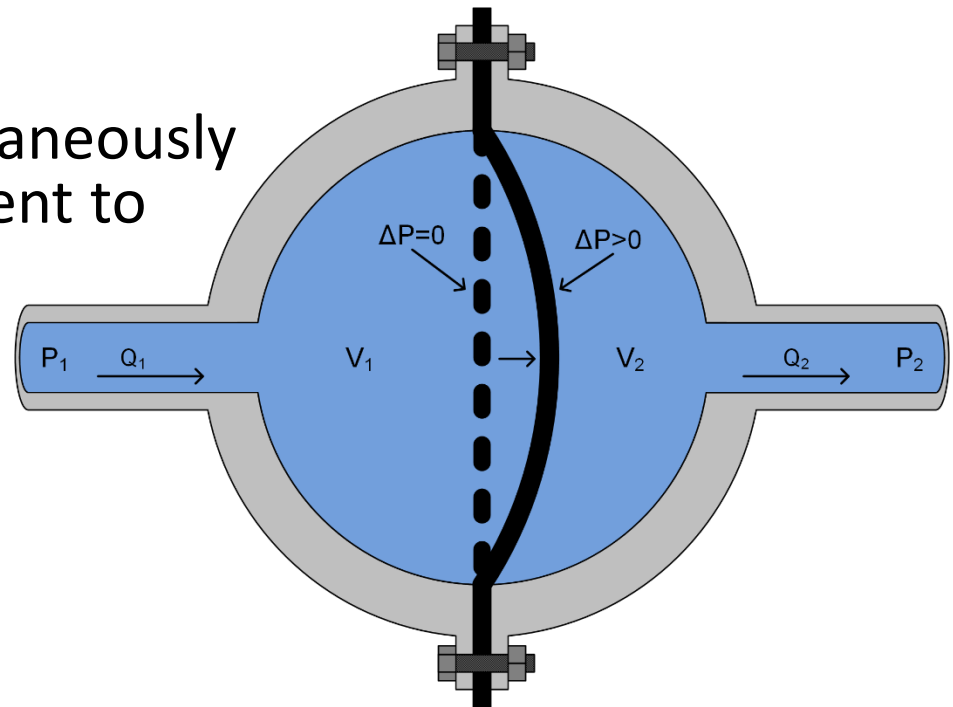
- A given ΔP corresponds to a particular membrane displacement
 - ▣ Forces must balance
- Membrane cannot instantaneously jump from one displacement to another
- Step change in displacement/pressure is impossible
 - ▣ Would require an infinite flow rate
- ***Pressure across a fluid capacitor cannot change instantaneously***



Fluid Capacitor – Energy Storage

16

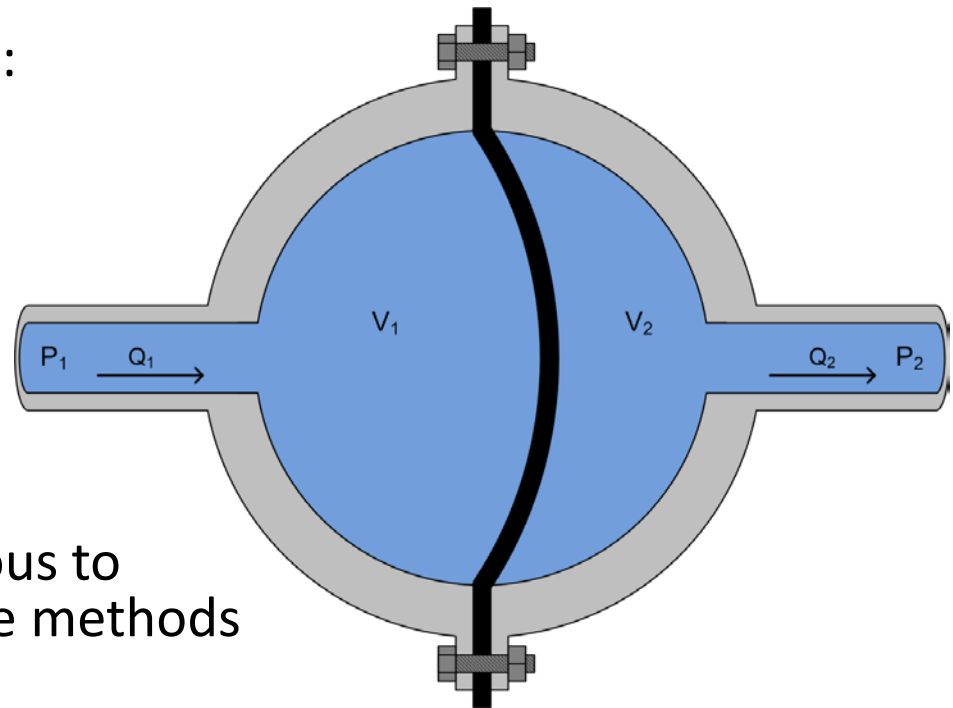- Stretched membrane *stores energy*
 - *Potential energy*
- Stored energy proportional to:
 - ΔP
 - ΔV
- Energy released as membrane returns
 - P and Q are supplied
- Not a real device, but analogous to other potential energy storage methods
 - PHES
 - CAES
 - *Electrical capacitors*



Electrical Capacitor

17

- In the electrical domain, our “working fluid” is ***positive electrical charge***
- In either domain, we have a ***potential-driven flow***

Fluid Domain	Electrical Domain
Pressure – P	Voltage – V
Volumetric flow rate – Q	Current – I
Volume – V	Charge – Q

Electrical Capacitor

18


- Parallel-plate capacitor
 - ▣ Parallel metal plates
 - ▣ Separated by an insulator
- ***Applied voltage creates charge differential***
 - ▣ Equal and opposite charge


$$Q_1 = -Q_2$$

- ▣ Zero net charge
- Equal current

$$I_1 = I_2$$

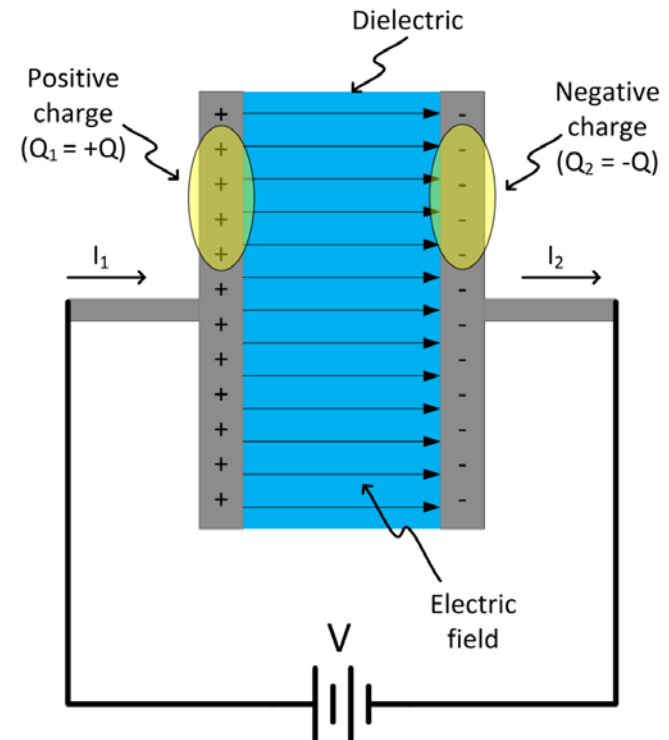- ▣ What flows in one side flows out the other




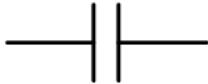- Schematic symbol: 
- Units: Farads (F)

Electrical Capacitor – Electric Field

19

- Charge differential results in an **electric field, E** , in the dielectric
 - ▣ Units: V/m
- $|E|$ is inversely proportional to dielectric thickness, d
- Above some maximum electric field strength, dielectric will **break down**
 - ▣ Conducts electrical current
 - ▣ Maximum capacitor voltage rating

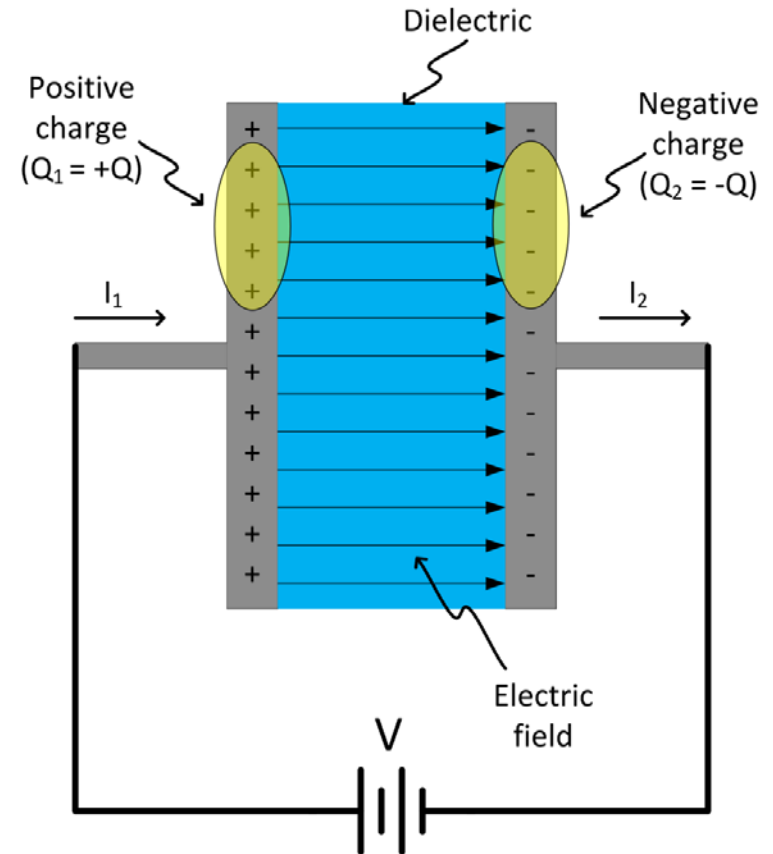

Electrical Capacitor - Capacitance


20

□ **Capacitance**

- ▣ Ratio of charge to voltage


$$C = \frac{Q}{V}$$

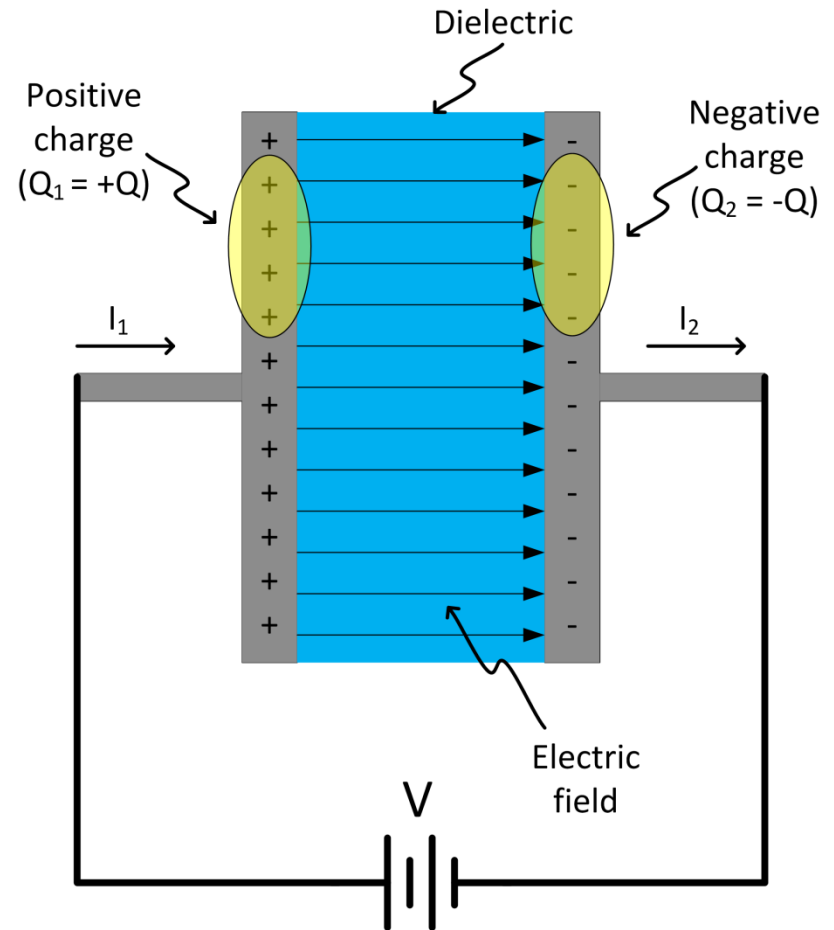- Intrinsic device property
- Proportional to physical parameters:
 - ▣ Dielectric thickness, d
 - ▣ Dielectric constant, ϵ
 - ▣ Area of electrodes, A



Parallel-Plate Capacitor

21

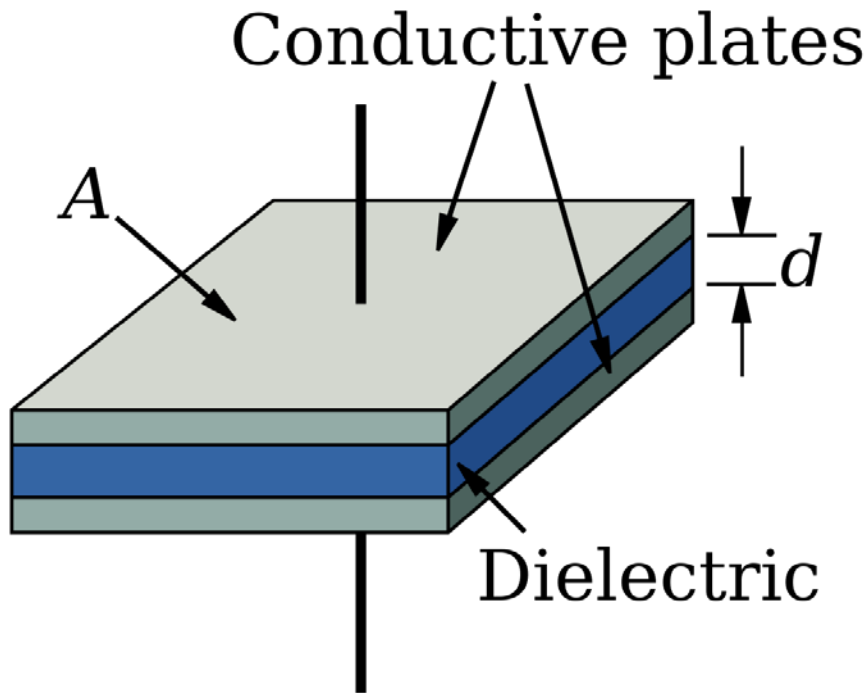

□ Capacitance

$$C = \frac{\epsilon A}{d}$$

- ϵ : dielectric permittivity
 - A : area of the plates
 - d : dielectric thickness
-
- Capacitance is maximized by using:
 - High-dielectric-constant materials
 - Thin dielectric
 - Large-surface-area plates

Capacitors – Voltage and Current


22

- Current through a capacitor is proportional to
 - ▣ Capacitance
 - ▣ Rate of change of the voltage

$$i(t) = C \frac{dv}{dt}$$

- Voltage across capacitor results from an accumulation of charge differential
 - ▣ Capacitor integrates current

$$v(t) = \frac{1}{C} \int i(t) dt$$

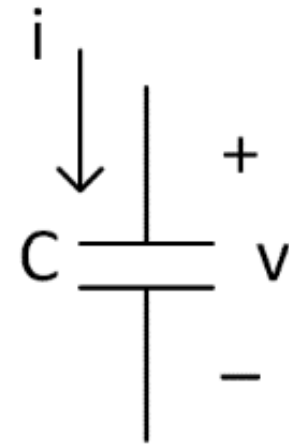

Voltage Change Across a Capacitor

23

- For a step change in voltage,

$$\frac{dv}{dt} = \infty$$

- The corresponding current would be *infinite*
- ***Voltage across a capacitor cannot change instantaneously***
- Current can change instantaneously, but voltage is the integral of current

$$\lim_{\Delta t \rightarrow 0} \Delta V = \lim_{\Delta t \rightarrow 0} \int_{t_0}^{t_0 + \Delta t} i(t) dt = 0$$

Capacitors – Open Circuits at DC

24

- Current through a capacitor is proportional to the time rate of change of the voltage across the capacitor

$$i(t) = C \frac{dv}{dt}$$



- A DC voltage does not change with time, so

$$\frac{dv}{dt} = 0 \quad \text{and} \quad i(t) = 0$$

- ***A capacitor is an open circuit at DC***

Capacitors in Parallel

25

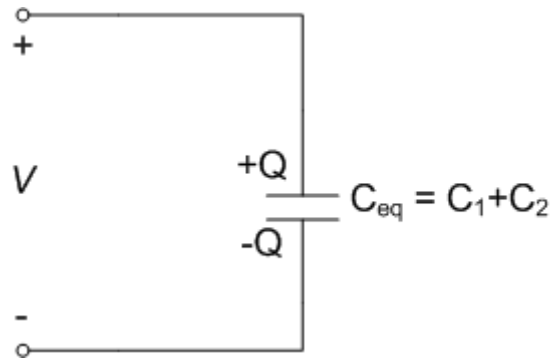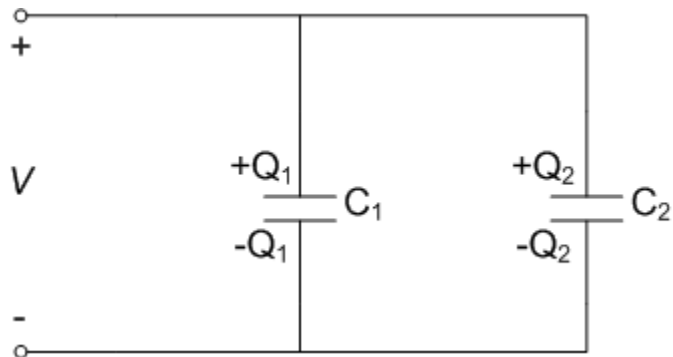

- Total charge on two parallel capacitors is

$$Q = Q_1 + Q_2$$

$$Q = C_1V + C_2V$$

$$Q = (C_1 + C_2)V$$


$$Q = C_{eq}V$$

- ***Capacitances in parallel add***

$$C_{eq} = C_1 + C_2$$

Capacitors in Series

26

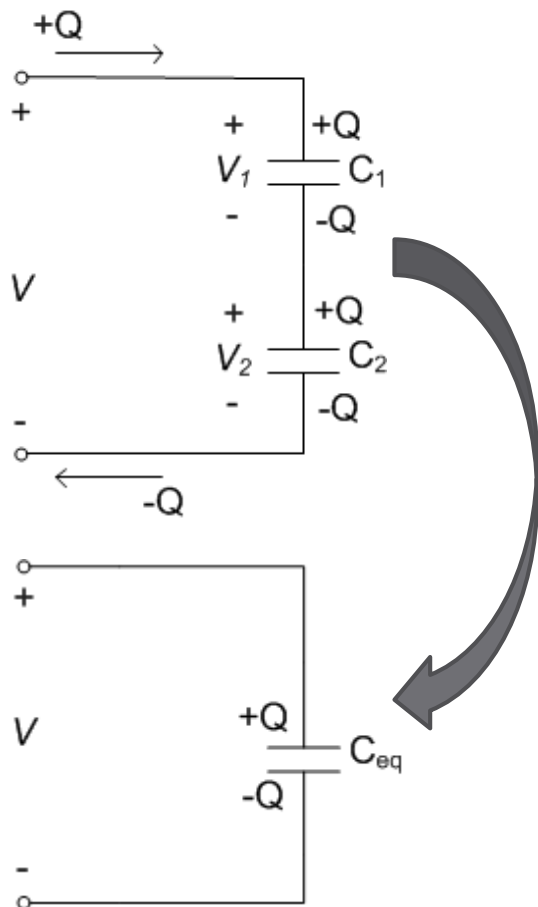

- Total voltage across the series combination is

$$V = V_1 + V_2$$

$$V = \frac{Q}{C_1} + \frac{Q}{C_2}$$



$$V = Q \left(\frac{1}{C_1} + \frac{1}{C_2} \right) = \frac{Q}{C_{eq}}$$

- ***The inverses of capacitors in series add***

$$C_{eq} = \left(\frac{1}{C_1} + \frac{1}{C_2} \right)^{-1} = \frac{C_1 C_2}{C_1 + C_2}$$


Constant Current Onto a Capacitor

27

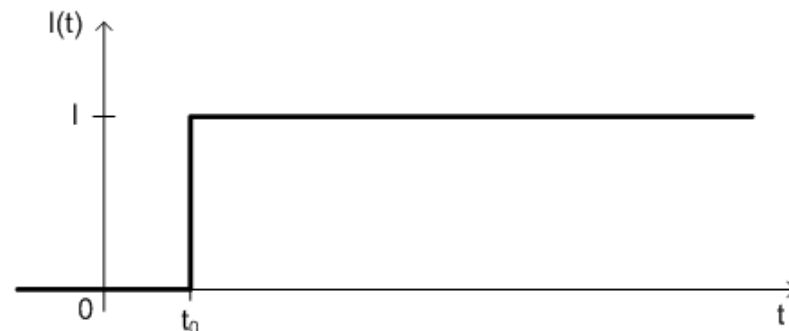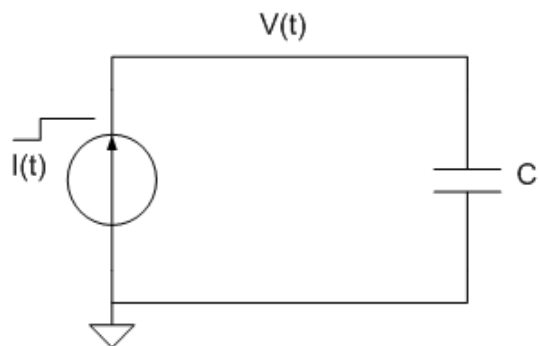

- Capacitor voltage increases linearly for constant current
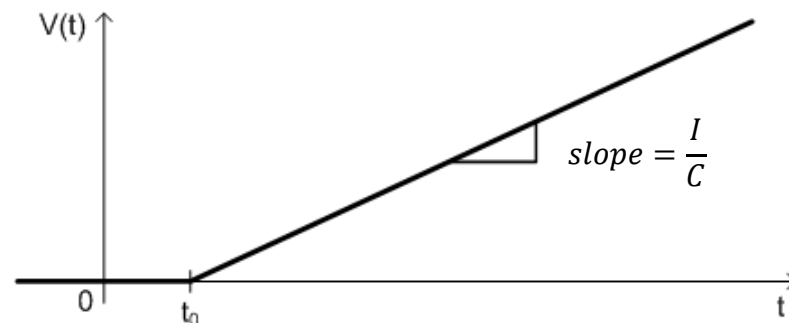
$$v(t) = \frac{I(t-t_0)}{C}, \quad t \geq t_0$$




Electrical Capacitor – Energy Storage

28

- Capacitors store **electrical energy**
 - ▣ Energy stored in the **electric field**
- Stored energy is proportional to:
 - ▣ Voltage
 - ▣ Charge differential

$$E = \frac{1}{2} QV = \frac{1}{2} CV^2 = \frac{1}{2} \frac{Q^2}{C}$$

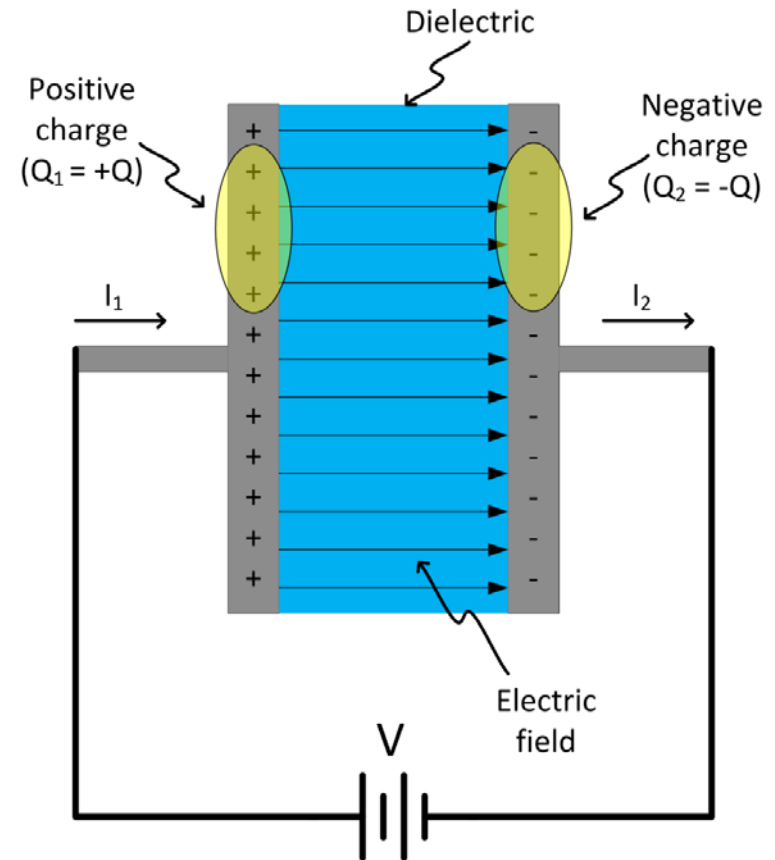- Energy released as E-field collapses
 - ▣ V and I supplied



Energy Storage – Example

29

- A capacitor is charged to 100 V
 - The stored energy will be used to lift a 1000 kg elevator car 10 stories (35 m)
 - Determine the required capacitance
-

- The required energy is

$$E = mgh = 1000 \text{ kg} \cdot 9.81 \frac{\text{m}}{\text{s}^2} \cdot 35 \text{ m}$$

$$E = 343.4 \text{ kJ}$$

- Energy stored on the capacitor is

$$E = \frac{1}{2} C (100 \text{ V})^2$$

- The required capacitance is

$$C = \frac{2 \cdot 343.4 \text{ kJ}}{(100 \text{ V})^2} = \underline{68.7 \text{ F}}$$

30

Ultracapacitors

Ultracapacitors - Introduction

31

- Energy stored by a capacitor

$$E = \frac{1}{2} CV^2$$

- Would like to maximize capacitance in order to maximize energy storage
- Recall the capacitance of a parallel-plate capacitor

$$C = \frac{\epsilon A}{d}$$




- To increase capacitance:
 - Use a higher-permittivity dielectric
 - Increase surface area of the plates
 - Decrease dielectric thickness
- Traditional capacitors do all of these things
 - ϵ limited by available materials and dielectric strength
 - A limited by practical overall device size
 - d limited by dielectric breakdown field strength

Traditional Capacitors – Construction

32

- Let's take a look at the construction of two high-capacitance traditional capacitors
 - ▣ Aluminum electrolytic
 - ▣ Tantalum electrolytic


- ***Aluminum electrolytic capacitor:***

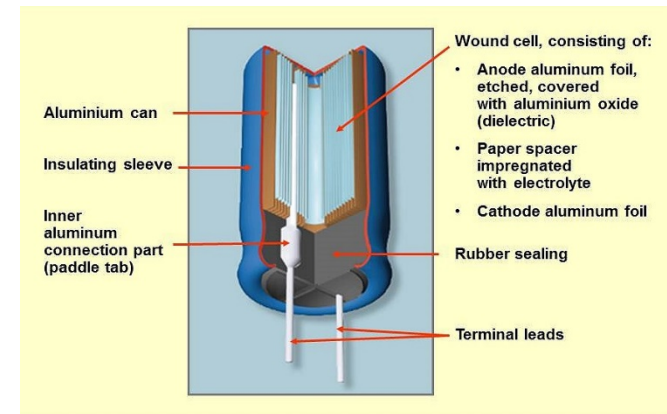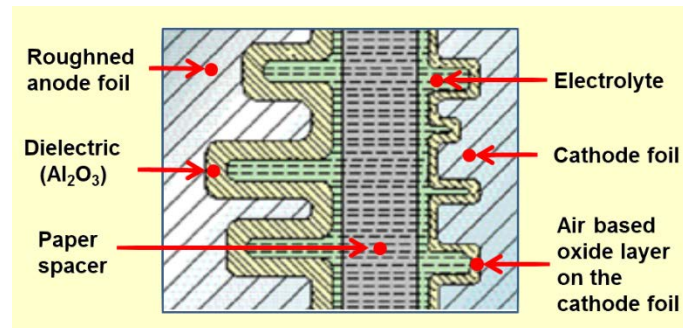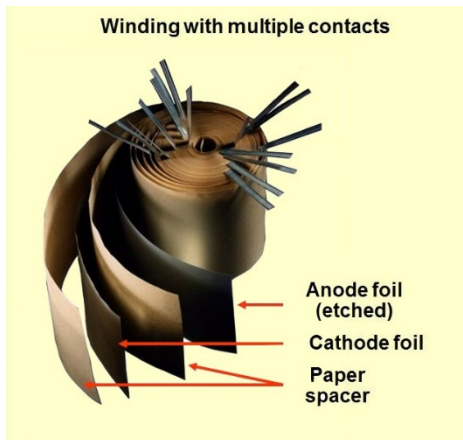



Traditional Capacitors – Construction

33

□ *Tantalum electrolytic capacitor:*

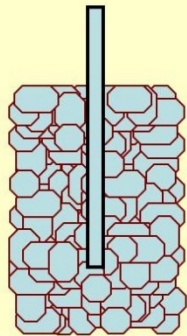

Tantalum sintered body

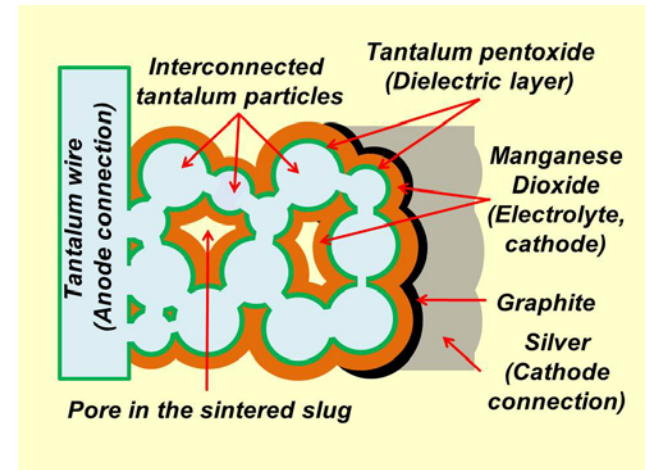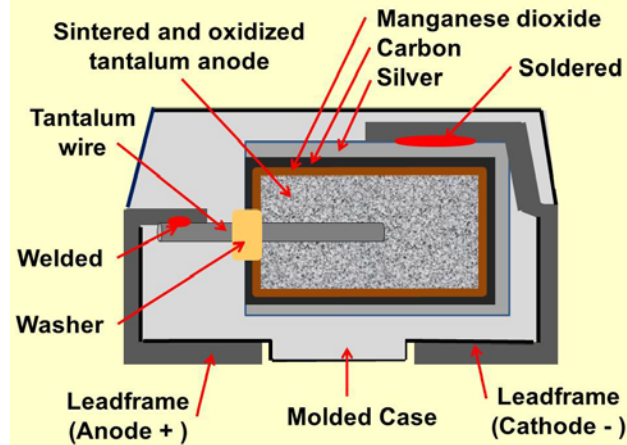

- In both of these types of capacitors, efforts are made to maximize A and minimize d
- But, a physical dielectric layer of non-zero thickness is used

Ultracapacitors


34

- In a previous example, we found we needed a capacitance of 68.7 F
 - ▣ Impractically large for a traditional capacitor
 - ▣ Not so for an ***ultracapacitor***
- ***Ultracapacitors*** or ***supercapacitors*** achieve very high capacitance values by eliminating the solid dielectric layer of traditional capacitors
- Energy is stored in an E-field
 - ▣ Not in a dielectric layer
 - ▣ In an ***electric double layer (Helmholtz double layer)***
 - ▣ ***Electric double-layer capacitors (EDLC)***

Ultracapacitors

35


□ Electric double-layer capacitor

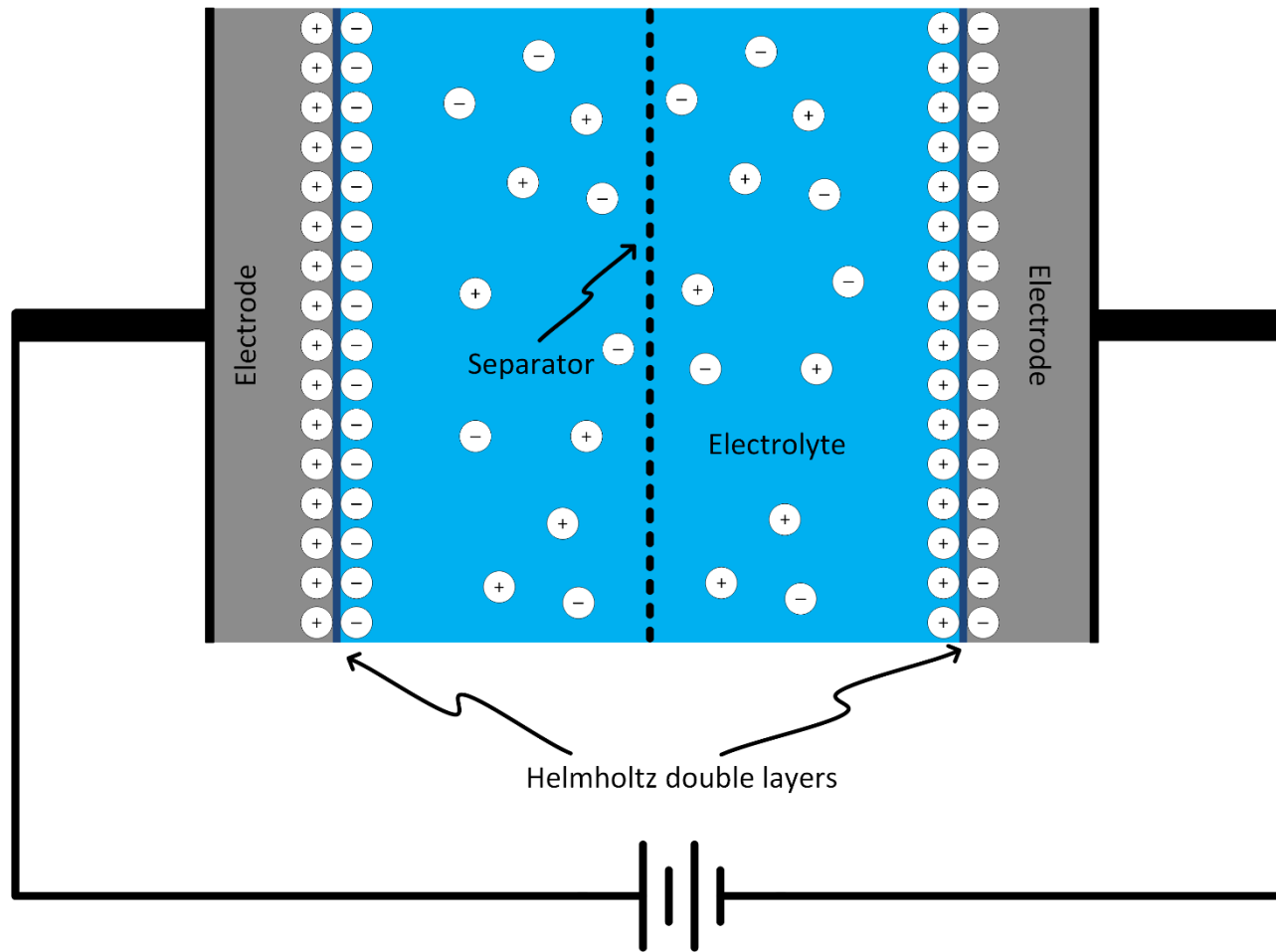

Ultracapacitors

36


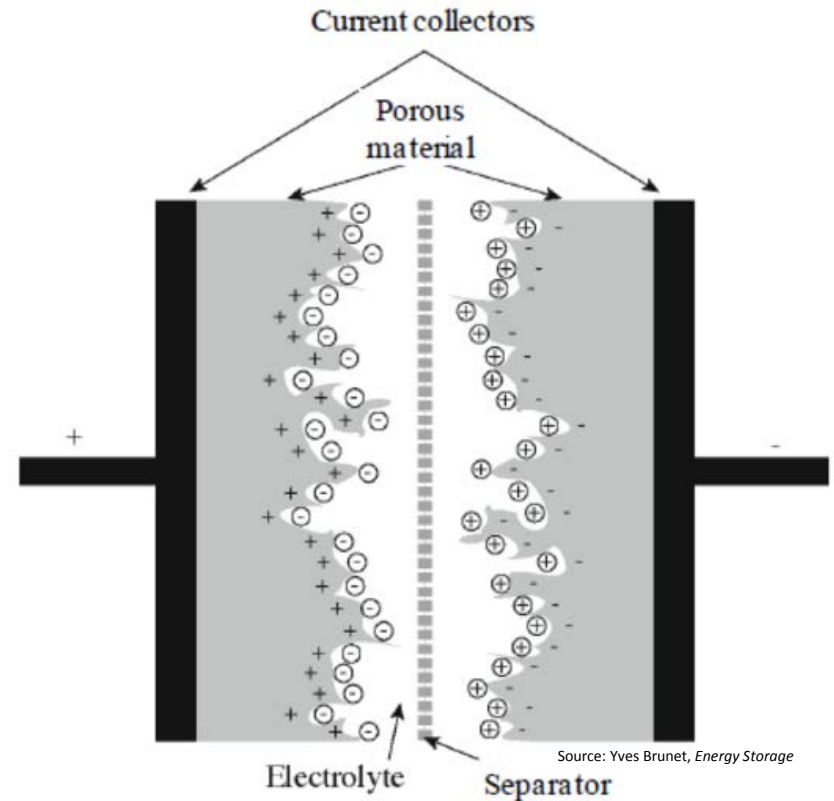
- Electrodes are rough and porous
 - ▣ Surface area is increased
 - ▣ Activated charcoal
 - ▣ Aerogel
- No charge transfer between the electrolyte and the electrode
- Separator is permeable
 - ▣ Mechanical separation preventing contact between electrodes
- Thickness of double layers is on the molecular scale



Ultracapacitors

37

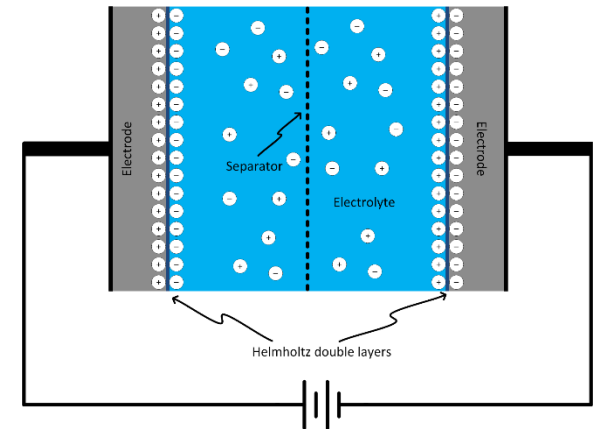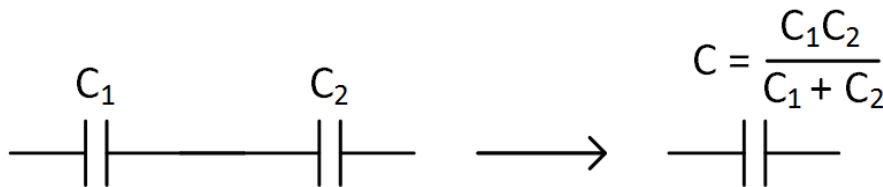- Two double layers
 - ▣ Two capacitors in series



- Capacitance values in the range of 1 ... 1000s of farads are common
- Ultracapacitors are **polarized**
 - ▣ Positive electrode must be kept at a higher potential
- **Maximum voltage** determined by the electrolyte dissociation voltage
 - ▣ Typically ~ 2.5 V
 - ▣ For higher-voltage operation, multiple ultracapacitors are connected in series


38

Equivalent Circuit Model

Equivalent Circuit Model

39

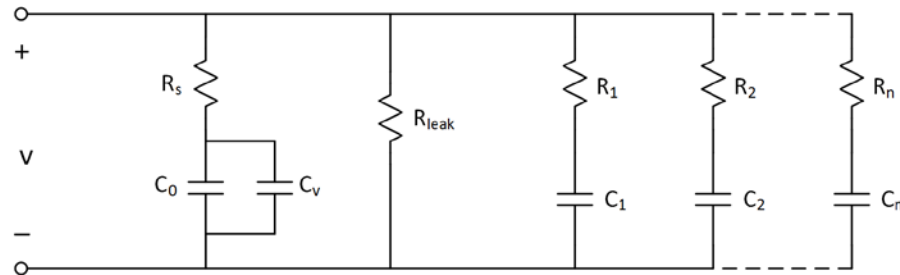□ *Ultracapacitor equivalent circuit model*




- R_s : equivalent series resistance (ESR)
 - Primarily due to ionic conduction in the electrolyte
- C_0 : primary capacitance of the ultracapacitor
- C_v : voltage-dependent capacitance
 - Associated with diffusion layers near the double layers
 - $C_v = k \cdot v$
- R_{leak} : leakage resistance
 - Typically specified as a leakage current at V_{max}
- $R_1, C_1, \dots, R_n, C_n$: distributed resistance and capacitance of the porous electrodes
 - Models multiple time constants

Equivalent Circuit Model

40

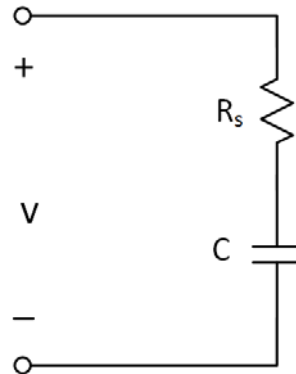- We will typically simplify this model significantly
 - ▣ Account for only capacitance and ESR
 - ▣ Typical ESR values: $0.5 \text{ m}\Omega \dots 500 \text{ m}\Omega$



- Account for leakage resistance, R_{leak} , when appropriate
 - ▣ Self-discharge
 - ▣ Typical leakage resistance: $100 \text{ }\Omega \dots 100 \text{ k}\Omega$
 - ▣ Typical leakage currents: $10\mu\text{A} \dots 10 \text{ mA}$

41

Charging and Discharging

Charging and Discharging

42

- The voltage seen across a capacitor is proportional to the stored charge differential

$$V = \frac{Q}{C}$$

- So, unlike batteries, capacitor voltage does not remain constant as a capacitor discharges
- Power electronic circuitry generally required to interface between ultracapacitors and load
 - ▣ DC-DC converters
 - ▣ Inverters – DC-AC and AC-DC converters
- Interface circuitry also provides charge/discharge control
 - ▣ Current/power control


Charging and Discharging

43


- Two primary modes of charging/discharging
 - ▣ ***Constant current***
 - ▣ ***Constant power***
- Unlike batteries, capacitors can be ***charged and discharged at the same rates***
- Constant-current charging is simple
 - ▣ Both in terms of circuitry and analysis/design
- Constant-power charging useful in many applications, such as ***regenerative braking***
 - ▣ Charging while drawing constant power from the vehicle
 - ▣ Discharging while supplying constant power to the vehicle

Constant-Current Charging

44

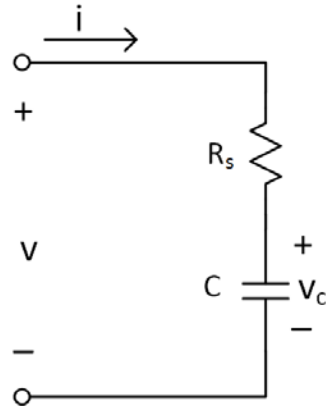


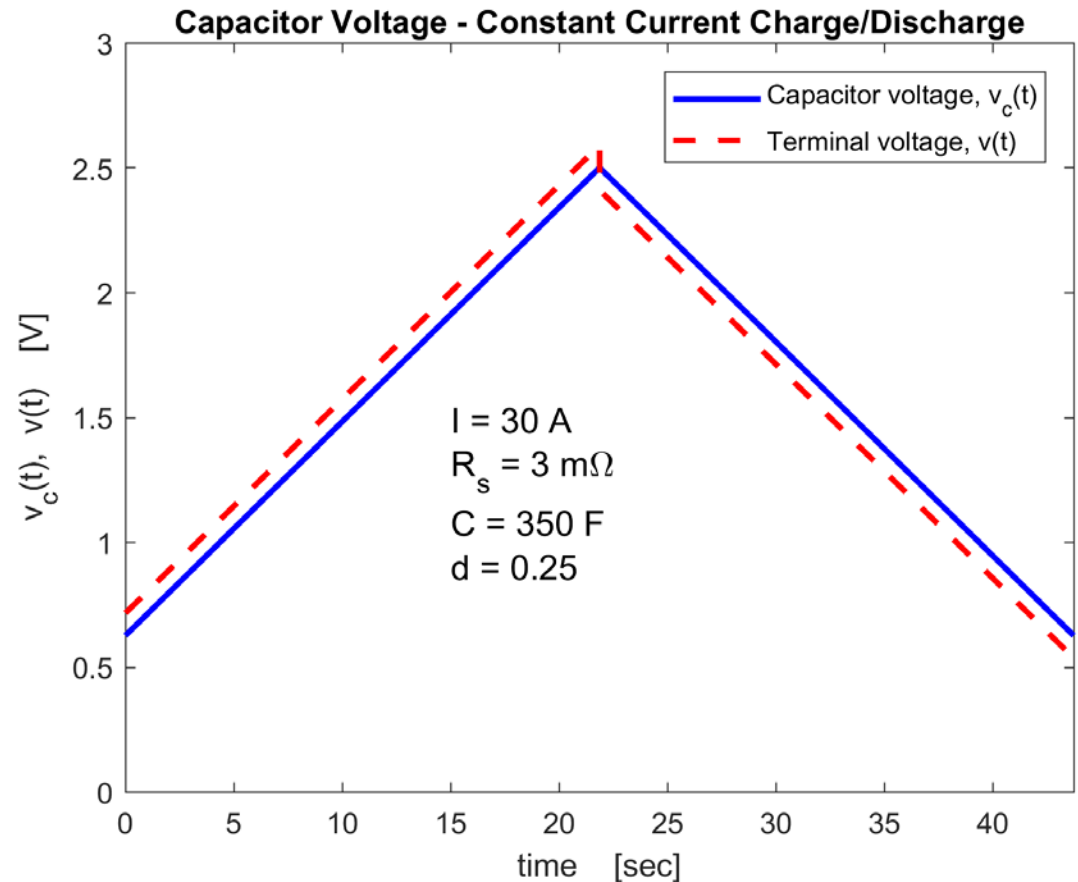- Voltage drop across R_s during charge/discharge
- Constant rate of voltage change
- Power varies




Constant-Power Charging

45

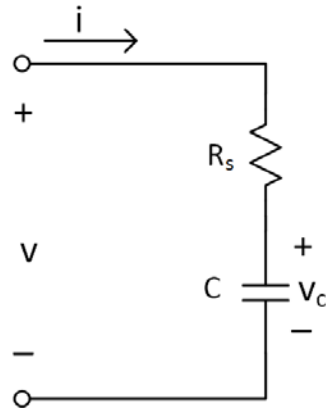

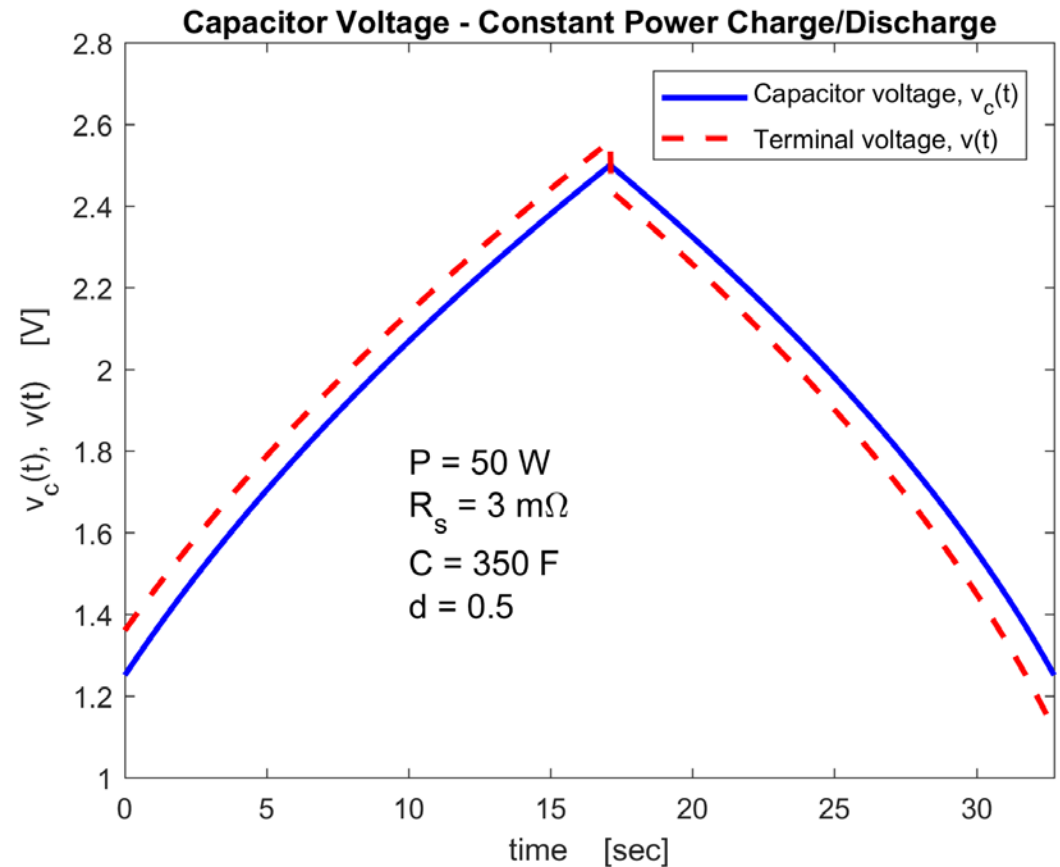- Varying rate of voltage change
- Current varies depending on state of charge
 - Higher current at lower state of charge
 - Lower current near full charge



46

Cell Balancing

Cell Balancing

47

- Typically, $V_{max} = 2.5 V \dots 3.0 V$
 - Series-connected cells provide higher voltages
- Consider a series connection of four cells
- Equal charge differential, $\pm Q$, on each cell
- The voltage across each capacitor is

$$V_1 = \frac{Q}{C_1}, V_2 = \frac{Q}{C_2}, V_3 = \frac{Q}{C_3}, V_4 = \frac{Q}{C_4}$$


- Nominally, all capacitors are equal

$$C_1 = C_2 = C_3 = C_4 = C$$

- Nominally, all voltages are equal

$$V_1 = V_2 = V_3 = V_4 = \frac{Q}{C} = 2.5V$$

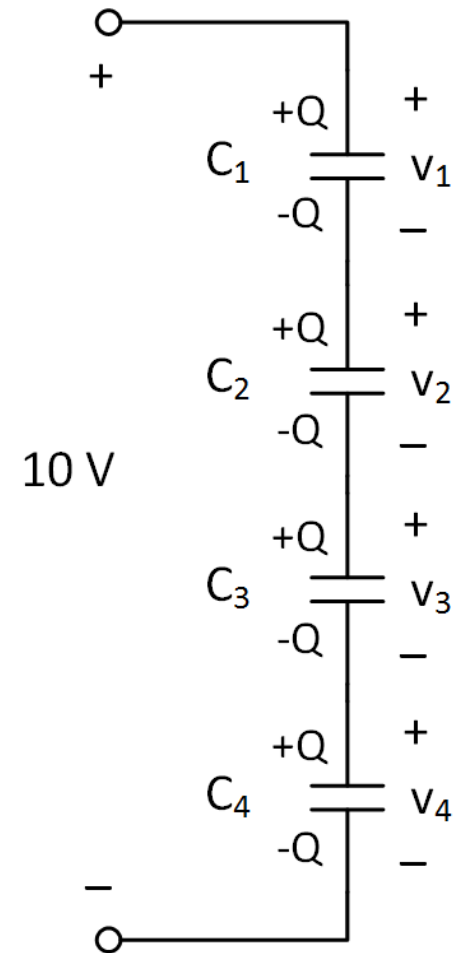- But, capacitances may vary by as much as $\pm 20\%$



Cell Balancing

48

- Consider the following scenario:
- Total equivalent capacitance

$$C_{eq} = 0.24C$$

- Stored charge


$$Q = 10 V \cdot 0.24C$$

- Now, **cell voltages are imbalanced**

$$V_1 = V_2 = \frac{Q}{1.2C} = \frac{10 V \cdot 0.24C}{1.2C} = 2 V$$

$$V_3 = V_4 = \frac{Q}{0.8C} = \frac{10 V \cdot 0.24C}{0.8C} = 3 V$$

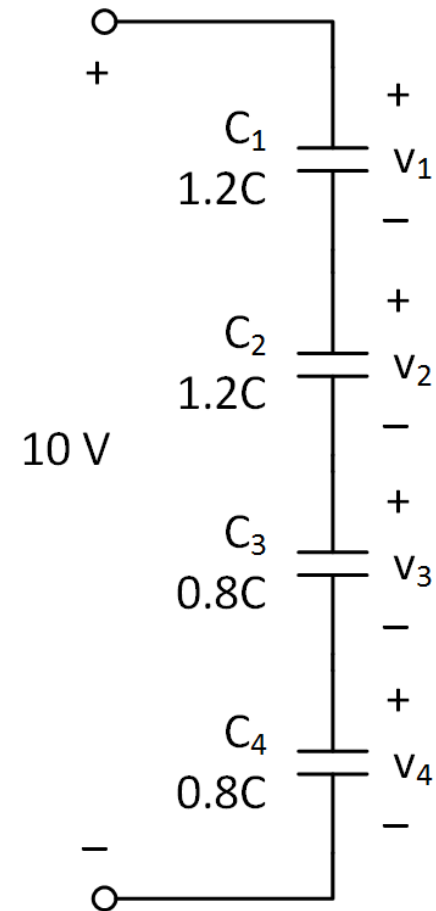
- If $V_{max} = 2.5 V$, then
 - C_1 and C_2 are **underutilized**
 - C_3 and C_4 are **overstressed**



Cell Balancing

49

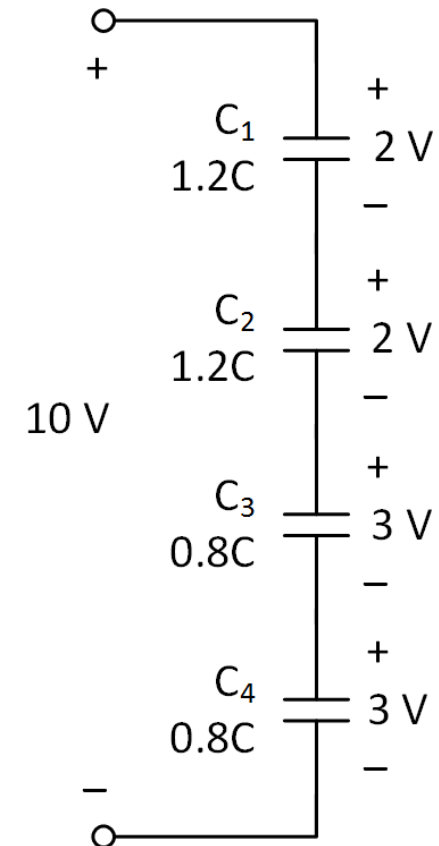- Cell balancing circuitry
 - Safely utilize each cell's storage capacity
- Two balancing approaches:
 - **Resistive balancing**
 - Resistors placed in parallel with the cells
 - Slow – not for high-duty-cycle applications
 - **Active balancing**
 - Cell voltages monitored and electronic switches balance voltages
 - Fast – good for high-duty-cycle applications



50

Efficiency

Ultracapacitors – Efficiency

51

- Ultracapacitors have small, but non-zero, ESR
 - ▣ They are lossy devices
 - ▣ Not all input energy is available for use
 - ▣ Efficiency is less than 100%
- We will define **round-trip efficiency** as the efficiency through an entire charge/discharge cycle
 - ▣ Ratio of output energy to input energy

$$\eta_{rt} = \frac{E_{out}}{E_{in}} \cdot 100\% \quad (1)$$

- Efficiency depends on how a capacitor is used
 - ▣ Rate of charge/discharge
 - ▣ Depth of discharge

Ultracapacitors – Efficiency

52

- Energy stored by a capacitor is proportional to the capacitor voltage squared

$$E_c = \frac{1}{2} CV^2 \quad (2)$$

- Capacitor's effectiveness at storing energy depends on its state of charge (SOC)
 - ▣ Energy stored more quickly at high SOC
 - ▣ Energy stored more slowly at low SOC
- Loss in ESR depends on the current
- Therefore, **instantaneous efficiency**, $\eta(t)$, varies with SOC
 - ▣ Total round-trip efficiency depends on depth of discharge
 - ▣ Ultracapacitors are typically not discharged completely

Discharge Factor

53

□ ***Discharge factor***

$$d = \frac{V_{min}}{V_{max}} \quad (3)$$

- V_{min} : voltage at the lowest allowable SOC
 - V_{max} : maximum allowable (fully-charged) capacitor voltage
-
- We'll now examine the round-trip efficiency for capacitors operated at constant current and at constant power

Efficiency – Constant Current

54

- For a capacitor operating at a non-zero discharge factor, only some of the stored energy is usable
- **Usable energy**

$$E_u = \frac{1}{2} C V_{max}^2 - \frac{1}{2} C V_{min}^2$$

$$E_u = \frac{1}{2} C V_{max}^2 - \frac{1}{2} C (d V_{max})^2$$


$$E_u = \frac{1}{2} C V_{max}^2 (1 - d^2) \quad (4)$$

- Power dissipated in the ESR at **constant current**, I , is

$$P_R = I^2 R_S$$

- Energy lost in the ESR is

$$E_R = I^2 R_S \cdot t$$

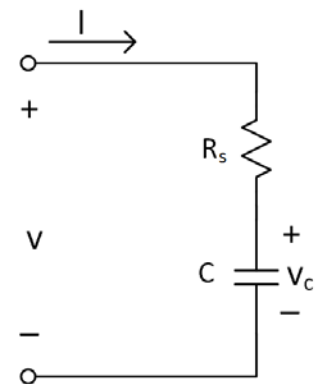

Charging efficiency – Constant Current

55

- During the charging cycle, the efficiency is

$$\eta_1 = \frac{E_u}{E_u + E_R} = \frac{\frac{1}{2}CV_{max}^2(1-d^2)}{\frac{1}{2}CV_{max}^2(1-d^2) + I^2R_S \cdot t_c}$$

where t_c is the duration of the charging cycle

- We can solve for t_c as follows

$$V_{max} - V_{min} = \frac{I \cdot t_c}{C} \quad \rightarrow \quad t_c = \frac{CV_{max}(1-d)}{I}$$

- The efficiency then becomes

$$\eta_1 = \frac{\frac{1}{2}CV_{max}^2(1-d^2)}{\frac{1}{2}CV_{max}^2(1-d^2) + IR_S CV_{max}(1-d)}$$

$$\eta_1 = \frac{\frac{1}{2}V_{max}(1-d^2)}{\frac{1}{2}V_{max}(1-d^2) + IR_S(1-d)} \quad (5)$$

Round-Trip Efficiency – Constant Current

56

- Similar loss is incurred in the ESR during discharge
 - ▣ Energy output is the stored energy minus resistive loss
- **Round-trip efficiency** is

$$\eta_{rt} = \frac{E_{out}}{E_{in}} = \frac{E_u - E_R}{E_u + E_R}$$

$$\eta_{rt} = \frac{\frac{1}{2}CV_{max}^2(1-d^2) - IR_S CV_{max}(1-d)}{\frac{1}{2}CV_{max}^2(1-d^2) + IR_S CV_{max}(1-d)}$$


$$\eta_{rt} = \frac{\frac{1}{2}V_{max}(1-d^2) - IR_S(1-d)}{\frac{1}{2}V_{max}(1-d^2) + IR_S(1-d)}$$

(6)

Instantaneous Efficiency – Constant Current

57

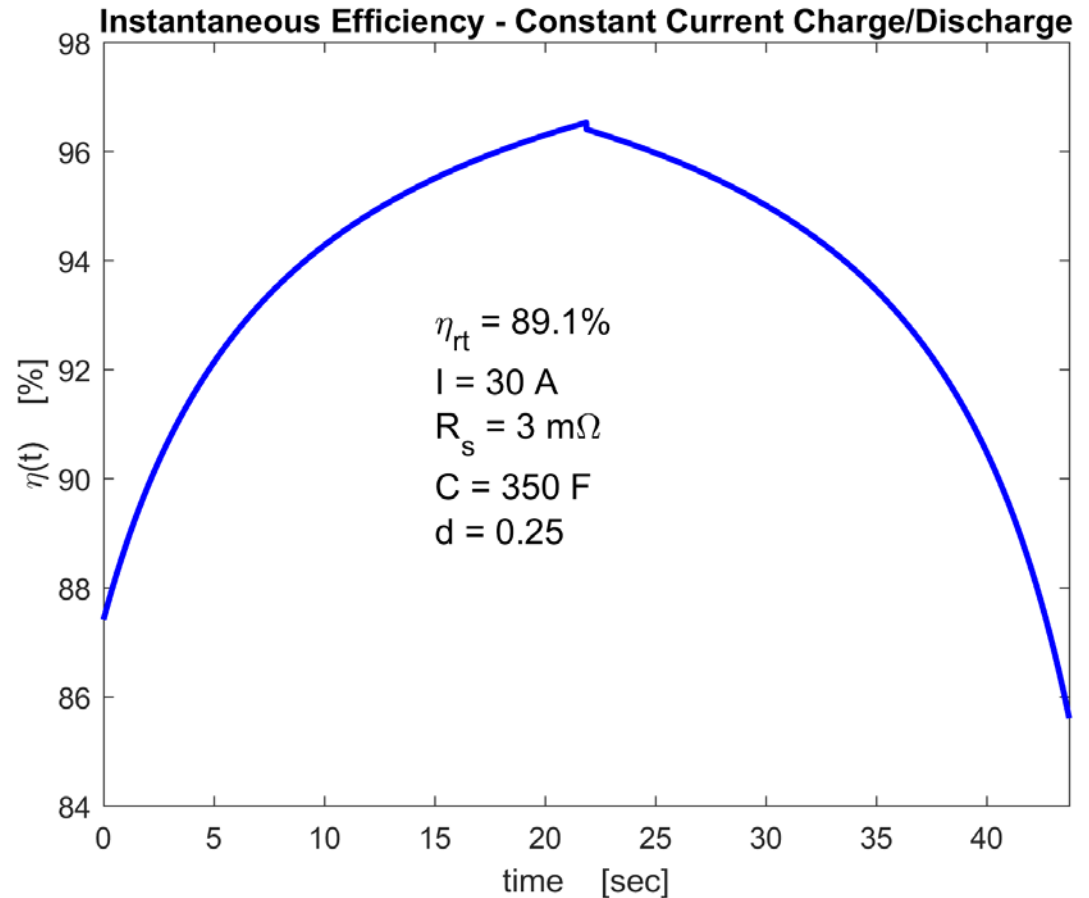
- At lower SOC:
 - ▣ Low rate of energy storage
 - ▣ Low efficiency
- At higher SOC:
 - ▣ Higher rate of energy storage
 - ▣ Higher efficiency



Efficiency vs. Current – Constant Current

58

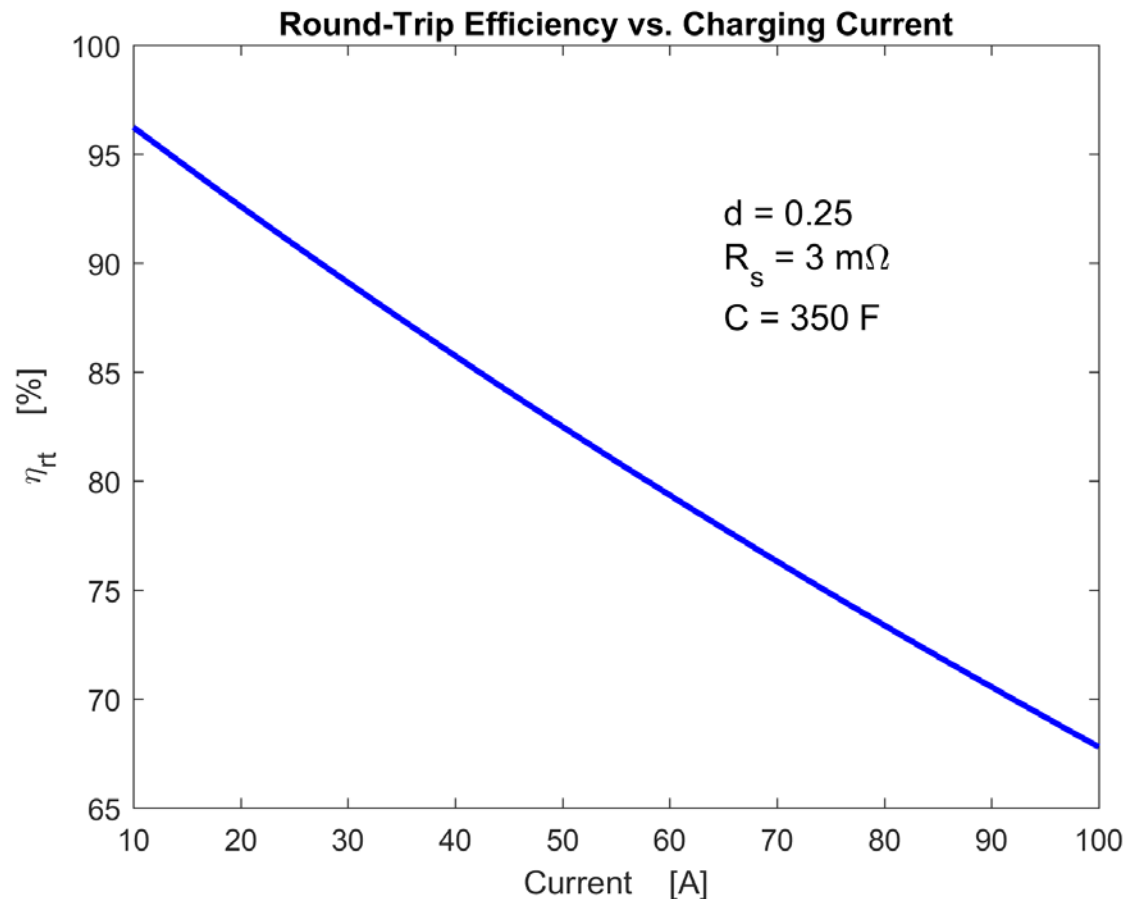
- As current increases, loss in ESR increases



Efficiency vs. Discharge Factor – Constant Current

59

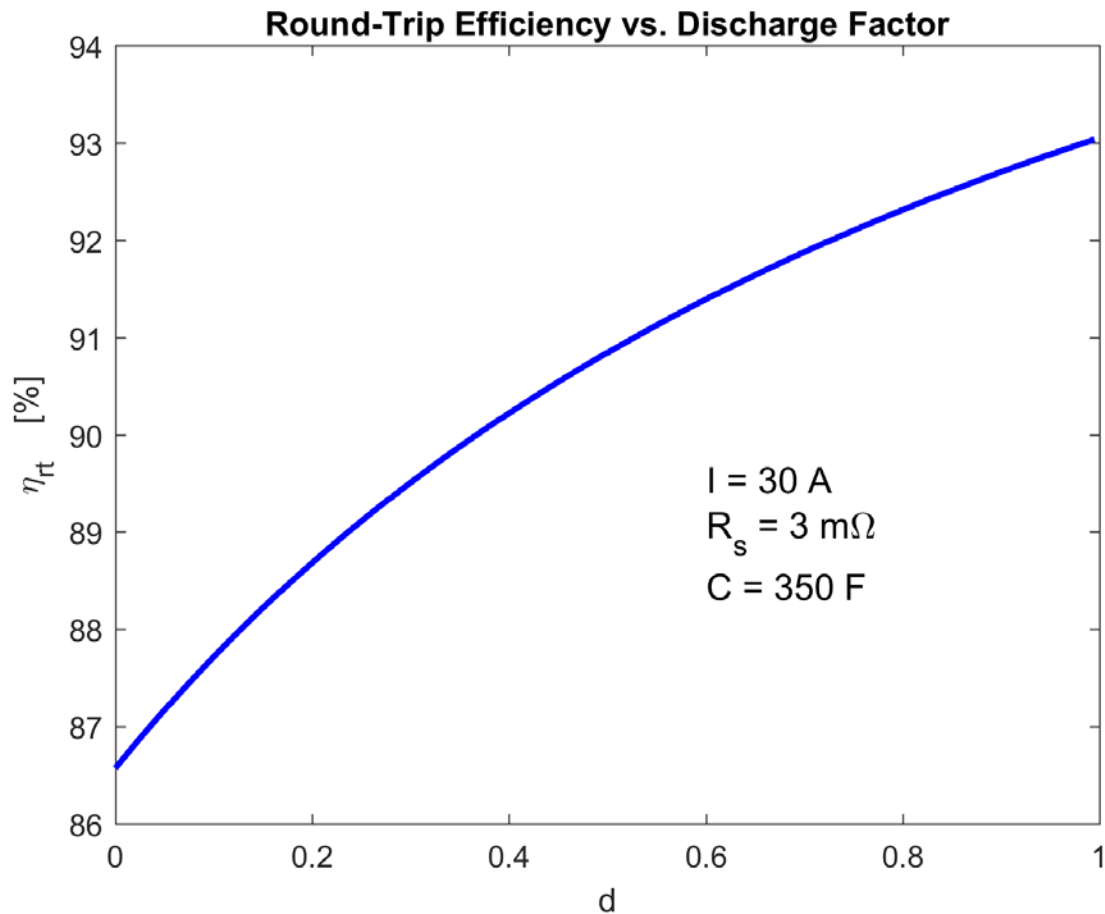- Greater depth-of-discharge corresponds to lower efficiency



Efficiency – Constant Power

60

- For constant-power charging/discharging, we start with the same expression for efficiency

$$\eta_{rt} = \frac{E_u - E_R}{E_u + E_R}$$

- Usable energy is the same

$$E_u = \frac{1}{2} C V_{max}^2 (1 - d^2)$$

- But, since current is now time varying, the energy lost in the resistance (in one direction) is

$$E_R = \int_0^{t_c} i^2(t) R_S dt$$

- Things get a bit more complicated, as we now need to solve a differential equation to determine the capacitor voltage

Efficiency – Constant Power

61

- The input to the capacitor is now constant power
 - ▣ Write a power-balance equation

$$P - i^2(t) \cdot R_s - i(t)v_c(t) = 0$$


- Current is given by

$$i(t) = C \frac{dv_c}{dt}$$

- The power balance becomes

$$R_s C^2 \left(\frac{dv_c}{dt} \right)^2 + C \frac{dv_c}{dt} v_c(t) - P = 0 \quad (7)$$

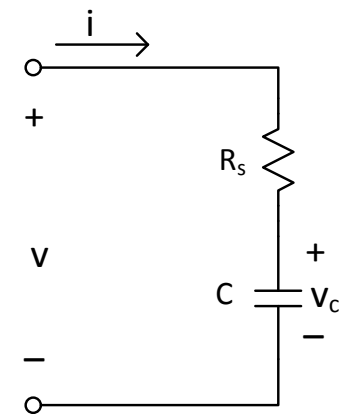- An ordinary differential equation in **quadratic** form



Efficiency – Constant Power

62

- Applying the quadratic formula to (7), we get

$$\frac{dv_c}{dt} = \frac{-Cv_c(t) \pm \sqrt{C^2v_c^2(t) + 4R_S C^2 P}}{2R_S C^2}$$

- Simplifying, and keeping only the valid '+' solution

$$\frac{dv_c}{dt} = \frac{-v_c(t) + \sqrt{v_c^2(t) + 4R_S P}}{2R_S C} \quad (8)$$

- For **discharging** this becomes

$$\frac{dv_c}{dt} = \frac{-v_c(t) + \sqrt{v_c^2(t) - 4R_S P}}{2R_S C} \quad (9)$$


- We don't have a nice closed-form solutions to (8) or (9), but we can solve them numerically

Instantaneous Efficiency – Constant Power

63

- At lower SOC:
 - ▣ High current
 - ▣ High I^2R loss
 - ▣ Low efficiency

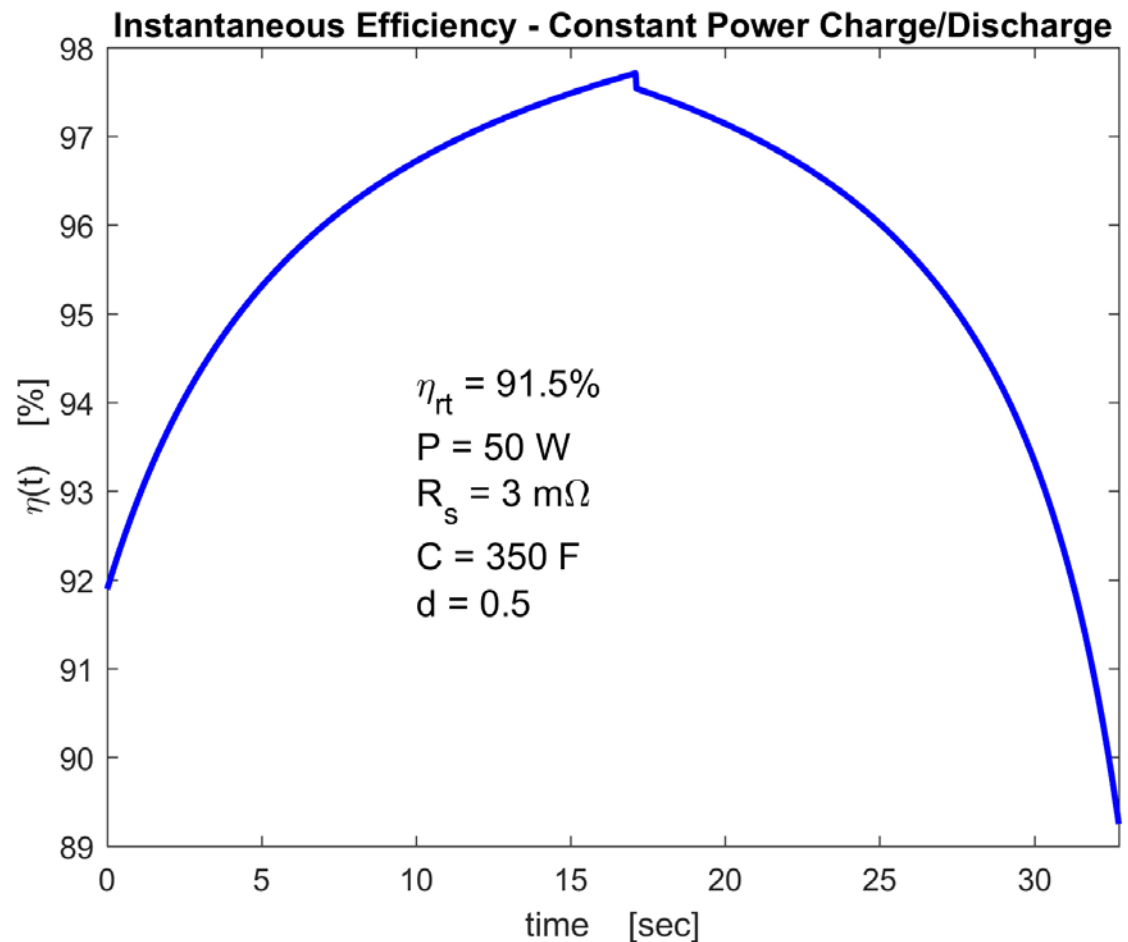
- At higher SOC:
 - ▣ Lower current
 - ▣ Lower I^2R loss
 - ▣ Higher efficiency



Efficiency vs. Current – Constant Power

64

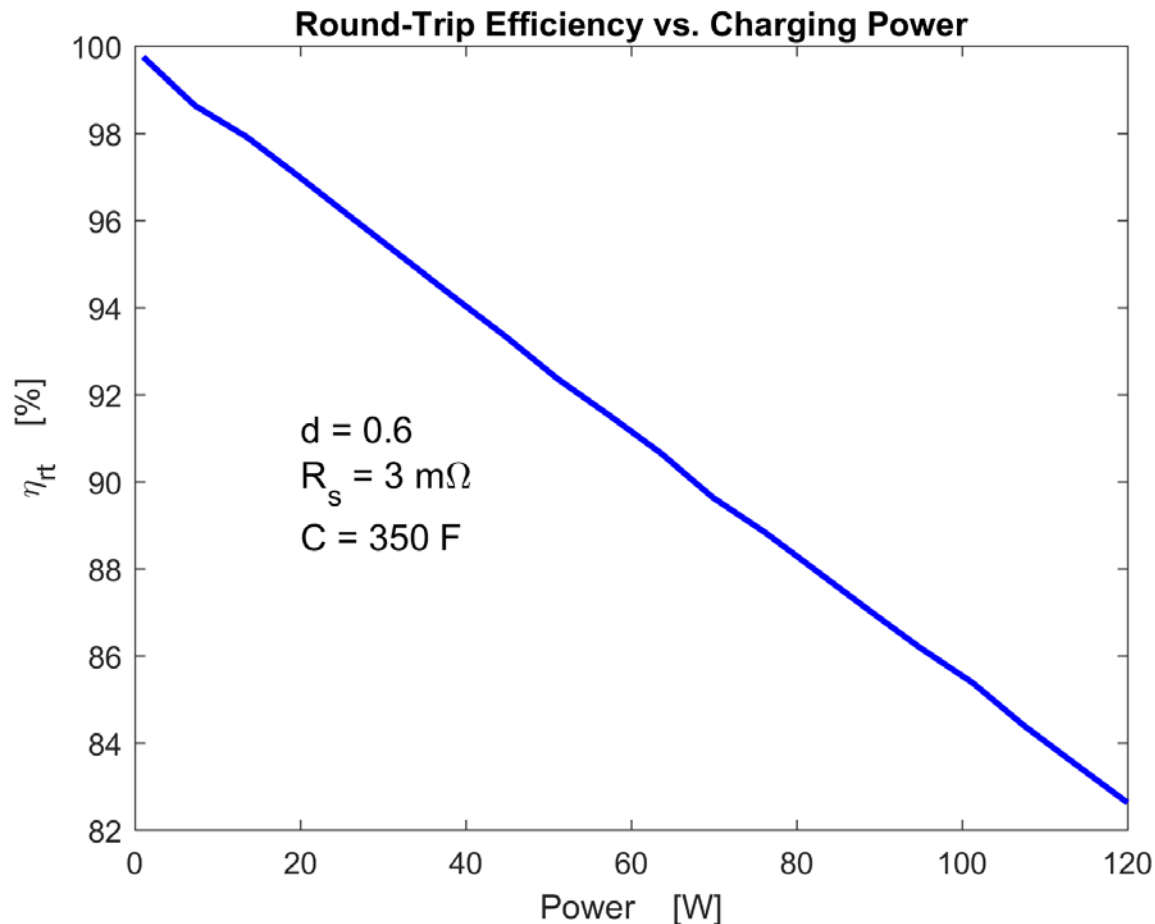
- As power increases, current increases and resistive loss increases



Efficiency vs. Discharge Factor – Constant Power

65

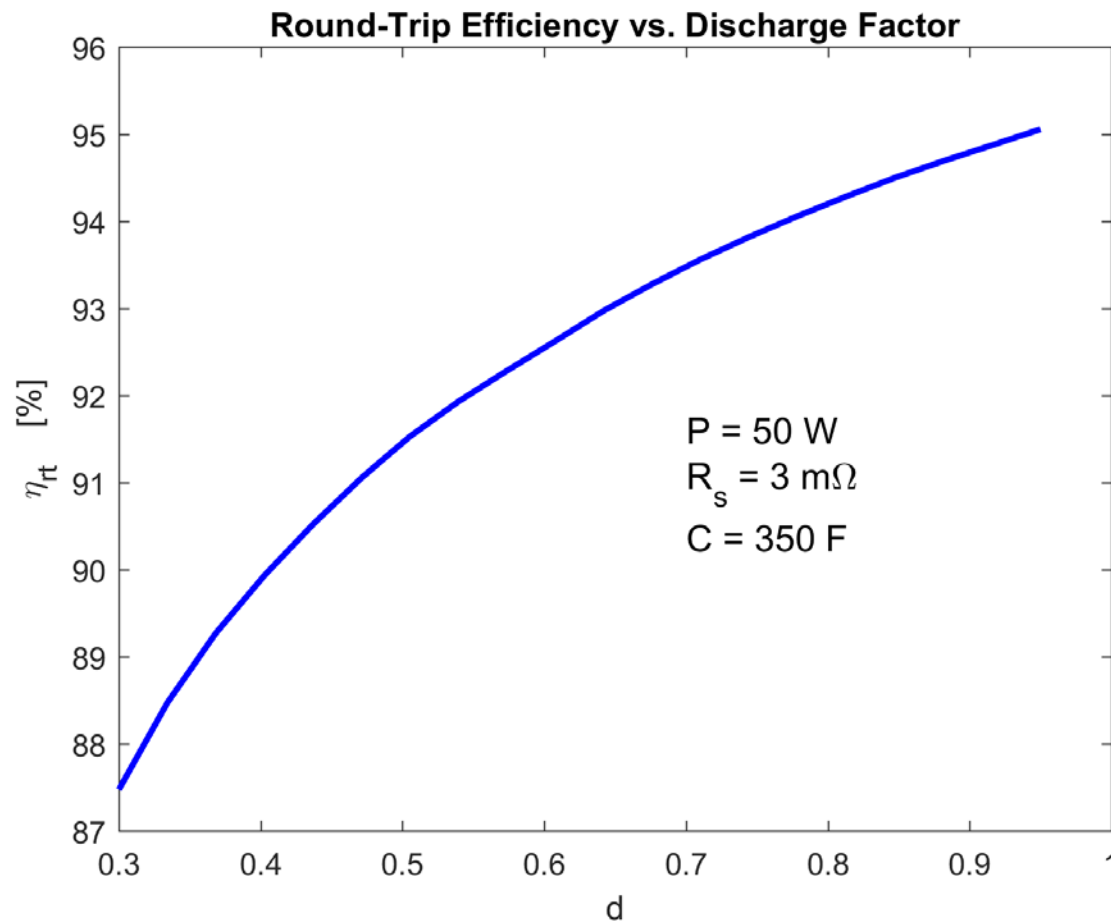- Greater depth-of-discharge corresponds to lower efficiency



Approximate Efficiency – Constant Power

66

- Sometimes we may want a quick way to approximate efficiency for constant-power charging/discharging
 - ▣ Calculate an average current
 - ▣ Calculate efficiency as you would for constant-current charging/discharging
- Approximate average current as the average of the maximum and minimum currents

$$I_{avg} \approx \frac{I_{max} + I_{min}}{2}$$

where

$$I_{max} = \frac{P}{V_{min}} \quad \text{and} \quad I_{min} = \frac{P}{V_{max}}$$

- Then, efficiency is approximately given by

$$\eta_{rt} \approx \frac{\frac{1}{2}V_{max}(1-d^2) - I_{avg}R_S(1-d)}{\frac{1}{2}V_{max}(1-d^2) + I_{avg}R_S(1-d)} \quad (10)$$


67

Series-Connected Capacitor Cells

Series-Connected Capacitor Cells

68

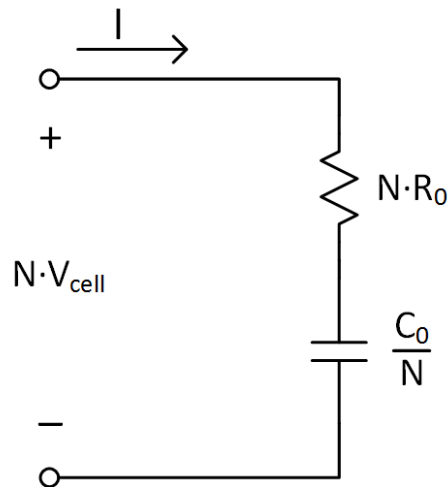- To achieve higher working voltages, multiple capacitor cells are connected in series
- How does this effect
 - ▣ Energy storage?
 - ▣ Efficiency?
- Consider a series connection of N cells, each with a capacitance of C_0 and a maximum voltage of V_{cell}
 - ▣ Equivalent circuit model:



Series-Connected Capacitor Cells

69

- Energy stored:

$$E = \frac{1}{2} \frac{C_0}{N} (N \cdot V_{cell})^2$$

$$E = N \cdot \frac{1}{2} C_0 V_{cell}^2$$

- As expected, this is N times the energy stored in a single cell
- For a discharge factor of d , the usable stored energy is

$$E_u = N \frac{1}{2} C_0 V_{cell}^2 - N \frac{1}{2} C_0 (dV_{cell})^2$$

$$E_u = N \frac{1}{2} C_0 V_{cell}^2 (1 - d^2) \quad (11)$$

Cells in Series – Constant Current

70

- Energy lost in the resistance during charging (or discharging):

$$E_R = I^2 N R_0 t_c$$

- For **constant-current** operation

$$V_{max} - V_{min} = V_{max}(1 - d) = N V_{cell}(1 - d)$$

$$N V_{cell}(1 - d) = \frac{I t_c}{C} = \frac{I t_c}{C_0/N}$$

- The charging (or discharging) time is

$$t_c = \frac{C_0 V_{cell}(1 - d)}{I}$$

- So, losses during charging (or discharging) are

$$E_R = I^2 N R_0 \frac{C_0 V_{cell}(1 - d)}{I}$$

$$E_R = N I R_0 C_0 V_{cell}(1 - d) \quad (12)$$

Cells in Series – Constant Current

71

- Round-trip efficiency is

$$\eta_{rt} = \frac{E_u - E_R}{E_u + E_R}$$

- Using (11) and (12), we get

$$\eta_{rt} = \frac{N \frac{1}{2} C_0 V_{cell}^2 (1 - d^2) - N I R_0 C_0 V_{cell} (1 - d)}{N \frac{1}{2} C_0 V_{cell}^2 (1 - d^2) + N I R_0 C_0 V_{cell} (1 - d)}$$


$$\eta_{rt} = \frac{\frac{1}{2} V_{cell} (1 - d^2) - I R_0 (1 - d)}{\frac{1}{2} V_{cell} (1 - d^2) + I R_0 (1 - d)}$$

- This is, of course, the same as for a single cell, *but*
 - ▣ **Current can be reduced at a higher maximum voltage**
 - Efficiency will improve

Cells in Series – Constant Power

72

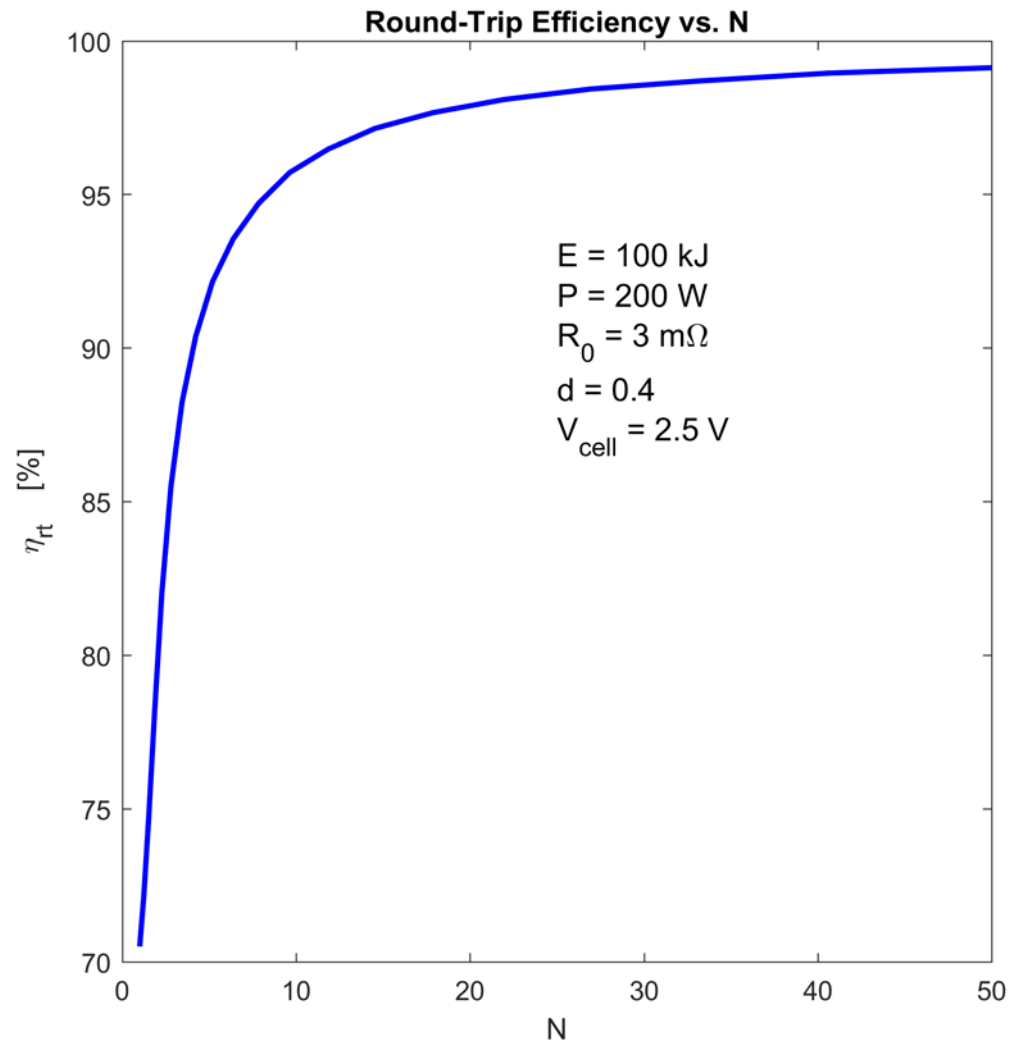- For **constant-power** operation, we'll again investigate numerically
- Round-trip efficiency vs. # of series-connected cells:
 - Assuming:
 - $E = 100 \text{ kJ}$
 - $P = 200 \text{ W}$
 - $R_0 = 3 \text{ m}\Omega$
 - $d = 0.25$
 - $V_{\text{cell}} = 2.5 \text{ V}$



73

Capacitor Bank Sizing

Ultracapacitor Sizing

74

- Sizing a capacitor bank involves determining the following parameters
 - Stored energy: E
 - Available power: P
 - Maximum voltage: V_{max}
 - Minimum voltage: V_{min}
 - Discharge factor: d
 - # of cells in series and/or parallel: N_s, N_p
 - Total capacitance: C
 - Cell capacitance: C_0
 - Efficiency: η
- Sizing procedure depends on which of these parameters are specified
- We'll outline a procedure assuming the specified requirements are:
 - Energy storage
 - Power
 - Voltage range

Ultracapacitor Sizing Procedure

75

1. Discharge factor

$$d = \frac{V_{min}}{V_{max}}$$

2. Number of series-connected cells

$$N_s = \frac{V_{max}}{V_{cell}}$$

3. Total required capacitance

$$E = \frac{1}{2} C V_{max}^2 (1 - d^2) \quad \rightarrow \quad C = \frac{2E}{V_{max}^2 (1 - d^2)}$$

4. Cell capacitance

$$C_0 = N_s \cdot C$$

5. Determine the resulting efficiency using the required power

- Evaluate numerically or approximate

6. Iterate if necessary

- Adjust N as needed

Ultracapacitor Sizing – Example

76

- Size a capacitor bank for an energy recovery system for a tower crane with the following specifications
 - Height: $h = 50 \text{ m}$
 - Capacity: $m = 5,000 \text{ kg}$
 - Time to lift max load: $t_d = 30 \text{ s}$
- Let's assume we have a power conversion system that can operate over the range of $60 V_{DC} \dots 150 V_{DC}$ at an efficiency of $\eta_{pcs} = 97\%$

-
- The required energy to lift the maximum load is

$$E = mgh \cdot \frac{1}{\eta_{pcs}} = 5000 \text{ kg} \cdot 9.81 \frac{\text{m}}{\text{s}^2} \cdot 50 \text{ m} \cdot \frac{1}{0.97}$$

$$E = 2.53 \text{ MJ}$$

- Performing that lift in 30 sec corresponds to a required power of

$$P = \frac{E}{t_d} = \frac{2.53 \text{ MJ}}{30 \text{ s}} = 84.3 \text{ kW}$$

Ultracapacitor Sizing – Example

77

- The discharge factor is

$$d = \frac{V_{min}}{V_{max}} = \frac{60 V}{150 V} = 0.4$$

- The required number of cells in series is

$$N_s = \frac{V_{max}}{V_{cell}} = \frac{150 V}{2.5 V} = 60$$

- The total required capacitance is

$$C = \frac{2E}{V_{max}^2(1 - d^2)}$$

$$C = \frac{2 \cdot 2.53 MJ}{(150 V)^2(1 - 0.4^2)}$$

$$C = 267.6 F$$

Ultracapacitor Sizing – Example

78

- The capacitance of each individual cell is

$$C_0 = N_s \cdot C = 60 \cdot 267.6 F$$

$$C_0 = 16.1 kF$$

- So, the capacitor bank would consist of sixty 16.1 *kF* capacitors connected in series
 - 16.1 *kF* is a large capacitance – likely unavailable
 - Connect multiple capacitors in parallel

- Let's say we have access to individual capacitor cells with the following specifications

- $C_0 = 3400 F$

- $R_0 = 0.28 m\Omega$

- Five capacitors in parallel will give

$$C_{0p} = N_p C_0 = 5C_0 = 17 kF$$

$$R_{0p} = \frac{R_0}{N_p} = \frac{R_0}{5} = \frac{0.28 m\Omega}{5} = 56 \mu\Omega$$

Ultracapacitor Sizing – Example

79

- Placing 60 of the 5-capacitor groups in series, the total series resistance is

$$R_s = N_s \cdot R_{op} = 60 \cdot 56 \mu\Omega = 3.36 m\Omega$$

- For constant-power charge/discharge, we can ***approximate efficiency***
- The maximum current is

$$I_{max} = \frac{P}{V_{min}} = \frac{84.3 kW}{60 V} = 1.4 kA$$

- The minimum current is

$$I_{min} = \frac{P}{V_{max}} = \frac{84.3 kW}{150 V} = 562 A$$

- The approximate average current is

$$I_{avg} \approx \frac{I_{max} + I_{min}}{2} = 981 A$$

Ultracapacitor Sizing – Example

80

- Using the average current, we can approximate the round trip efficiency for the capacitor bank as

$$\eta_{rt} \approx \frac{\frac{1}{2}V_{cell}(1 - d^2) - I_{avg}R_{op}(1 - d)}{\frac{1}{2}V_{cell}(1 - d^2) + I_{avg}R_{op}(1 - d)}$$

$$\eta_{rt} \approx \frac{1.25 V(1 - 0.4^2) - 981 A \cdot 56 \mu\Omega(1 - 0.4)}{1.25 V(1 - 0.4^2) + 981 A \cdot 56 \mu\Omega(1 - 0.4)}$$

$$\eta_{rt} \approx 0.92 \quad \rightarrow \quad \eta_{rt} \approx 92\%$$

- Note that R_{op} is used, because that is the resistance of each of the 60 series-connected parallel combinations
- Total round-trip efficiency must include the power conversion system

$$\eta_{rt} = 0.97 \cdot 0.92 \cdot 0.97 = 0.87 \quad \rightarrow \quad \eta_{rt} = 87\%$$

Ultracapacitor Sizing – Example

81


- Solving numerically, we find that the efficiency of the capacitor bank is a bit higher

$$\eta_{rt} = 94.6\%$$

- ▣ I_{avg} overestimates the time-average current

- Accounting for conversion losses, we have

$$\eta_{rt} = 89\%$$

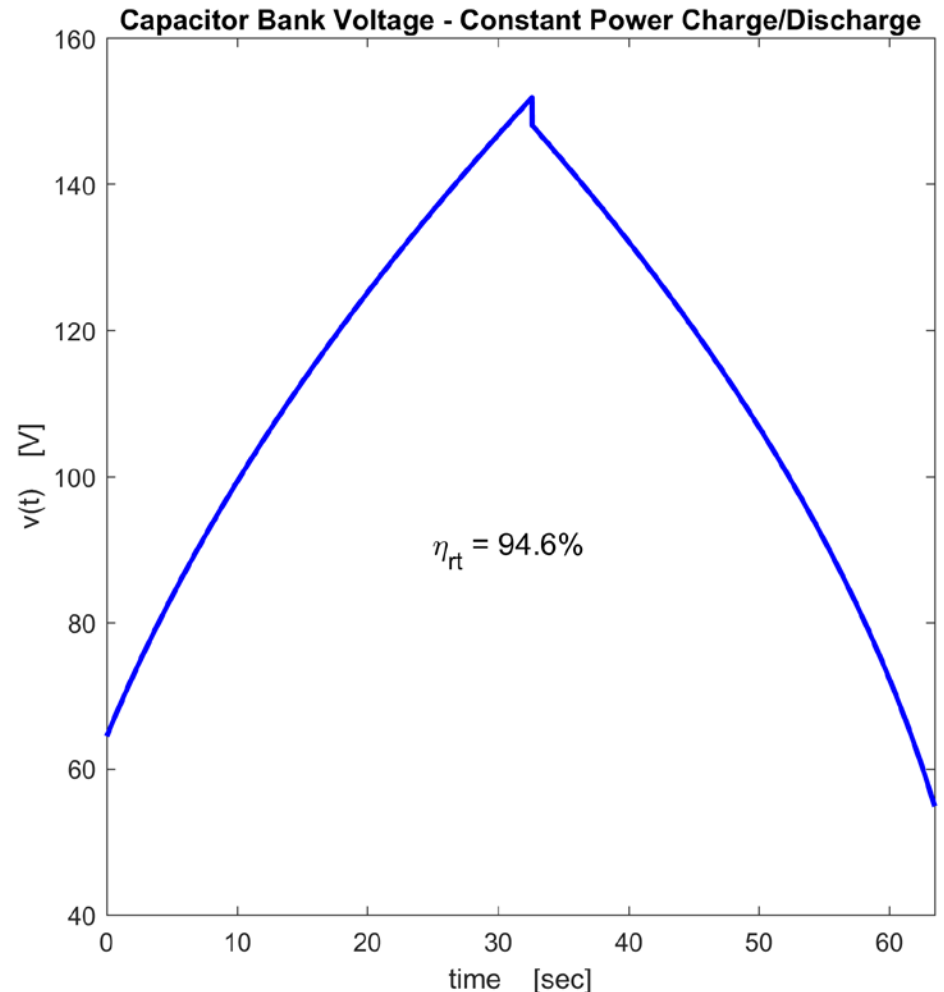

82

Ultracapacitor Efficiency Summary

Efficiency Summary

83

Configuration	Round-trip efficiency
Single capacitor	$\eta_{rt} = \frac{\frac{1}{2}V_{cell}(1 - d^2) - IR_0(1 - d)}{\frac{1}{2}V_{cell}(1 - d^2) + IR_0(1 - d)}$
N_s in series	$\eta_{rt} = \frac{\frac{1}{2}N_s V_{cell}(1 - d^2) - IN_s R_0(1 - d)}{\frac{1}{2}N_s V_{cell}(1 - d^2) + IN_s R_0(1 - d)}$
	$\eta_{rt} = \frac{\frac{1}{2}V_{max}(1 - d^2) - IR_s(1 - d)}{\frac{1}{2}V_{max}(1 - d^2) + IR_s(1 - d)}$
	$\eta_{rt} = \frac{\frac{1}{2}V_{cell}(1 - d^2) - IR_0(1 - d)}{\frac{1}{2}V_{cell}(1 - d^2) + IR_0(1 - d)}$

Efficiency Summary

84

Configuration	Round-trip efficiency
N_p in parallel	$\eta_{rt} = \frac{\frac{1}{2}V_{cell}(1 - d^2) - I\frac{R_0}{N_p}(1 - d)}{\frac{1}{2}V_{cell}(1 - d^2) + I\frac{R_0}{N_p}(1 - d)}$ $\eta_{rt} = \frac{\frac{1}{2}V_{cell}(1 - d^2) - IR_{0p}(1 - d)}{\frac{1}{2}V_{cell}(1 - d^2) + IR_{0p}(1 - d)}$

Efficiency Summary

85

Configuration	Round-trip efficiency
N_s in series, N_p in parallel	$\eta_{rt} = \frac{\frac{1}{2} N_s V_{cell} (1 - d^2) - I \frac{N_s}{N_p} R_0 (1 - d)}{\frac{1}{2} N_s V_{cell} (1 - d^2) + I \frac{N_s}{N_p} R_0 (1 - d)}$
	$\eta_{rt} = \frac{\frac{1}{2} V_{cell} (1 - d^2) - I R_{0p} (1 - d)}{\frac{1}{2} V_{cell} (1 - d^2) + I R_{0p} (1 - d)}$
	$\eta_{rt} = \frac{\frac{1}{2} V_{max} (1 - d^2) - I R_{eq} (1 - d)}{\frac{1}{2} V_{max} (1 - d^2) + I R_{eq} (1 - d)}$

- All of the expressions on this and the previous two pages are for **constant-current** charging/discharging
 - ▣ For **constant power**, use an approximate **average current**