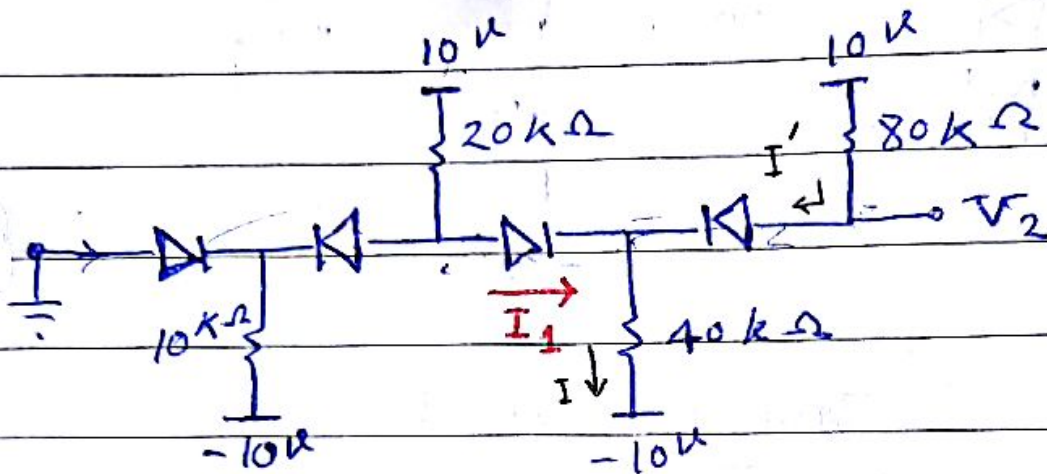


1. Calculate

$V_2, I_1$  ?




Sol: (1) all diodes are on:  $\rightarrow V_2 = 0^{\text{V}}$

$$I_1 = I - I'$$

$$\left\{ \begin{array}{l} I = \frac{10^{\text{V}}}{40\text{k}\Omega} = \frac{1}{4} \text{ mA} \\ I' = \frac{10^{\text{V}}}{80\text{k}\Omega} = \frac{1}{8} \text{ mA} \end{array} \right. \rightarrow I_1 = \frac{1}{4} - \frac{1}{8} = \frac{1}{8} \text{ mA}$$

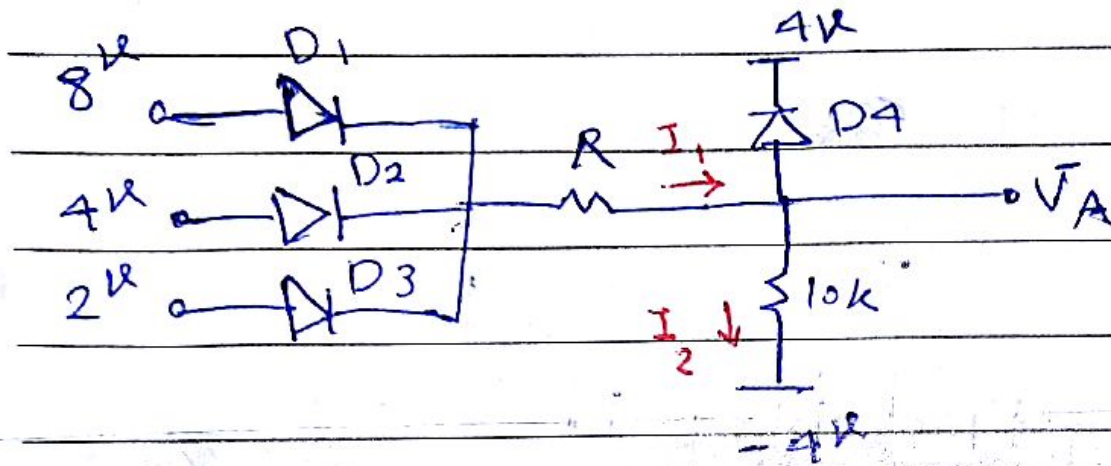2. In The Fig-1 assuming ideal diodes, calculate  $R$  while  $V_A = 2V$  and in this case calculate  $I_1, I_2$ ?




SOL (2): if  $V_A = 2V$   $\Rightarrow$  Assume  $\begin{cases} D_1: on \\ D_2: off \\ D_3: off \\ D_4: off \end{cases}$

$$\hookrightarrow \frac{8 - V_A}{R} = \frac{V_A - (-4)}{10k\Omega} \rightarrow \frac{8 - 2}{R} = \frac{2 + 4}{10k}$$

$$\hookrightarrow \frac{6}{R} = \frac{6}{10k} \Rightarrow R = 10k\Omega$$


$$I_1 = \frac{8 - 2}{10k} = \frac{6}{10k} = \frac{6}{10} \text{ mA}$$

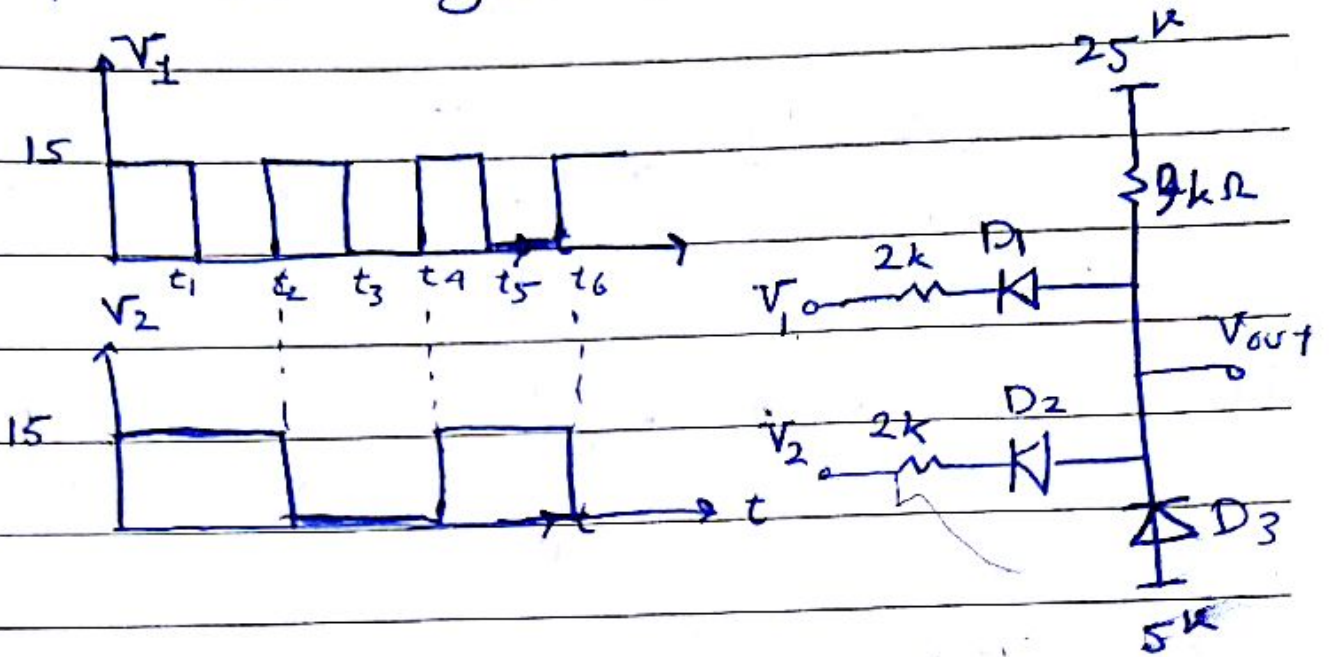3. In the fig all diodes are ideal  
plot the voltage  $V_{out}$ .



Sol: (3)

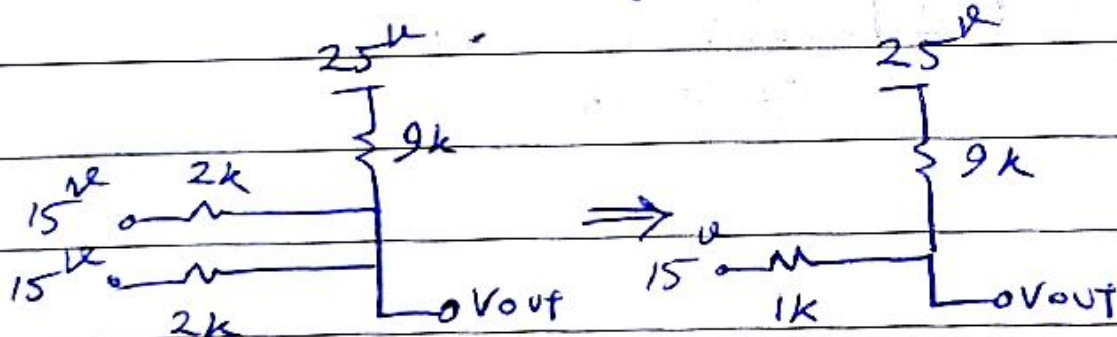in  $0 < t < t_1$   $\left\{ \begin{array}{l} D_1: \text{on} \\ D_2: \text{on} \\ D_3: \text{off} \end{array} \right.$  So.



$V_{out} = ?$  KCL  $\frac{V_{out} - 15}{1k\Omega} + \frac{V_{out} - 25}{9k} = 0$


$$\frac{V_{out} - 15}{1k} = \frac{25 - V_{out}}{9k} \rightarrow 9(V_{out} - 15) = 25 - V_{out}$$

$10 V_{out} = 160 \rightarrow V_{out} = 16 \text{ Volt}$


in  $t_1 < t < t_2 \rightarrow \begin{cases} D_1 : \text{on} \\ D_2 : \text{off} \\ D_3 : \text{on} \end{cases} \rightarrow V_{out} = 5\text{V}$

in  $t_2 < t < t_3 \rightarrow \begin{cases} D_1 : \text{off} \\ D_2 : \text{on} \\ D_3 : \text{on} \end{cases} \rightarrow V_{out} = 5\text{V}$

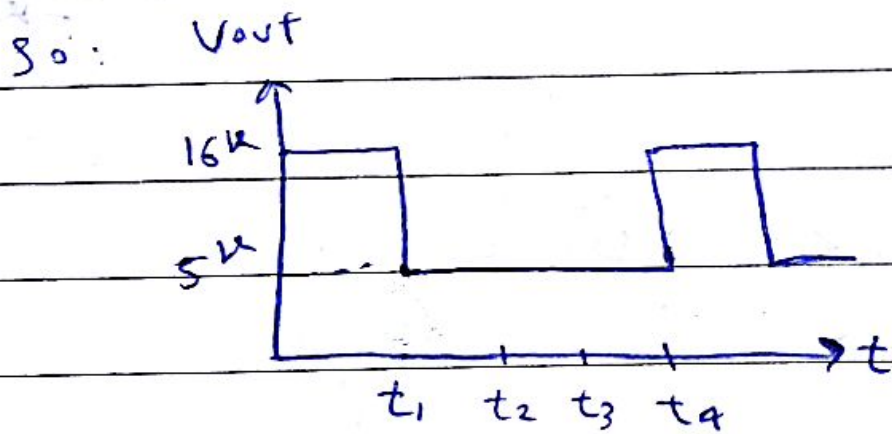in  $t_3 < t < t_4 \rightarrow \begin{cases} D_1 : \text{on} \\ D_2 : \text{on} \\ D_3 : \text{on} \end{cases} \rightarrow V_{out} = 5\text{V}$



4.  $V_{th}$  &  $R_{th}$ ?

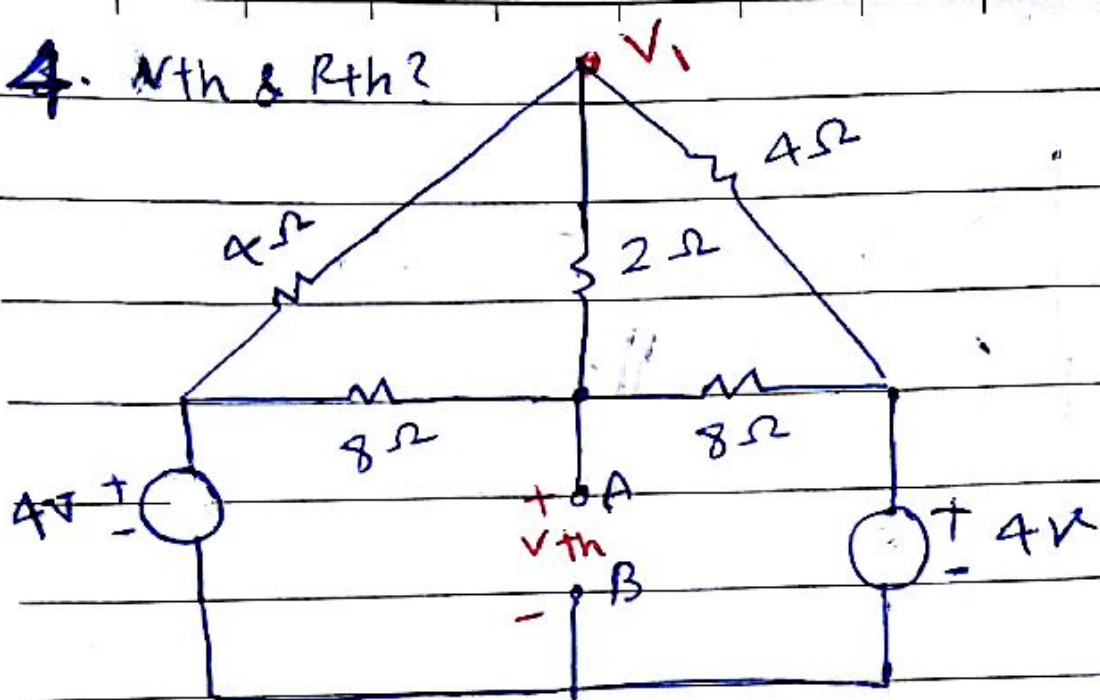

Sol (4) KCL 1)  $\frac{V_1 - 4}{4\Omega} + \frac{V_1 - V_{th}}{2\Omega} + \frac{V_1 - 4}{4\Omega} = 0$

$V_1 - 4 + 2V_1 - 2V_{th} + V_1 - 4 = 0$

$4V_1 = 2V_{th} + 8$  (1)

KCL 2)  $\frac{V_{th} - 4}{8\Omega} + \frac{V_{th} - V_1}{2\Omega} + \frac{V_{th} - 4}{8\Omega} = 0$

$V_{th} - 4 + 4V_{th} - 4V_1 + V_{th} - 4 = 0$


$4V_1 = 6V_{th} - 8$  (2)

(2)  $\rightarrow$  (1)  $\Rightarrow 6V_{th} - 8 = 2V_{th} + 8$

$4V_{th} = 16 \rightarrow V_{th} = 4V$



R<sub>th</sub>:

Sol (4)

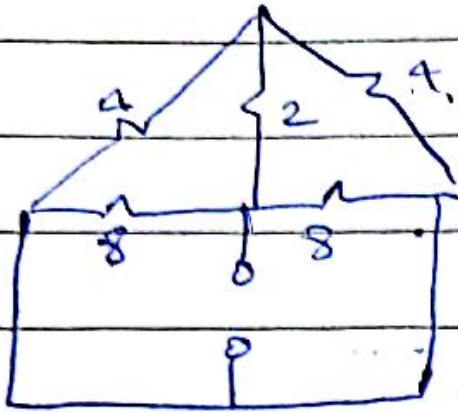


$$8 \parallel 8 = 4 \Omega$$

$$4 \parallel 4 = 2 \Omega$$

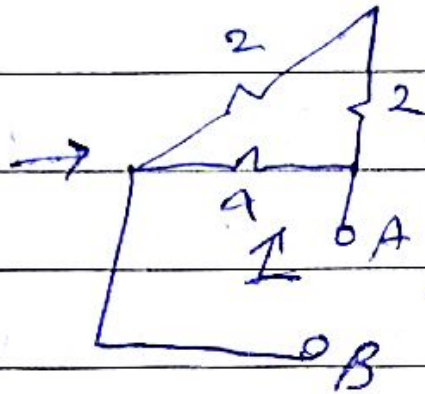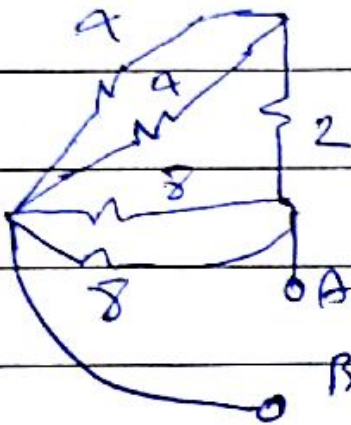


$$\rightarrow R_{th} = 1 \Omega$$

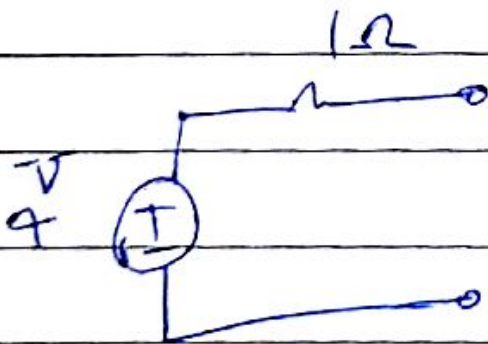


Thevenin

5.  $V_{th}$  &  $R_{th}$  ?

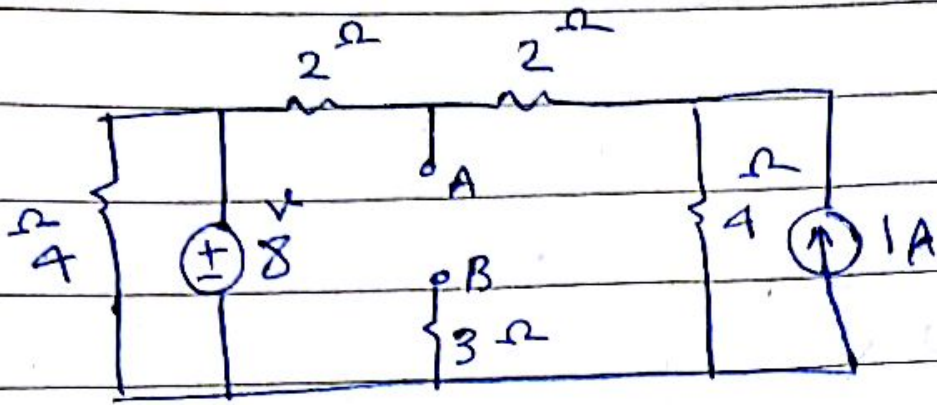


Sol: (5)  $V_{th}$ : KCL)

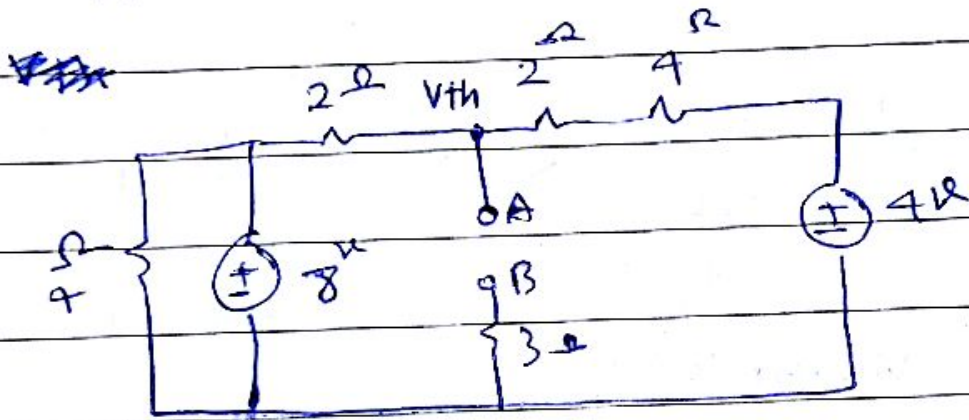

$$KCL: \frac{V_{th} - 8}{2} + \frac{V_{th} - 4}{6} = 0$$


$$3V_{th} - 24 + V_{th} - 4 = 0 \rightarrow 4V_{th} = 28$$
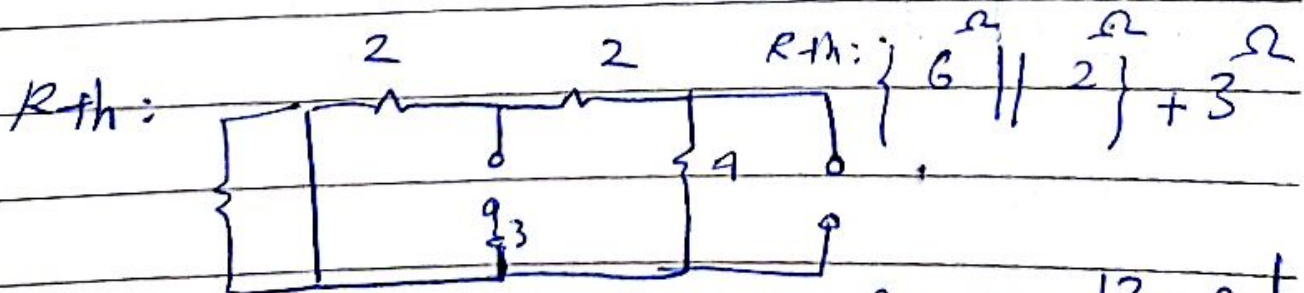
$$V_{th} = \frac{28}{4} = \frac{14}{2} \text{ Volt}$$




$$R_{th} = \frac{12}{3} + 3 = \frac{4}{3} + 3 = \frac{13}{3} \Omega$$

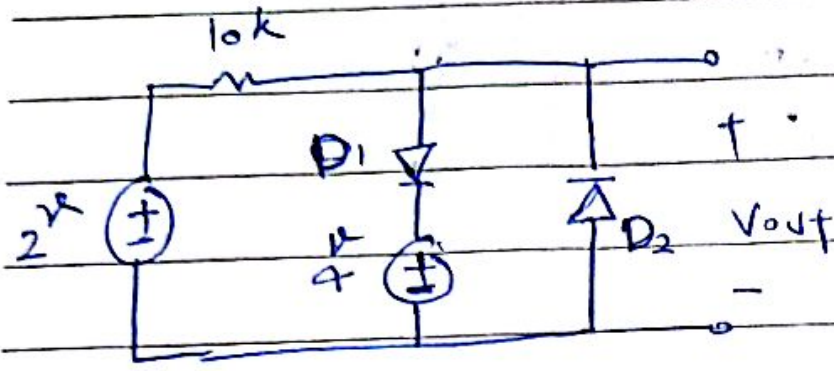6. Calculate  $V_{out}$   
(assume diodes are ideal)




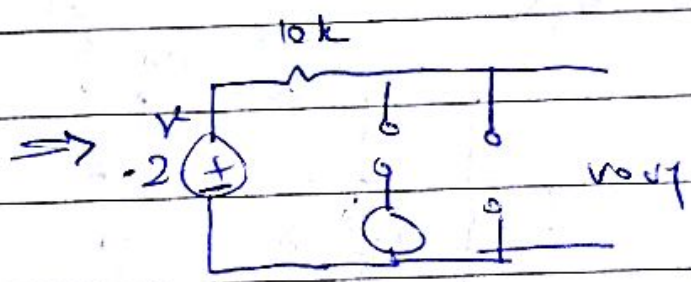Sol (6)  $D_1 : \text{off}$   
 $D_2 : \text{off}$



$V_{out} = 2 \text{ Volt}$

7. Calculate  $V_{out}$ ?

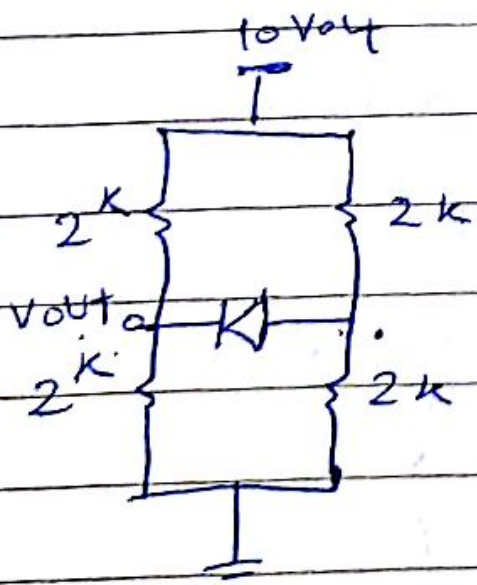


Sol (7)

$$V_{out} = \frac{10 \text{ Volt} \times 2k}{2k + 2k} = 5 \text{ Volt}$$




8. calculate  $V_{out}$ ? "Diodes ideal"

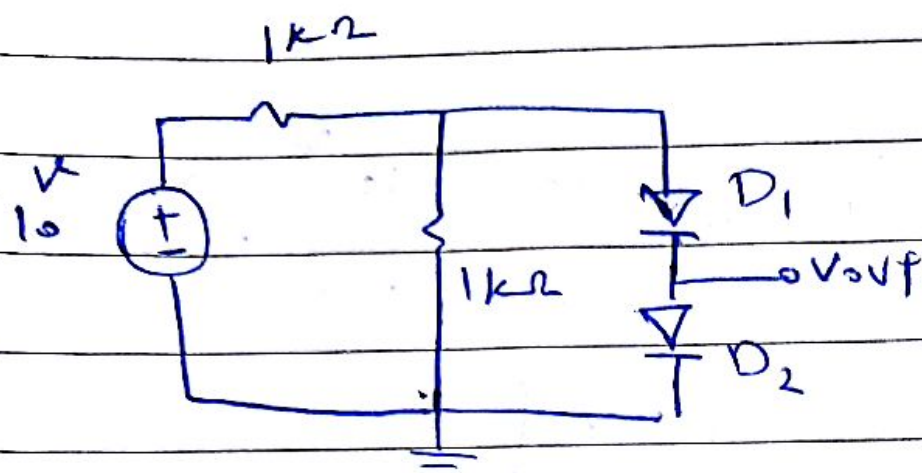

Sol (8)  $D_1$  &  $D_2$  : on  $\Rightarrow V_{out} = 0$

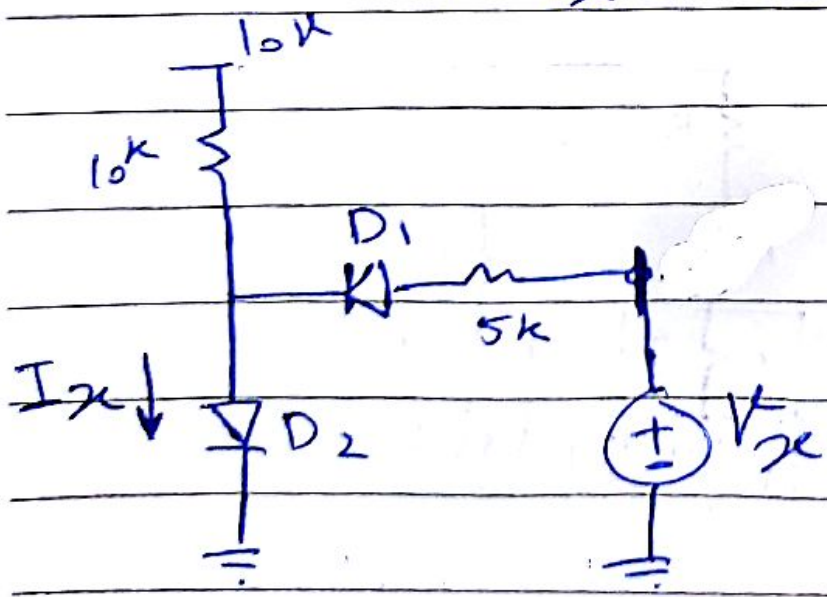9. calculate  $I_x$ ?  
if  $V_x = -15$  Volt



Sol (9)  $\left. \begin{array}{l} D_1 : \text{off} \\ D_2 : \text{on} \end{array} \right\} \Rightarrow I_x = \frac{10}{10k} = 1\text{mA}$


10. in question 9 calculate  $I_{x2}$  while

$$V_{x2} = +15 \text{ Volt ?}$$


Sol (10)  $\left. \begin{array}{l} D_1 : \text{on} \\ D_2 : \text{on} \end{array} \right\} I_{x2} = \frac{10}{10k} + \frac{15}{5k} = 1 + 3 \text{ mA} = 4 \text{ mA}$

11. Calculate  $R_{th}$ ? (Extra bonus!!)

all  $R = 1 \Omega$

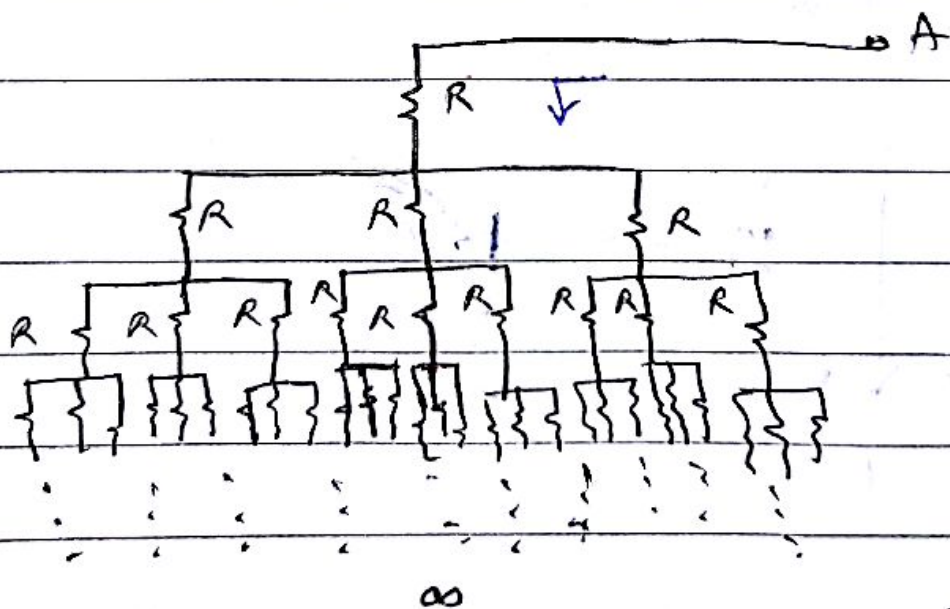

Sol (11)

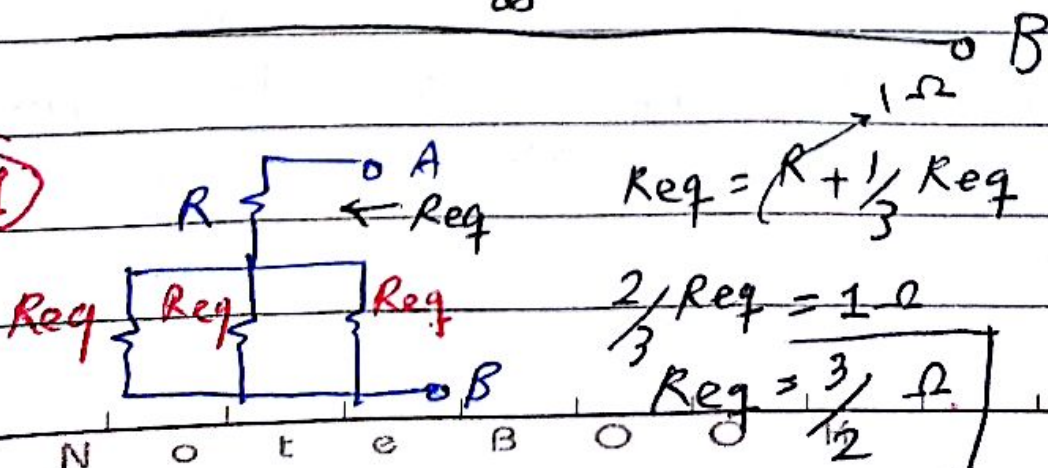

$$R_{eq} = R + \frac{1}{3} R_{eq}$$

$$\frac{2}{3} R_{eq} = 1 \Omega$$

$$R_{eq} = \frac{3}{2} \Omega$$