
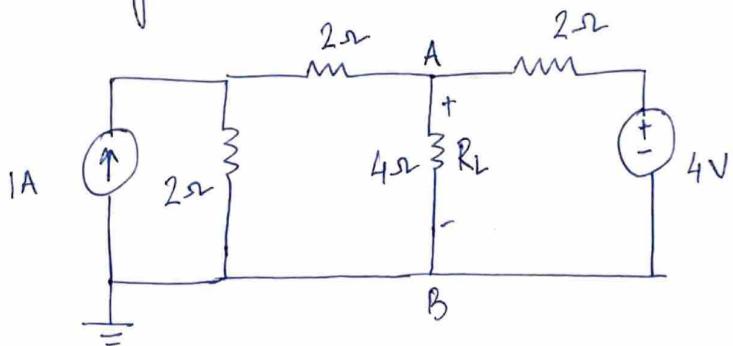


▷ The given circuit:

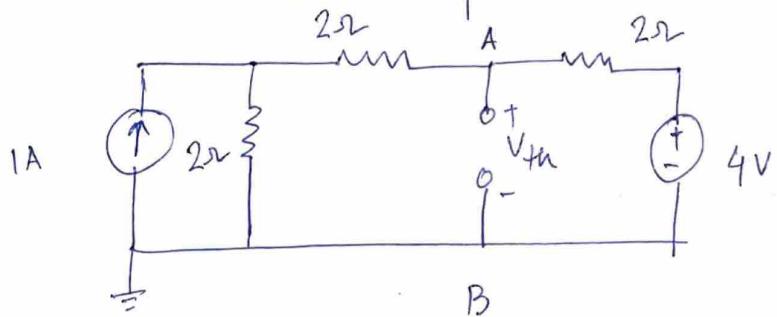


To calculate the Thevenin voltage, R_L is removed and the voltage V_{AB} is calculated.

The circuit is modified as:




The Thevenin voltage can be calculated using different methods (Source transformation, KCL, KVL etc)

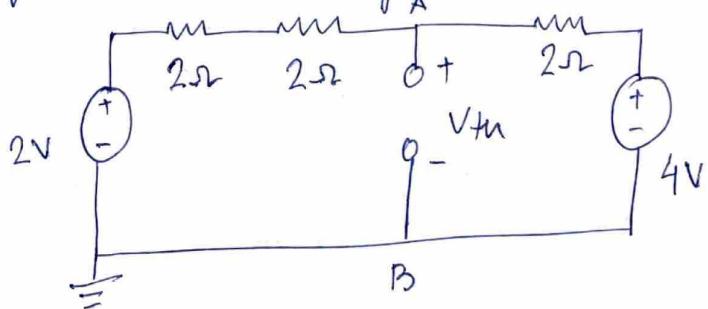Converting the current source and the shunt resistor to an equivalent voltage source we get,




$$\begin{aligned} V_{th} &= 4V - \frac{(4-2)V}{6\Omega} \times 2\Omega \\ &= \frac{10V}{3} \end{aligned}$$

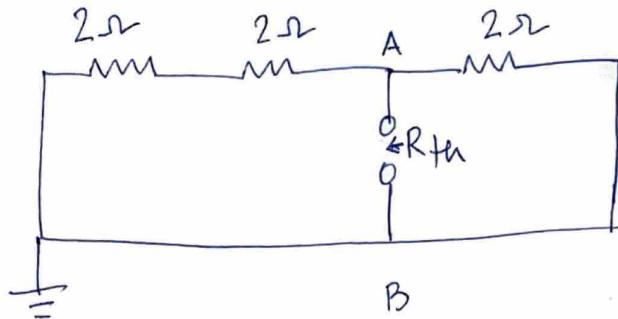To calculate the Thevenin resistance, voltage sources are replaced by short circuits,



$$R_{th} = R_{AB} = 4\Omega \parallel 2\Omega = \frac{4}{3}\Omega$$

Hence the simplified Thevenin circuit,

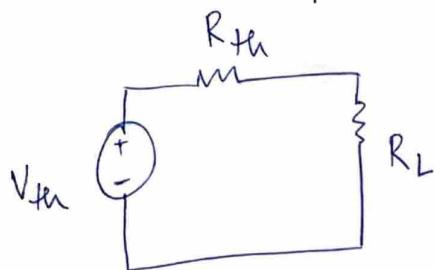


$$V_{th} = \frac{10}{3} V, R_{th} = \frac{4}{3} \Omega, R_L = 4\Omega$$


$$\text{Hence } V_L = \frac{V_{th}}{R_{th} + R_L} \times R_L = \left(\frac{\frac{10}{3} V}{\frac{4}{3} \Omega + 4\Omega} \right) \times 4\Omega$$

$$\Rightarrow V_L = 2.5 V$$

2) The given circuit,

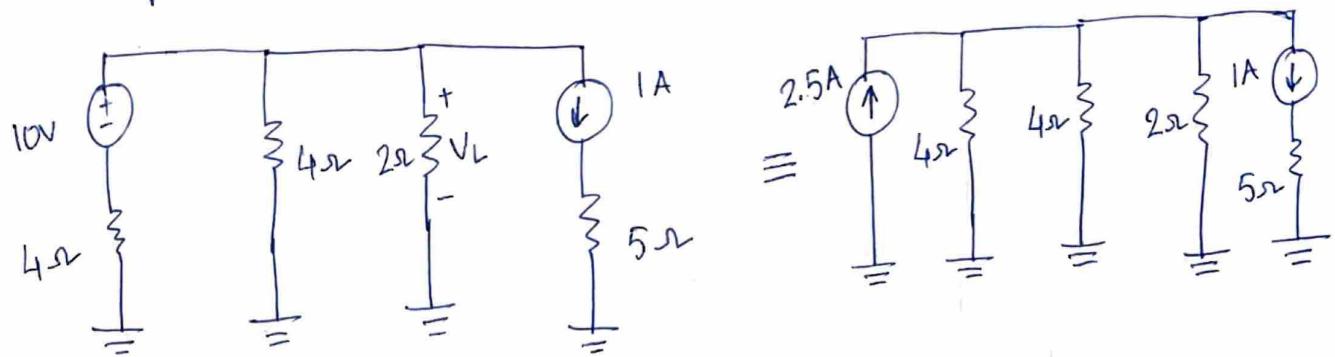


Thevenin voltage calculation:

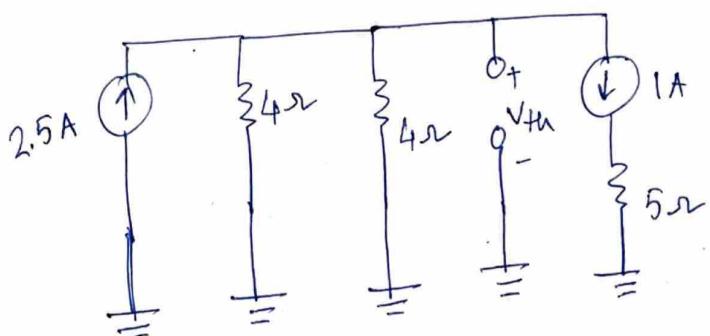


$$V_{th} = (2.5A - 1A)(4\Omega \parallel 4\Omega) = (1.5A)(2\Omega) = 3V$$

Thevenin resistor calculation:

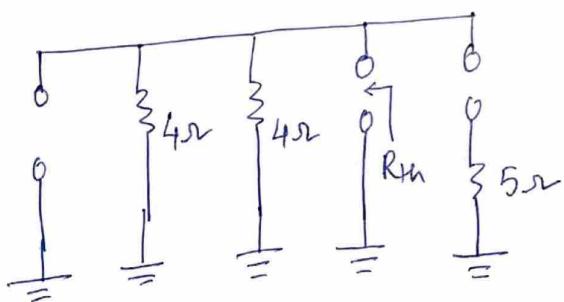

$$R_{th} = (4\Omega \parallel 4\Omega) = 2\Omega$$

The final simplified circuit:

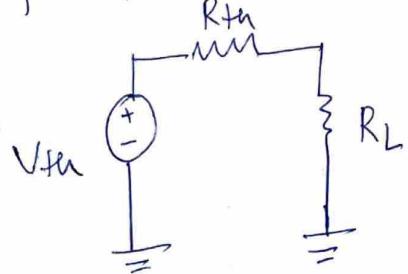


$$V_{th} = 3V, R_{th} = 2\Omega, R_L = 2\Omega$$


$$\therefore V_L = \left(\frac{V_{th}}{R_{th} + R_L} \right) R_L = 1.5V$$

$$\Rightarrow V_L = 1.5V$$

3) The given circuit,

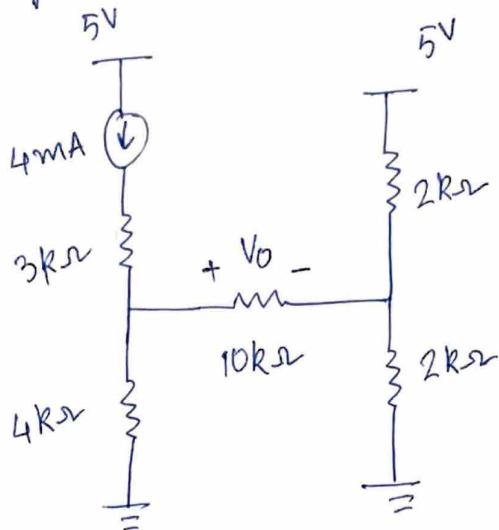

Thevenin circuit,

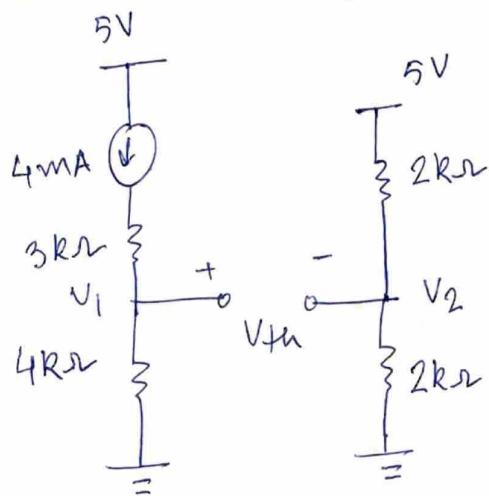

$$V_{th} = V_1 - V_2$$

where,

$$V_1 = (4\text{mA})(4\text{k}\Omega)$$

$$\Rightarrow V_1 = 16\text{V}$$

$$V_2 = \frac{5\text{V}}{(2\text{k}\Omega + 2\text{k}\Omega)} \times 2\text{k}\Omega$$


$$= 2.5\text{V}$$

$$\Rightarrow V_{th} = 16\text{V} - 2.5\text{V} = 13.5\text{V}$$

To calculate Thevenin resistor, voltage sources are short circuited and current sources are open circuited.

$$R_{th} = (4\text{k}\Omega) + (2\text{k}\Omega \parallel 2\text{k}\Omega) = 5\text{k}\Omega$$


Simplified Thevenin circuit,

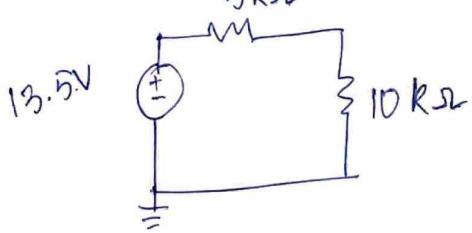


$$V_0 = \frac{13.5\text{V}}{(5\text{k}\Omega + 10\text{k}\Omega)} \times 10\text{k}\Omega = 9\text{V}$$

$$\boxed{V_0 = 9\text{V}}$$

4) The given circuit,

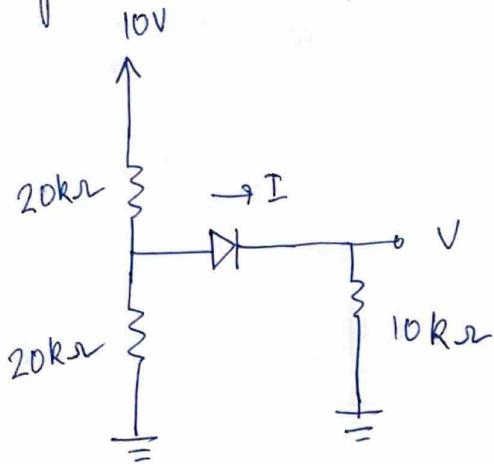

The simplified circuit,

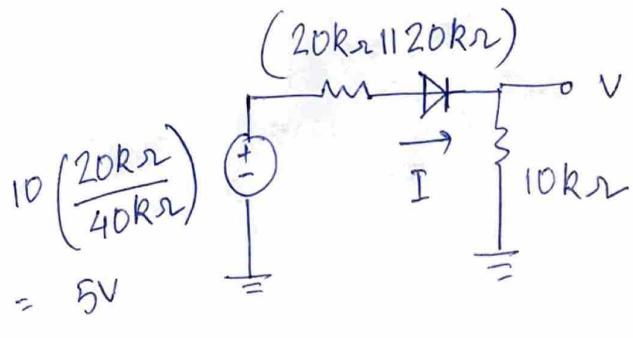


$$I = \frac{5V}{(20k\Omega || 20k\Omega) + 10k\Omega}$$

$$\Rightarrow I = \frac{5V}{10k\Omega \times 2}$$


$$\Rightarrow I = \frac{0.25}{= 0.25 \text{ mA}}$$

$$V = I \times 10 \text{ k}\Omega = 2.5 \text{ V}$$


5) The given circuit,

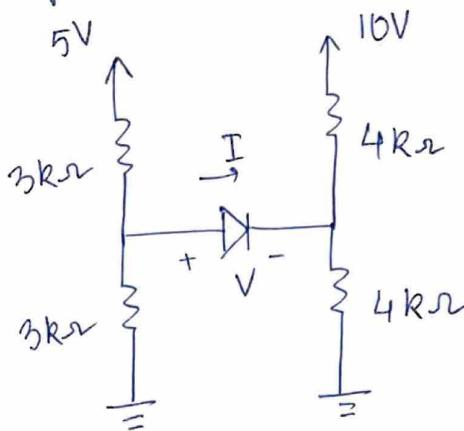

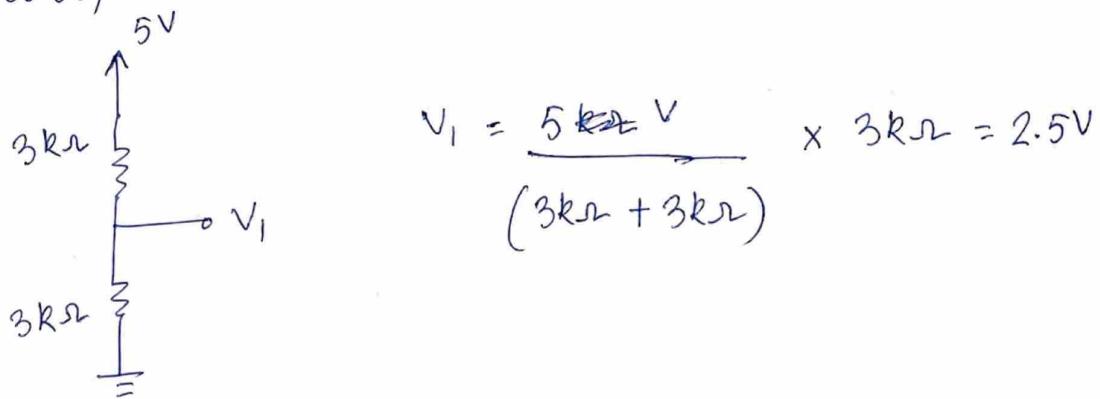
Applying Thevenin's theorem to the left hand side of the circuit,



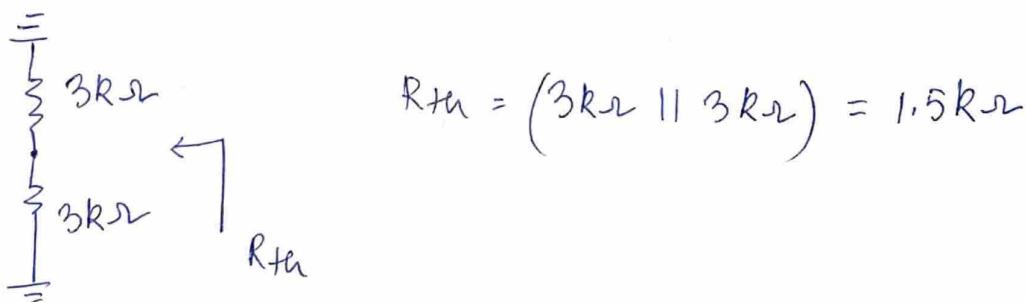
For calculating R_{Th} for the left hand side of the circuit,



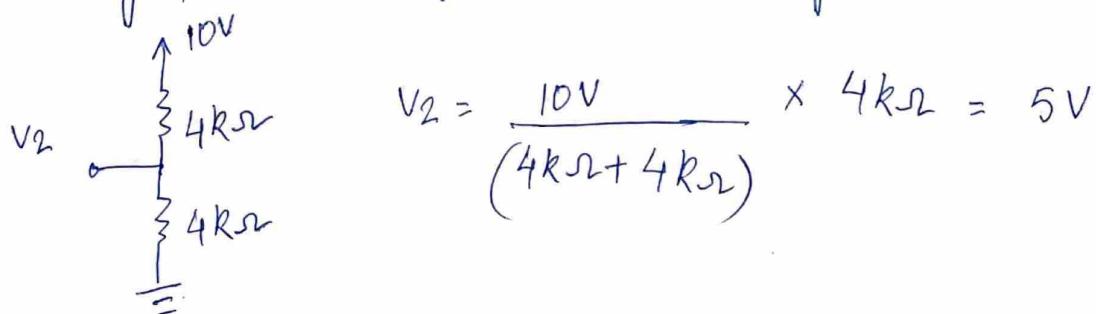Similarly for the right hand side of the circuit,




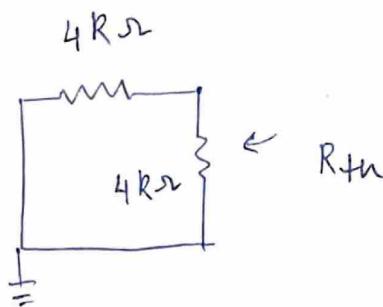For calculating R_{th} for the right hand side of the circuit,




$$R_{th} = (4\text{ k}\Omega \parallel 4\text{ k}\Omega) \\ = 2\text{ k}\Omega$$

Hence the complete simplified circuit,

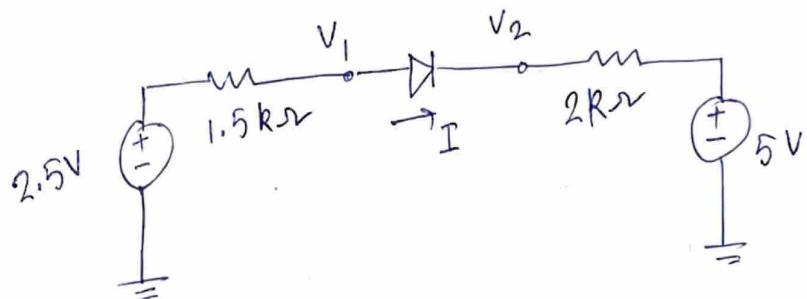

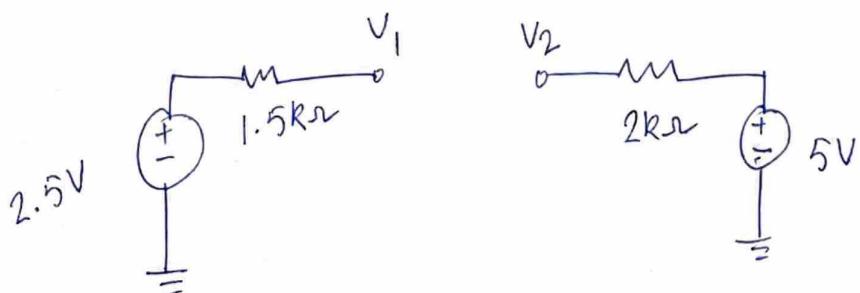Since $V_1 < V_2$, the diode is reverse biased. $I = 0$
Thus the circuit reduces to,




Nodes 1 and 2 are electrically isolated.

$$\therefore V = V_1 - V_2 = 2.5\text{ V} - 5\text{ V} = -2.5\text{ V}$$

2) Diode is reverse biased
 $V = -2.5\text{ V}$
 $I = 0$

6) The given circuit,

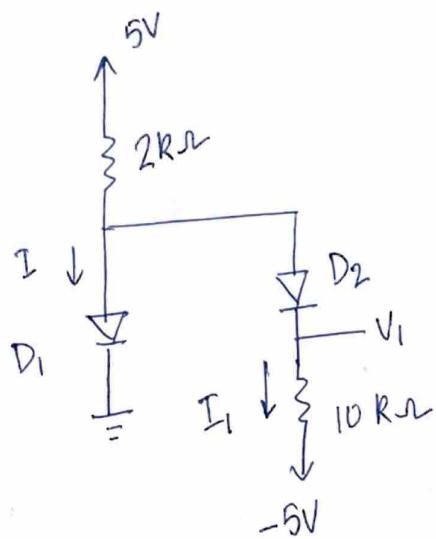

Assuming both the diodes are forward biased.

$$\therefore V_1 = 0V$$

$$I_1 = \frac{V_1 - (-5V)}{10k\Omega} = \frac{5V}{10k\Omega} = 0.5 \text{ mA}$$

With V₁ = 0V, the initial assumption is also satisfied.

Current through the diode D₁,


$$I = \frac{5V}{2k\Omega} - I_1 = 2 \text{ mA}$$

Hence,

$$V_1 = 0V$$

$$I_1 = 0.5 \text{ mA}$$

7) The quiescent circuit,

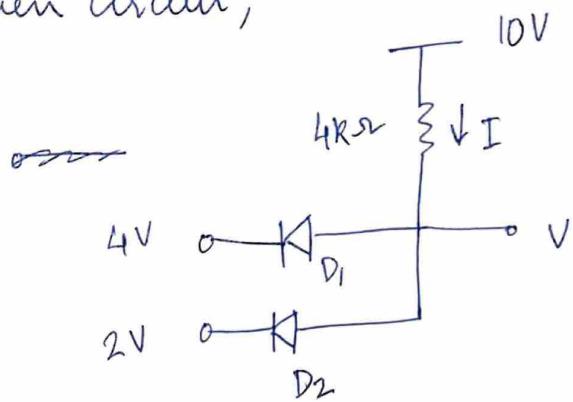

Since the value of the voltage V is unknown, we cannot estimate the operating condition of D_1 and D_2 intuitively.

There can be four possible cases, depending on the biasing condition of each diode.

Case 1: D_1 is off, D_2 is off

\Rightarrow both the paths are open circuit, so not a feasible configuration.

Case 2: D_1 is on, D_2 is on

\Rightarrow The voltage V has to simultaneously be equal to 4V and 2V. This is also not a feasible option.

Case 3: D_1 is on, D_2 is off

$\Rightarrow V = 4V \Rightarrow D_2$ is on.

Hence there is a contradiction to the assumption

\Rightarrow Not a feasible option

Case 4: D_1 is off, D_2 is on

$\Rightarrow V = 2V \Rightarrow D_2$ is on $\Rightarrow D_1$ is off \rightarrow Acceptable configuration

Hence,


D_1 is off (reverse biased)

D_2 is on (forward biased)

$$V = 2V$$

$$I = \frac{10V - 2V}{4k\Omega} = 2 \text{ mA}$$

8) The given circuit,

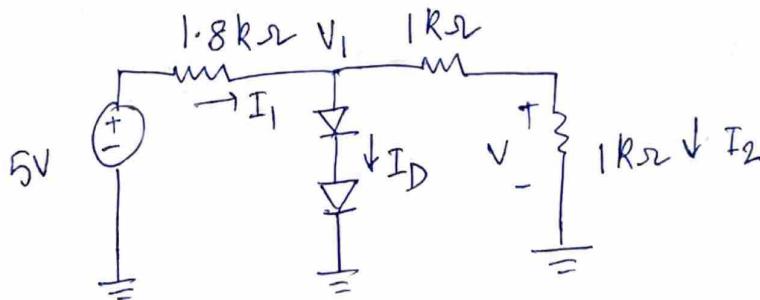

Assuming both the diodes are forward biased.

$$V_1 = 2 \times 0.7V = 1.4V$$

$$I_1 = I_D + I_2 \quad (\text{KCL})$$


$$I_1 = \frac{5V - V_1}{1.8 \text{ k}\Omega} = \frac{5V - 1.4V}{1.8 \text{ k}\Omega} = 2 \text{ mA}$$

$$I_2 = \frac{V_1}{2 \text{ k}\Omega} = \frac{1.4V}{2 \text{ k}\Omega} = 0.7 \text{ mA}$$

Hence $I_D = I_1 - I_2 = 2 \text{ mA} - 0.7 \text{ mA} = 1.3 \text{ mA}$

$$V = I_2 \times 1 \text{ k}\Omega = (0.7 \text{ mA})(1 \text{ k}\Omega) = 0.7V$$

Since $V_1 = 1.4V$, the initial approximation is satisfied.

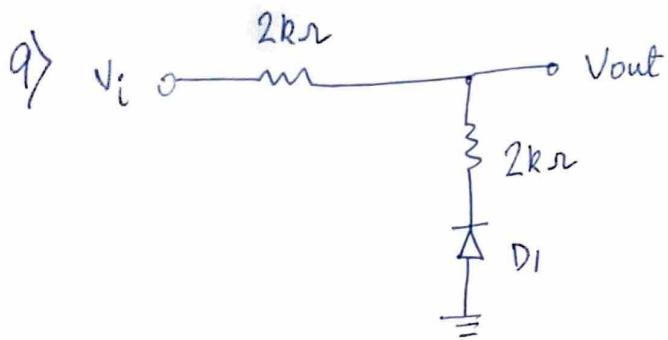


Region 1: $V_i > 0 \Rightarrow D_1$ is reverse biased.


$\Rightarrow V_{out}$ follows V_i

Region 2: $V_i < 0 \Rightarrow D_1$ is forward biased.
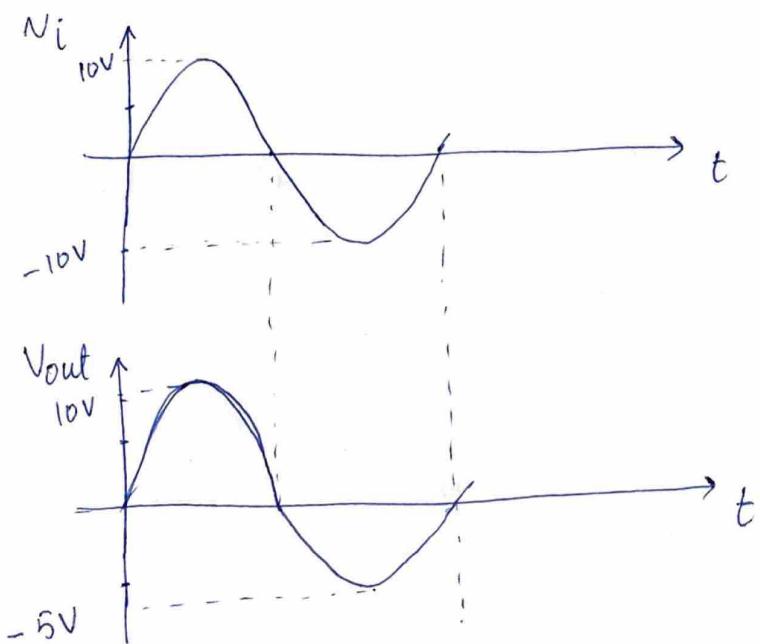
$$\Rightarrow V_{out} = \frac{V_i}{(2k\Omega + 2k\Omega)} \times 2k\Omega = \frac{V_i}{2}$$



10) The given circuit,

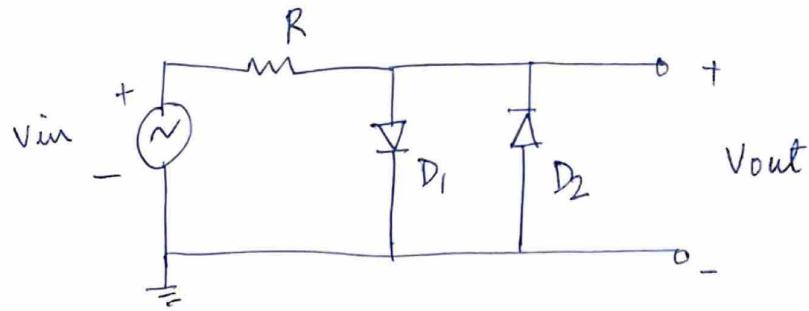


Region 1: $V_{in} > 0.7V \Rightarrow D_1$ is forward biased. $\Rightarrow V_{out} = 0.7V$

Region 2: $V_{in} < -0.7V \Rightarrow D_2$ is forward biased. $\Rightarrow V_{out} = -0.7V$


Region 3: $-0.7V < V_{in} < 0.7V \Rightarrow V_{out}$ follows V_{in}
 $\Rightarrow D_1$ and D_2 are reverse biased.

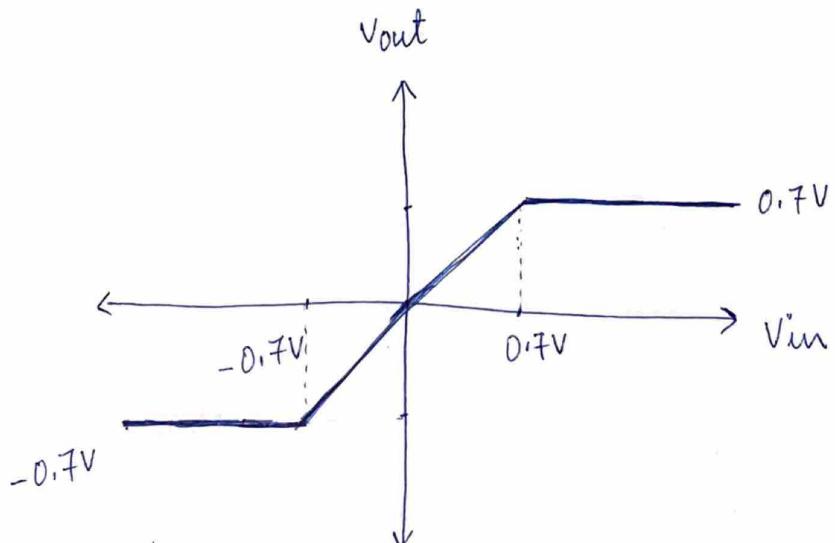Hence, the input output characteristics is given by,



limiting Circuits

11) The quen circuit,

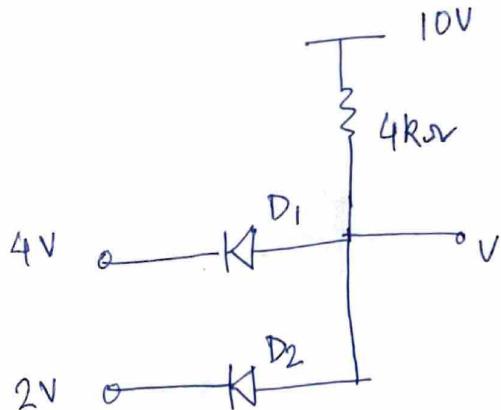


For real diodes, voltage drop across the diode in forward biased = 0.7V

Referring to the solution for problem 7, we know that D_1 is reverse biased and D_2 is forward biased.

$$V = 2V + 0.7V = 2.7V$$

$$I = \frac{10V - 2.7V}{4k\Omega} = 1.825 \text{ mA}$$

12) The quen circuit,

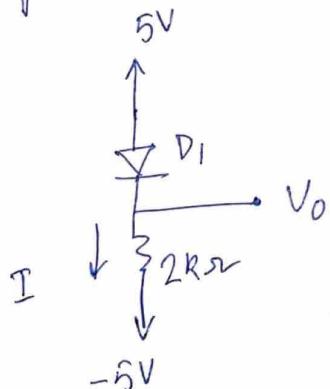

Assuming D_1 is forward biased,

$$V_0 = 5V - 0.7V = 4.3V$$

$$I = \frac{4.3V - (-5V)}{2k\Omega} = 4.65 \text{ mA}$$