

1) Given:

$$I_E = 3 \text{ mA}$$

$$\beta = 50$$

NPN Transistor

$$I_E = I_C \left( \frac{\beta + 1}{\beta} \right) \Rightarrow I_C = \frac{I_E \beta}{(\beta + 1)} = 2.94 \text{ mA}$$

$$I_B = \frac{I_E}{(1 + \beta)} = 0.05882 \text{ mA} = 58.82 \text{ } \mu\text{A}$$

Hence,  $I_C = 2.94 \text{ mA}$ ,  $I_B = 58.82 \text{ } \mu\text{A}$

2) Given:

$$I_E = 1 \text{ mA}$$


$$\beta = 10$$

$$I_B = \frac{I_E}{(1 + \beta)} = 0.09 \text{ mA}$$

$$\alpha = \frac{\beta}{1 + \beta} = 0.9$$

Hence,  $I_B = 0.09 \text{ mA}$ ,  $\alpha = 0.9$

3) The given circuit,

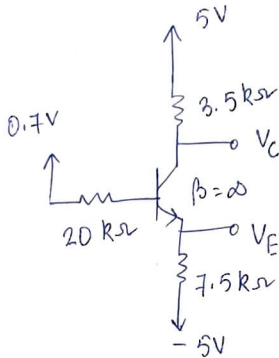

$$\beta = \infty \Rightarrow I_B = 0$$

$$I_C = I_E$$

$$\text{Given } V_{BE} = 0.7V \Rightarrow V_E = V_B - 0.7V = \cancel{0.7V} \text{ (} V_B = 0.7V \text{)} \\ = 0V$$


$$I_E = \frac{V_E + 5V}{7.5k\Omega} = 0.67 \text{ mA}$$

$$\therefore I_C = 0.67 \text{ mA} = \frac{5V - V_C}{3.5k\Omega}$$

$$\Rightarrow V_C = 2.66V$$

$$\text{Thus, } \boxed{V_E = 0V}, \quad \boxed{V_C = 2.66V}$$

4) The quiescent circuit,

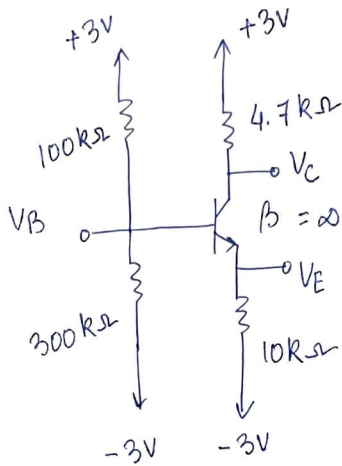

For the node at the base of the transistor,

$$\frac{3V - V_B}{100k\Omega} = \frac{V_B + 3V}{300k\Omega} \quad (\text{KCL})$$

$$\Rightarrow V_B = 1.5V$$

Quiescent  $V_{BE} = 0.7V \Rightarrow V_E = 0.8V$

$$\beta = \infty \Rightarrow I_C = I_E \quad (I_B = 0)$$


$$\text{Since, } I_E = \frac{V_E + 3V}{10k\Omega} = 0.38 \text{ mA} = I_C = \frac{3V - V_C}{4.7k\Omega}$$

$$\Rightarrow 0.38 \text{ mA} = \frac{3V - V_C}{4.7k\Omega}$$

$$\Rightarrow V_C = 1.214V$$

Hence,  $V_B = 1.5V$ ,  $V_E = 0.8V$ ,  $V_C = 1.214V$

5) The quiescent circuit,

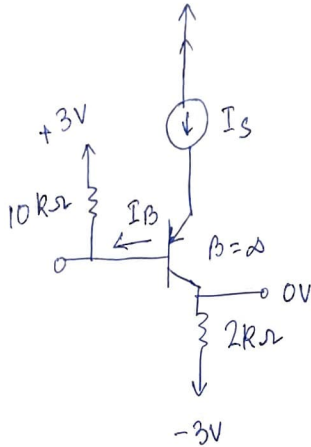


Quiescent,  $\beta = \infty \Rightarrow I_C = I_E$ ,  $I_B = 0A$

$$I_C = \frac{0V + 3V}{2k\Omega} = 1.5 \text{ mA} = I_E$$

Since  $I_B = 0A$ ,  $V_B = 3V$  since there is no potential drop across the  $10k\Omega$  resistor.

6) The quiescent circuit,

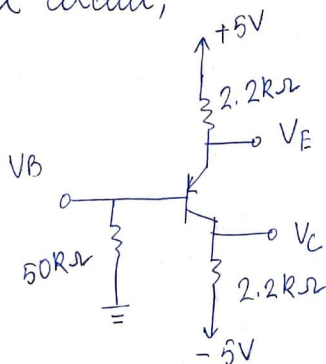

Quiescent:  $|V_{BE}| = 0.7V$ ,  $V_B = 0.8V$

$$\Rightarrow V_E = 0.7V + 0.8V = 1.5V$$

6) contd...

$$\text{Base current, } I_B = \frac{V_B}{50k\Omega} = \frac{0.8V}{50k\Omega} = 16 \mu A$$

$$\text{Emitter current, } I_E = \frac{5V - V_E}{2.2k\Omega} = 1.59 \text{ mA}$$

$$\text{We know, } I_E = I_B + I_C \Rightarrow I_C = 1.574 \text{ mA}$$

$$V_C = I_C \times 2.2k\Omega - 5V = -1.54V$$

$$\text{Common emitter current gain, } \beta = \frac{I_C}{I_B} \approx 98$$


$$\text{Common base current gain } \alpha = \frac{\beta}{1+\beta} \approx 0.99$$

The final answers:

$$V_E = 1.5V, \quad V_C = -1.54V, \quad I_B = 16 \mu A, \quad I_C = 1.574 \text{ mA}$$

$$I_E = 1.59 \text{ mA}, \quad \beta \approx 98, \quad \alpha \approx 0.99$$

7) The quiescent circuit,

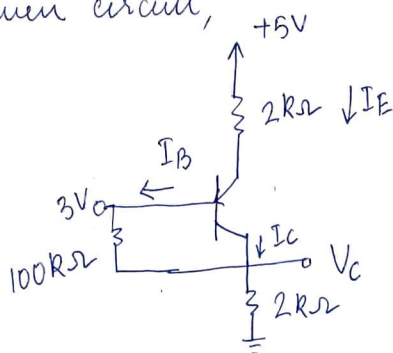

$$|V_{BE}| = 0.7V$$

We know,  $I_E = I_B + I_C \dots (1)$

and  $I_E = \frac{V_C}{2k\Omega} \dots (2)$

$V_B = 3V, |V_{BE}| = 0.7V$

$\Rightarrow V_E = 3.7V \dots (3)$

$\therefore I_E = \frac{5V - V_E}{2k\Omega} = 0.65 \text{ mA} \dots (4)$

From eqn(s) (1) to (4),

$$I_E = 0.65 \text{ mA} = \frac{V_C}{2k\Omega}$$

$$\Rightarrow V_C = 1.3V$$

$$I_B = \frac{3V - V_C}{100k\Omega} = \frac{3V - 1.3V}{100k\Omega} = 17 \mu\text{A}$$

$$\beta = \frac{I_C}{I_B} = \frac{I_E}{I_B} - 1 \approx 38$$

$$\alpha = \frac{\beta}{1 + \beta} \approx 0.97$$

The final answers:


$$I_B = 17 \mu\text{A}$$

$$V_C = 1.3V$$

$$\beta \approx 38$$

$$\alpha \approx 0.97$$

8) The quiescent circuit,

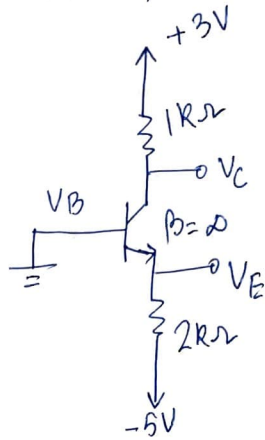

$$\beta = \infty \Rightarrow I_B = 0, \quad I_C = I_E$$

For the quiescent circuit,  $V_B = 0V$

$$V_{BE} = 0.7V \Rightarrow V_E = -0.7V$$

$$\therefore I_E = \frac{V_E + 5V}{2k\Omega} = 2.15 \text{ mA} = I_C$$

$$I_C = \frac{3V - V_C}{1k\Omega} \Rightarrow V_C = 0.85V$$


Hence,  $V_E = -0.7V$

$$V_B = 0V$$

$$V_C = 0.85V$$


→ Active region.

9) The given circuit,

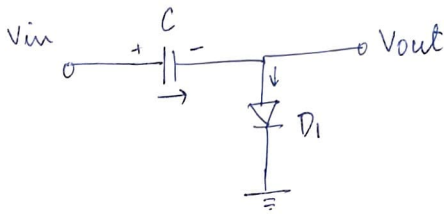

$V_{out} = V_{in} - V_c$   
 $V_{in} < 0 \Rightarrow D_1$  is off,  
~~the~~ Capacitor gets charged to the negative value of ~~the~~  $(-2V) - 3V = -5V$

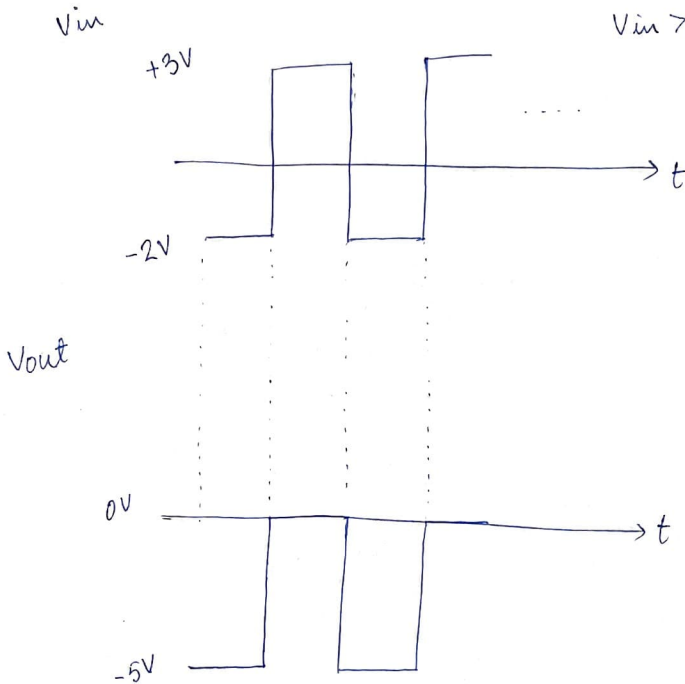$V_{in} > 0 \Rightarrow D_1$  is on,  
 $V_{out} = 0$



10) Case 1:  $V_E < V_B$   $\Rightarrow$  EBJ is forward biased } Active region  
 $V_C < V_B$   $\Rightarrow$  CBJ is reverse biased }

Case 2:  $V_E > V_B$   $\Rightarrow$  Active region  
 $V_C < V_B$

Case 3:  $V_E > V_B$   $\Rightarrow$  Saturation region (EBJ is fwd biased)  
 $V_C > V_B$  (CBJ biased)