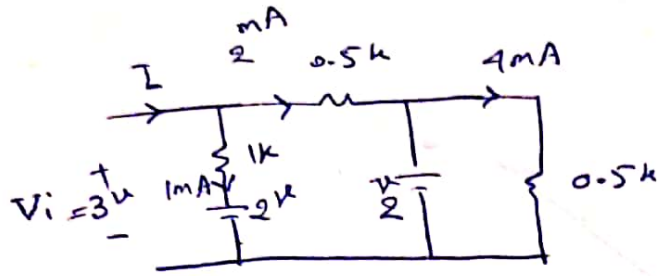




①

D_1 & D_2 : on



$$I = \frac{3-2}{0.5k\Omega} + \frac{3-2}{1k\Omega} = 2\text{mA} + 1\text{mA} = 3\text{mA}$$

②

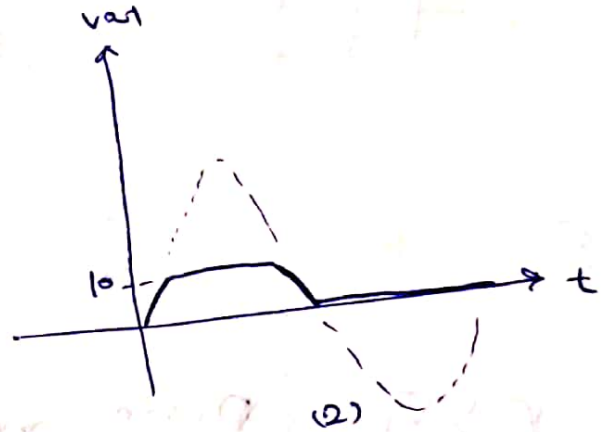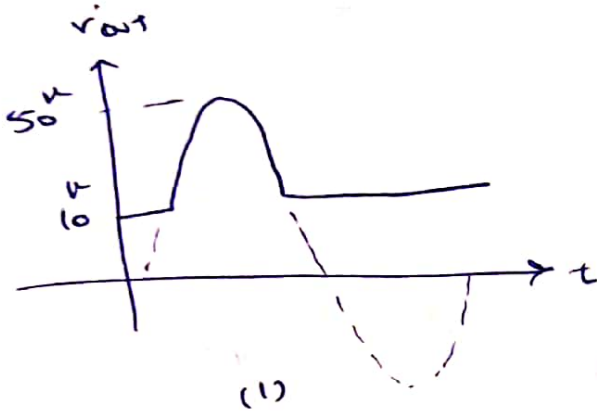

$v_i < 0$ D_1 off D_2 on

$0 < v_i < 10$ D_1 off D_2 on


$v_i > 10$ D_2 off D_1 on

$v_i < 10$ D_1, D_2 off


$0 \leq v_i \leq 20$ $\begin{cases} D_1 \text{ on} \\ D_2 \text{ off} \end{cases}$

$v_i > 20$ $\begin{cases} D_1 \text{ on} \\ D_2 \text{ on} \end{cases}$

③

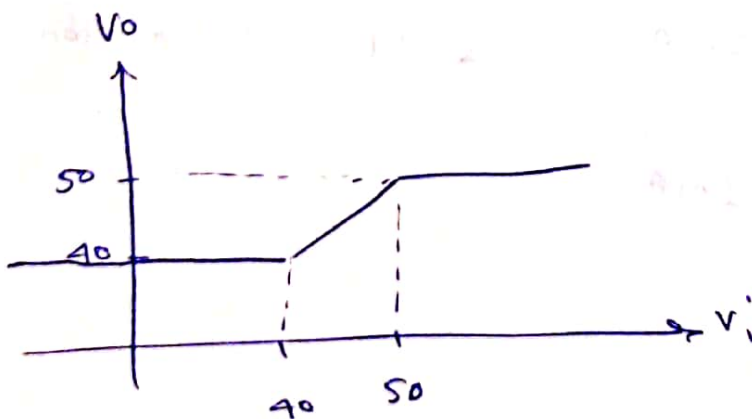

4

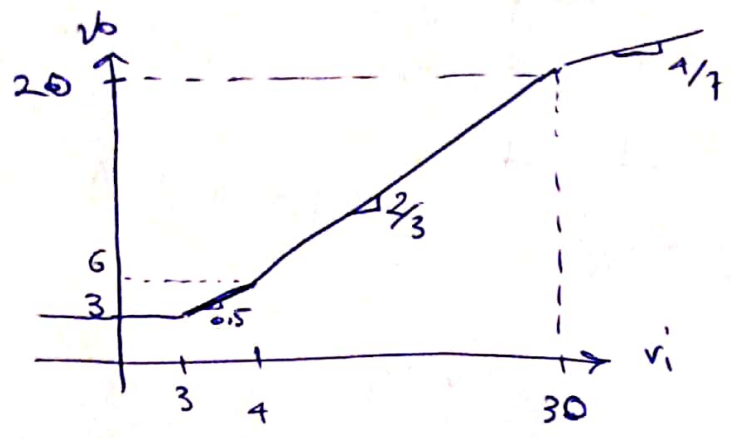


5

$$v_i > V_1 \quad \left\{ \begin{array}{l} D_1: \text{on} \\ D_2: \text{off} \end{array} \right. \rightarrow v_o = V_1$$

$$-V_2 < v_i < V_1 \quad \left\{ \begin{array}{l} D_1: \text{off} \\ D_2: \text{off} \end{array} \right. \rightarrow v_o = v_i$$
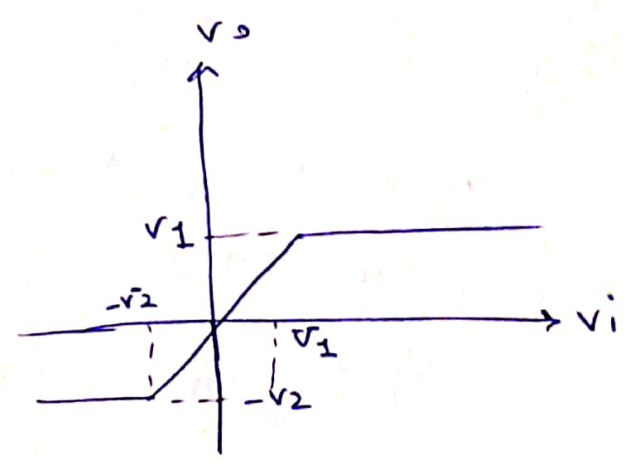
$$v_i < -V_2 \quad \left\{ \begin{array}{l} D_1: \text{off} \\ D_2: \text{on} \end{array} \right. \rightarrow v_o = -V_2$$



6

$$i_{R_1} = \frac{3-1}{1k\Omega} = 2mA$$

$$i_{R_2} = \frac{3-2}{1k\Omega} = 1mA$$

$$i_{R_3} = 0$$

* All diodes are on.

7

D_1 : off


D_2 : on

$$\text{KCL) } \frac{V_0 - 2}{2k} + \frac{V_0 - 5}{2k} = 0$$

$$V_0 - 2 + V_0 - 5 = 0$$

$$2V_0 = 7 \rightarrow V_0 = \frac{7}{2} = 3.5 \text{ V}$$

8

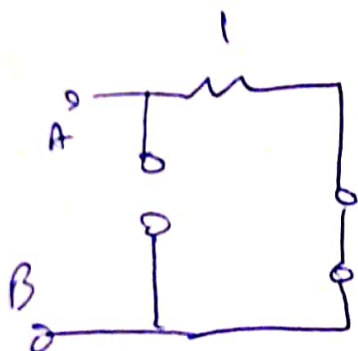

$$R_{th} = 1 \Omega$$

9

D_5 : off

D_1 : off

D_2 : on

$$\Rightarrow V_{out} = 0$$

D_4 : on

D_3 : It's not important to consider "off" or "on"

10

$$I = \frac{0 - (-10)}{10k} = \frac{10 \text{ V}}{10k} = 1 \text{ mA}$$