

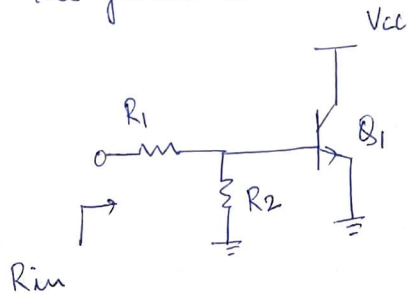


Q1) The given circuit:

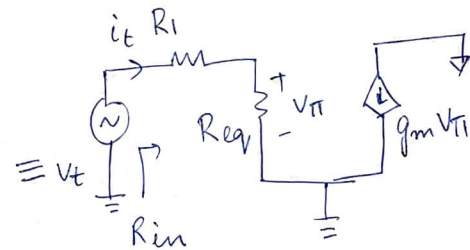

The small signal model will be given by,

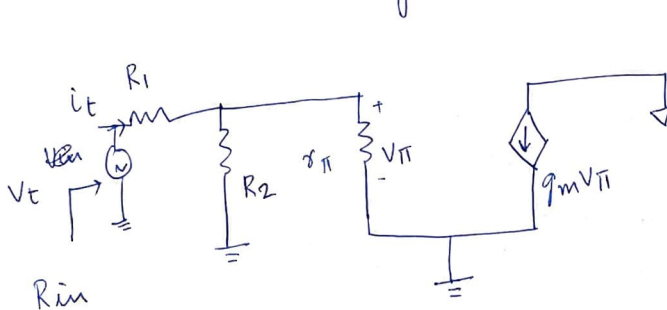


$$R_{in} = \frac{V_t}{i_t} = R_1 + R_{eq}$$

$$\text{where } R_{eq} = (r_{\pi} \parallel R_2)$$


$$\Rightarrow \boxed{R_{in} = R_1 + (R_2 \parallel r_{\pi})}$$

Q2) The quiescent circuit,

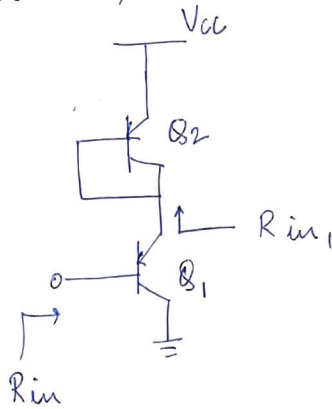


Looking up from the emitter of Q_1 , we have an equivalent impedance $R_{in1} = \frac{1}{g_{m2}} \parallel r_{\pi 2}$

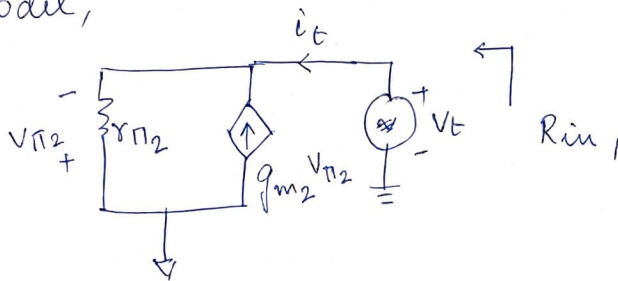To calculate R_{in1} , we can use the following small signal model,




$$R_{in1} = \frac{V_t}{i_t} = \frac{r_{\pi 2}}{1 + g_{m2} r_{\pi 2}} = \left(\frac{1}{g_{m2}} \parallel r_{\pi 2} \right)$$

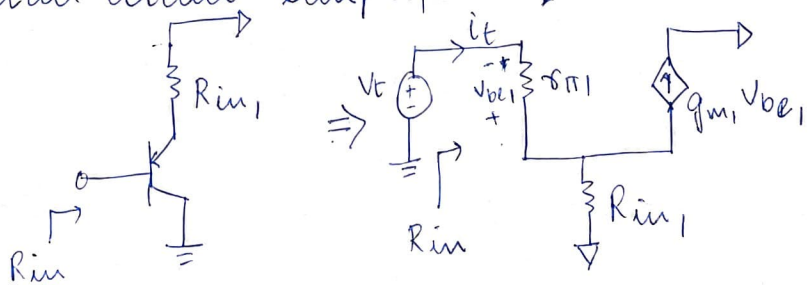Hence the overall circuit simplifies to the small signal model



Q2) The simplified small signal model,

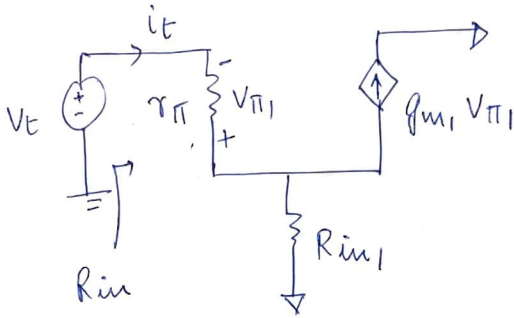


Thus, $\frac{V_t}{i_t} = R_{in}$, $v_{\pi_1} = -r_{\pi_1} i_t$

$$\begin{aligned} V_t &= r_{\pi_1} i_t + i_{R_{in1}} R_{in1} \\ &= r_{\pi_1} i_t + (i_t + g_{m1} i_t r_{\pi_1}) R_{in1} \\ &= i_t \left\{ r_{\pi_1} + (1 + \beta_1) R_{in1} \right\} \end{aligned}$$

$$\Rightarrow R_{in} = \frac{V_t}{i_t} = r_{\pi_1} + (1 + \beta_1) R_{in1}$$

$$\Rightarrow R_{in} = \frac{V_t}{i_t} = r_{\pi_1} + (1 + \beta_1) \left(\frac{1}{g_{m2}} \parallel r_{\pi_2} \right)$$

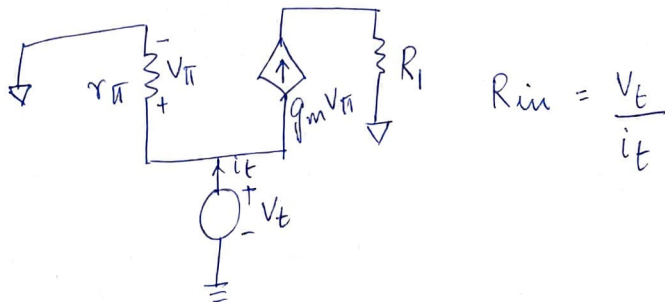Q3) The small signal model to calculate R_{in} ,



$$R_{in} = \frac{V_t}{i_t}$$


Using KCL,

$$i_t = g_m V_{\pi} + \frac{V_{\pi}}{r_{\pi}}$$

$$V_{\pi} = V_t$$


$$\Rightarrow R_{in} = \frac{V_t}{i_t} = \frac{V_{\pi}}{i_t} = \frac{1}{g_m + \frac{1}{r_{\pi}}} = \frac{1}{g_m} \parallel r_{\pi}$$

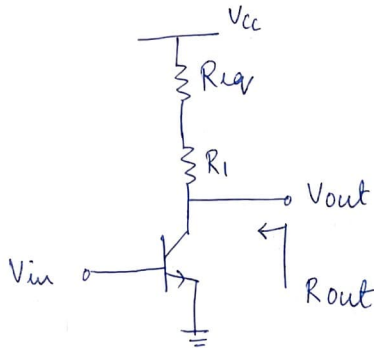Q4) The given circuit can be simplified to,



where $Req = \left(\frac{1}{g_{m2}} \parallel r_{\pi 2} \right)$ (refer to Q2 solution)

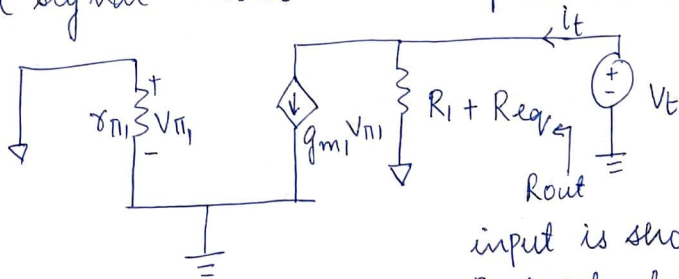
Hence the small signal model can be represented as,



input is shorted for Rout calculation

$$\text{Hence } R_{out} = \frac{V_t}{i_t} = R_1 + Req = R_1 + \left(\frac{1}{g_{m2}} \parallel r_{\pi 2} \right)$$

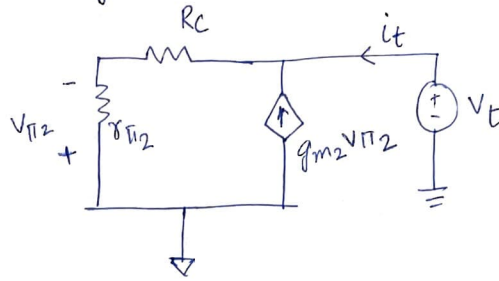Q5) The small signal model to calculate R_{out} ,




$$i_t = -g_{m2} v_{\pi 2} - \frac{v_{\pi 2}}{r_{\pi 2}}$$

$$V_t = -v_{\pi 2}$$

$$\Rightarrow R_{out} = \frac{V_t}{i_t} = \frac{-v_{\pi 2}}{i_t} = \frac{1}{g_{m2} + \frac{1}{r_{\pi 2}}}$$

$$\Rightarrow R_{out} = \frac{1}{g_{m2}} \parallel r_{\pi 2}$$

Q6) The circuit can be simplified to,

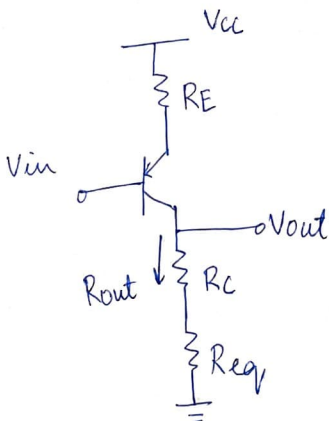

$$\text{where } R_{eq} = \left(\frac{1}{g_{m2}} \parallel r_{\pi 2} \right)$$


as solved in Q2.

Hence, output resistance

$$R_{out} = R_c + R_{eq}$$


$$R_{out} = \left(\frac{1}{g_{m2}} \parallel r_{\pi 2} \right) + R_c$$

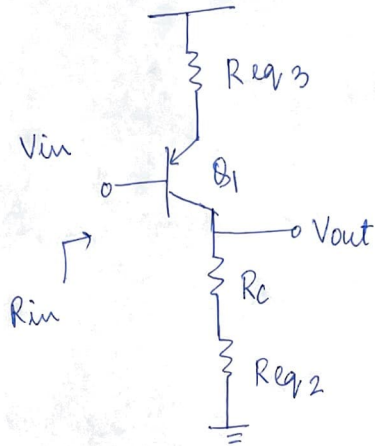Q7) The given circuit can be simplified to,



where $R_{eq2} = \left(\frac{1}{g_{m2}} \parallel r_{\pi 2} \right)$, $R_{eq3} = \left(\frac{1}{g_{m3}} \parallel r_{\pi 3} \right)$

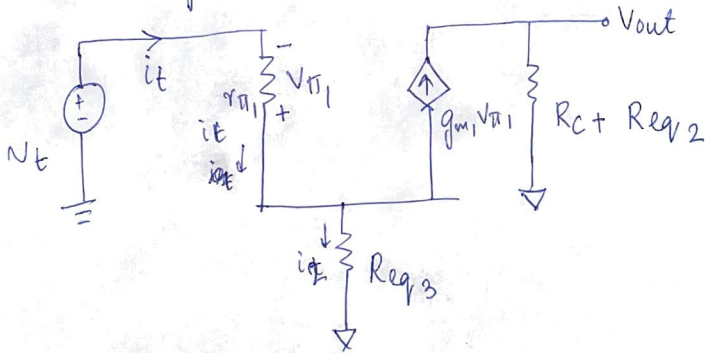The small signal model to calculate R_{in} ,



$$i_e \approx V_t = -V_{\pi} + i_2 R_{eq3} \dots (1)$$

$$V_{\pi} = -r_{\pi 1} i_t$$

$$i_2 = i_t - g_{m1} V_{\pi} = i_t (1 + g_{m1} r_{\pi 1})$$

$$\Rightarrow i_2 = i_t (1 + \beta_1) \dots (2)$$

From eq (1) and eq (2),

$$V_t = -V_{\pi} + i_t (1 + \beta_1) R_{eq3}$$


$$V_t = i_t [r_{\pi 1} + (1 + \beta_1) R_{eq3}]$$

$$Q7) \therefore V_t = i_t [r_{\pi 1} + (1 + \beta_1) R_{eq 3}]$$


$$\Rightarrow R_{in} = \frac{V_t}{i_t} = r_{\pi 1} + (1 + \beta_1) R_{eq 3}$$

$$\Rightarrow R_{in} = r_{\pi 1} + (1 + \beta_1) \left(\frac{1}{g_{m3}} \parallel r_{\pi 3} \right)$$

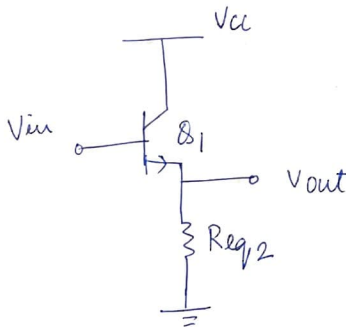Q8) The given circuit can be simplified to,



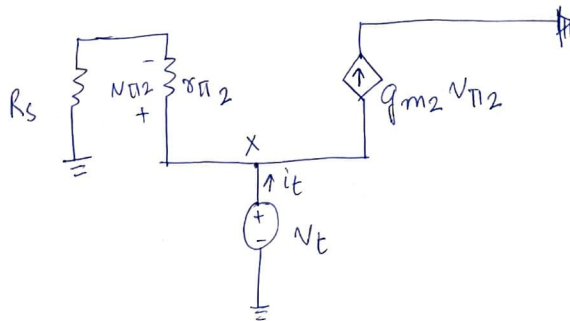$R_{eq 2}$ can be calculated using the small signal model of Q_2 .




$$i_t - g_{m2} V_{\pi 2} = \frac{V_t}{r_{\pi 2} + R_s} \dots \dots (1) \quad \left[\text{KCL at node } X \right]$$

$$V_{\pi 2} = \frac{+V_t}{r_{\pi 2} + R_s} r_{\pi 2} \dots \dots (2)$$

From eq (1) and eq (2)

$$R_{eq2} = \frac{V_E}{i_t} = \frac{r_{\pi2} + R_S}{(1 + \beta_2)}, \quad \beta_2 = g_{m2} r_{\pi2}$$

Thus the overall circuit reduces to,

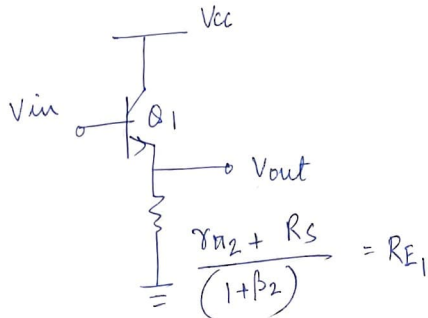

The small signal model to calculate R_{out} , can hence be constructed for the Emitter follower configuration alone. The R_{out} derivation can be observed in the lecture notes, ~~—————~~

$$R_{out} = \frac{r_{\pi1}}{\beta_1 + 1} \parallel R_{E1}$$

$$\Rightarrow R_{out} = \left(\frac{r_{\pi1}}{1 + g_{m1} r_{\pi1}} \right) \parallel \left(\frac{r_{\pi2} + R_S}{1 + \beta_2} \right)$$


$$\Rightarrow R_{out} = \frac{1}{g_{m1}} \parallel r_{\pi1} \parallel \left(\frac{r_{\pi2} + R_S}{1 + \beta_2} \right)$$

Referring to the lecture notes,

$$R_{in} = r_{\pi1} + R_{E1} (\beta_1 + 1)$$


$$\Rightarrow R_{in1} = r_{\pi1} + \left(\frac{r_{\pi2} + R_S}{1 + \beta_2} \right) (\beta_1 + 1)$$

Q9) The simplified circuit,

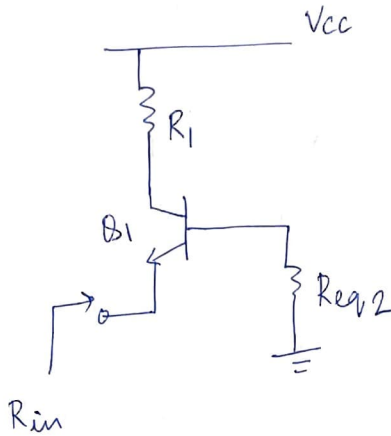

where $R_{eq2} = \left(r_{\pi 2} \parallel \frac{1}{g_{m2}} \right)$ as derived previously.

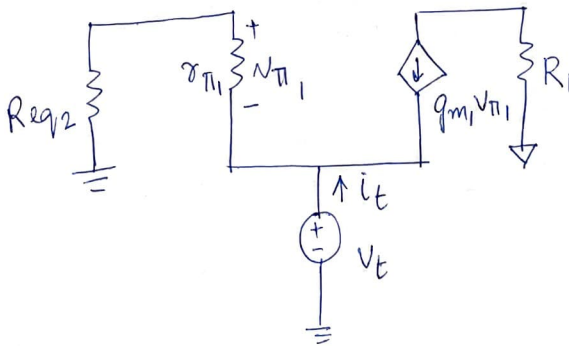The small signal model to calculate R_{in} ,




$$V_{\pi 1} = - \frac{V_t}{r_{\pi 1} + R_{eq2}} \cdot r_{\pi 1} \dots \dots (1)$$

$$\Rightarrow \frac{V_t}{i_t} = \frac{r_{\pi 1} + R_{eq2}}{\beta_1 + 1}$$

$$i_t + g_{m1} V_{\pi 1} + \frac{V_{\pi 1}}{r_{\pi 1}} = 0 \dots \dots (2)$$

$$\Rightarrow R_{in} = \left\{ r_{\pi 1} + \left(r_{\pi 2} \parallel \frac{1}{g_{m2}} \right) \right\} / (\beta_1 + 1)$$

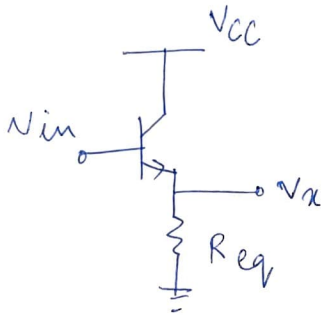Q10) The circuit can be divided into two sections since it is a cascade of two different configurations,



where $R_{eq} = R_E \parallel r_{\pi 2}$

R_{eq} can be calculated from the small signal model of Q_2 , looking at the impedance into the node at the base of Q_2 .

$$\text{Thus, } \frac{v_x}{v_{in}} = \frac{R_{eq} \parallel r_{\pi 1}}{\frac{1}{g_{m1}} + R_{eq} \parallel r_{\pi 1}} = \frac{(R_E \parallel r_{\pi 2}) \parallel r_{\pi 1}}{\frac{1}{g_{m1}} + (R_E \parallel r_{\pi 2}) \parallel r_{\pi 1}}$$

This is the generalized solution.

For $V_A = \infty$, $r_{\pi 1} \rightarrow \infty$.

$$\frac{v_x}{v_{in}} = \frac{(R_E \parallel r_{\pi 2})}{(R_E \parallel r_{\pi 2}) + \frac{1}{g_{m1}}}$$

For the CE configuration, $\frac{v_{out}}{v_x} = -g_{m2} R_C$

$$\therefore \frac{v_{out}}{v_{in}} = \frac{v_{out}}{v_x} \frac{v_x}{v_{in}} = (-g_{m2} R_C) \left\{ \frac{(R_E \parallel r_{\pi 2})}{(R_E \parallel r_{\pi 2}) + \frac{1}{g_{m1}}} \right\}$$

$$\Rightarrow A_V = (-g_{m2} R_C) \left\{ \frac{(R_E \parallel r_{\pi 2})}{(R_E \parallel r_{\pi 2}) + \frac{1}{g_{m1}}} \right\}$$