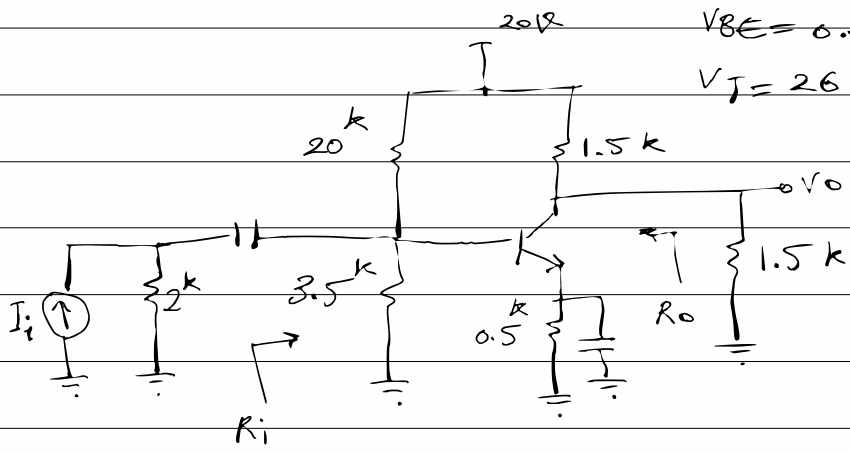


1. Calculate R_i & R_o :

$\beta = 100$

$V_{BE} = 0.7V$

$V_T = 26mV$




2. Calculate R_i ?

$\beta = 100$

$V_{BE} = 0.7V$

$V_T = 26mV$

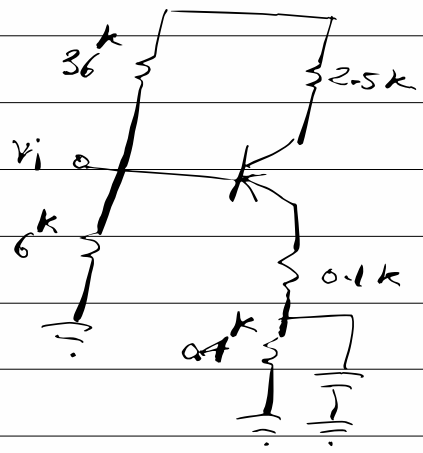


3. Calculate A_v ?

$$V_T = 26 \text{ mV}$$

$$V_{BE} = 0.7 \text{ V}$$

$$\beta = 100$$

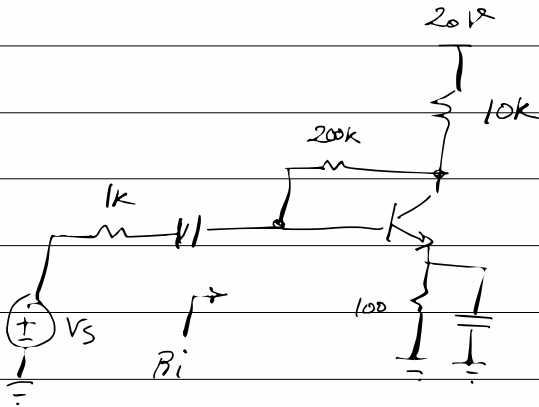


4. Calculate R_i in Q3?

5. Calculate R_i :

$$V_{BE} = 0.7$$


$$\beta = 100$$

$$V_T = 26 \text{ mV}$$

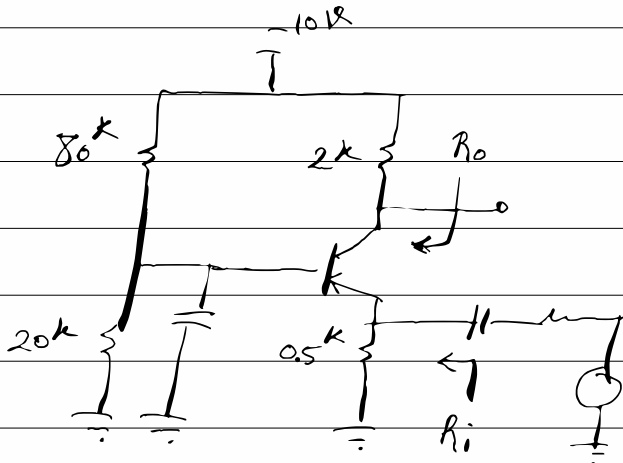

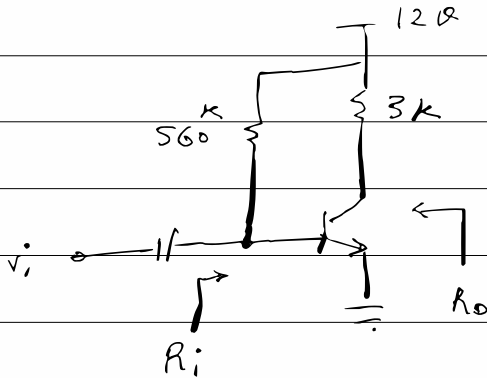6. Calculate R_i & R_o ?


$$\beta = 100 \quad I_C = 2 \text{ mA} \quad r_x = 1.3 \text{ k}\Omega$$



7. Calculate R_o

$$V_T = 25 \text{ mV}$$

$$\beta = 100$$

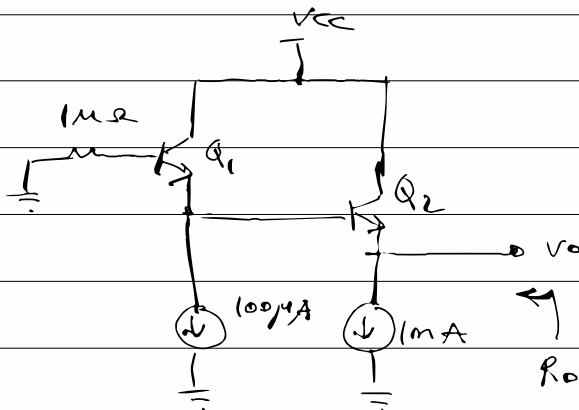


8. The circuit is in Active Region.

Calculate R_{in}

$$\beta = 100$$

$$V_A = \infty$$

$$V_T = 25 \text{ mV}$$

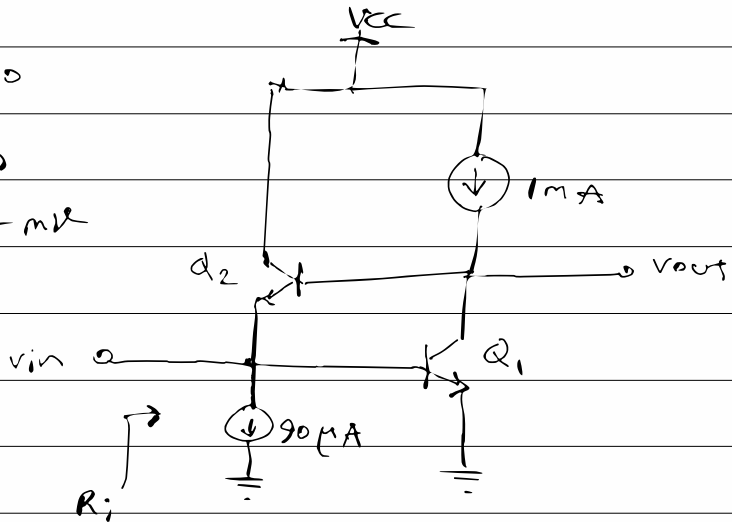


9. The circuit is in Active Region.

Calculate R_{in}

$$\beta = 100$$


$$V_A = \infty$$

$$V_T = 25 \text{ mV}$$

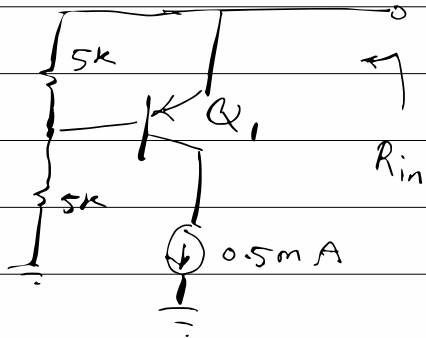


10. The circuit is in Active Region.

Calculate R_{in} :

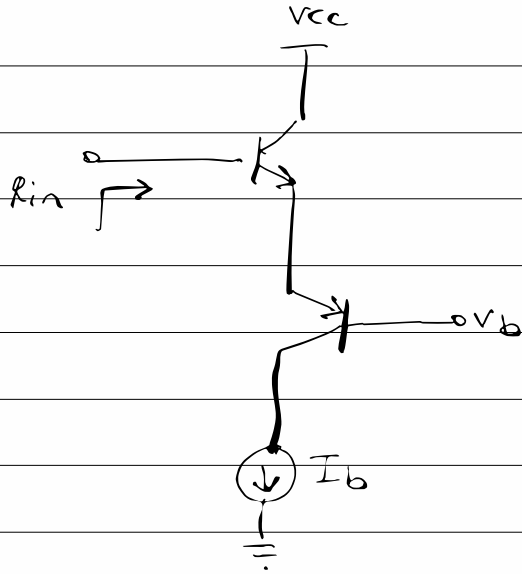

1.

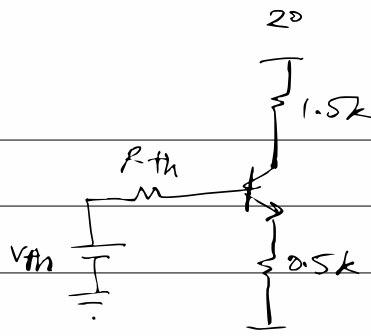


$$V_{th} = \frac{20 \times 3.5 \text{ k}}{3.5 + 1.5 \text{ k}} = 2.98 \quad R_{th} = 20 \text{ k} \parallel 3.5 \text{ k} = 2.98 \text{ k}$$

$$I_E = \frac{V_{th} - V_{BE}}{R_E + R_{th}/(1+\beta)} = 4.31 \text{ mA}$$

$$r_x = \beta \frac{V_T}{I_C} \approx 0.61 \text{ k}\Omega$$

ac model

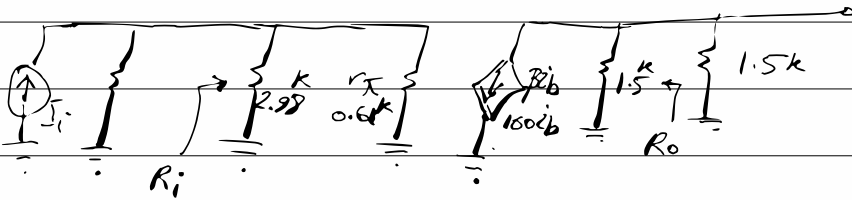

$$R_i = 2.98 \text{ k} \parallel 0.61 \text{ k} = 0.505 \text{ k}\Omega$$

$$R_o: \text{ if } I_i = 0 \rightarrow i_b = 0 \Rightarrow R_o = 1.5 \text{ k}$$

$$2. \quad R_{th} = 36^k \parallel 6^k = 5.14^k$$


$$v_{th} = \frac{-12}{36+6} \times 6 = -1.71V$$

$$I_E = \frac{-v_{th} - V_{EB}}{R_{E1} + R_{E2} + R_{th} / (1+\beta)} = 1.83 \text{ mA}$$

$$I_C = \alpha I_E = 1.81 \text{ mA} \quad r_x = \beta \frac{V_T}{I_C} = 1.44 \text{ k}\Omega$$

$$R_i' = r_x + (\beta+1) 0.1^k = 11.54^k$$

$$R_i = 5.14^k \parallel R_i' = 3.56^k$$

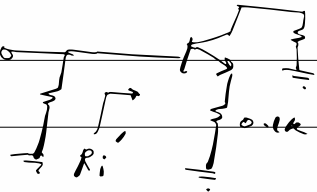


$$3. \quad \text{KVL: } 20 = R_C (I_B + I_C) + R_B I_B + V_{BE} + R_E I_E$$

$$I_E = (\beta+1) I_B$$

$$I_E = 1.6 \text{ mA} \quad I_C = 1.58 \text{ mA}$$

$$r_x = \beta \frac{V_T}{I_C} = 1.645 \text{ k}\Omega$$

3.

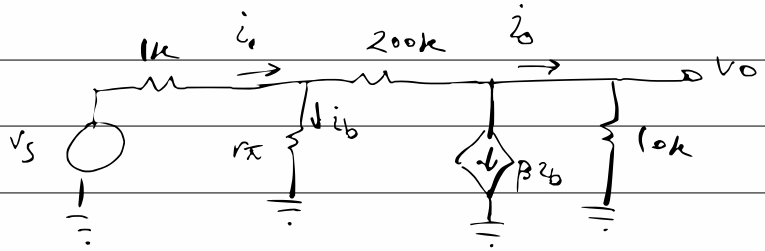

$$v_i = 200^k (i_o + \beta i_b) + v_o, \quad i_b = \frac{v_i}{r_x}, \quad i_o = \frac{v_o}{10^k}$$

$$v_i = 200^k v_o + \frac{200^k \beta v_i}{r_x} + v_o$$

$$211 v_o = \left(1 - \frac{200 \beta}{r_x}\right) v_i \Rightarrow A_v = \frac{v_o}{v_i} = -579$$

4.

$$v_i = 200 (i_i - i_b) + v_o, \quad i_b = \frac{v_i}{r_x}, \quad v_o = A_v v_i$$

$$v_i = 200 \left(i_i - \frac{v_i}{r_x}\right) + A_v v_i \rightarrow$$

$$v_i \left(1 + \frac{200^k}{r_x} - A_v\right) = 200 i_i \rightarrow R_i = \frac{v_i}{i_i} \approx 285 \Omega$$

$$5. \quad R_{Th} = 20 \text{ k} \parallel 80 \text{ k} = 16 \text{ k}$$


$$V_{Th} = \frac{-10}{20+80} \times 20 = -2 \text{ V}$$

$$I_E = \frac{-V_{Th} - V_{EB}}{R_E + R_{Th}/(1+\beta)} = 1.97 \text{ mA}$$

$$I_C = \alpha I_E = 1.95 \text{ mA}, \quad r_\pi = \beta \frac{V_T}{I_C} = 1.33 \text{ k}\Omega$$

Common Base model:
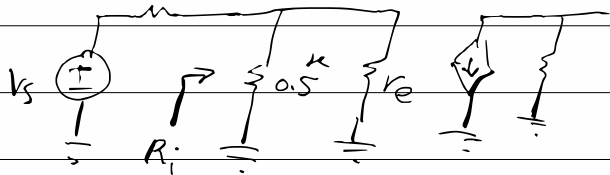
$$r_e = \frac{r_\pi}{\beta+1} = 13.2 \Omega$$



$$R_i = 500 \Omega \parallel 13.2 \approx 12.86 \Omega$$


6.

$$R_i \approx r_\pi = 1.3 \text{ k}\Omega$$

$$R_o = 3 \text{ k}\Omega$$

7.

ac-model

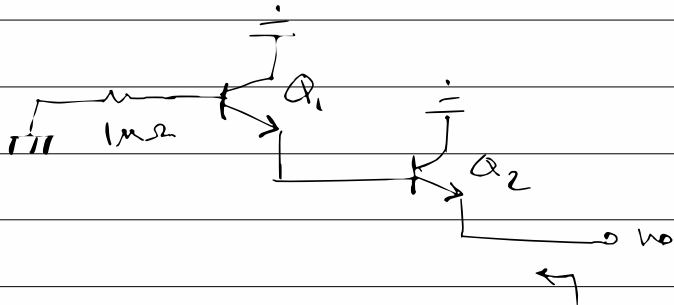

$$R_o \approx \frac{1\text{M}\Omega}{\beta^2} + \frac{r_{e1}}{\beta} + r_{e2}$$

$$r_{e1} = \frac{V_T}{I_{C1}} = \frac{25\text{mV}}{0.1\text{mA}} = 250\Omega$$

$$r_{e2} = \frac{V_T}{I_{C2}} = \frac{25\text{mV}}{1\text{mA}} = 25\Omega$$

$$R_o = \frac{10^6\Omega}{10000} + \frac{250\Omega}{100} + 25\Omega = 127.5\Omega$$

8.

$$I_{C1} \approx 1\text{mA} \quad I_{B1} = \frac{I_{C1}}{\beta} = 10\mu\text{A}$$


$$I_{C2} \approx I_{E2} = 90\mu\text{A} + I_{B1} = 100\mu\text{A}$$

$$r_{e1} = \frac{25\text{mV}}{1\text{mA}} = 25\Omega$$

$$R_{in} = r_{\pi 1} = \beta r_{e1} = 2.5\text{k}\Omega$$

9.

ac-model

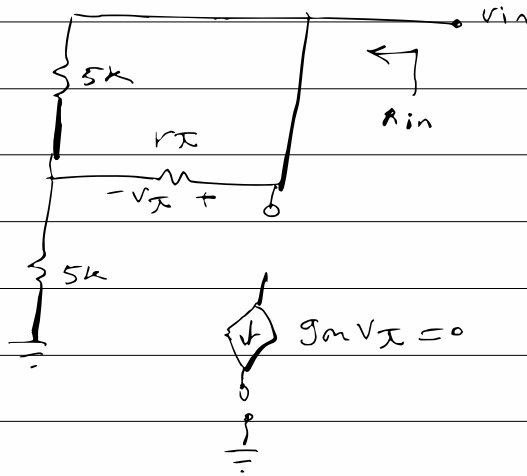


$$r_e = \frac{25 \text{ mV}}{0.5 \text{ mA}} = 50 \Omega \quad r_{\pi} = \beta r_e = 5 \text{ k}\Omega$$

$$R_{in} = (5 \text{ k} \parallel r_{\pi}) + 5 \text{ k} = 7.5 \text{ k}\Omega$$

10.

ac-model

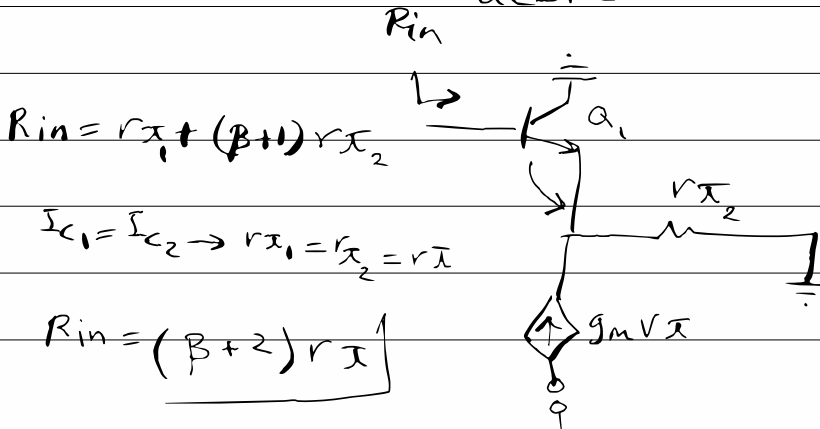

$$R_{in} = r_{\pi 1} + (\beta + 1) r_{\pi 2}$$

$$I_{c1} = I_{c2} \rightarrow r_{\pi 1} = r_{\pi 2} = r_{\pi}$$

$$R_{in} = (\beta + 2) r_{\pi}$$