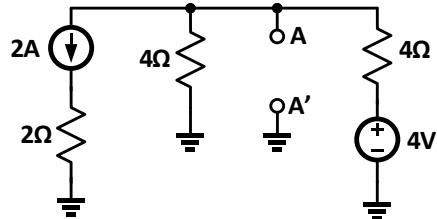
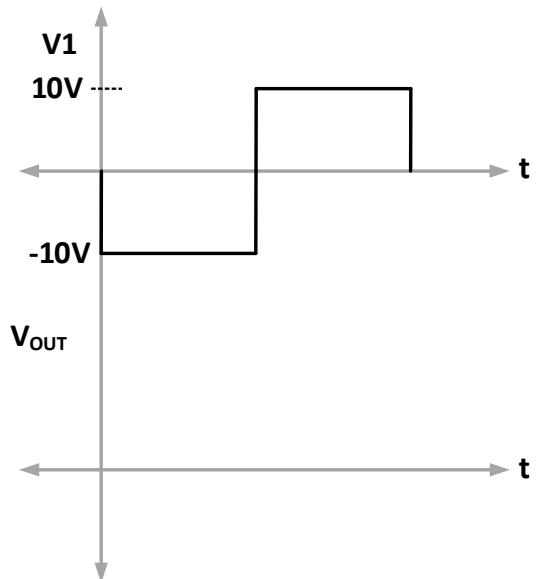
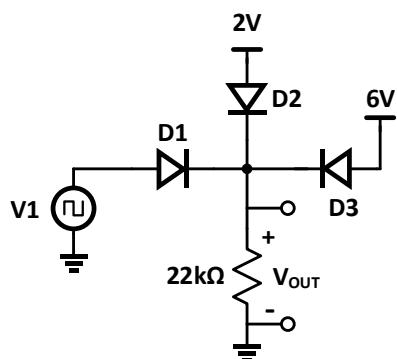


Duration: 20 minutes.**Good Luck!**

Name _____

Score _____

Q1 (10pts): Draw the Thevenin's equivalent circuit across terminal A-A'

Q2 (10pts): Assuming ideal diodes, plot the voltage V_{OUT} .Q3 (10pts): Assuming ideal diodes, calculate current I_2 in D_2 and voltage at node A.