

Test 1 (02/01/16)

Total # Pages 4

Total # Problems 4

Name _____

1. (10 points) _____

2. (25 points) _____



3. (40 points) _____

4. (25 points) _____

Total (100 points) _____



GOOD LUCK

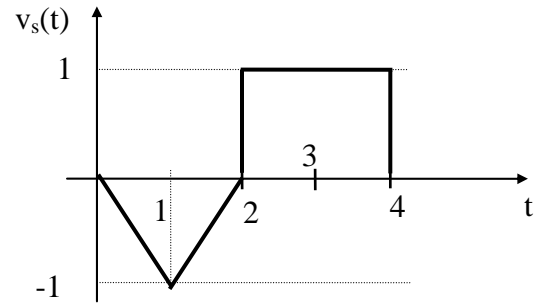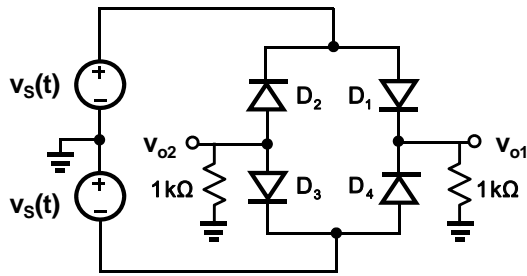1. A diode circuit and voltage waveform $v_s(t)$ are shown. (10 points).



<u>List</u> which diodes are ON (i.e., forward biased and conducting current) and which are OFF for $0 < t < 2$. Assume ideal diodes.	<u>List</u> which diodes are ON and which are OFF for $2 < t < 4$. Assume ideal diodes.
ON Diodes:	ON Diodes:
OFF Diodes:	OFF Diodes:

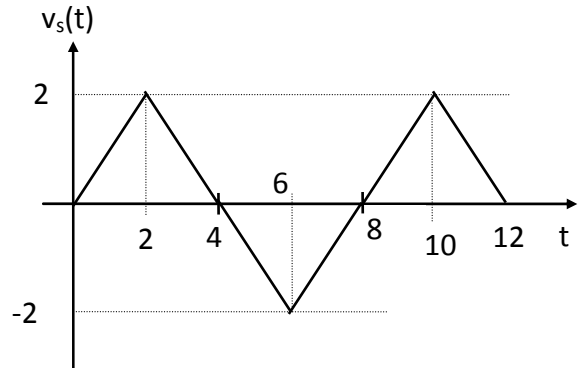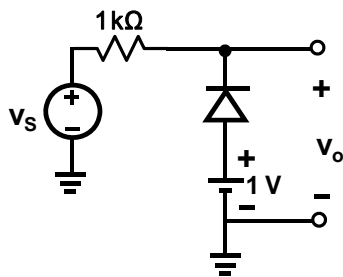2. Consider the diode circuit shown below with a signal voltage waveform $v_s(t)$ as shown. Draw the specified voltage waveforms in the table below. (25 points).



<u>Sketch</u> the voltage waveform for $v_o(t)$ assuming an ideal diode. Label the time axes and the signal values.	<u>Sketch</u> the voltage waveform for $v_o(t)$ assuming a constant voltage drop model for the diode (the diode voltage is at 0.5V when conducting). Label the time axes and the signal values.

3. Answer the following questions. $|V_{BE}| = 0.7V$ for an ON transistor and $|V_{CE}| = 0.2V$ when the transistor is in saturation.


a) For the bipolar transistors and conditions shown in the following table calculate the missing entries. (15 points).

Device	I_C (mA)	I_B (mA)	I_E (mA)	α	β
a	2				50
b			1	0.98	
c		10	110		10


b) In the circuit shown, calculate the collector current and collector voltage assuming $\beta = 100$. (10 points).

$I_C =$ _____

$V_C =$ _____

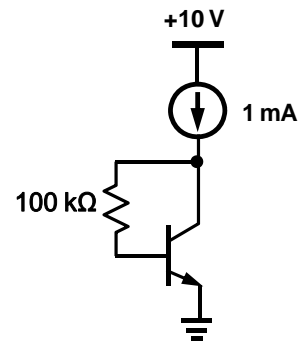

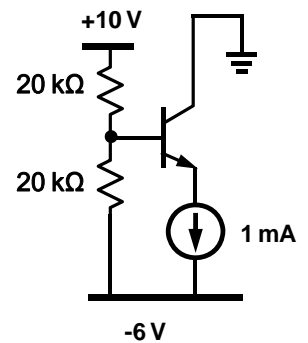c) For the circuit shown determine the region of operation (cutoff, active, or saturation) for the transistor with $\beta = 49$. (15 points).



4. For the circuit shown, the emitter voltage is 4 V. Calculate the collector voltage and collector, base, and emitter currents for the transistor. Use this information to calculate α and β . **Do not assume large β .** $|V_{BE}| = 0.7V$ for an ON transistor. (25 points).

$$I_C = \underline{\hspace{2cm}}$$

$$I_B = \underline{\hspace{2cm}}$$

$$I_E = \underline{\hspace{2cm}}$$

$$V_C = \underline{\hspace{2cm}}$$

$$\alpha = \underline{\hspace{2cm}}$$

$$\beta = \underline{\hspace{2cm}}$$

