

ECE 322 Electronics-1, Fall 2017

Test Date: 10/25/2017

Problems: 4

Total Pages: 6

Name: _____

1. (10 points) _____

2. (20 points) _____



3. (30 points) _____

4. (30 points) _____

Total (90 points) _____

Good Luck

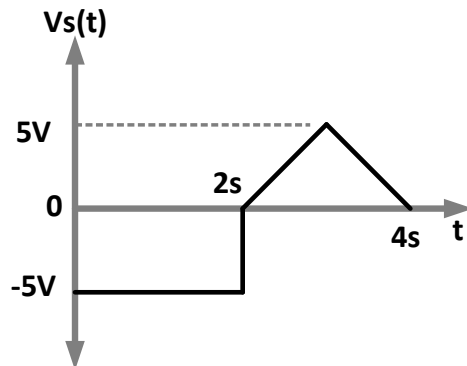
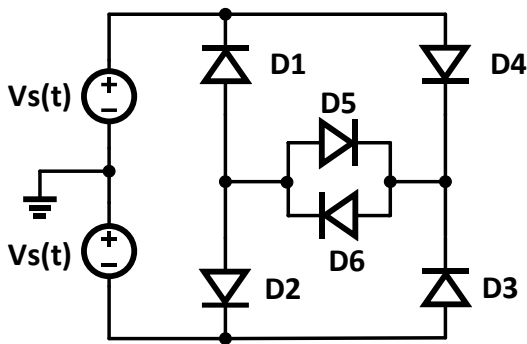
Problem 1: (10 points) A circuit with 6 diodes is shown below along with the waveform of the input source. Assume **ideal diodes** answer the following:




1(a): Write the diodes which are turned on during time 0s to 2s.

1(b): Write the diodes which are turned on during time 2s to 4s.

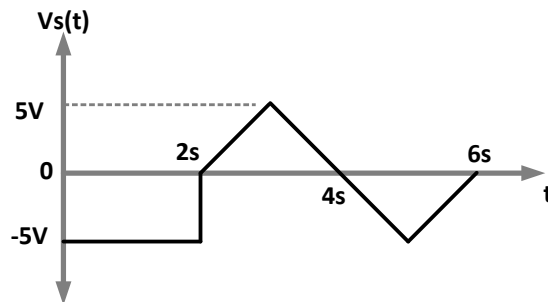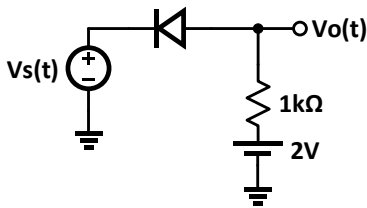
Problem 2: (20 points) A circuit with one diodes is shown below along with the waveform of the input source.



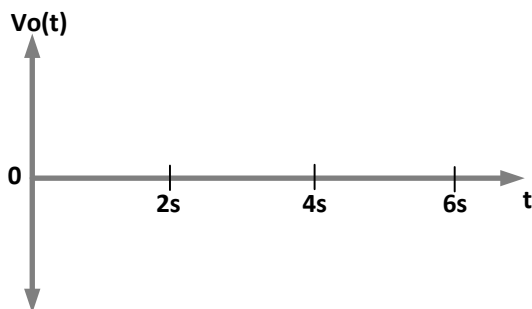2(a): Assume idea diode, draw the waveform at node Vo



2(a): Assume diode drop in forward bias is 1V, draw the waveform at node Vo.

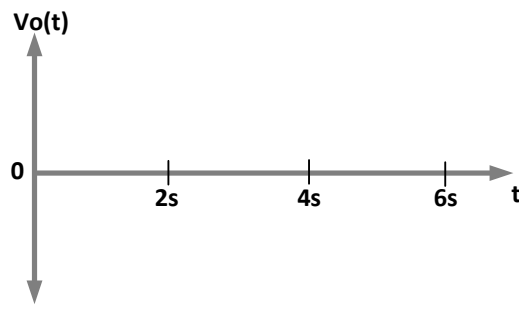

Problem 3: (30 points)


- (a) For a pnp transistor, the emitter current I_E is 2mA and the value of $\beta=20$. Calculate the following quantities:

Base Current $(I_B) =$ _____
Collector current $(I_C) =$ _____
Current Gain $(\alpha) =$ _____

- (b) For the circuit shown below, assume $|V_{BE}| = 0.7V$, calculate the following quantities:


$V_C =$ _____

$I_E =$ _____

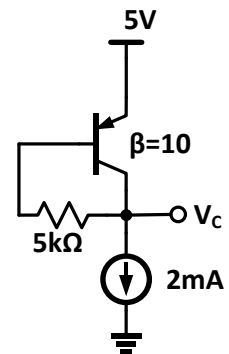

(c) For the circuit shown below, assume $|V_{BE}| = 0.7V$, determine the region of operation for the transistor (cutoff, active, or saturation).

Answer _____

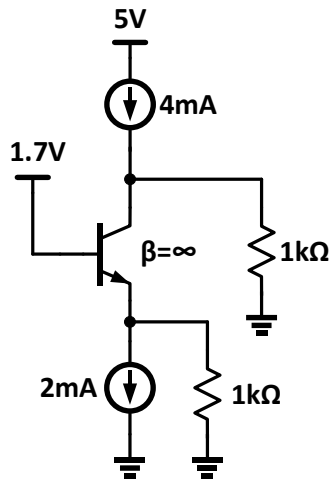

Problem 4: (30 points) For the circuit shown below $|V_{BE}| = 0.7V$, calculate the voltages V_1 , V_2 , V_3 , V_4 , and V_5 .

$V_1 =$ _____
 $V_2 =$ _____
 $V_3 =$ _____
 $V_4 =$ _____
 $V_5 =$ _____

