

ECE 322 Electronics-1, Fall 2018

Test Date: 10/24/2018

Problems: 4

Total Pages: 6

Name: _____

1. (10 points) _____

2. (20 points) _____


3. (30 points) _____

4. (30 points) _____

Total (90 points) _____

Good Luck

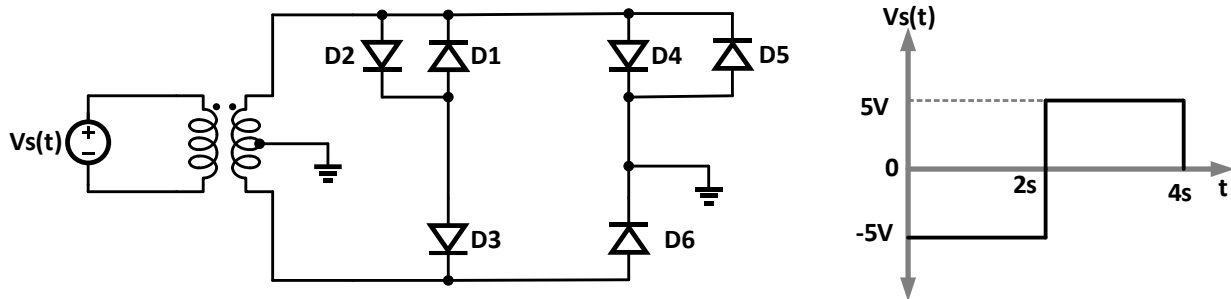
Problem 1: (10 points) A circuit with 6 diodes is shown below along with the waveform of the input source. Assume **ideal diodes** answer the following:



1(a): Write the diodes which are turned on during time 0s to 2s.



1(b): Write the diodes which are turned on during time 2s to 4s.

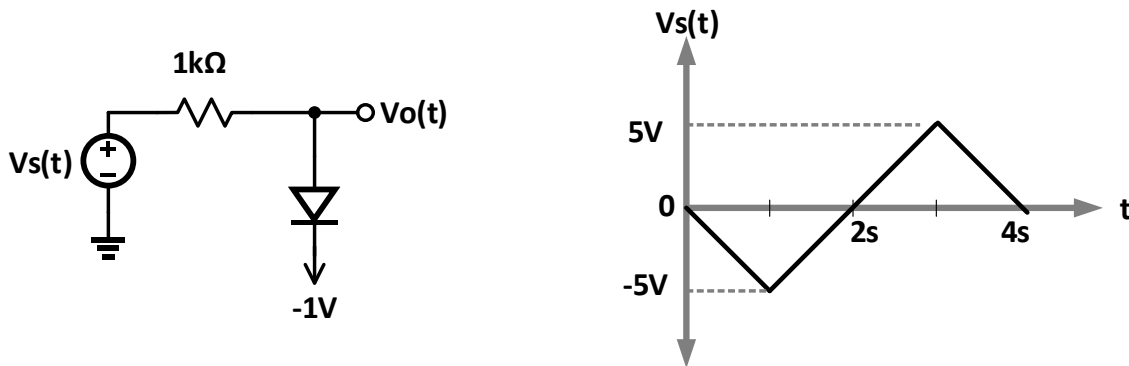Problem 2: (20 points) A circuit with one diode is shown below along with the waveform of the input source.



2(a): Assume ideal diode, draw the waveform at node Vo

2(a): Assume diode drop in forward bias is 1V, draw the waveform at node Vo.

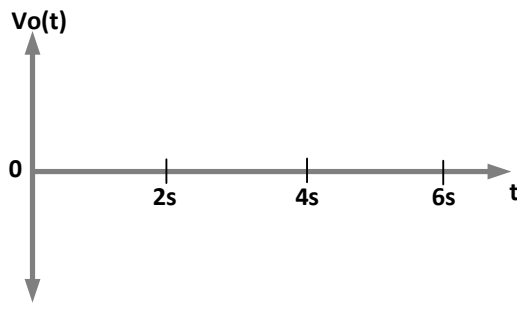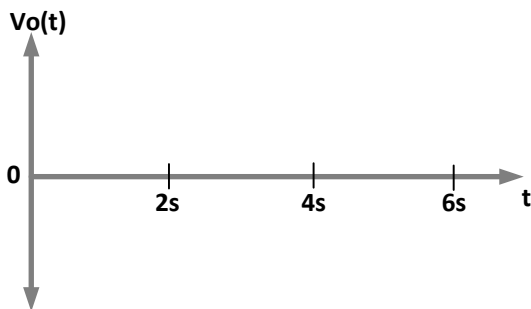

Problem 3: (30 points)


- (a) For a npn transistor, the emitter current I_E is $10\mu\text{A}$ and the value of $\alpha=0.99$. Calculate the following quantities:

Emitter Current $(I_E) =$ _____
Collector current $(I_C) =$ _____
Current Gain $(\beta) =$ _____

- (b) For the circuit shown below, assume $|V_{BE}| = 0.7\text{V}$, calculate the following quantities:

$V_C =$ _____


$I_E =$ _____

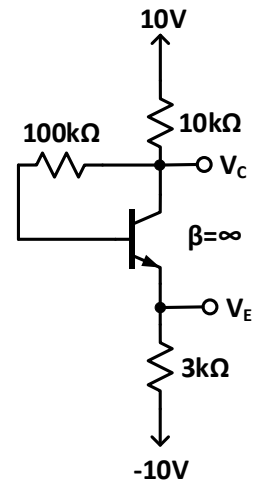

(c) For the circuit shown below, assume $|V_{BE}| = 0.7V$, determine the region of operation for the transistor (cutoff, active, or saturation) and calculate V_c

Region of Operation = _____

$V_c =$ _____

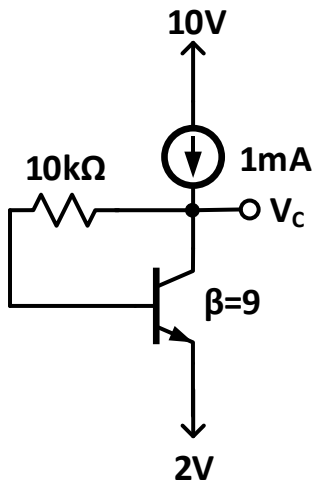

Problem 4: (30 points) For the circuit shown below $|V_{BE}| = 0.7V$ and $V_E=1V$, calculate the voltages V_C and V_B ; calculate currents I_C and I_B ; calculate β and α ;

$V_C =$ _____
 $V_B =$ _____
 $I_C =$ _____
 $I_B =$ _____
 $\beta =$ _____
 $\alpha =$ _____

