

ECE 322 Electronics-1, Fall 2020

Test Date: 10/21/2020

Problems: 4

Total Pages: 6

Name: _____

1. (10 points) _____

2. (20 points) _____

3. (30 points) _____



4. (30 points) _____

Total (90 points) _____


Good Luck

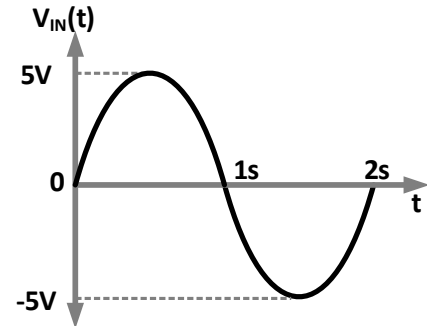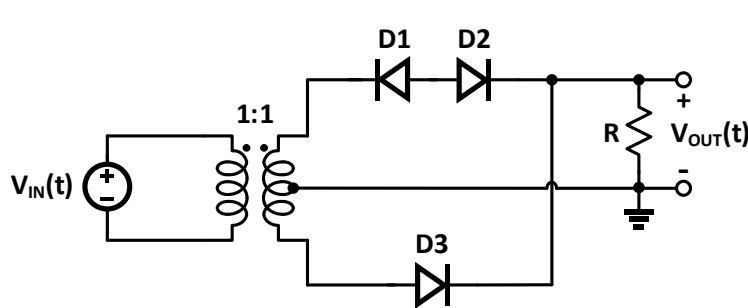Problem 1: (10 points) A circuit with 3 diodes is shown below along with the waveform of the input source. Assume real diodes (Diode Drop = 0.7V) answer the following:




1(a) Draw V_{OUT} as a function of time and mark the peak voltage.



<p>1(b): Write the diode which is turned on during time 0s to 1s.</p>	<p>1(c): Write the diode which is turned on during time 1s to 2s.</p>
---	---

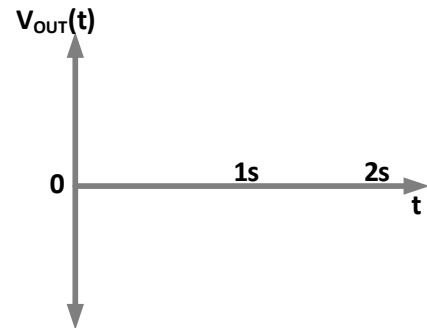

Problem 2: (20 points) A circuit with one diode is shown below along with the waveform of the input source. Draw the output waveform $V_{OUT}(t)$. Assume the diode is ideal.

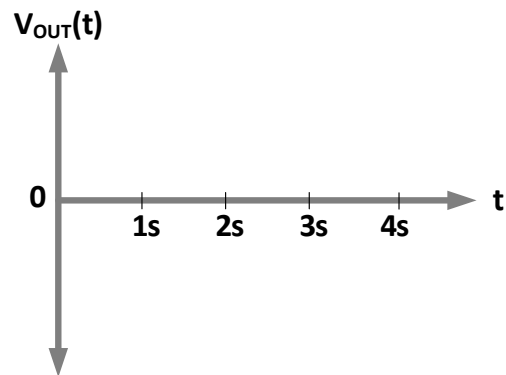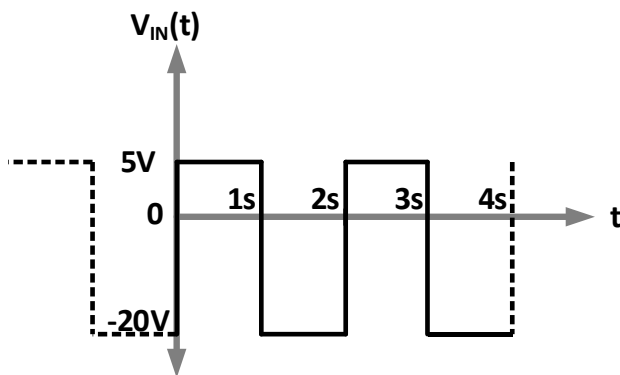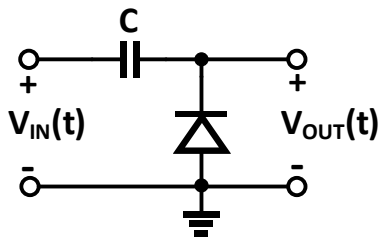

Problem 3: (30 points)


(a) For a PNP transistor, the base current I_B is $50\mu\text{A}$ and the value of $\beta=100$.
Calculate the following quantities:

Emitter Current $(I_E) =$ _____
Current Gain $(\alpha) =$ _____

(b) For the circuit shown below, assume $|V_{BE}| = 0.7\text{V}$, calculate the following quantities:


$I_C =$ _____

$V_E =$ _____

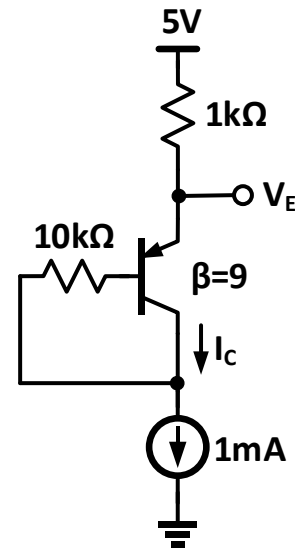

(c) For the circuit shown below, assume $|V_{BE}| = 0.7V$, determine the region of operation for the transistor (cutoff, active, or saturation)

Region of Operation = _____

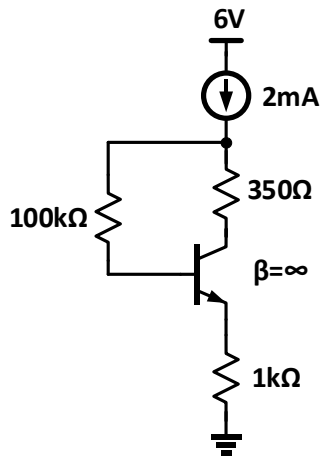

Problem 4: (30 points) For the circuit shown below $|V_{BE}| = 0.7V$, calculate the following quantities:

$V_C =$ _____
 $V_E =$ _____
 $I_C =$ _____
 $I_B =$ _____
 $I_E =$ _____
 $\alpha =$ _____

