

ECE 322 Electronics-1, Fall 2018

Test Date: 11/19/2018

Problems: 3

Total Pages: 8

Name: _____

1. (20 points) _____

2. (20 points + 5 Bonus) _____


3. (20 points) _____

Total (60 points) _____

Good Luck!


Problem 1 (a) (10 points): For circuit show below, draw the small signal model and derive the small signal resistance R_{OUT} .

$R_{OUT} =$ _____

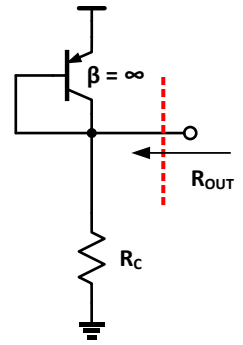


(b) (10 points): For circuit show below, draw the small signal model and derive the small signal resistance R_{OUT} . Transconductance of both BJTs are same – gm.

$R_{OUT} =$ _____

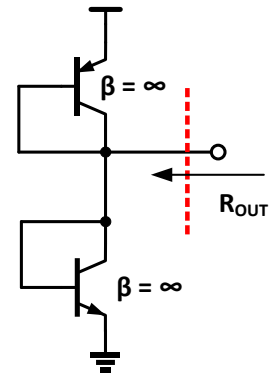


Problem 2(a): (10 points) The circuit shown below is known as Darlington transistor connection. Draw the small signal “Hybrid pi” model and derive the small signal resistance R_{IN1} . You can assume transconductance of the BJTs as g_{m1} and g_{m2} .

$R_{IN1} =$ _____

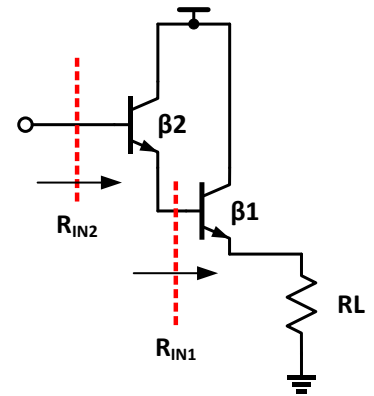


(b): (10 points) For circuit show below, draw the small signal “Hybrid pi” model and derive the small signal resistance R_{IN2} . You can assume transconductance of the BJTs as g_{m1} and g_{m2} .

$R_{IN2} =$ _____

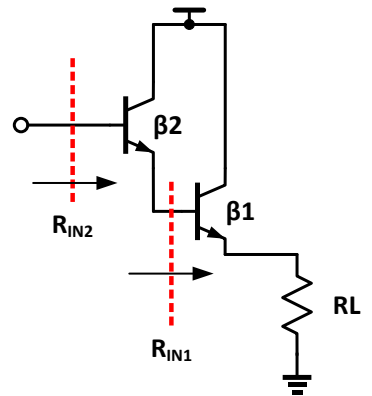


Bonus (5 points) For circuit show below, draw the small signal “Hybrid pi” model and derive the small signal resistance R_{IN} .

$R_{IN} =$ _____

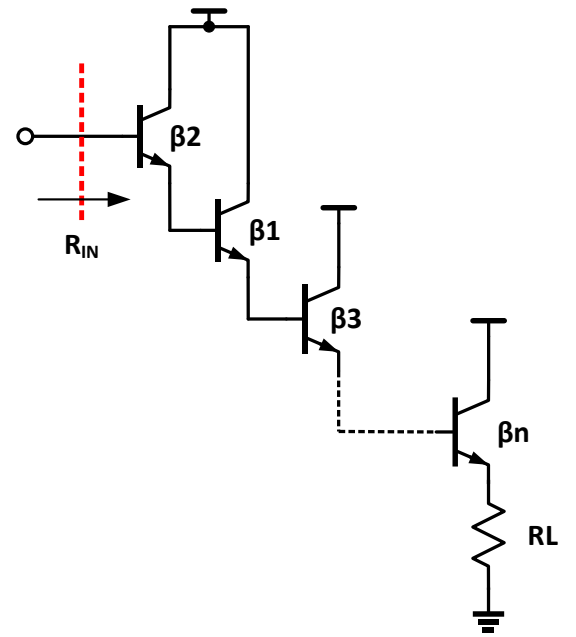

Problem 3: (20 points) For the amplifier circuit shown below, calculate the amplifier gain V_{OUT}/V_{IN} through small signal analysis (show the complete analysis). Assume $|V_{BE}|=0.7V$

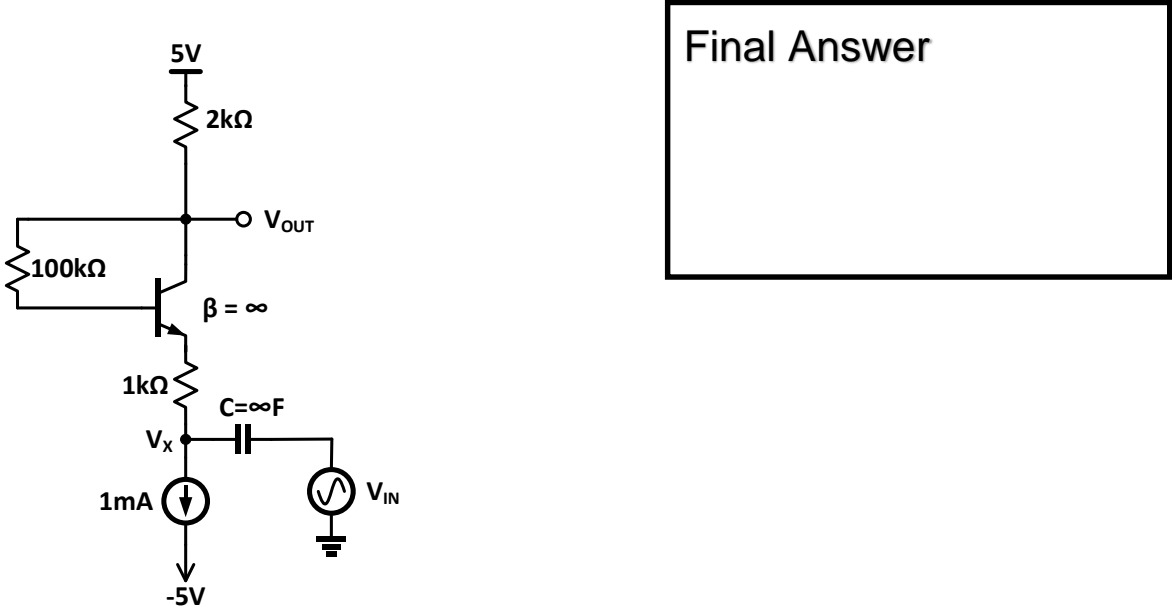

Final Answer

