

ECE 322 Electronics-1, Fall 2020

Test Date: 11/18/2020

Problems: 3

Total Pages: 7

Name: _____

1. (20 points) _____

2. (20 points + 10 Bonus) _____


3. (20 points) _____

Total (60 points) _____

Good Luck!


Problem 1 (a) (10 points): For circuit shown below, draw the small signal model and derive the small signal resistance R_o . The current gain β is infinite. Both the BJTs are similar. Assume transconductance of both the BJTs = g_m .

$R_o =$ _____

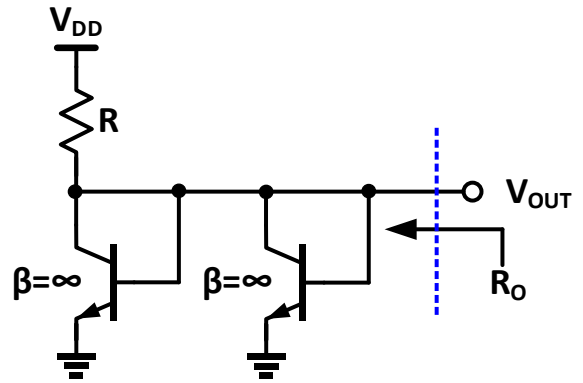


(b) (10 points): For circuit shown below, draw the small signal model and derive the small signal resistance R_o . The current gain β is **finite**. Both the BJTs are similar. Assume transconductance of both the BJTs = g_m .

$R_o =$ _____

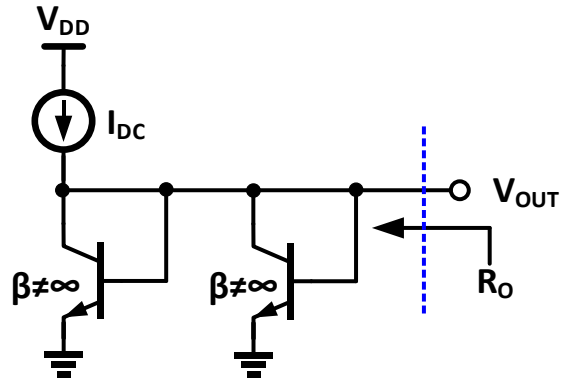

Problem 2: (20 points) For circuit shown below, draw the small signal model and derive the small signal resistance R_o .


$R_o =$ _____

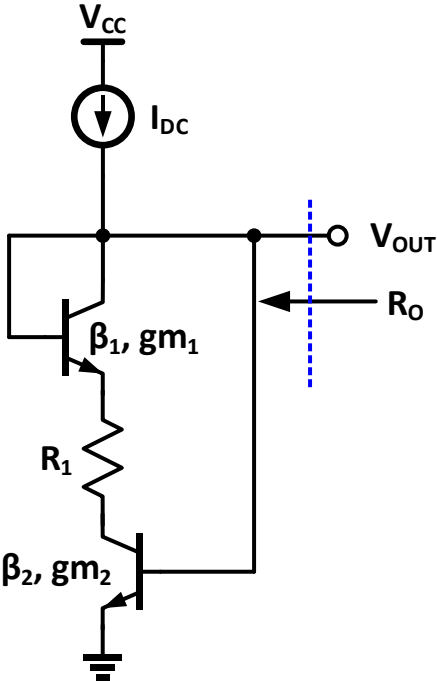


Bonus (10 points) For circuit shown below, draw the small signal model and derive the small signal resistance R_{IN} .

(Note: No partial credit in Bonus Problem)

$R_{IN} =$ _____

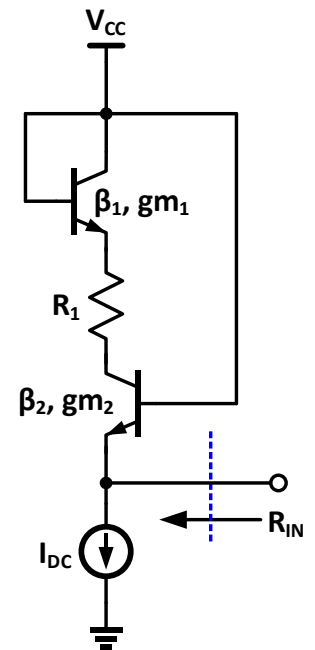

Problem 3: (20 points) For the amplifier circuit shown below, calculate the amplifier gain V_{OUT}/V_{IN} through small signal analysis (show the complete analysis). Assume $|V_{BE}|=0.7V$

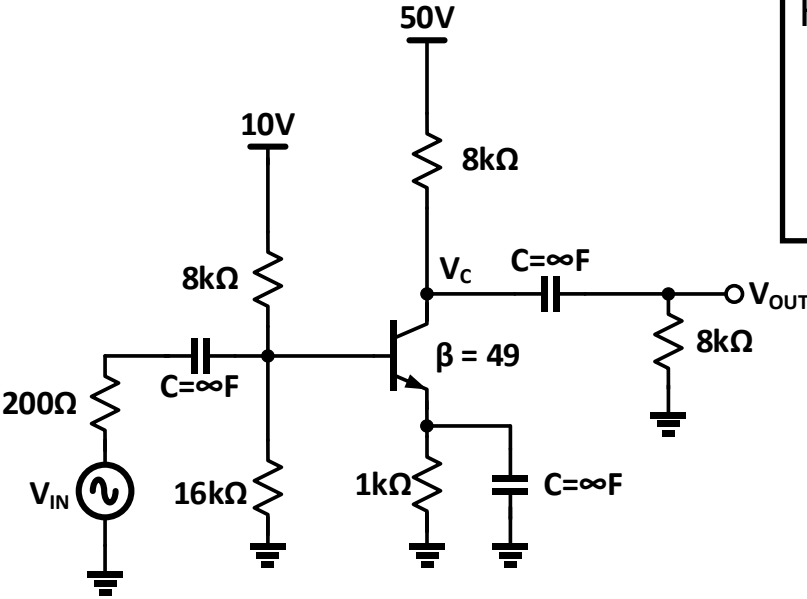

Final Answer

