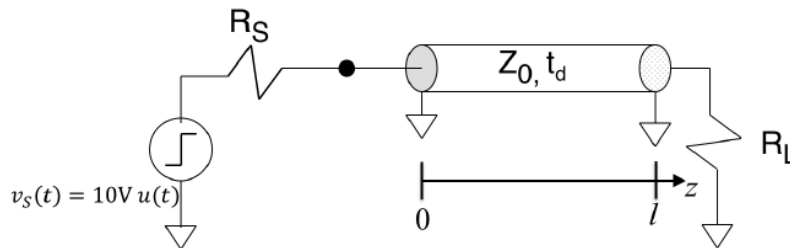


ECE 391: Transmission Lines  
 Spring Term 2020  
 Homework Assignment #2  
 Monday, Apr. 27 Online (Canvas)


1. Consider the transmission line circuit given below. Let  $R_S = 5Z_0 = 250\Omega$  and  $R_L = 0\Omega$ . At time  $t = 0$  a 10V battery is connected at the near end of the transmission line ( $v_S(t) = 10V u(t)$ ). Draw a lattice diagram including the numerical values for voltage of the first four traveling waves. Sketch  $v(t)$  at  $z = 0$  and  $z = l$ . Determine the steady-state response for  $v(t)$  for  $t = \infty$ .



2. At time  $t = t_0$ , a source with open-circuit voltage,  $V_S$ , and source resistance,  $R_S$ , is connected to an oscilloscope having infinite input impedance through a lossless  $60\Omega$  transmission line of length  $z = l$  and with velocity factor  $VP = 66.6\%$  (i.e. 66.6% the speed of light). After some delay, a voltage of 60V is observed on the oscilloscope.  $10\mu\text{sec}$  later, the voltage on the oscilloscope drops to 30V.

- (a) Draw a lattice diagram for the first four wave components and determine the source voltage,  $V_S$ , and battery resistance,  $R_S$ .
- (b) Determine the length of the transmission line,  $l$ , in meters.
- (c) Sketch the voltage at the input of the line from  $t = t_0$  to  $t = t_0 + 25\mu\text{sec}$ .
- (d) Calculate the steady-state voltage at time  $t = \infty$ .

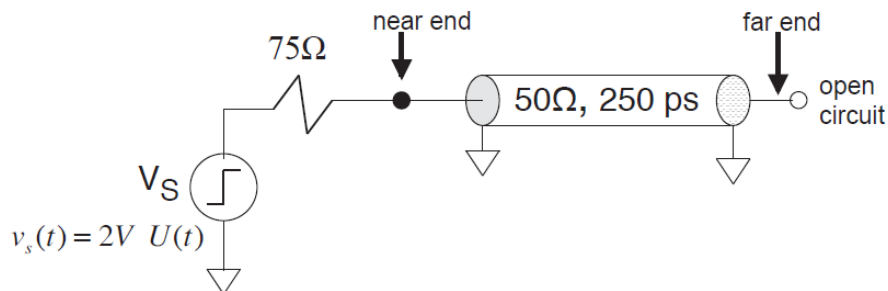3. For the transmission line circuit shown below, draw a lattice diagram from  $t = 0\text{ns}$  through  $t = 1.7\text{ns}$ .



4. Given the transmission line circuit shown below with  $V_G(t) = 30u(t)$  (V),  $R_G = 150$ ,  $Z_0 = 75$ , length  $z_r = 20$  m, and velocity factor  $VP = 66.6\%$ .
- (a) Draw a lattice diagram and plot the voltage and current waveforms at  $z = 0$ , and  $z = z_r$  for  $0 \leq t \leq 430$  ns for the cases (i)  $R_T = 0\Omega$ , (ii)  $R_T = 15\Omega$ , and (iii)  $R_T = 125\Omega$ .
- (b) What are the final values of voltage and current (i.e., for  $t = \infty$ ) for the three terminations?

