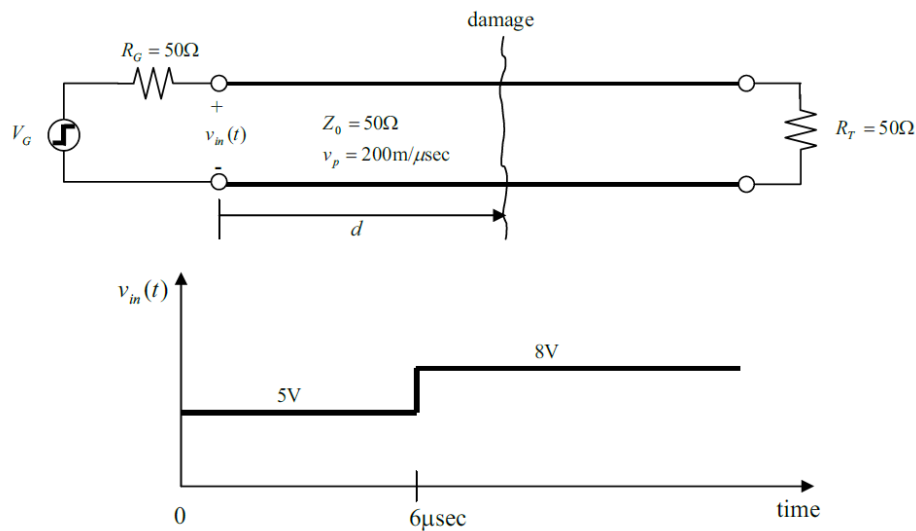




ECE 391: Transmission Lines
 Spring Term 2020
 Homework Assignment #3
 Friday, May. 8 Online (Canvas)

1. A lossless transmission line cable ($Z_0 = 50$, $v_p = 200\text{m}/\mu\text{sec}$) is suspected to be damaged at an unknown distance d from the input. The cable is terminated in a matched resistance $R_T = 50$. In order to find the location of the damaged cable, a step voltage is applied at the input at time $t = 0$, and the voltage waveform is observed at the input of the cable (time-domain reflectometry). The step-voltage generator is matched to the transmission line ($R_G = 50$).




- (a) What are the voltage and current amplitudes of the first outgoing wave?
 - (b) Determine the generator voltage.
 - (c) Determine distance d at which the cable is damaged.
 - (d) Determine the voltage of the returning wave (reflected at the damaged location).
 - (e) What is the reflection coefficient at the location of the damaged cable?
2. You have found a piece of 2m long piece of coaxial cable of unknown characteristic impedance, Z_0 . To characterize the cable, you connect one end of the cable to the TDR instrument in your lab and short-circuit the other end, as illustrated in the figure below. The open circuit voltage of the TDR system is $V_0 = 10\text{V}$ and the output impedance is $R_s = 50\Omega$. The recorded step response $v_{in}(t)$ at the input of the coaxial cable is shown below for $-5 \leq t \leq 30 \text{ nsec}$ (dashed curve).
 - (a) Determine the delay time (TD) of the coaxial transmission line.

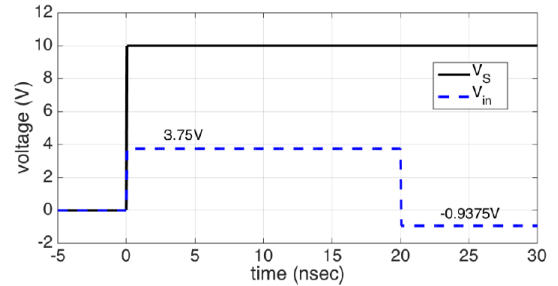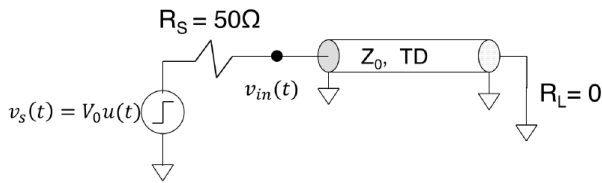- (b) Determine the propagation velocity on the coaxial cable.
- (c) Determine the characteristic impedance of the coaxial cable.
- (d) Determine the reflection coefficient at the source (Γ_s) and the load (Γ_L).
- (e) Draw lattice diagram and show the numerical values for voltage and current for the first 5 wave components.
- (f) Determine the voltage at the input of the coaxial cable, v_{in} , at time $t = 45\text{nsec}$.
- (g) Determine the current into the coaxial cable (source side) at $t = 5\text{nsec}$ and $t = 25\text{nsec}$.
- (h) What are the steady-state voltage and current at the input of the coaxial cable?



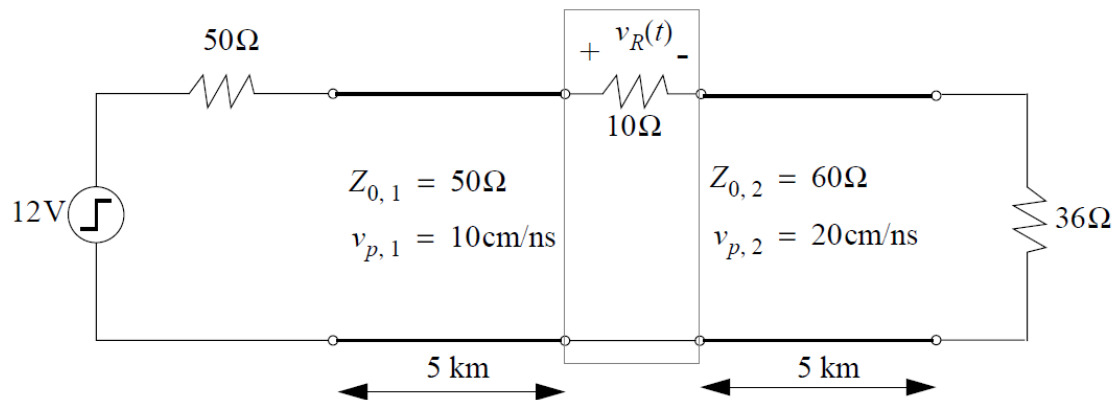3. Two lossless transmission lines are connected in tandem through a series resistance, as shown below.
- (a) Determine the delay time of each line.
 - (b) Determine the reflection and transmission coefficients at the junction between the two lines.
 - (d) Draw a lattice diagram and specify the voltage and current of each wave component up to $t = 80\mu\text{sec}$.
 - (e) Plot the voltage across the 10Ω series resistance as a function of time for $0 \leq t \leq 80\mu\text{sec}$;
 - (f) Determine the steady-state voltage across the 36Ω load resistor.



4. An ideal coaxial line with characteristic impedance $Z_0 = 50\Omega$ is connected to a source having $V_s = 18V$ and $R_s = Z_0 = 50$. The termination of the coaxial line at the far end is unknown. At time $t = 0$ the source is turned on and the transient response at the near end ($z = 0$) is observed on an oscilloscope (see figure below).
- (a) Determine the delay time t_d of this transmission line.
- (b) Determine the unknown lumped-element termination (show the terminating circuit and include the lumped-element values with appropriate units).

