

## ECE 391: Transmission Lines

Spring Term 2020

### Homework Assignment #4

due Friday, May 22

0.

1. The following data are specified at  $f = 200\text{KHz}$  for a given transmission line.

$$\begin{aligned}Z_0 &= (52 - j0.4)\Omega \\ \alpha &= 5 \times 10^{-3}\text{dB/m} \\ \beta &= 8.3776 \times 10^{-3}\text{rad/m}\end{aligned}$$

Determine the per-unit-length  $R, L, G, C$  transmission line parameters, wavelength, and phase velocity.

2. (a) The voltage amplitude of a sinusoidal wave at the input of a 200m long transmission line is  $V_{in} = 5\text{V}$ . The far end of the line is matched (no reflected waves are excited) and the voltage is measured as  $V_{out} = 3\text{V}$ . What is the attenuation in (i) dB/m, (ii) Np/m? (b) A coaxial cable has a specified attenuation constant of  $\alpha = 0.05\text{dB/m}$ . Specify the attenuation constant in (i) dB/cm, (ii) Np/m, (iii) dB/100ft. How much is the voltage amplitude of a single traveling sinusoidal wave attenuated after 100 meters? Give your answer in %, dB, and nepers.
3. A lossless  $50\Omega$  transmission line of length  $z_r = 50\text{m}$  ( $v_p = 30\text{cm/ns}$ ) is terminated in (a)  $Z_T = Z_0/4$ , (b)  $Z_T = 4Z_0$ , (c)  $L = 398\text{nH}$ , (d)  $C = 79.6\text{pF}$ . Using Matlab, plot the voltage and current standing-wave patterns on the line for  $f = 7.5\text{MHz}$  and specify the voltage standing-wave ratio for each of the cases (a)-(d). The amplitude of the incident wave is  $10\text{V}$ . Use one graph for all voltage plots and one for current plots.
4. A lossless  $50\Omega$  coax of length  $z_r = 5\text{m}$  ( $\epsilon_r = 2.25$ ) is terminated in an impedance  $Z_T = (70 - j30)\Omega$ . (a) What is the standing-wave ratio on the line? (b) Using Matlab, plot the voltage and current standing-wave patterns on the line for  $f_0 = 10\text{MHz}$ . (c) Determine the input impedance of the line if the operating frequency is (i)  $f_0 = 10\text{MHz}$ , (ii)  $f_0 = 20\text{MHz}$ , (iii)  $f_0 = 30\text{MHz}$ .
5. A lossless transmission line with characteristic impedance  $Z_0 = 50\Omega$  is terminated in a resistive load  $R_L > Z_0$ . A portion of the voltage standing-wave plot is shown below (dashed curve). (a) What is the standing-wave ratio on the line for the resistive termination (dashed curve)? (b) Determine  $R_L$ . (c) Determine the voltage magnitude of the incident wave,  $|V_0^+|$ . (d) Determine the wavelength on the line.

Now, the resistive load is replaced with unknown load impedance  $Z_T$  and the new standing-wave pattern is obtained (solid curve above). e) Determine the standing-wave ratio on the

line terminated in unknown load impedance  $Z_T = R_T + jX_T$  (solid curve). (f) Determine the unknown terminating impedance  $Z_T = R_T + jX_T$ .

