


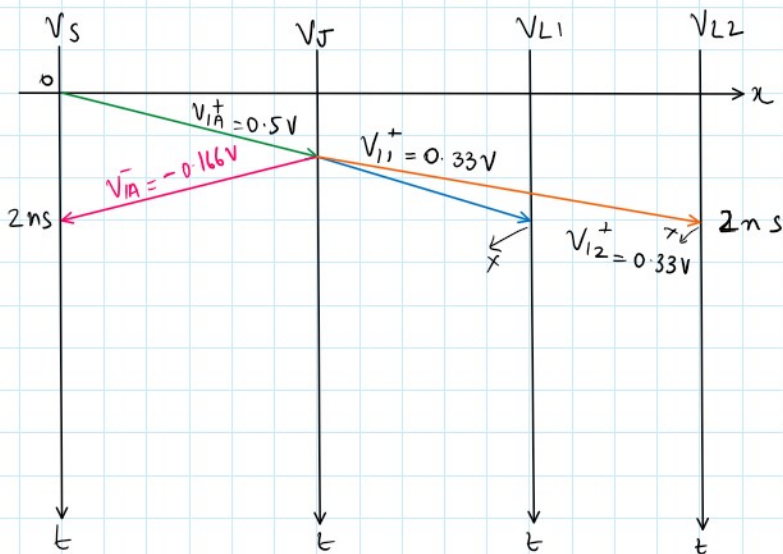
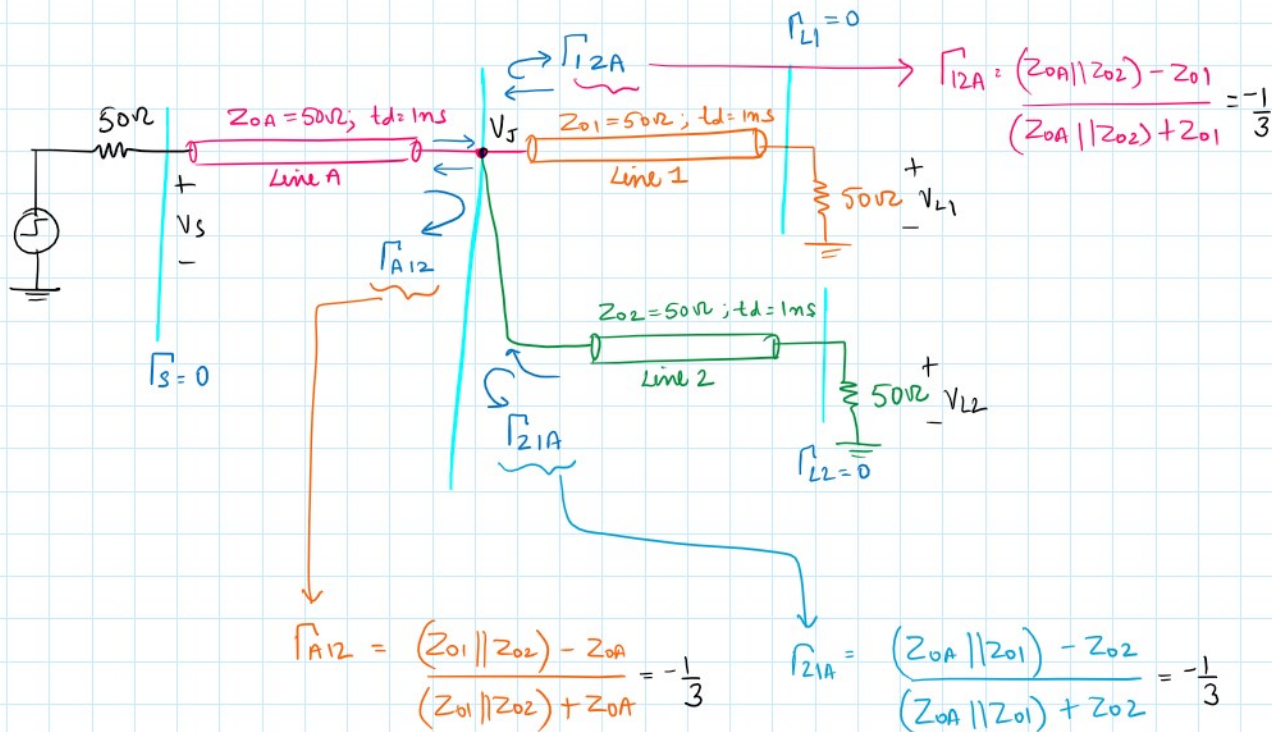
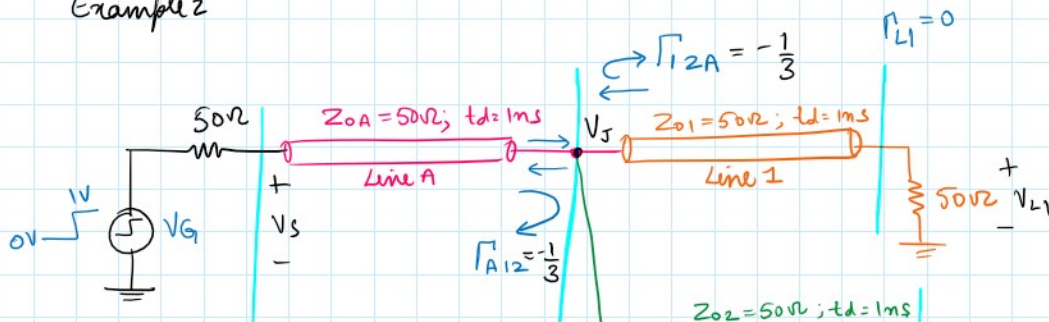


Three Parallel Transmission Lines

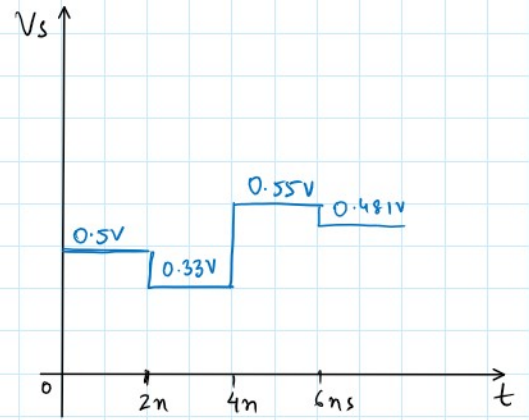

Example 2

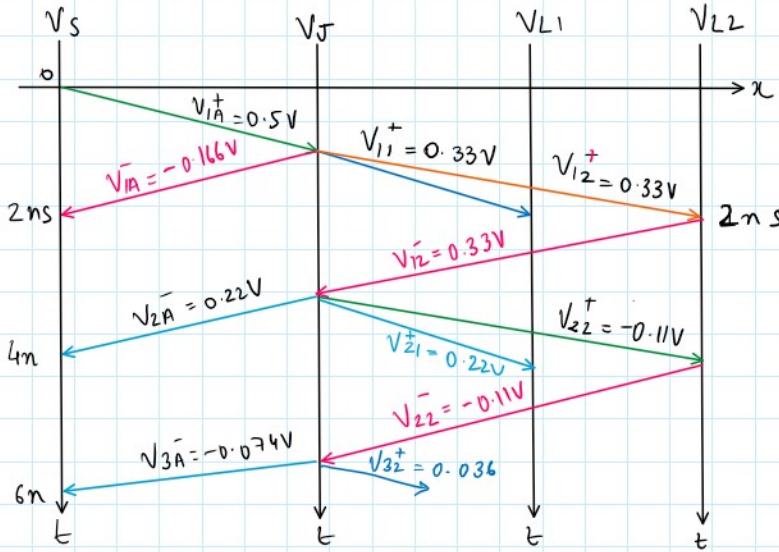

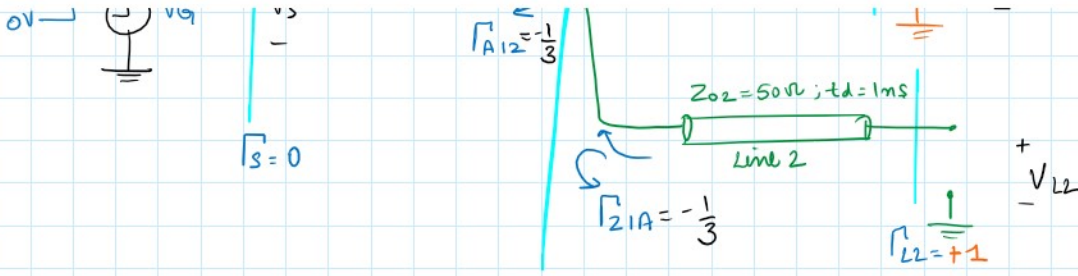


$V_s(t=\infty) = 0.5V$

Characteristic Impedance:

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

1) Coaxial Cable

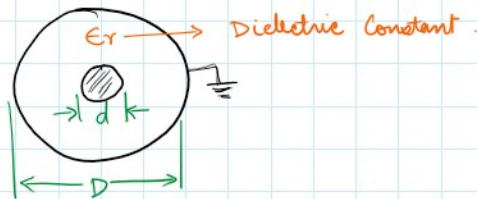

$$Z_0 = \frac{138}{\sqrt{\epsilon_r}} \log\left(\frac{D}{d}\right)$$

} many accurate ways to write  $Z_0$  }

Assume  $\epsilon_r = 4$

$$Z_0 = 69 \log\left(\frac{D}{d}\right)$$

Observations

- $\frac{D}{d}$  increases exponentially as  $Z_0$  increases.

$$\frac{D}{d} = 10^{Z_0/69}$$

a)  $Z_0 = 50 \Omega$  ;  $\frac{D}{d} = 5.3$

b)  $Z_0 = 75 \Omega$  ;  $\frac{D}{d} = 12.2$

c)  $Z_0 = 200 \Omega$  ;  $\frac{D}{d} \approx 800$

2)

### Two Wire Transmission Line



Dielectric is air

Ribbon cable  $\rightarrow$

$$Z_0 = \frac{276}{\sqrt{\epsilon_r}} \log\left(\frac{2D}{d}\right)$$

$$\epsilon_r = 1$$

$$Z_0 = 276 \log\left(\frac{2D}{d}\right)$$

•  $D$  can be as small as  $d$



This is the limit of  $Z_{0 \min}$

$$Z_{0 \min} = 276 \log(2)$$

a)  $Z_{0 \min} = 83 \Omega$

b)  $D/d = 5$   
 $Z_0 = 276 \Omega$

Observation: Two wire transmission lines can have higher characteristic impedance.