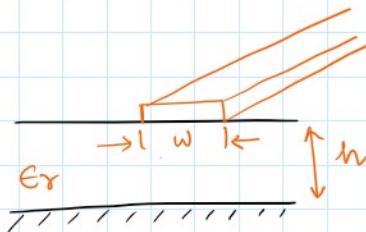


Characteristic Impedance cont...




3) Microstrip Line



$$Z_0 = \frac{377}{\sqrt{\epsilon_r} ((w/h) + 2)}$$

↑


Discontinuity / Reflections in a PCB trace.

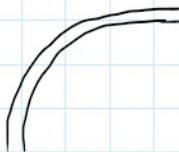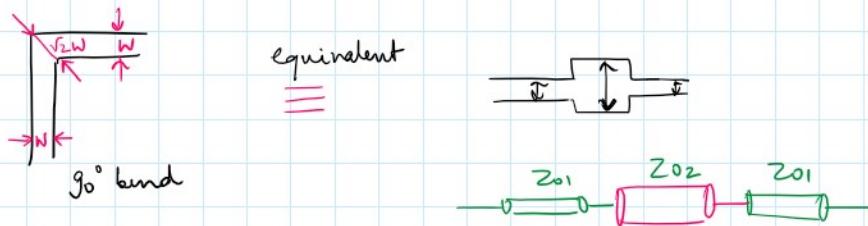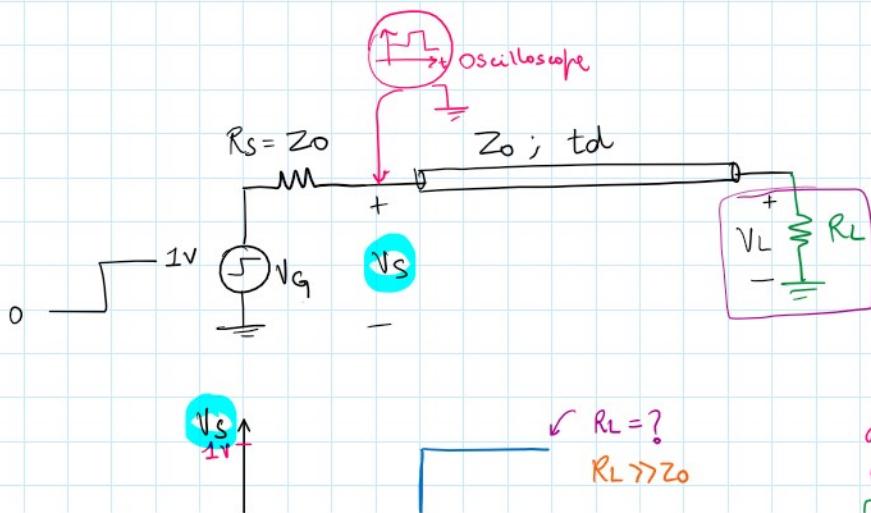Observations on a Transmission Line with different resistive termination


How to know the load by observing the voltage V_s.

$$\frac{R_L - Z_0}{R_L + Z_0}$$


- a) $R_L < Z_0 \rightarrow |V_s| < 0$
b) $R_L > Z_0 \rightarrow |V_s| > 1$
c) $R_L \approx Z_0 \rightarrow |V_s| \approx 1$

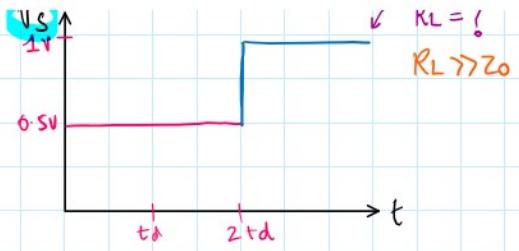

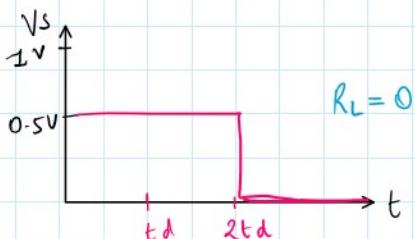- a) $K_L < Z_0 \rightarrow I_L < 0$
 - b) $R_L > Z_0$
 - c) $R_L \gg Z_0 \rightarrow R_L \approx 1$
 - d) $R_L \approx 0 \rightarrow R_L = -1$
- \checkmark




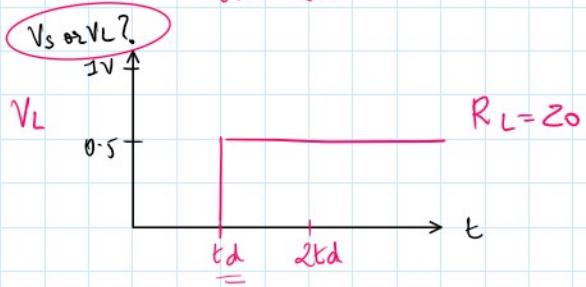- Reverse travelling wave will have a +ve amplitude.
- It will add on to the forward travelling wave




$$R_L = \frac{R_L - Z_0}{R_L + Z_0} \quad R_L = Z_0 \rightarrow R_L = 0$$

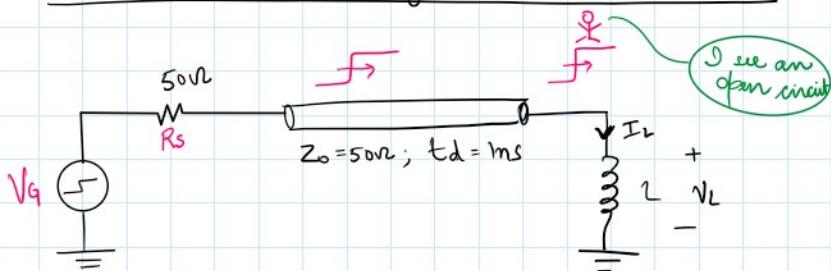Reactive Termination of Transmission Line



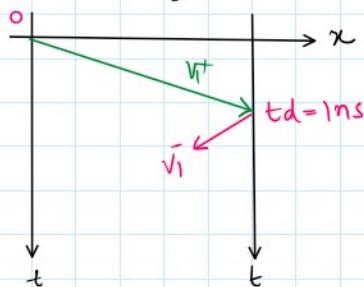- Inductor acts like an open circuit to the incident voltage.
- $R_L = 1 \rightarrow$ Voltage is double at load (instantaneously).
- Current in the inductor goes to zero.



$$V_1^+ = 0.5V$$

$$V_1^- = 0.5V \text{ } (@ t=t_d)$$

$$V_L(t) = L \frac{d}{dt} I_L(t)$$

$$\left. \begin{aligned} V_L(t) &= V_i^+(t) + V_i^-(t) \\ I_L(t) &= I_i^+(t) + I_i^-(t) \end{aligned} \right\}$$

$$I_i^+ = \frac{V_i^+}{Z_0}; \quad I_i^- = -\frac{V_i^-}{Z_0}$$

$$\left. \begin{aligned} I_L(t) &= \frac{V_i^+(t)}{Z_0} - \frac{V_i^-(t)}{Z_0} \end{aligned} \right\} \rightarrow \text{Because } V_i^+(t) = V_i^-(t) @ t = t_d \\ \Rightarrow I_L(t) &= 0 @ t = t_d \end{aligned}$$

$$V_i^+(t) + V_i^-(t) = L \left[\frac{d}{dt} \left(\frac{V_i^+(t)}{Z_0} - \frac{V_i^-(t)}{Z_0} \right) \right]$$

$$\left. \begin{aligned} V_i^+(t) + V_i^-(t) &= \frac{L}{Z_0} \frac{d}{dt} V_i^+(t) - \frac{L}{Z_0} \frac{d}{dt} V_i^-(t) \end{aligned} \right\}$$

$$\left. \begin{aligned} V_i^+(t) &= \text{Constant} = \left(\frac{Z_0}{Z_0 + R_S} \right) V_0 \end{aligned} \right\} \rightarrow V_0$$

$$\frac{dV_i^+(t)}{dt} = 0$$

$$\left. \begin{aligned} \frac{dV_i^-(t)}{dt} + \frac{Z_0}{L} V_i^-(t) + \frac{Z_0}{L} V_0 &= 0 \end{aligned} \right\}$$

$$V_i^-(t) = -V_0 + K e^{-(Z_0/L)(t-t_d)}$$

↓
Integration constant

$$\text{Boundary condition} \rightarrow @ t = t_d \\ V_i^-(t) = V_0 = V_i^+(t),$$

$$K = 2V_0$$

$$\boxed{\begin{aligned} V_i^-(t) &= -V_0 + 2V_0 e^{-(Z_0/L)(t-t_d)} \\ V_L(t) &= 2V_0 e^{-(Z_0/L)(t-t_d)} \end{aligned}}$$

