
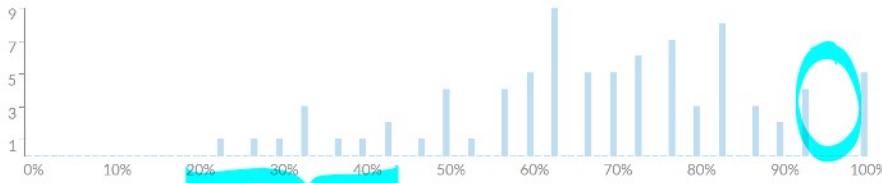


- HW #3 will be posted today.
- Bonus points - 3

Average Score	High Score	Low Score	Standard Deviation	Average Time
69% / 30	100%	23%	5.49	48:59

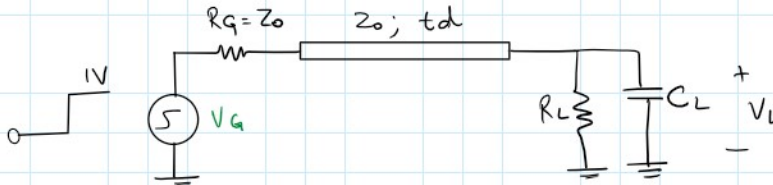

Termination with a lossy capacitor.



Discharged capacitor acts like a short circuit.
 $\Gamma = -1$ at the instant of incident wave.

$$V_L(t) = V_i^+(t) + V_i^-(t)$$

$$I_L(t) = I_i^+(t) + I_i^-(t)$$

$$I_L(t) = \frac{V_i^+(t)}{Z_0} - \frac{V_i^-(t)}{Z_0}$$

$$I_L(t) = \frac{V_L(t)}{R} + C \frac{dV_L(t)}{dt}$$

$$V_i^- = -V_i^+ \text{ at } t = td$$

$$I_i^- = -\frac{V_i^-}{Z_0}$$

$$\frac{V_i^+(t)}{Z_0} - \frac{V_i^-(t)}{Z_0} = \frac{V_i^+(t)}{R_L} + \frac{V_i^-(t)}{R_L} + C \frac{dV_i^-(t)}{dt} \quad ; \quad \begin{cases} C \frac{dV_i^+(t)}{dt} = 0 \\ V_i^+(t) = \frac{V_G}{2} \end{cases}$$

$$\frac{dV_i^-(t)}{dt} + \left[\frac{R_L + Z_0}{Z_0 R_L} \right] V_i^-(t) - \left[\frac{R_L - Z_0}{Z_0 R_L} \right] V_i^+(t) = 0$$

$\downarrow V_G/2$

$$V_i^-(t) = K_1 + K_2 e^{-[(R_L + Z_0) / R_L Z_0 C] (t - td)}$$

K_1 & K_2 are integration constants. Can be calculated from the boundary conditions.


1. At $t = t_d$ $V_i^- = -V_i^+ = -V_g/2$

2. At $t \rightarrow \infty$ $V_i^- = \left(\frac{R_L - Z_0}{R_L + Z_0} \right) \cdot V_i^+$

$$V_i^-(t) = V_i^+(t) \left[\frac{R_L - Z_0}{R_L + Z_0} - \frac{2 R_L}{R_L + Z_0} e^{-[(R_L + Z_0) / R_L Z_0 C_L] (t - t_d)} \right]$$

$$V_L(t) = V_i^-(t) + V_i^+(t)$$
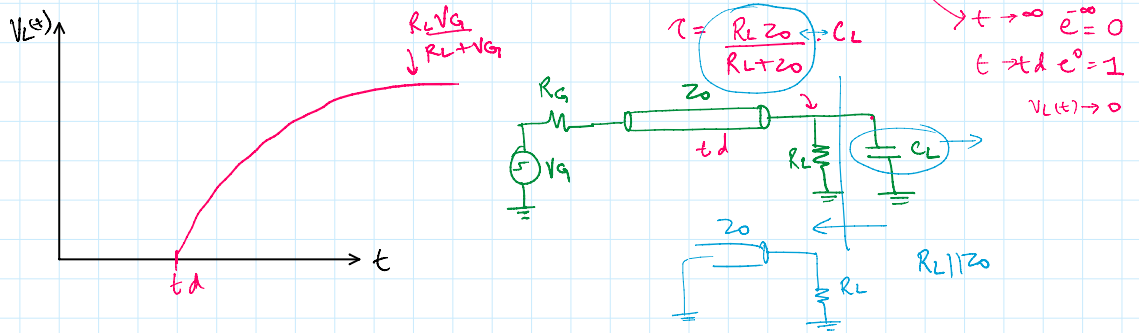
$$V_L(t) = \frac{R_L V_g}{R_L + Z_0} \left[1 - e^{-[(R_L + Z_0) / R_L Z_0 C_L] (t - t_d)} \right]$$



Measuring Bond Wire Inductance

