

Open Circuit Transmission Line - Standing Wave Pattern.

$$V(l) = V^+ e^{j\beta l} + V^- e^{-j\beta l}$$


$$I(l) = \frac{V^+}{Z_0} e^{j\beta l} - \frac{V^-}{Z_0} e^{-j\beta l}$$

Open circuit $V^- = V^+$ $\{ I_l = 1 \}$


$$V(l) = 2V^+ \cos(\beta l)$$

$$I(l) = j \frac{2V^+}{Z_0} \sin(\beta l)$$

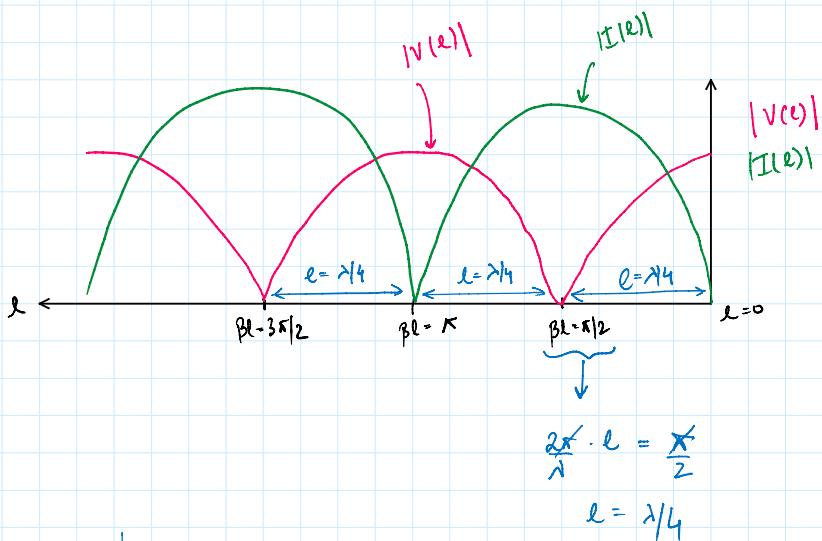
$$Z(l) = \frac{V(l)}{I(l)} = -j Z_0 \cot(\beta l)$$



Note :
Point of $|V(l)|_{\max}$ = Point of $|I(l)|_{\min}$

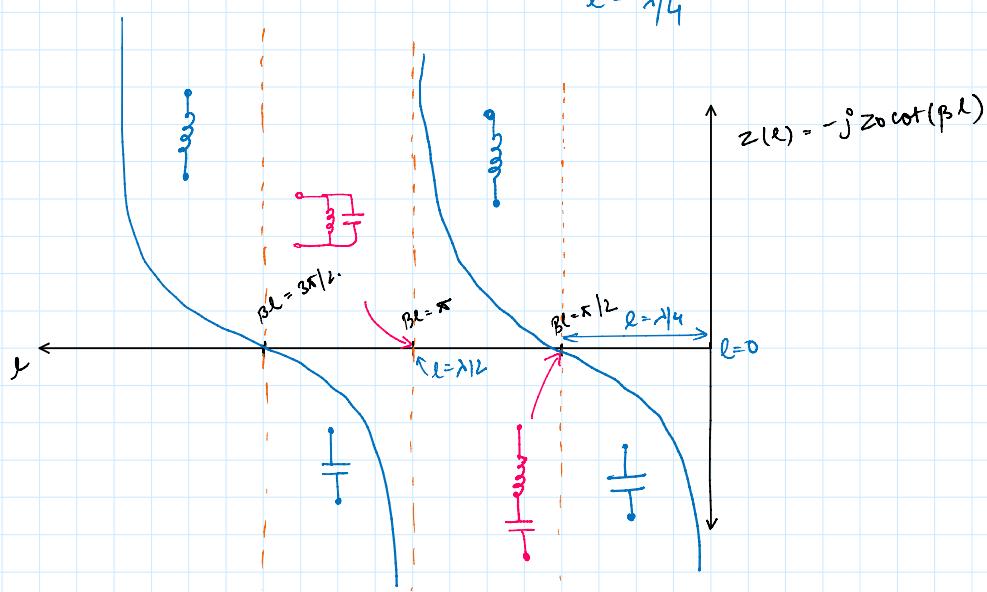

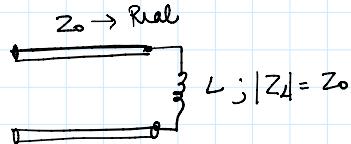
$$\begin{aligned} \bullet & \quad 0 \leq l < \lambda/4 \quad \equiv \quad \frac{1}{T} \\ \bullet & \quad \frac{\lambda}{4} < l < \frac{\lambda}{2} \quad \equiv \quad \text{---} \\ \bullet & \quad \frac{\lambda}{2} < l < 3\lambda/4 \quad \equiv \quad \frac{1}{T} \\ & \quad \vdots \end{aligned}$$



$$|\Gamma_L| = 1 \quad \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{j\omega L - Z_0}{j\omega L + Z_0}$$

$$\left| \frac{a - jb}{a + jb} \right| = ? \quad ?$$

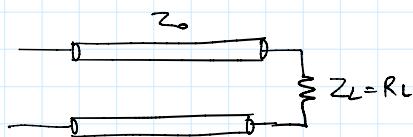Voltage & Current Standing Wave on a Pure Resistive Load



$$V(r) = V^+ e^{j\beta r} (1 + |\Gamma_L| e^{j(\phi_L - 2\beta r)})$$

$$I(r) = \frac{V^+}{Z_0} e^{j\beta r} (1 - |\Gamma_L| e^{j(\phi_L - 2\beta r)})$$

$Z_L = R_L \rightarrow$ Pure Resistive
 $Z_0 \rightarrow$ Real (lossless line) } $\Rightarrow \Gamma_L = \text{Real}$
 $\phi_L = 0$

$$V(r) = V^+ e^{j\beta r} (1 + \Gamma_L e^{-j2\beta r})$$

$$I(r) = \frac{V^+}{Z_0} e^{j\beta r} (1 - \Gamma_L e^{-j2\beta r})$$


$l=0$
(at the load)

\rightarrow

$$V(l) = V^+ (1 + \Gamma_L)$$

$$I(l) = \frac{V^+}{Z_0} (1 - \Gamma_L)$$

$$V(l) = V^+ (1 + \Gamma_L)$$

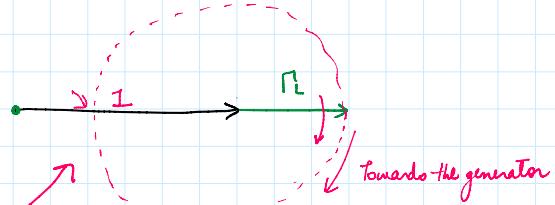


Case 1 : $R_L > Z_0$; $\Gamma_L > 0$

$V(l)$ is maximum at the load.

$I(l)$ is minimum at the load

Observations

- As $l \uparrow$ $V(l)$ reduces + $I(l)$ increases.
- $|V(l)|$ does not go to 0 because $|\Gamma_L| < 1$
- ρ (VSWR) is not infinite.

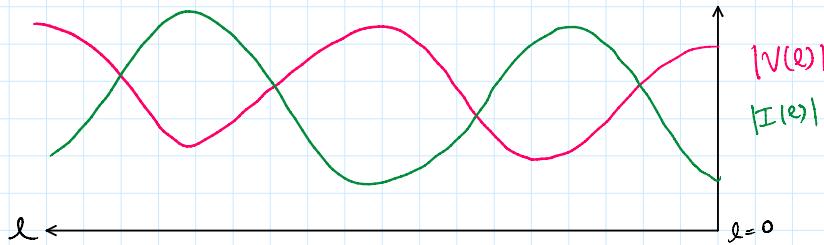

Case 2 : $R_L < Z_0$; $\Gamma_L < 0$

@ $l=0$ $V(l)$ is minimum
 $I(l)$ is minimum.

