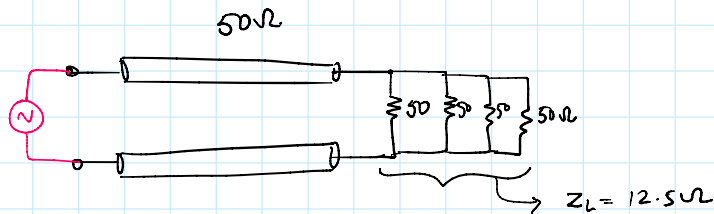


HW#4 has been posted

Example 1: Resistive Load



$$(a) \quad \Gamma_L = \frac{12.5 - 50}{12.5 + 50} = -0.6 = 0.6 e^{j\pi}$$


(b) Calculate V_{max} , V_{min} , I_{max} , I_{min} ; Assume $V^+ = 1V$

$$V_{max} = |V^+|_{max} = |V^+| (1 + |\Gamma_L|) = 1.6V$$

$$V_{min} = |V^+| (1 - |\Gamma_L|) = 0.4V$$

$$I_{max} = \frac{|V^+|}{Z_0} (1 + |\Gamma_L|) = \frac{1.6}{50} = 32mA$$

$$I_{min} = \frac{|V^+|}{Z_0} (1 - |\Gamma_L|) = \frac{0.4}{50} = 8mA$$

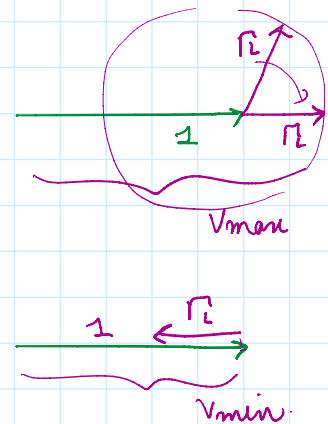

(c) Sketch $|V(l)|$ & $|I(l)|$ as a function of l/λ starting with $l=0$

$$V(l) = V^+ e^{j\beta l} (1 + |\Gamma_L| e^{j(\phi_L - 2\beta l)})$$

$$\Rightarrow I(l) = \frac{V^+ e^{j\beta l}}{Z_0} (1 - |\Gamma_L| e^{j(\phi_L - 2\beta l)})$$

$$V(l) = 1 \cdot e^{j \frac{2\pi}{\lambda} \cdot l} (1 + 0.6 e^{j(\pi - 2 \cdot \frac{2\pi}{\lambda} l)})$$

$$|V(\ell)| = 1 \left| \left(1 + 0.6 e^{j\pi(1-4\ell/\lambda)} \right) \right|$$


$$|V(\ell)| = 1 + 0.6 \left\{ \cos[\pi(1-4\ell/\lambda)] + j \sin[\pi(1-4\ell/\lambda)] \right\}$$

$$\frac{\ell}{\lambda} = 0 \Rightarrow |V(\ell)| = 0.4 \text{ V} \quad V_{\min}$$

$$\frac{\ell}{\lambda} = \frac{1}{4} \rightarrow \ell = \frac{\lambda}{4} \Rightarrow |V(\ell)| = 1.6 \text{ V} \quad V_{\max}$$

$$\frac{\ell}{\lambda} = \frac{1}{2} \Rightarrow |V(\ell)| = 0.4 \text{ V} \quad V_{\min}$$

$$\frac{\ell}{\lambda} = \frac{3}{4} \Rightarrow |V(\ell)| = 1.6 \text{ V} \quad V_{\max}$$

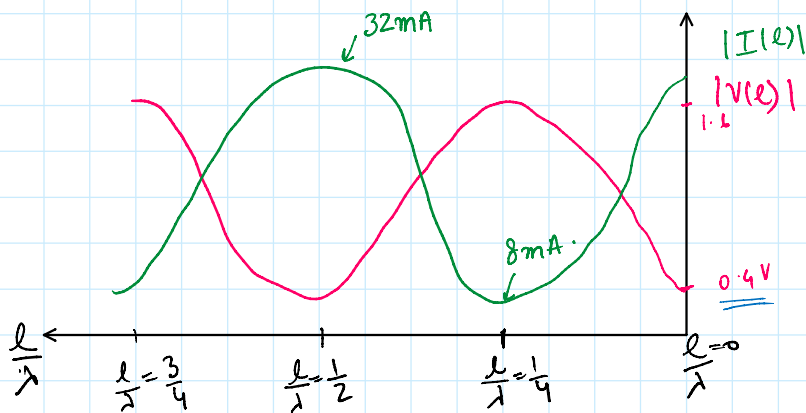

Example 2:

Transmission Line as Circuit Component.

$$v_p = 2.07 \times 10^8 \text{ m/s}$$

$$Z_0 = 50 \Omega$$

- (a) • We want 15 nH of inductance with minimum length for a short circuited line @ 3 GHz.


$$Z_{sc} = Z(l) = j Z_0 \tan(\beta l)$$

\downarrow
 15 nH

$$j 2\pi \cdot 3 \times 10^9 \times 15 \times 10^{-9} = j 50 \tan\left(\frac{2\pi}{\lambda} \cdot l\right)$$

\uparrow unknown
 v, f, λ
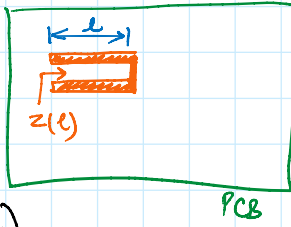
$$\frac{2.07 \times 10^8}{3 \times 10^9} = \frac{v}{f} = \lambda$$



$$l = \frac{\lambda}{2\pi} \tan^{-1}\left(\frac{2\pi \times 3 \times 10^9 \times 15 \times 10^{-9}}{50}\right)$$

$l = 1.53 \text{ cm}$

(b) What happens to the impedance at $f = 4 \text{ GHz}$ for transmission line trace of $l = 1.53 \text{ cm}$?

$$Z_{sc} = j Z_0 \tan(\beta l)$$

\uparrow 1.53 cm
 \downarrow
 $\frac{2\pi}{\lambda} \rightarrow \frac{2.07 \times 10^8}{4 \times 10^9} = 5.175 \text{ cm.}$

-ve sign


$$Z_{sc} = -j 167.4 \Omega = \frac{1}{j \omega C}$$


\downarrow
 $2\pi f$
 \downarrow
 4×10^9

$C = 0.238 \text{ pF}$


Transmission line acts like a capacitor @ 4 GHz.

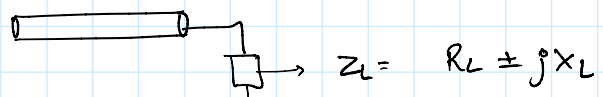Voltage & Current Standing Wave on a Complex Load.



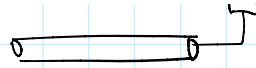

1. Case I Inductive Load

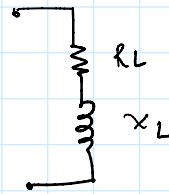

$$\Gamma_L = \frac{R_L - Z_0 + jX_L}{R_L + Z_0 + jX_L}$$

$R_L = 0 ; X_L = Z_0$

$|\Gamma_L| = ? = 1$

$\angle \Gamma_L = ? =$