
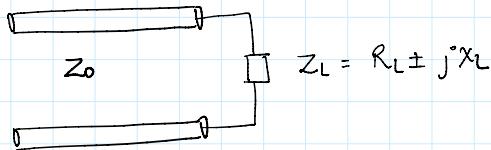


Voltage and Current Standing Wave Pattern on a Complex Load

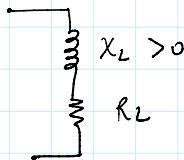

Case 1: Inductive Load -



$$\underline{\Gamma}_L = \frac{R_L + jX_L - Z_0}{R_L + jX_L + Z_0}$$

Magnitude and phase of $\underline{\Gamma}_L$

a) $R_L = 0$ $X_L = Z_0$ \rightarrow purely inductive load

$$\rightarrow |\underline{\Gamma}_L| = 1$$

$$\phi_L = \angle \underline{\Gamma}_L = X_L = Z_0$$


$$\underline{\Gamma}_L = \frac{jX_L - Z_0}{jX_L + Z_0} \rightarrow \frac{j-1}{j+1} = \frac{\angle(j-1)}{\angle(j+1)} = \begin{cases} 135^\circ \\ 45^\circ \end{cases}$$

$$\angle \underline{\Gamma}_L = 90^\circ$$

b) $R_L = 0$ $X_L \gg Z_0$


$$|\underline{\Gamma}_L| = 1$$
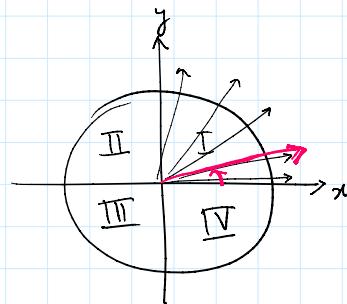
$$\phi_L = \angle \underline{\Gamma}_L = \sim 0 \text{ close to } 0$$




$$\frac{a-jb}{a+jb} = \frac{re^{j\theta_1}}{ze^{j\theta_2}}$$
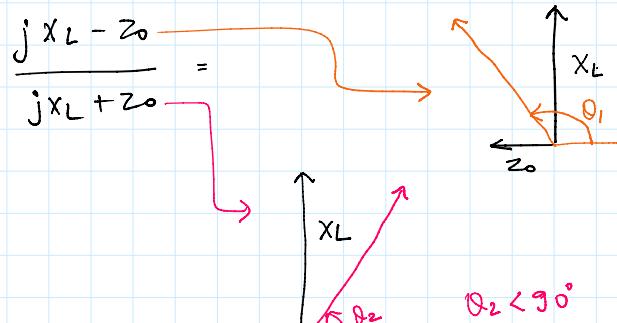
$$\begin{aligned} \cancel{z} & e^{j(\theta_1-\theta_2)} \\ z &= r \\ 1 & e^{j(\theta_1-\theta_2)} \end{aligned}$$



$$\theta_1 > 90^\circ$$

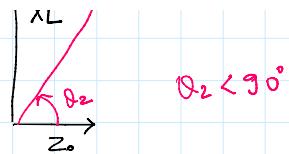

c) $R_L = 0 \quad X_L \ll Z_0$

$$|I_L| = 1$$


$$\phi_L = \angle I_L = \pi \text{ (close to } 180^\circ\text{).}$$

For inductive + resistive load $\pi < \angle I_L < 0$




$$V(l) = \underbrace{V^+ e^{j\beta l}}_{1} \left(1 + |I_L| e^{j(\phi_L - 2\beta l)} \right)$$

- $|I_L| < 1$ for $R_L > 0$

Voltage Phasor $l=0$

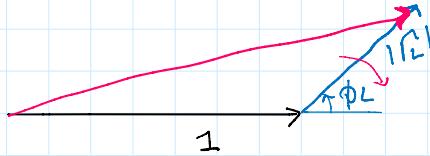


$l > 0$

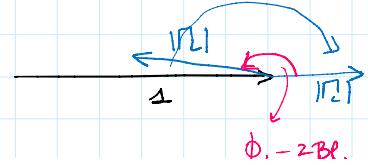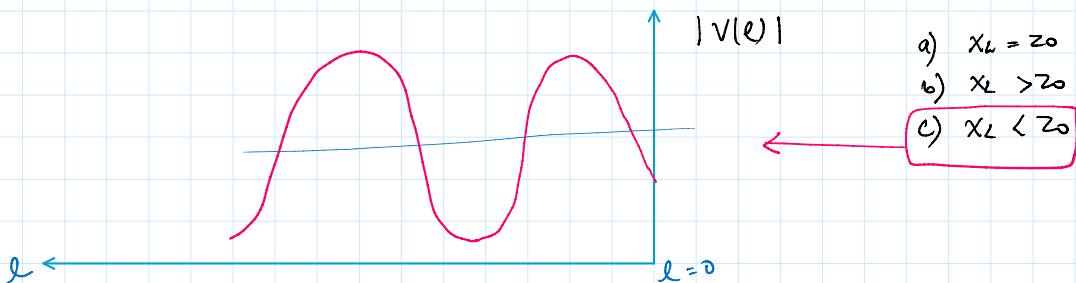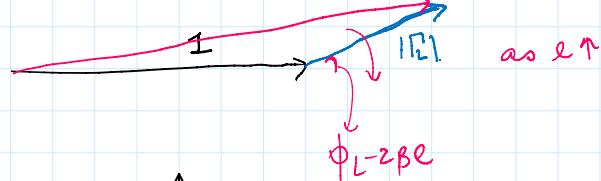



Case 2 : Capacitive Load.

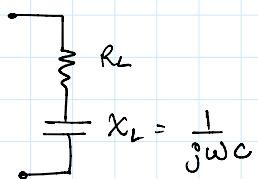


$$Z_L = \frac{R_L + jX_L - Z_0}{R_L - jX_L + Z_0}$$

a) $R_L = 0 \rightarrow$ Pure capacitance.

$$|X_L| = Z_0$$

$$|Z_L| = 1$$

$$\angle Z_L = ? - 90^\circ$$

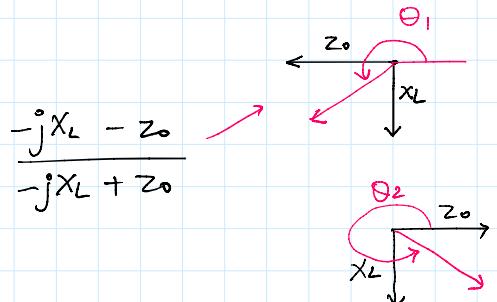


$-\pi < \angle Z_L < 0$ Capacitive load.


- Figure out $\angle Z_L$
- (b) $|X_L| > Z_0$
- (c) $|X_L| < Z_0$

Voltage Phasor


$$l=0$$

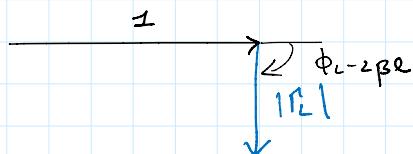

$$l>0$$

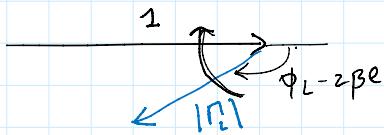

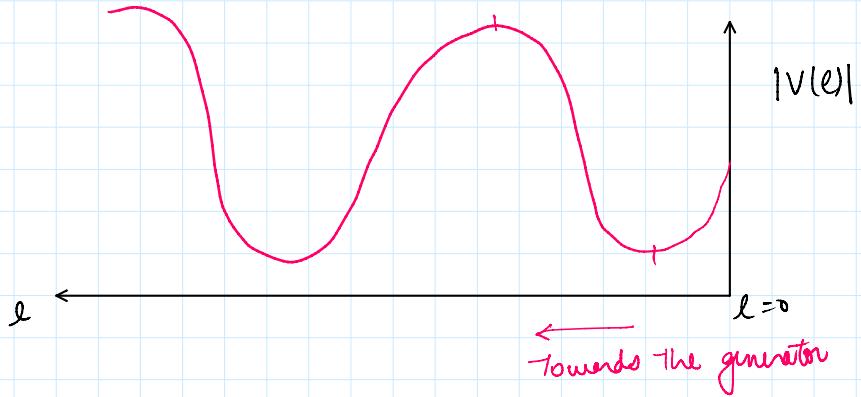
Observation : Magnitude of voltage will be minima first then it will be maxima as we go from load towards the generator.



Example :

$$Z_0 = 50\Omega$$

Z_L = Unknown.

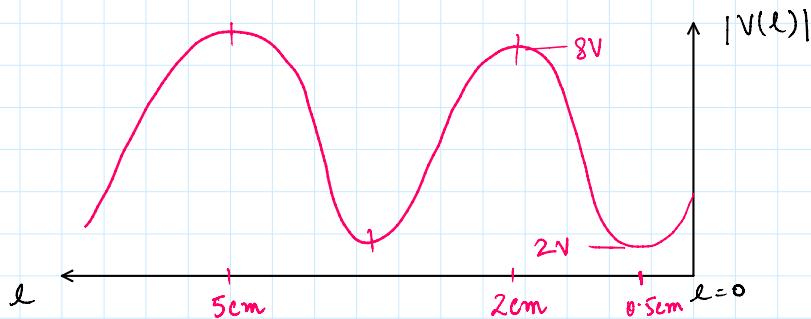

Q1: What is the VSWR ?

$$\text{g} = \text{VSWR} = \frac{|V|_{\max}}{|V|_{\min}} = \frac{8V}{2V} = 4$$

Q2: Wavelength on this transmission line

Distance between two voltage maxima or two voltage minima
 $= \frac{\lambda}{2}$

$$\frac{\lambda}{2} = 3\text{cm}$$

$$\lambda = 6\text{cm} .$$

Q3 : Calculate V^+