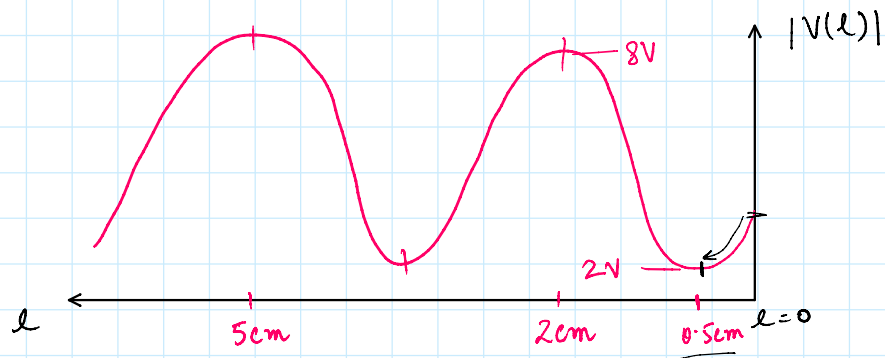


Example:

$$Z_0 = 50\Omega$$

$Z_L = \text{unknown.}$



Q1: What is the VSWR?

$$\rho = \text{VSWR} = \frac{|V|_{\max}}{|V|_{\min}} = \frac{8\text{V}}{2\text{V}} = 4$$

Q2: Wavelength on this transmission line

Distance between two voltage maxima or two voltage minima
 $= \frac{\lambda}{2}$

$$\frac{\lambda}{2} = 2\text{cm}$$

$$\lambda = 4\text{cm}$$

Q3: Calculate V^+

$$V_{\max} = V^+ (1 + |\Gamma_L|) = 8\text{V}$$

$$V_{\min} = V^+ (1 - |\Gamma_L|) = 2\text{V}$$

$$V^+ = ?$$

$$V^+ = \frac{V_{\max} + V_{\min}}{2} = \frac{8 + 2}{2} = 5\text{V}$$



$$V^+ = ? \quad V^+ = \frac{V_{\max} + V_{\min}}{2} = \frac{8+2}{2} = 5V$$

Q4: Calculate the magnitude & phase of the reflection coefficient

$$VSWR = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} = \rho$$

$$\frac{VSWR - 1}{VSWR + 1} = |\Gamma_L| = \frac{4 - 1}{4 + 1} = 0.6$$

Phase calculation:

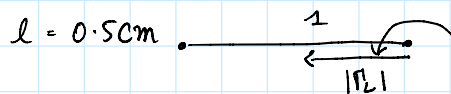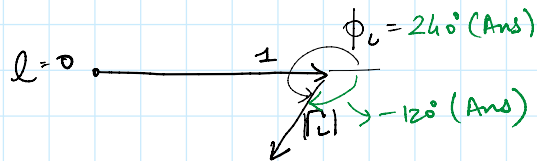

$$\phi_L - 2\beta l = \pi \text{ @ } l = 0.5 \text{ cm}$$

$$\phi_L - 2\beta l = \pi$$

$$\phi_L - 2 \cdot \frac{2\pi}{\lambda} \cdot l = \pi$$

$$\phi_L - 2 \cdot \frac{2\pi}{63} \times 0.5 = \pi$$

$$\phi_L = \pi + \frac{\pi}{3} = \frac{4\pi}{3}$$


$$\phi_L = 180^\circ + 60^\circ = 240^\circ = -120^\circ$$

Q5: Calculate I_{\max} , I_{\min} .

$$I_{\max} = \frac{V_{\max}}{Z_0} = \frac{8V}{50\Omega} = 160 \text{ mA}$$

$$I_{\min} = \frac{V_{\min}}{Z_0} = \frac{2}{50} = 40 \text{ mA}$$

Q6 What type of load is this?

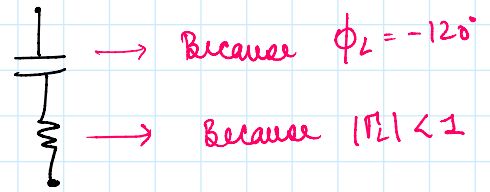


Impedance Transformation Relation & Quarter Wavelength Matching

$$V(l) = V^+ e^{\gamma l} + V^- e^{-\gamma l}$$

$$I(l) = \frac{V^+}{Z_0} e^{\gamma l} - \frac{V^-}{Z_0} e^{-\gamma l}$$
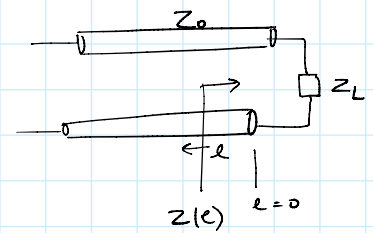
$$Z(l) = \frac{V(l)}{I(l)} = Z_0 \left\{ \frac{1 + \frac{V^-}{V^+} e^{-2\gamma l}}{1 - \frac{V^-}{V^+} e^{-2\gamma l}} \right\}$$



$$Z(l) = Z_0 \left\{ \frac{1 + \Gamma_L e^{-2\gamma l}}{1 - \Gamma_L e^{-2\gamma l}} \right\}$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$Z(l) = Z_0 \left\{ \frac{1 + \frac{Z_L - Z_0}{Z_L + Z_0} e^{-2\gamma l}}{1 - \frac{Z_L - Z_0}{Z_L + Z_0} e^{-2\gamma l}} \right\}$$

$$Z(l) = Z_0 \left\{ \frac{Z_L \cosh \gamma l + Z_0 \sinh \gamma l}{Z_0 \cosh \gamma l + Z_L \sinh \gamma l} \right\}$$

$$\cosh \gamma l = \frac{e^{\gamma l} + e^{-\gamma l}}{2}$$

$$\sinh \gamma l = \frac{e^{\gamma l} - e^{-\gamma l}}{2}$$

Normalized Impedance

$$\bar{Z}(l) = \frac{Z(l)}{Z_0}$$

$$\bar{Z}(l) = \frac{\bar{Z}_L \cosh \gamma l + \sinh \gamma l}{\cosh \gamma l + \bar{Z}_L \sinh \gamma l}$$

For a lossless line $\gamma = j\beta$ ($\alpha = 0$)

$$\cosh(j\beta l) = \cos \beta l$$

$$\sinh(j\beta l) = j \sin \beta l$$

$$\bar{Z}(l) = \frac{\bar{Z}_L \cos \beta l + j \sin \beta l}{\cos \beta l + j \bar{Z}_L \sin \beta l}$$