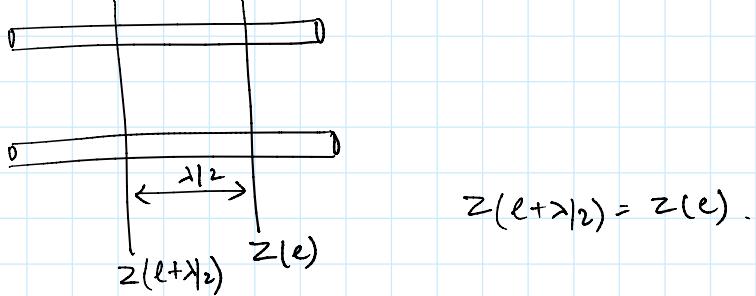


## 1. Characteristics of Impedance on a Loss Less Line.

### Observation.

\* Impedance value repeats after every  $\lambda/2$  distance on the transmission line.



Let at a location  $l$ , the impedance is  $Z(l)$

$$\bar{Z}(l) = \frac{\bar{Z}_L \cos \beta l + j \sin \beta l}{\cos \beta l + j \bar{Z}_L \sin \beta l}$$

$$\bar{Z}(l+\lambda/2) = \frac{\bar{Z}_L \cos \beta(l+\lambda/2) + j \sin \beta(l+\lambda/2)}{\cos \beta(l+\lambda/2) + j \bar{Z}_L \sin \beta(l+\lambda/2)}$$

$$\beta(l+\lambda/2) = \frac{2\pi}{\lambda} (l+\lambda/2) = \beta l + \pi$$

$$\begin{aligned} \cos \beta(l+\lambda/2) &= \cos(\beta l + \pi) = -\cos \beta l \\ \sin \beta(l+\lambda/2) &= \sin(\beta l + \pi) = -\sin \beta l \end{aligned}$$

$$\boxed{\bar{Z}(l+\lambda/2) = \frac{j \bar{Z}_L \cos \beta l + j \sin \beta l}{\cos \beta l + j \bar{Z}_L \sin \beta l} = \bar{Z}(l)}$$

## 2. Impedance at a distance of $\lambda/4$

### Observation

\* Normalized Impedance inverts itself at every  $\lambda/4$ .

$$\bar{Z}(l+\lambda/4) = \frac{1}{\bar{Z}(l)}$$

$$\beta(l+\lambda/4) = \beta l + \frac{2\pi}{\lambda} \cdot \frac{\lambda}{4} = \beta l + \frac{\pi}{2}$$

$$\cos(\beta l + \frac{\pi}{2}) = -\sin \beta l$$

$$\sin(\beta l + \frac{\pi}{2}) = \cos \beta l$$

$$\bar{Z}(l+\lambda/4) = \frac{-\bar{Z}_L \sin \beta l + j \cos \beta l}{-\sin \beta l + j \bar{Z}_L \cos \beta l}$$

take  $j$  common from  $N^r L^d$

$$= \frac{j}{j} \left\{ \frac{\cos \beta l + j \bar{Z}_L \sin \beta l}{\bar{Z}_L \cos \beta l + j \sin \beta l} \right\}$$

$$\boxed{\bar{Z}(l+\lambda/4) = \frac{1}{\bar{Z}(l)}}$$

3.

Matched transmission line.



$$Z_L = Z_0 \Rightarrow \bar{Z}_L = \frac{Z_L}{Z_0} = 1$$

$$\bar{Z}(l) = \left\{ \frac{\cos \beta l + j \sin \beta l}{\cos \beta l + j \sin \beta l} \right\} = 1$$

Observation :


If the line is terminated with the characteristic impedance, then impedance seen at any point on the transmission line is equal to the characteristic impedance.

$$\bar{Z}(l) = 1$$

$$\frac{Z(L)}{Z_0} = 1$$

$$Z(l) = Z_0.$$

### Quarter Wave Transformer Matching.

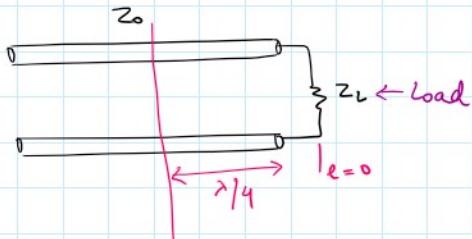

$$\bar{Z}(l) = \frac{1}{\bar{Z}_L}$$

$$\frac{Z(l)}{Z_0} = \frac{Z_0}{Z_L}$$



$$\boxed{l = \lambda/4 \quad Z(\lambda/4) = \frac{Z_0^2}{Z_L}}$$

$$\begin{aligned} Z(l=0) &= Z_L \\ Z(l=0) &= Z_L @ l=0 \end{aligned}$$

$\bar{Z}$  = normalize

$$Q: \text{What is } Z(\frac{3\lambda}{4})? = \frac{Z_0^2}{Z_L}$$
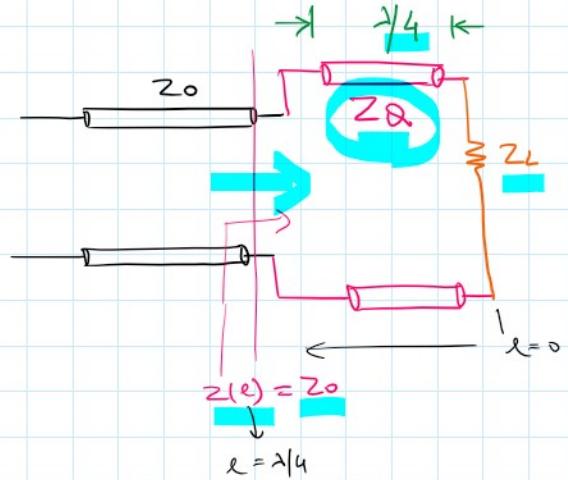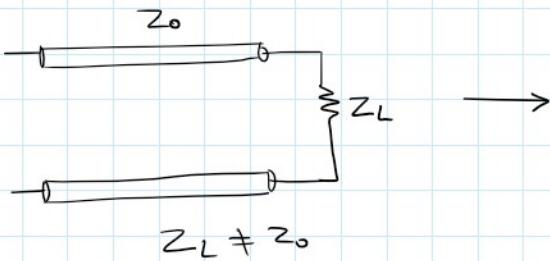
$$Q: \text{What is } Z(\lambda/2)? = Z_L$$





$$Z(\lambda/4) = Z_0 = \frac{Z_0^2}{Z_L}$$

Goal  $\rightarrow$  To estimate  $Z_0$  to achieve quarter wave transformer.

$$\boxed{Z_0 = \sqrt{Z_0 \cdot Z_L}}$$

Example 1 Resistive Load.

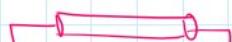

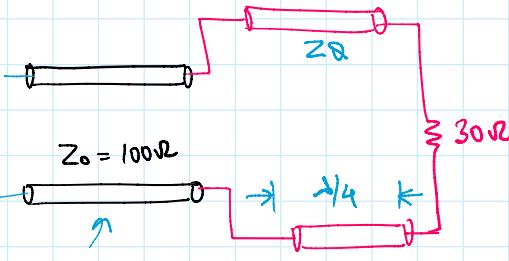

$$Z_0 = ?$$

$$Z_0 = \sqrt{30 \times 100} = 54.77\Omega$$

### Example 2 Complex Load.


$$Z_L = 73 + j42.5\Omega$$

$$Z_0 = 100\Omega$$

Q: Where to insert the quarter wave Transformer?


Q: What will be the  $Z_0$ ?

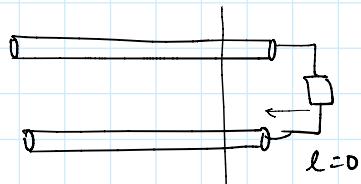Find a length / point on a line away from your load such that  $Z(e)$  is real at that point



$$Z(e) = \text{real} = \frac{V(e)}{I(e)} \quad \text{when } \angle \Gamma_i = 0^\circ \text{ or } 180^\circ$$
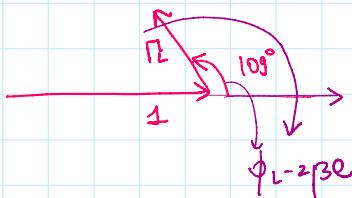
$$\Gamma_L = \frac{73 + j42.5 - 100}{73 + j42.5 + 100} = 0.283 e^{j105^\circ}$$



Estimate  $l$  for maxima in  $|V(e)|$  & minima in  $|I(e)|$  or vice versa


$$\phi_L - 2\beta L = 0$$

$105^\circ$

$$105 \times \frac{2\pi}{360} - \frac{22\pi}{\lambda} \cdot l = 0$$

$$l = 0.151\lambda$$

Invert the quarter wave Transformer here

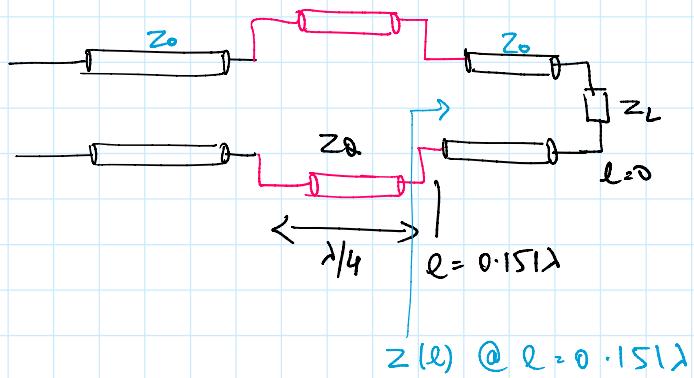

$$\bar{Z}(l) = \frac{\bar{Z}_L + j \tan(\beta l)}{1 + j \bar{Z}_L \tan(\beta l)}$$

$$\bar{Z}(l) = 1.79$$

$$Z(l) = 179 \Omega \text{ @ } l = 0.151\lambda$$

$$Z_0 = \sqrt{179 \Omega \times 100} = 183.7 \Omega$$