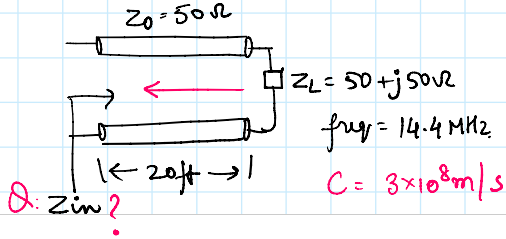


# Smith Chart-5


Friday, May 22, 2020 8:21 AM

- HW #5 is due tomorrow
- Extra office hours - Monday - 1:30pm - 2:30pm

Example 4:




## Smith Chart

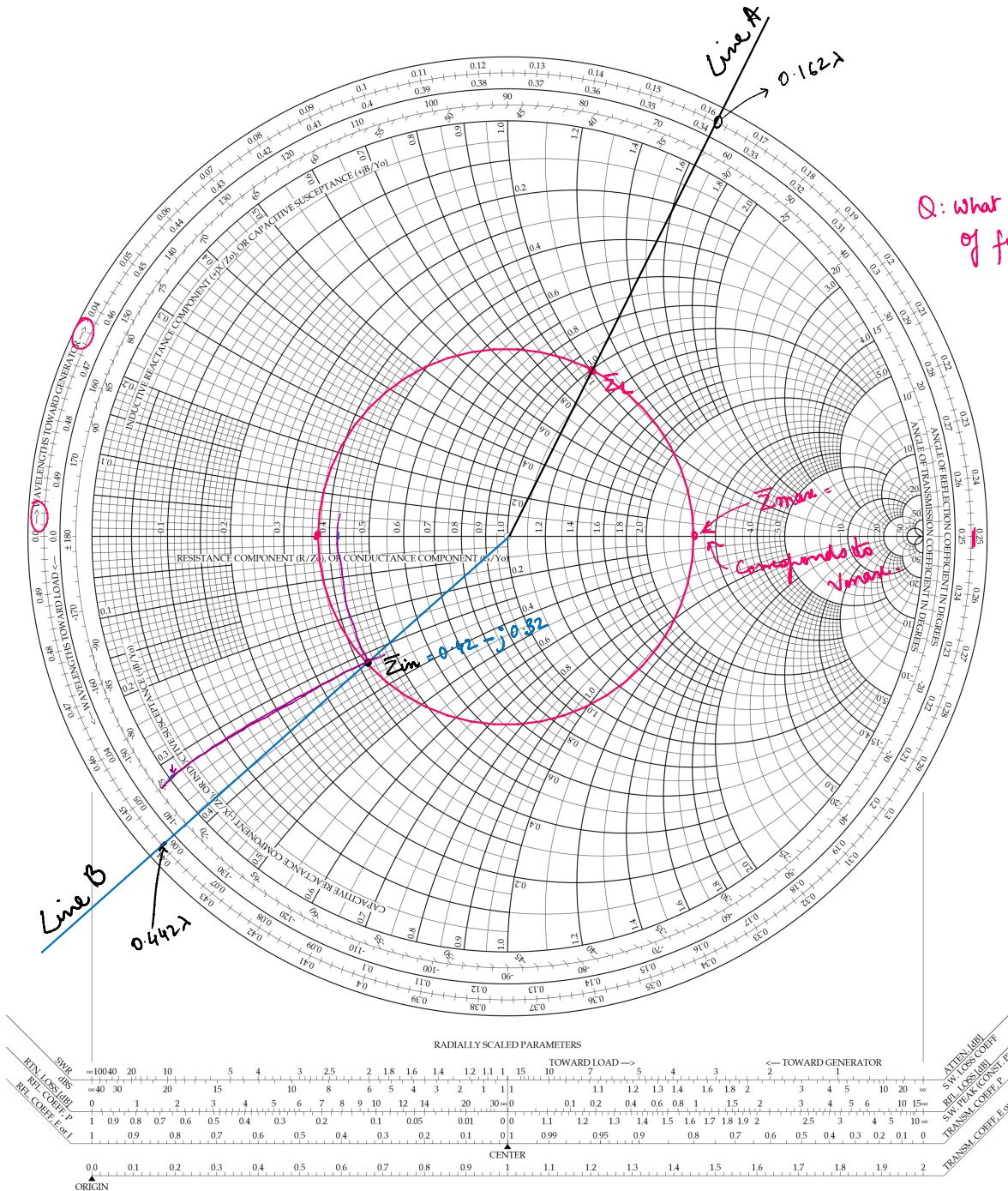

Q: what is the distance of first  $V_{max}$  from the load?

$$Z_{max} = \frac{V_{max}}{I_{min}}$$

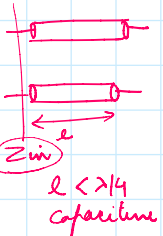

Step 1:  $\bar{Z}_L = \frac{50 + j50}{50} = 1 + j$  Mark on Smith Chart

Step 2: Calculate the electrical length of the transmission line.

$$\text{length (meters)} = 20 \text{ ft} \times \frac{0.304 \text{ m}}{\text{ft}} \approx 6.096 \text{ m}$$

$$\lambda = \frac{c}{f} = \frac{3 \times 10^8}{14.4 \times 10^6} = 21.276 \text{ m}$$

$$\text{length } (\lambda) = \frac{6.096 \text{ m}}{21.276 \text{ m}} \approx 0.28 \lambda$$

Step 3: Find the starting point (in  $\lambda$ ) on the Smith Chart = 0.162  $\lambda$

Step 4: Go clockwise (Towards Generator) by 0.28  $\lambda$

Final point (in  $\lambda$ ) on the Smith Chart = 0.442  $\lambda$

Step 5: Intersection of Line B & VSWR circle is  $\bar{Z}_{in} = 0.42 - j0.32$

Step 6:  $Z_{in} = 50(0.42 - j0.32) \Omega$

$$Z_{in} = 21 - j16 \Omega$$