

$$\text{Power loss (dBs)} = -20 \log(e^{-\alpha x})$$

$$\text{Power loss (dBs)} = +20 \alpha x \log(e)$$


$$x=1 ; \alpha=1$$

$$= 8.68 \text{ dB} \quad \left. \right\} \rightarrow \alpha = 1 \text{ neper/m}$$

Example

$$17.36 \text{ dB} \rightarrow \alpha = 2 \text{ neper/m}$$

Example 2:

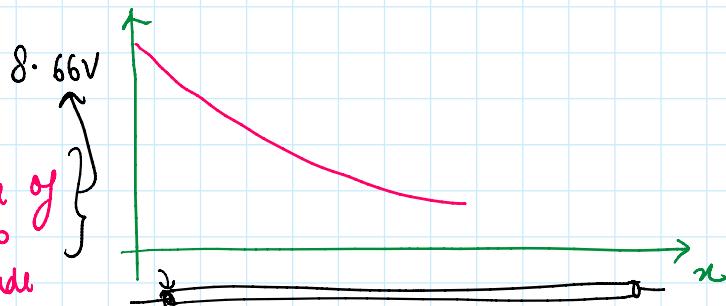

- Given the amplitude of wave at $t=0 \& x=0$
- Estimate the amplitude at $t = 100 \text{ ns} \quad x = 1 \text{ m}$
Use $\text{Ex } 1 \alpha = \beta$.
- Initial phase of the signal is 30°

$$f_{\text{mag}} = 1 \text{ GHz}$$

$$V(t, x) = \text{Re} \left\{ V^+ e^{-\alpha x} e^{-j\beta x + j\omega t} \right\} \leftarrow$$

$$8.66V \rightarrow V(t, x) \underbrace{|V^+|}_{\uparrow} \cos(\phi_0 + \omega t - \beta x) \underbrace{e^{-\alpha x}}_{\downarrow} \left. \right\} \quad t=0 ; x=0$$

Initial phase

$$8.66 = |V^+| \cos(\phi_0)$$

\downarrow
 30°

$$|V^+| = \frac{8.66}{\cos(30^\circ)} = \frac{8.66 \times 2}{\sqrt{3}} = 10 \text{ V}$$

$$V(x, t) = 10 \cos(\phi_0 + \omega t - \beta x) e^{-\alpha x}$$

$$\alpha = 2.23 \text{ nper/m}$$

$$\beta = 28.2 \text{ rad/m}$$

$$\omega = 2\pi \times 1 \times 10^3$$

$$t = 100 \text{ ns}$$

$$x = 1 \text{ m}$$

$$V(x, t) = -0.88 \text{ V}$$

- Continue with the derivation of transmission line voltage and current.

$$\frac{dV}{dx} = -(R + j\omega L) I$$

Substitute the solution of $V + I$

$$\frac{d}{dx} (V^+ e^{-rx} + V^- e^{rx}) = -(R + j\omega L) \{ I^+ e^{-rx} + I^- e^{rx} \}$$

$$-\gamma V^+ e^{-rx} + \gamma V^- e^{rx} = -(R + j\omega L) (I^+ e^{-rx} + I^- e^{rx})$$

Separate the forward and reverse travelling waves.


$\text{FTW} : \cancel{\gamma V^+ e^{-rx}} = \cancel{(R + j\omega L)} I^+ e^{-rx}$

Forward Travelling Wave

$\text{RTW} : \cancel{\gamma V^- e^{rx}} = -(R + j\omega L) I^- e^{rx}$

$$\frac{V^+}{I^+} = \frac{R + j\omega L}{\gamma} ; \quad \frac{V^-}{I^-} = -\frac{(R + j\omega L)}{\gamma}$$
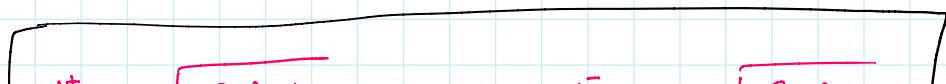
$$\gamma = \sqrt{(R + j\omega L)(g + j\omega C)}$$




$$\frac{V^+}{I^+} = \sqrt{\frac{R+jWL}{G+jWC}} ; \quad \frac{V^-}{I^-} = -\sqrt{\frac{R+jWL}{G+jWC}}$$

Negative Sign

Characteristic Impedance

$$Z_0 = \sqrt{\frac{(R+jWL)}{(G+jWC)}}$$

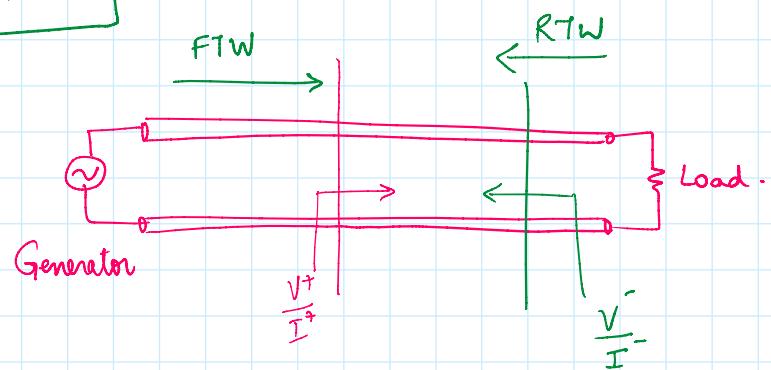

Energy source is on the left; Load is on the right

RTW goes from right to left \rightarrow I see that the energy is increasing.

Observations


$$Z_0 = \sqrt{\frac{R+jWL}{G+jWC}}$$

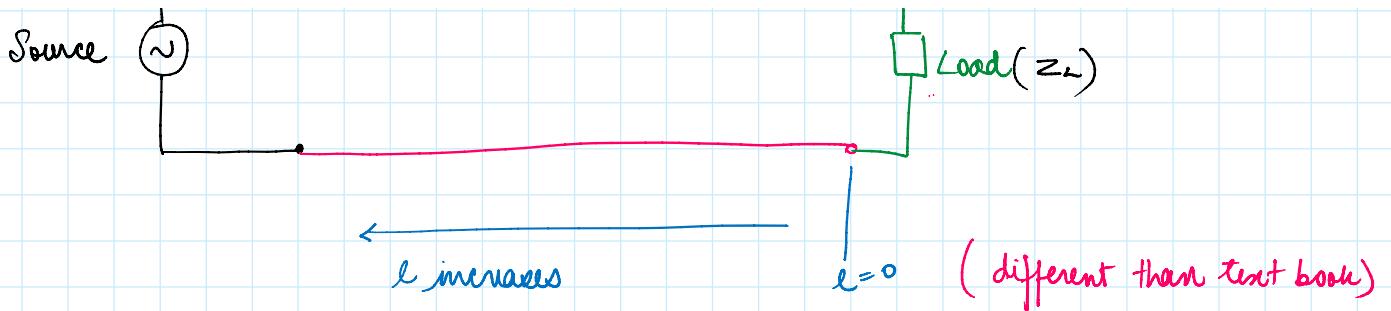1. Z_0 = Real for a lossless line
2. Z_0 = Imaginary for a lossy line.

$$\text{Loss Less} \rightarrow R=0; G=0 \quad Z_0 = \sqrt{\frac{L}{C}}$$

Boundary Conditions on a Transmission Line.





$$\left. \begin{aligned} V &= V^+ e^{rl} + V^- e^{-rl} \\ I &= I^+ e^{rl} + I^- e^{-rl} \end{aligned} \right\} \quad (1) \quad (2)$$

$$I = \frac{V^+}{Z_0} e^{rl} - \frac{V^-}{Z_0} e^{-rl} \quad (3)$$

l is made negative because we have assumed that l increases from right to left.

Boundary conditions : $l=0$; $Z = Z_L$ (load impedance)

Take the ratio of eq (1) & (3)

$$Z = \frac{V}{I} = Z_0 \left(\frac{V^+ e^{rl} + V^- e^{-rl}}{V^+ e^{rl} - V^- e^{-rl}} \right) \rightarrow \text{Apply the boundary conditions.}$$

$l=0$; $Z = Z_L$

$$Z_L = Z_0 \left(\frac{V^+ + V^-}{V^+ - V^-} \right)$$

Reflection Coefficient : $\Gamma(l) = \frac{V^- e^{-rl}}{V^+ e^{rl}}$

at $l=0$ $\Gamma(0) = \frac{V^-}{V^+}$

It is a measure of how much energy is reflected from the load end of the transmission line.

Ideal $\Gamma(0) = 0$

Typically $-1 \leq \Gamma \leq 1$

$\boxed{\Gamma(0) = \frac{Z_L - Z_0}{Z_L + Z_0}}$ \rightarrow Char Impedance

\downarrow Load Impedance.

$$Z_L = ? \rightarrow \Gamma(0) = 0$$

$$Z_L = Z_0 \rightarrow \Gamma(0) = 0 \rightarrow \text{Matched Condition}$$

Transmission line is terminated by the
Characteristic Impedance.