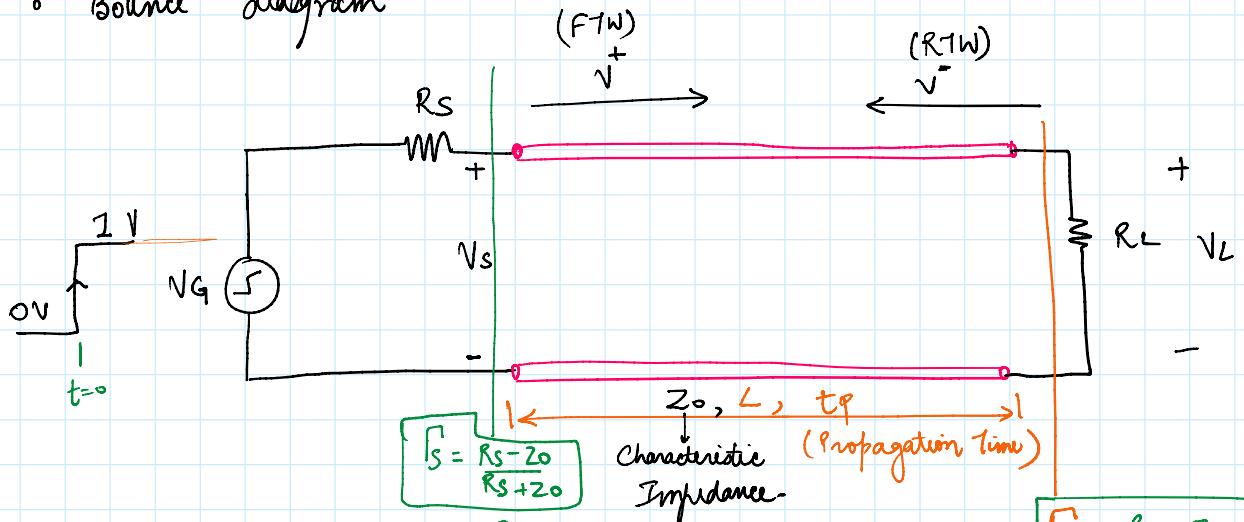


Reflections in a Transmission Line.

- Reflection diagram
- Lattice diagram
- Bounce diagram




$$V_i^+ = \frac{Z_0}{Z_0 + R_s} \cdot V_G$$

$$V_1^+ = \frac{Z_0}{Z_0 + R_s} \cdot V_G$$

$$V_2^+ = f_s V_1^-$$

$$V_3^+ = f_s V_2^-$$

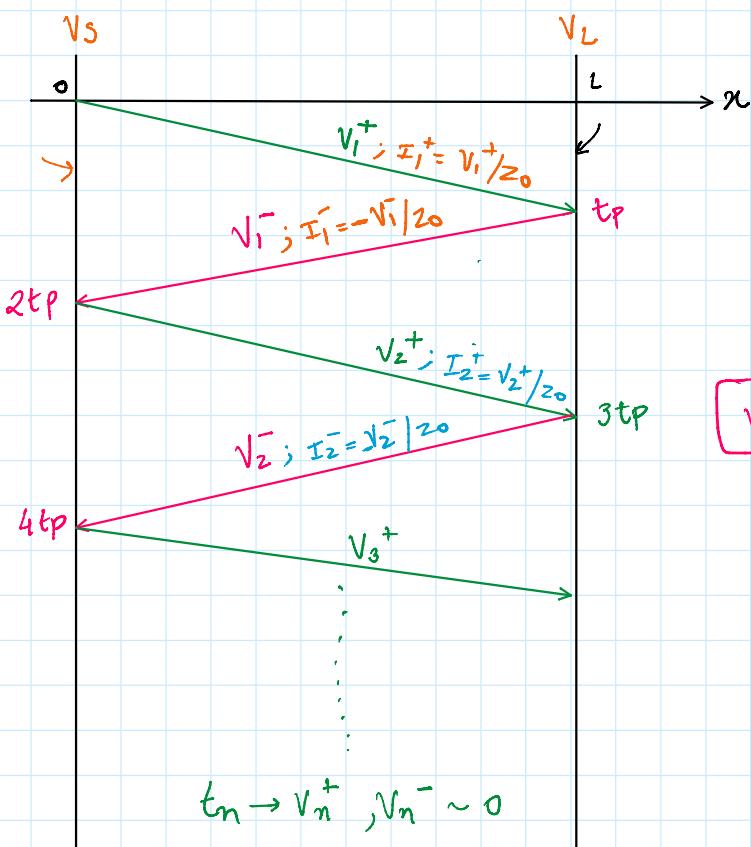

$$\downarrow \quad \quad \quad \downarrow$$

$$t_n \rightarrow V_n^+, V_n^- \sim 0$$

$$\text{At } t = \infty \quad \lim_{n \rightarrow \infty} V_n^+ = 0$$

Voltage at the load end (V_L) at $t = \infty$

$$\begin{aligned}
 V_L &= V_1^+ + V_1^- + V_2^+ + V_2^- + V_3^+ + V_3^- + \dots \\
 &= V_1^+ + V_1^+ R_L + V_1^- R_S + V_2^+ R_L + \dots \\
 &= V_1^+ + V_1^+ R_L + V_1^+ R_L R_S + V_1^+ R_L R_S R_L + \dots \\
 &= V_1^+ [1 + R_L + R_L R_S + R_L R_S R_L + R_L R_S R_L R_S + \dots] \\
 &= V_1^+ [1 + R_L + R_L R_S + R_L^2 R_S + R_L^2 R_S^2 + \dots] \\
 &= V_1^+ [(1 + R_L R_S + R_L^2 R_S^2 + \dots) + R_L (1 + R_L R_S + R_L^2 R_S^2 + \dots)] \\
 &= V_1^+ \left[\frac{1}{1 - R_L R_S} + \frac{R_L}{1 - R_L R_S} \right]
 \end{aligned}$$

$$V_L = V_1^+ \left[\frac{1 + R_L}{1 - R_L R_S} \right]$$

$$V_L = \frac{V_G \cdot R_L}{R_L + R_S}$$

$$\left\{
 \begin{array}{l}
 V_1^+ = \frac{V_G Z_0}{Z_0 + R_S} \\
 R_L = \frac{R_L - Z_0}{R_L + Z_0} \\
 R_S = \frac{R_S - Z_0}{R_S + Z_0}
 \end{array}
 \right.$$