
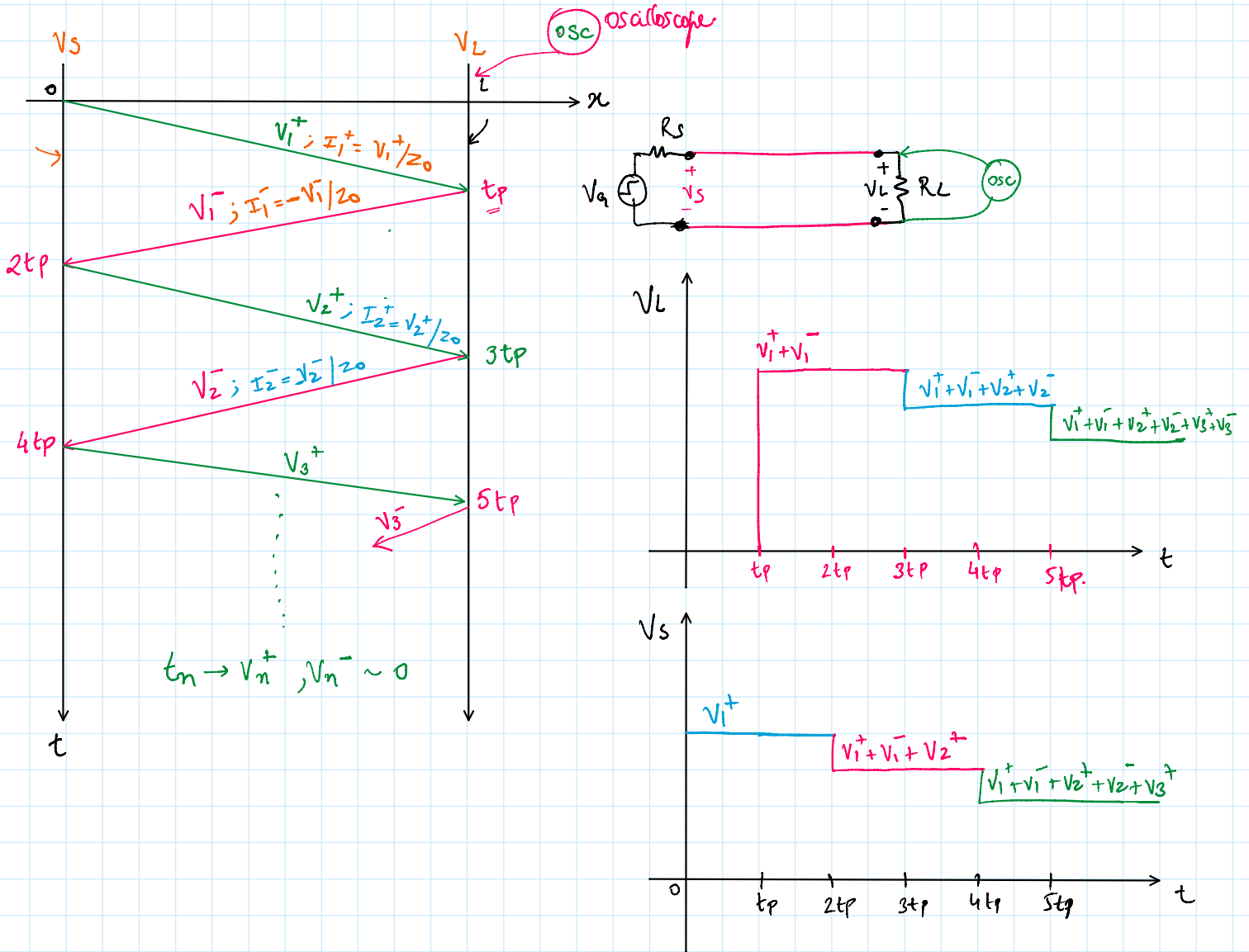


HW-1 Due Today

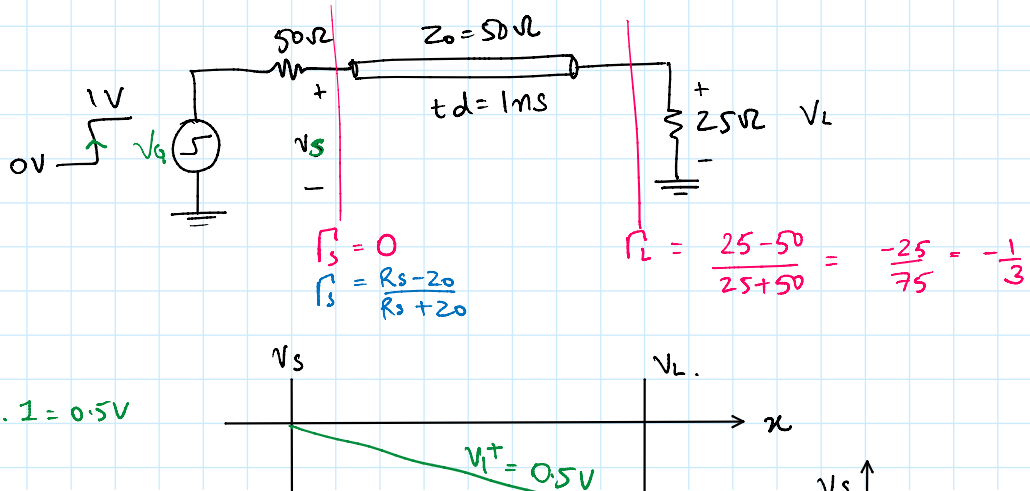

Example 1:



$$V_i' = \frac{50}{50+50} \cdot 1 = 0.5V$$

