
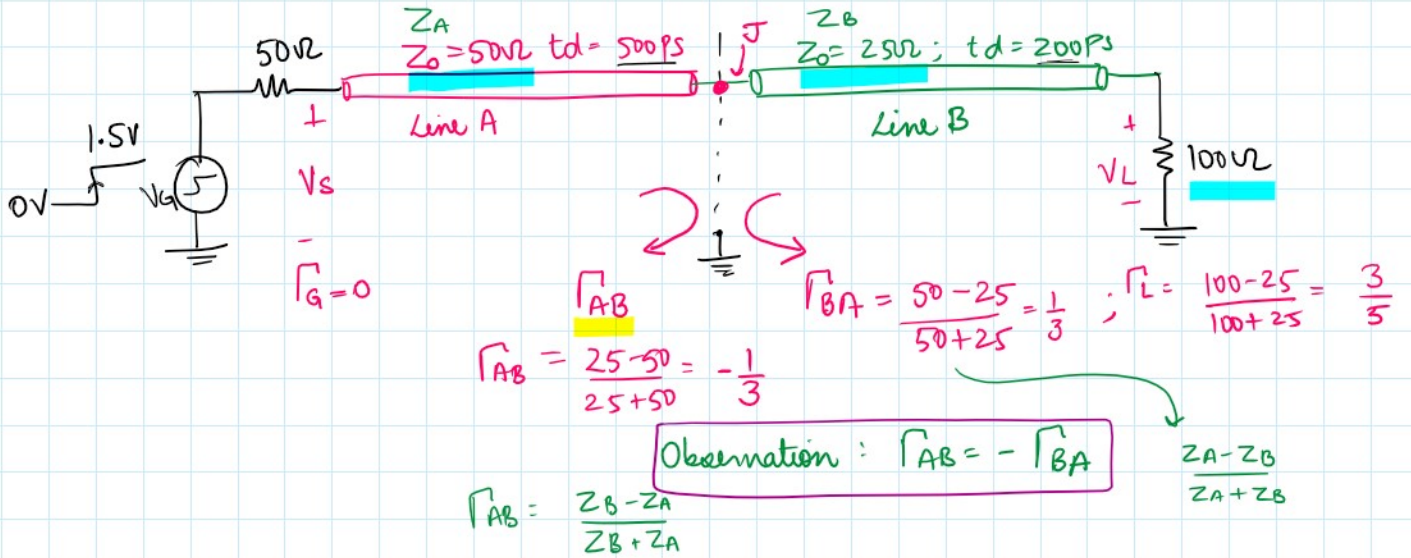


Text book reading - Chapter 1 & Chapter 2 (up to and including 2.4)

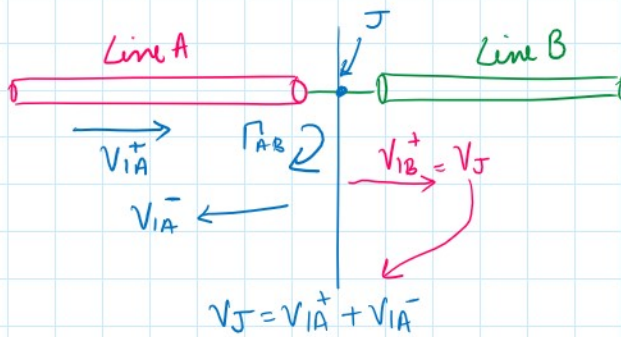Reflections at the junction of transmission lines.




Boundary Condition : At the boundary / junction of two transmission lines, the voltage is same.




$$\left. \begin{aligned} V_{1A}^+ + V_{1A}^- &= V_{1B}^+ \\ \downarrow & \quad \downarrow \\ \text{Incident wave} & \quad \text{Reflected wave} \end{aligned} \right\} \rightarrow V_{1A}^+ + \Gamma_{AB} V_{1A}^+ = (1 + \Gamma_{AB}) V_{1A}^+ = V_{1B}^+$$

\hookrightarrow Transmitted wave.

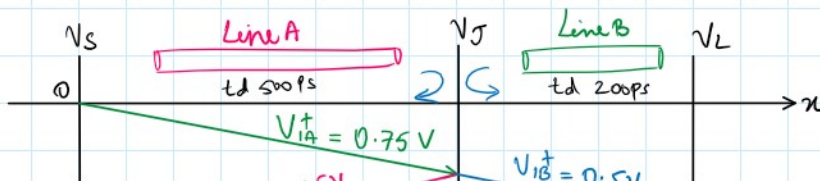$\Gamma_G = 0$
 $\Gamma_L = 3/5 = 0.6$
 $\Gamma_{AB} = -1/3$
 $\Gamma_{BA} = 1/3$



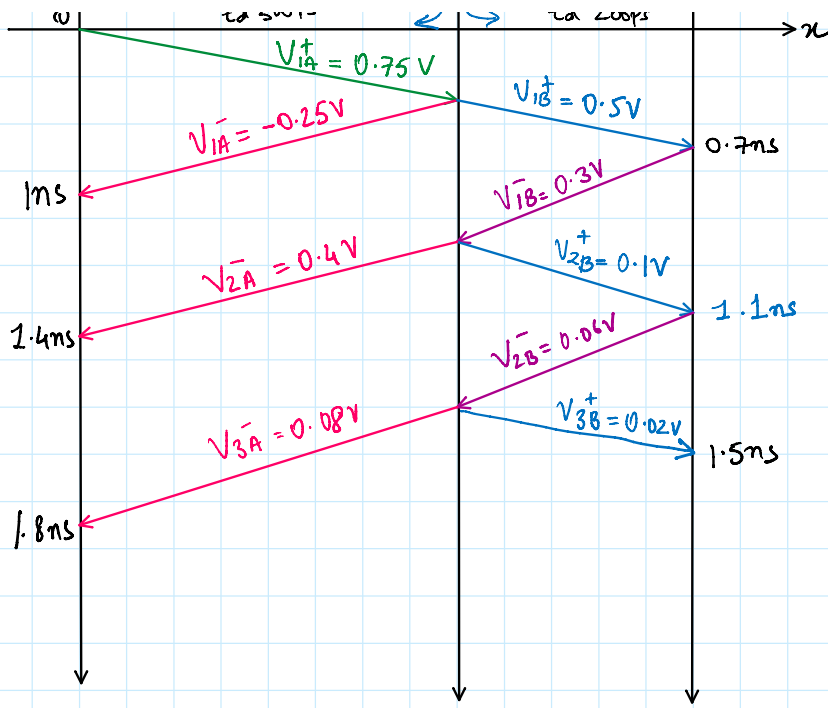

$$\Gamma_{BA} = \frac{1}{3}$$

$$V_{2B}^+ = V_{1B}^- \cdot \Gamma_{BA}$$

$$V_{1B}^- + V_{2B}^+ = V_{2A}^-$$

