

ECE 391 Transmission Lines, Winter 2020

Test Date: 02/05/2020

Problems: 4

Total Pages: 6

Name: SOLUTION KEY

1. (10 points) _____

2. (10 points) _____

3. (20 points) _____

4. (20 points) _____

Total (60 points) _____

Good Luck

Problem 1: (10 points) A surface mount resistor is 2mm in length. Propagation velocity of the signal through this resistor is 0.6c (where $c=3\times 10^8 \text{ m/s}$). Up to what frequency can you consider this component as lumped parameter?

Note: Transit time effect can be safely ignored if the length of the transmission line is less than 1% of the signal wavelength.

$$\text{Frequency} = \underline{0.9 \text{ GHz}}$$

To be considered a lumped element,

$$l \leq 1\% \text{ of } \lambda \Rightarrow 100l \leq \lambda$$

$$\Rightarrow 100l \leq \frac{NP}{f} \Rightarrow f \leq \frac{NP}{100l}$$

$$\Rightarrow f \leq \frac{0.6c}{100l} \Rightarrow f \leq \frac{0.6 \times 3 \times 10^8}{100 \times 2 \times 10^{-3}} \text{ Hz} \Rightarrow f \leq 0.9 \text{ GHz}$$

Problem 2: (10 points) Parameters of a transmission lines are: $R = 0.5\Omega/\text{m}$; $L=0.237\mu\text{H}$; $G = 6.21 \times 10^{-4} \text{ S/m}$; $C=106\text{pF}$; Calculate the characteristic impedance of the transmission line at 1MHz and 10GHz?

$$Z_0(1\text{MHz}) = \underline{40.59 + 8.79j}$$

$$Z_0(10\text{GHz}) = \underline{47.28 + 0.0014j}$$


$$f_1 = 1\text{MHz}, \omega_1 = 2\pi f_1$$

$$Z_{01} = \sqrt{\frac{R + j\omega_1 L}{G + j\omega_1 C}} = 40.59 + 8.79j$$

$$f_2 = 10\text{GHz}, \omega_2 = 2\pi f_2$$

$$Z_{02} = \sqrt{\frac{R + j\omega_2 L}{G + j\omega_2 C}} = 47.28 + 0.0014j$$

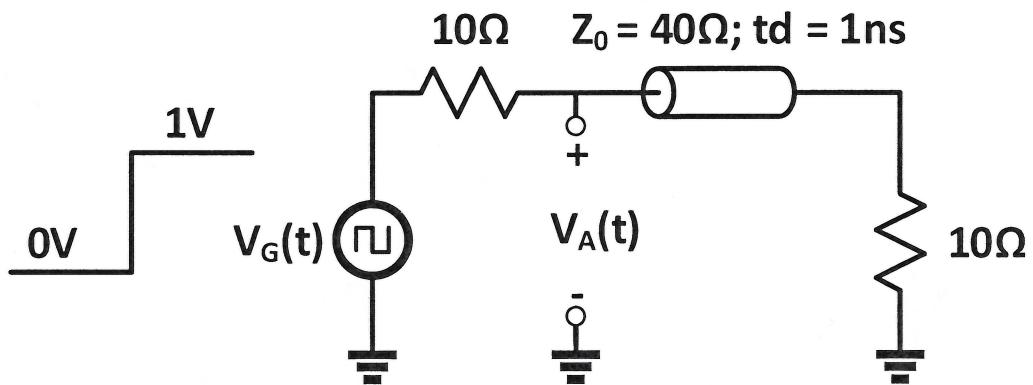Problem 3: (20 points) Given the following transmission line:



(a) (5 points) Calculate the reflection coefficient at the generator side and load side:


$$\begin{array}{ll} \text{Reflection Coefficient on Generator} & (\Gamma_G) = \frac{-0.6}{-0.6} \\ \text{Reflection Coefficient on Load} & (\Gamma_L) = \underline{\underline{-0.6}} \end{array}$$

$$\Gamma_G = \frac{R_G - Z_0}{R_G + Z_0} = \frac{10 - 40}{10 + 40} = -0.6$$

$$\Gamma_L = \frac{R_L - Z_0}{R_L + Z_0} = \frac{10 - 40}{10 + 40} = -0.6$$

(b) (10 points) Draw lattice diagram for up to 5ns.

$$td = 1 \text{ ms}$$

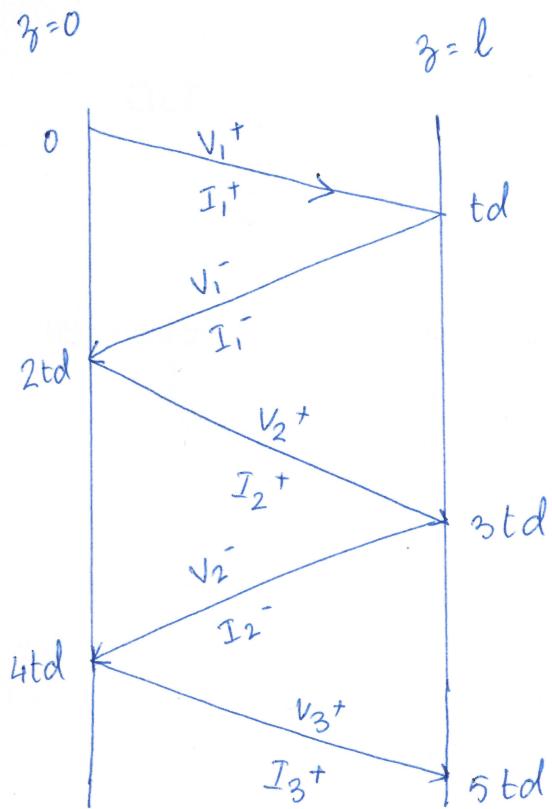

$$\Pi_L = -0.6$$

$$\Pi_G = -0.6$$

$$V_1^+ = V_{inc} = \frac{V_G \cdot Z_0}{Z_0 + R_G} = 0.8V$$

$$I_1^+ = V_1^+ / Z_0 = 0.02A$$

$$I_1^- = \Pi_L I_1^+ = +0.012A = -V_1^- / Z_0$$

$$I_2^+ = \Pi_S I_1^- = 0.0072A = V_2^+ / Z_0$$

$$I_2^- = \Pi_L I_2^+ = +0.00432A = -V_2^- / Z_0$$

$$I_3^+ = \Pi_S I_2^- = 0.0002592A = V_3^+ / Z_0 \\ = 0.002592A$$

$$V_1^- = \Pi_L V_1^+ = -0.48V$$

$$V_2^+ = \Pi_S V_1^- = \Pi_S \Pi_L V_1^+ = 0.288V$$

$$V_2^- = \Pi_L V_2^+ = \Pi_L^2 \Pi_S V_1^+ = -0.1728V$$

$$V_3^+ = \Pi_S V_2^- = \Pi_L^2 \Pi_S^2 V_1^+ = 0.10368V$$


(c) (10 points) Plot $V_A(t)$ up to 6ns.

$$V_A(t) \text{ at } t = 0^+ = V_1^+ = 0.8V$$


$$\text{at } t = 2td^+ = V_1^+ + V_1^- + V_2^+ = 0.608V$$

$$\text{at } t = 4td^+ = V_1^+ + V_1^- + V_2^+ + V_2^- + V_3^+ = 0.539V$$

$$\text{at } t = 6td^+ = V_1^+ + V_1^- + V_2^+ + V_2^- + V_3^+ + V_3^- + V_4^+ = 0.514V$$

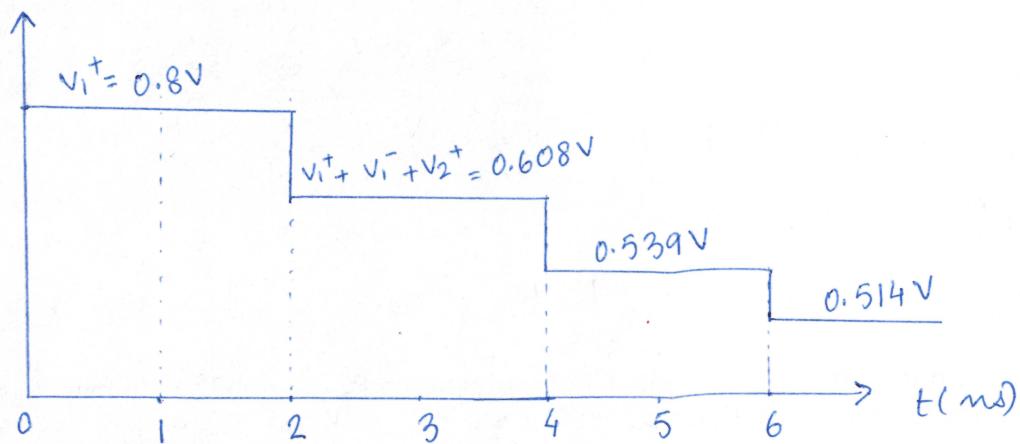

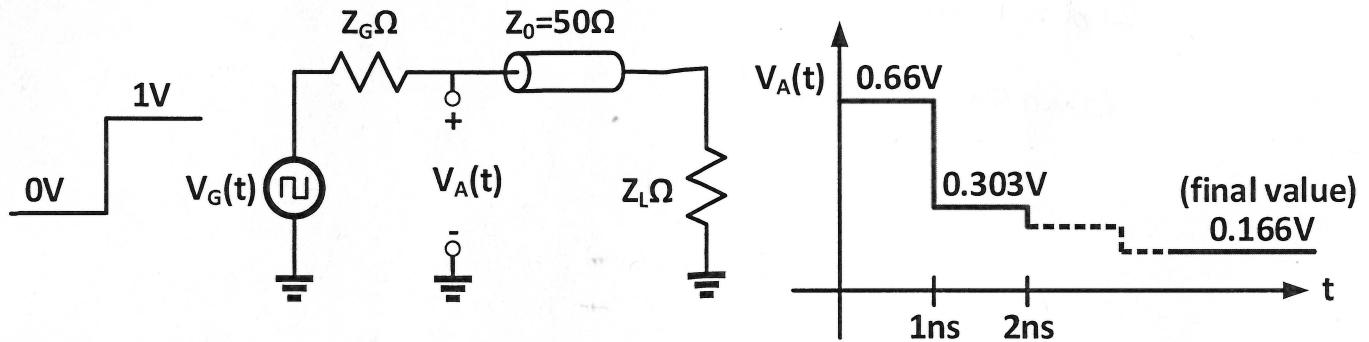Problem 4: (20 points) Given the following transmission line and measurement of voltage near generator $V_A(t)$:



(a) (14 points) Calculate the impedance Z_G and Z_L .

$$Z_G = \underline{25 \Omega}$$

$$Z_L = \underline{5 \Omega}$$

$$V_A(t) \text{ at } t=0^+ = V_i^+ = \frac{V_G \cdot Z_0}{Z_0 + Z_G} = 0.666 \text{ V}$$

$$\Rightarrow Z_G = 25 \Omega$$

$$V_A(t) \text{ at } t \rightarrow \infty = \frac{V_G \cdot Z_L}{Z_L + Z_G} = 0.166 \text{ V} \Rightarrow Z_L = 5 \Omega$$

Alternate approach, $V_A(t) \text{ at } t = 2t_d^+ = V_i^+ + V_i^- + V_2^+ = 0.303 \text{ V}$
 $\Rightarrow V_i^+ (1 + \Gamma_L + \Gamma_L \Gamma_G) = 0.303 \text{ V}$

$$\Rightarrow \Gamma_L = (Z_L - Z_0)/(Z_L + Z_0) = -0.818 \Rightarrow Z_L = 5 \Omega$$

(b) (6 points) Given the propagation velocity of the signal through this transmission line is $0.5c$ (where $c=3 \times 10^8 \text{ m/s}$), calculate the length of the transmission line.

$$\text{Length} = \underline{75 \text{ mm}}$$

$$V_p = 0.5 c$$

$$2t_d = 1 \text{ ns}$$

\therefore Length of the transmission line

$$= \frac{1}{2} \cdot (V_p) \cdot (2t_d)$$

$$= \frac{1}{2} \cdot (0.5c) \cdot (2t_d)$$

$$= \frac{1}{2} \cdot (0.5 \times 3 \times 10^8) (1 \times 10^{-9}) \text{ m}$$

$$= 75 \text{ mm}$$