

ECE 391 Transmission Lines, Winter 2020

Test Date: 02/05/2020

Problems: 4

Total Pages: 6

Name: _____

1. (10 points) _____

2. (10 points) _____

3. (20 points) _____

4. (20 points) _____

Total (60 points) _____

Good Luck

Problem 1: (10 points) A surface mount resistor is 2mm in length. Propagation velocity of the signal through this resistor is $0.6c$ (where $c=3 \times 10^8 \text{m/s}$). Up to what frequency can you consider this component as lumped parameter?

Note: Transit time effect can be safely ignored if the length of the transmission line is less than 1% of the signal wavelength.


Frequency = _____

Problem 2: (10 points) Parameters of a transmission lines are: $R = 0.5 \Omega/\text{m}$; $L=0.237 \mu\text{H}/\text{m}$; $G = 6.21 \times 10^{-4} \text{S}/\text{m}$; $C=106 \text{pF}/\text{m}$; Calculate the characteristic impedance of the transmission line at 1MHz and 10GHz?

Z_0 (1MHz) = _____

Z_0 (10GHz) = _____

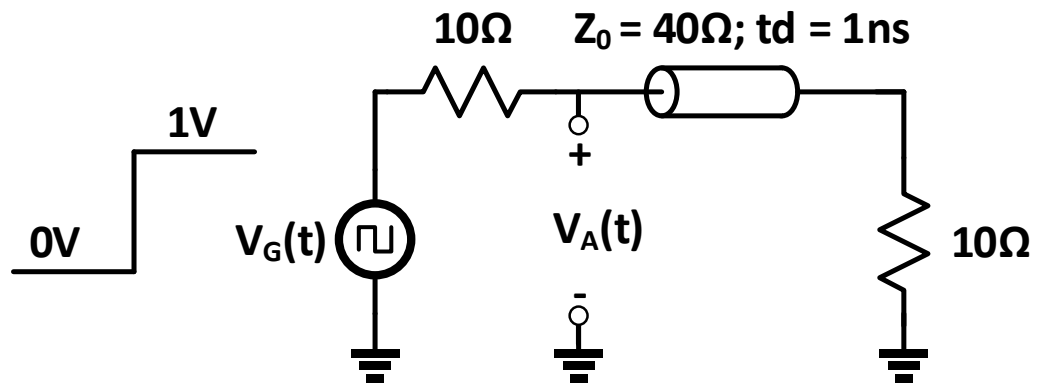Problem 3: (20 points) Given the following transmission line:




(a) **(5 points)** Calculate the reflection coefficient at the generator side and load side:

Reflection Coefficient on Generator $(\Gamma_G) = \underline{\hspace{2cm}}$
 Reflection Coefficient on Load $(\Gamma_L) = \underline{\hspace{2cm}}$

(b) **(10 points)** Draw lattice diagram for up to 5ns.

(c) (10 points) Plot $V_A(t)$ up to 6ns.

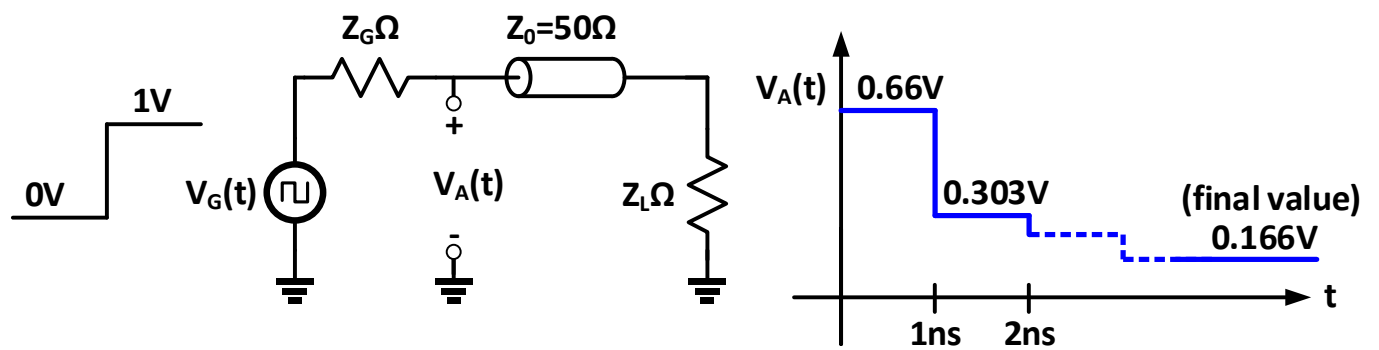Problem 4: (20 points) Given the following transmission line and measurement of voltage near generator $V_A(t)$:



(a) **(14 points)** Calculate the impedance Z_G and Z_L .

$$Z_G = \underline{\hspace{2cm}}$$

$$Z_L = \underline{\hspace{2cm}}$$

(b) **(6 points)** Given the propagation velocity of the signal through this transmission line is $0.5c$ (where $c=3 \times 10^8 \text{m/s}$), calculate the length of the transmission line.

$$\text{Length} = \underline{\hspace{2cm}}$$