

Name: Solutions
(Last name, first name)

Student ID: _____

ECE 391

TRANSMISSION LINES

Spring Term 2017

Midterm II

Exam is closed book, closed notes; **one** sheet (2 pages) of notes and formulas allowed; 50 minutes. Show all work on the pages provided. No extra pages (use back if necessary). **Read each question very carefully.**

Box your final answer and include units where appropriate. Number of points for each problem is given in parenthesis (40 points total).


Problem 1 (18 pts.) _____

Problem 2 (12 pts.) _____

Problem 3 (10 pts.) _____

Total (40 pts.) _____

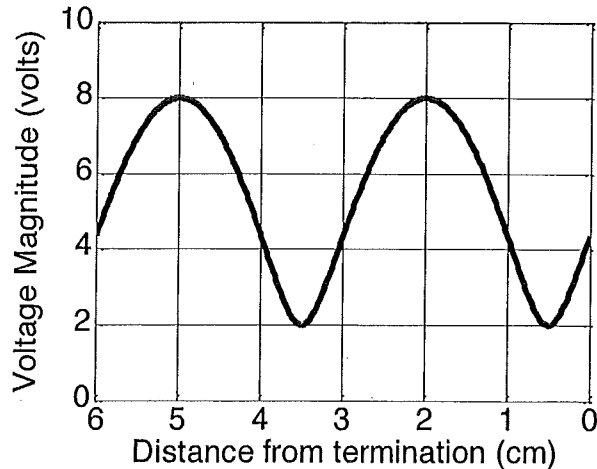1. (18 pts.) A transmission line of characteristic impedance $Z_0 = 50\Omega$ is terminated in an **unknown** load impedance Z_L . The voltage standing-wave pattern along the transmission line as function of distance from the termination is shown below.



- (a) What is the standing-wave ratio on the line terminated in the unknown load impedance Z_L ?

$$VSWR = \frac{8V}{2V} = \boxed{4}$$

- (b) Determine the wavelength on the line.

$$\frac{\lambda}{2} = 5\text{cm} - 2\text{cm} = 3\text{cm} \Rightarrow \boxed{\lambda = 6\text{cm}}$$

- (c) Determine the voltage magnitude of the outgoing wave, $|V_0^+|$.

$$|V_0^+| = \frac{V_{\max} + V_{\min}}{2} = \frac{8V + 2V}{2} = \boxed{5V}$$

- (d) Determine the reflection coefficient at the termination in **magnitude and phase**.

$$|\Gamma| = \frac{VSWR - 1}{VSWR + 1} = \frac{4 - 1}{4 + 1} = \boxed{\frac{3}{5} = 0.6}$$

$$\text{distance to } V_{\max} = 2\text{cm} \stackrel{\wedge}{=} \frac{2}{6}\lambda = \frac{\lambda}{3} \stackrel{\wedge}{=} 120^\circ$$


$$\Rightarrow \frac{\theta_L}{2} = 120^\circ \Rightarrow \theta_L = 240^\circ = \boxed{-120^\circ}$$

$$\text{or distance to } V_{\min} = 0.5\text{cm} = \frac{0.5}{6}\lambda = \frac{\lambda}{12} \stackrel{\wedge}{=} 30^\circ$$

$$90^\circ + \frac{\theta_L}{2} = 30^\circ \Rightarrow \frac{\theta_L}{2} = -60^\circ \Rightarrow \boxed{\theta_L = -120^\circ}$$

(e) Indicate the type of termination from the list shown below that produces the standing-wave pattern shown above.

Moving towards the source, V_{min} is seen first
 \Rightarrow Capacitive (also: $0 \geq \theta_L \geq -180^\circ$) + $|r_L| < 1 \Rightarrow$ resistive

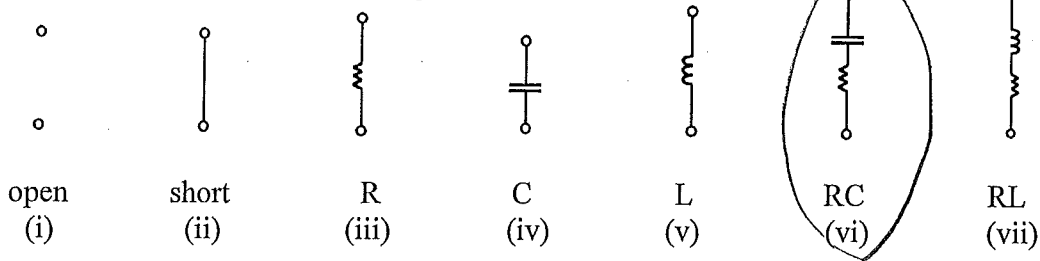


(f) Determine $|I|_{max}$ and $|I|_{min}$ on the line.

$$|I_{max}| = \frac{|V_{max}|}{Z_0} = \frac{8V}{50\Omega} = \boxed{160mA}$$

$$|I_{min}| = \frac{|V_{min}|}{Z_0} = \frac{2V}{50\Omega} = \boxed{40mA}$$

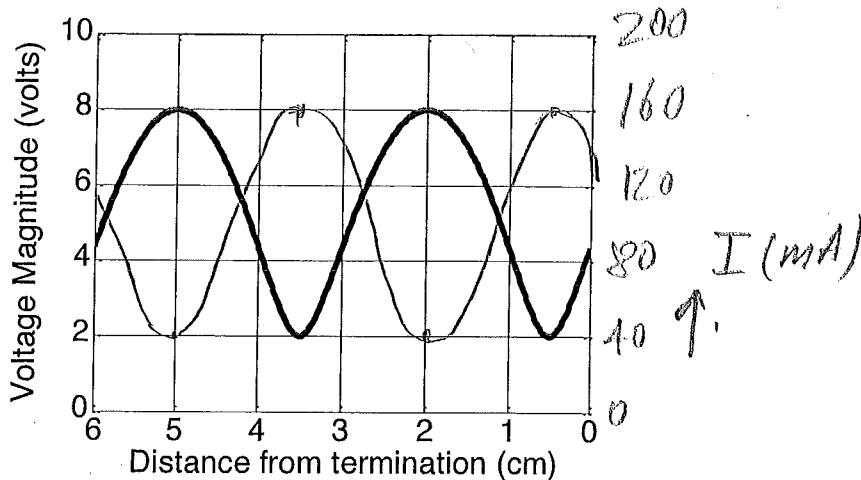(g) Sketch the corresponding current standing-wave plot in the graph below.



2. (12 pts.) A low-loss 50Ω transmission line of 100m length is found to attenuate a sinusoidal wave traveling from one end to the other by 6dB. It is known that dielectric loss is negligible.

(a) What is the voltage magnitude across a matched load if the magnitude of the voltage across the input terminals of the line is 10V?

$$20 \log_{10} \frac{V_2}{V_1} = -6 \text{ dB} \Rightarrow \frac{V_2}{V_1} = 10^{-\frac{6}{20}} = 0.5$$

$$\boxed{V_2 = V_{FE} = 5 \text{ V}}$$

(b) Determine the attenuation constant in Np/m.

$$\alpha_{\text{dB}} = \frac{6 \text{ dB}}{100 \text{ m}} = 0.06 \frac{\text{dB}}{\text{m}} \Rightarrow \alpha_{\text{Np}} = \alpha_{\text{dB}} \cdot \frac{1}{8.686 \frac{\text{dB}}{\text{Np}}} =$$

$$= \frac{0.06}{8.686} \frac{\text{Np}}{\text{m}} = \boxed{0.0069 \frac{\text{Np}}{\text{m}}}$$

(c) Applying the low-loss approximation, determine the resistance per-unit-length, R , of the transmission line in ohms/meter.

$$\alpha_{\text{Np}} \approx \frac{R}{2Z_0} \Rightarrow R = \alpha_{\text{Np}} 2Z_0 = 0.0069 \frac{1}{\text{m}} 2 \cdot 50 \Omega$$

$$= \boxed{0.69 \frac{\Omega}{\text{m}}}$$


(d) Applying the low-loss approximation, determine the remaining per-unit-length parameters L , C , and G (don't forget to specify the proper units). Assume a phase velocity of $v_p = 20$ cm/ns.

$$Z_0 \approx \sqrt{\frac{L}{C}}; v_p \approx \frac{1}{\sqrt{LC}} \Rightarrow L = \frac{Z_0}{v_p} = \frac{50 \Omega}{0.2 \text{ m/ns}} = \boxed{250 \frac{\text{nH}}{\text{m}}}$$

$$C = \frac{1}{Z_0 v_p} = \frac{1}{50 \Omega \times 0.2 \frac{\text{m}}{\text{ns}}} = \frac{1}{10} 10^{-9} \frac{\text{F}}{\text{m}} = \boxed{100 \frac{\text{pF}}{\text{m}}}$$

$$G \approx 0 \text{ (dielectric loss is negligible)}$$

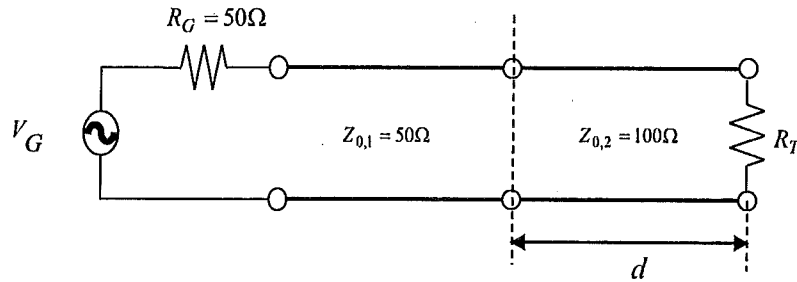3. (10 pts.) An unknown resistive load R_T is connected through a transmission line section of length d and characteristic impedance $Z_{0,2} = 100\Omega$ to a $Z_{0,1} = 50\Omega$ transmission line, as shown below. At frequency f_0 , line length d corresponds to a quarter-wavelength ($d = \lambda/4$).



- (a) What is the physical length of the 100Ω line if $f = f_0 = 200\text{MHz}$ and the effective dielectric constant of the transmission line is $\epsilon_{r,\text{eff}} = 4$?

$$\text{at } f = f_0: d = \lambda/4 \quad \lambda = \frac{v_p}{f} = \frac{3 \times 10^8 \frac{\text{m}}{\text{s}}}{\sqrt{4} (200 \times 10^6 \frac{1}{\text{s}})} = \frac{3}{4} \text{ m} = 75 \text{ cm}$$

$$\Rightarrow d = \frac{\lambda}{4} = \boxed{18.75 \text{ cm}}$$

- (b) Determine R_T if at $f = f_0$ the voltage standing-wave ratio on the 50Ω line is $VSWR = 1$.

line 1 sees a match

$$\Rightarrow Z_{in} = \frac{Z_{0,2}^2}{R_T} = Z_{0,1} = 50\Omega \Rightarrow R_T = \frac{Z_{0,2}^2}{Z_{0,1}} = \frac{100^2}{50} \Omega = \boxed{200\Omega}$$

- (c) What is the voltage standing-wave ratio on the 50Ω line (with R_T from part b) if the frequency is doubled ($f = 2f_0$)?

$$\text{if } f = 2f_0 \Rightarrow d = \frac{\lambda}{2} \Rightarrow Z_{in} = R_T$$

$$\Gamma = \frac{R_T - Z_0}{R_T + Z_0} = \frac{200 - 50}{200 + 50} = \frac{150}{250} = \frac{3}{5} = 0.6 \Rightarrow SWR = \frac{1 + 0.6}{1 - 0.6}$$

$$\text{or: } SWR = \frac{R_T}{Z_0} = \frac{200}{50} = 4 \quad \boxed{4}$$

- (d) What is the voltage standing-wave ratio on the 50Ω line if the load resistor R_T is replaced with an inductor $L = 4\text{ nH}$ and the frequency is $f = f_0 = 200\text{MHz}$?

Termination is purely reactive

$$\Rightarrow |\Gamma_L| = 1 \Rightarrow VSWR \rightarrow \infty$$