

ECE 391 Transmission Lines, Winter 2020

Test Date: 03/04/2020

Problems: 4

Total Pages: 7

Name: _____

1. (10 points) _____

2. (10 points) _____

3. (15 points) _____

4. (15 points) _____

Total (50 points) _____

Good Luck

Problem 1: (10 points) The following data are specified at $f=1\text{MHz}$ for a given transmission line. $Z_0=(99.85 - j3.008)\Omega$; $\alpha=4.345\text{dB/m}$; $\beta= 16.328\times 10^{-3}\text{rad/m}$. Determine the per-unit-length R, L, G, C transmission line parameters.

R = _____


L = _____

G = _____

C = _____

Problem 2: (10 points) Circle the termination load on the transmission line from the voltage standing wave and give reason for your answer.

(a)

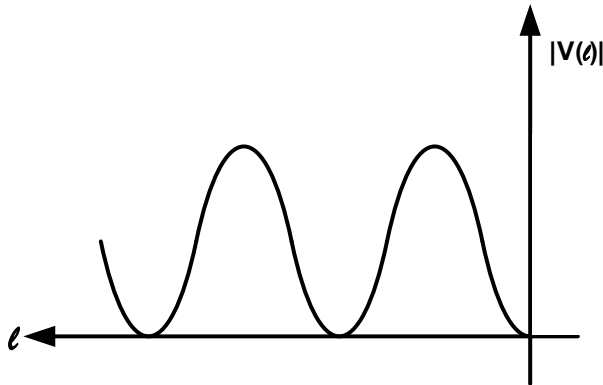

$$Z_L = R; R > Z_0$$

$$Z_L = j\omega L$$

$$Z_L = R; R < Z_0$$

$$Z_L = 1/j\omega C$$

$$Z_L = 0$$


$$Z_L = R + 1/j\omega C$$

$$Z_L = \infty$$

$$Z_L = R + j\omega L$$

Reason:

(b)

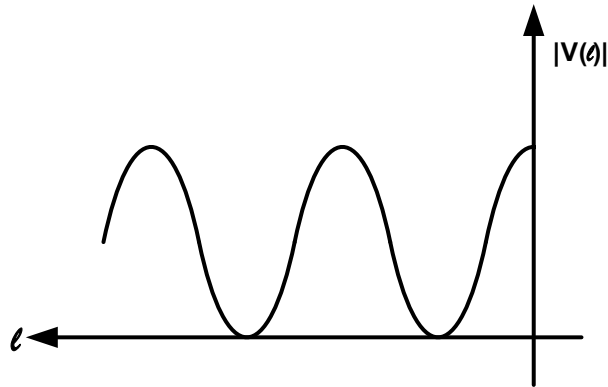

$$Z_L = R; R > Z_0$$

$$Z_L = j\omega L$$

$$Z_L = R; R < Z_0$$

$$Z_L = 1/j\omega C$$

$$Z_L = 0$$


$$Z_L = R + 1/j\omega C$$

$$Z_L = \infty$$

$$Z_L = R + j\omega L$$

Reason:

(c)

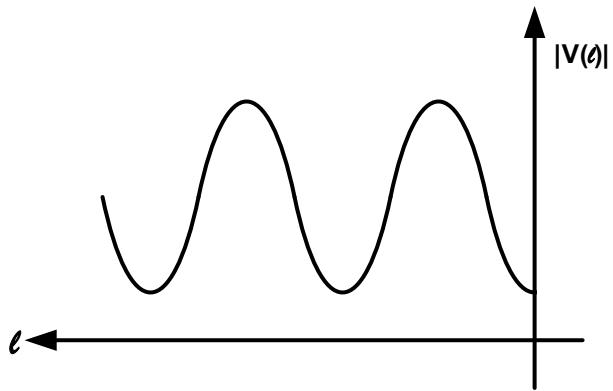

Reason:

$$Z_L = R; R > Z_0$$

$$Z_L = R; R < Z_0$$

$$Z_L = 0$$

$$Z_L = \infty$$


$$Z_L = j\omega L$$

$$Z_L = 1/j\omega C$$

$$Z_L = R + 1/j\omega C$$

$$Z_L = R + j\omega L$$

(d)

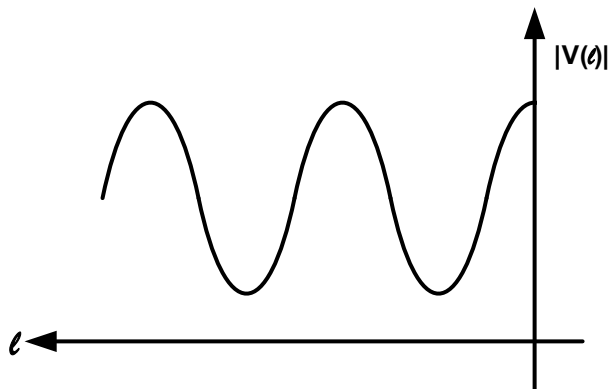

Reason:

$$Z_L = R; R > Z_0$$

$$Z_L = R; R < Z_0$$

$$Z_L = 0$$

$$Z_L = \infty$$


$$Z_L = j\omega L$$

$$Z_L = 1/j\omega C$$

$$Z_L = R + 1/j\omega C$$

$$Z_L = R + j\omega L$$

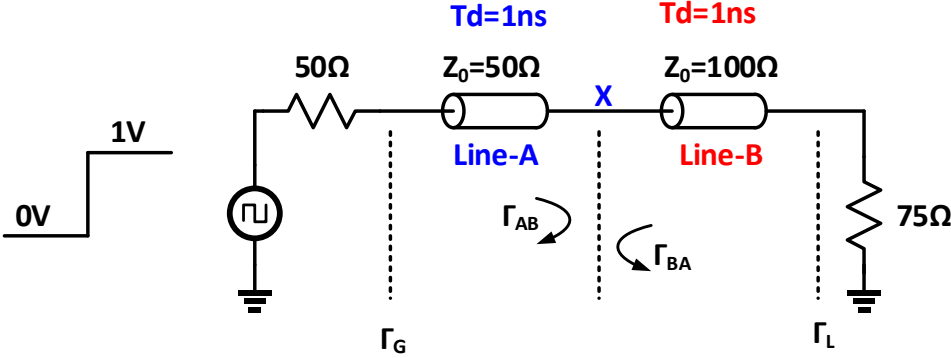
Problem 3: (15 points) Given the following transmission line:



(a) (10 points) Draw lattice diagram for up to 6ns.

(b) (5 points) Draw waveform of voltage on node X versus time for up to 6ns.

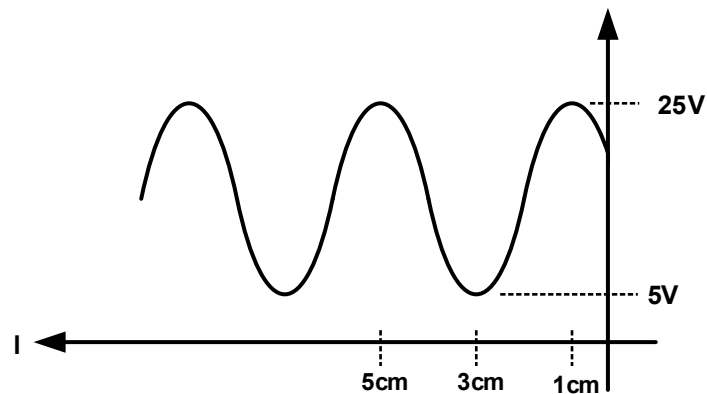Problem 4: (15 points) A transmission line with characteristic impedance of $Z_0=50\Omega$ is terminated with an un-known load impedance Z_L . The voltage standing wave pattern along the transmission line as a function of distance is shown below.



(a) (10 points) Calculate VSWR, wavelength on the line, magnitude of outgoing wave $|V^+|$, magnitude of maximum and minimum current.

VSWR = _____

λ = _____

$|V^+|$ = _____

$|I_{max}|$ = _____

$|I_{min}|$ = _____

(b) **(5 points)** Calculate the phase of the reflection coefficient at the load-end and circle the load Z_L at the end of the transmission line.

Phase = _____

$$Z_L = R; R > Z_0$$

$$Z_L = j\omega L$$

$$Z_L = R; R < Z_0$$

$$Z_L = 1/j\omega C$$

$$Z_L = 0$$

$$Z_L = R + 1/j\omega C$$

$$Z_L = \infty$$

$$Z_L = R + j\omega L$$