
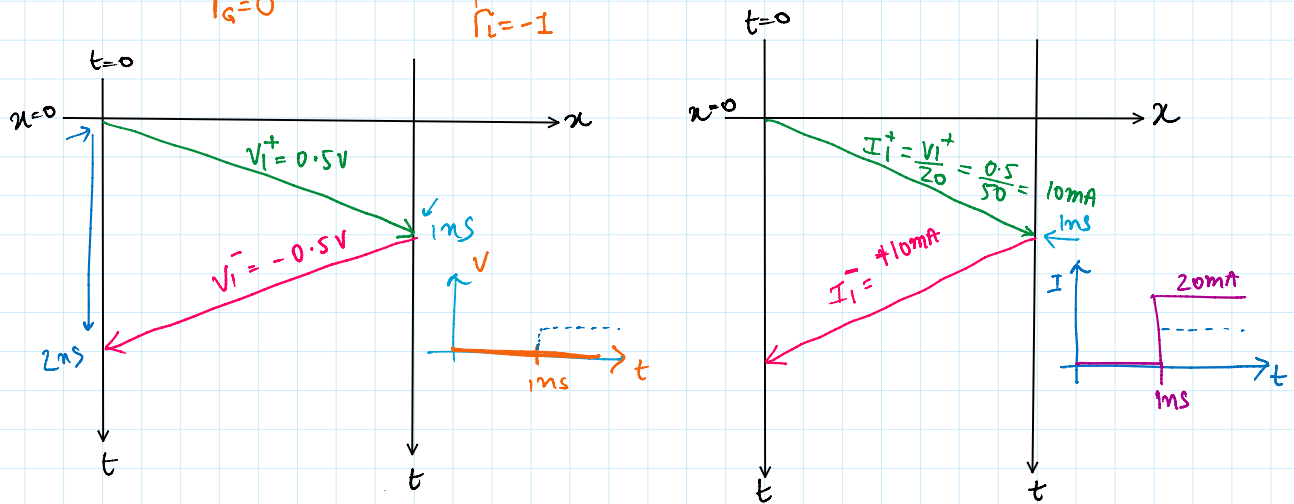




Midterm-1 - Wed


HW-2 Due Today → 11:59 pm.

Transmission Line with short load.

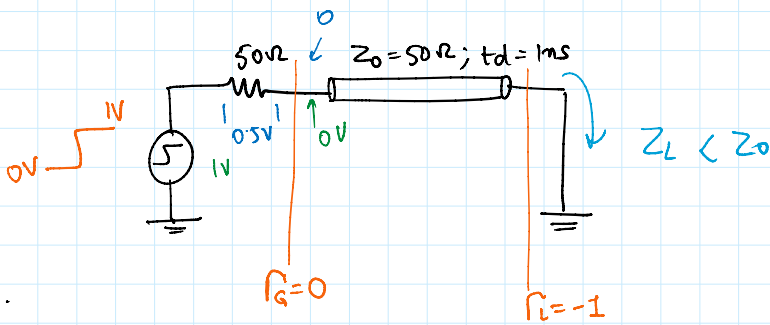


Transmission Line with open circuit.

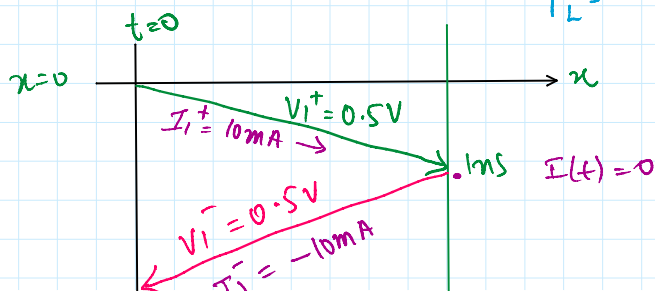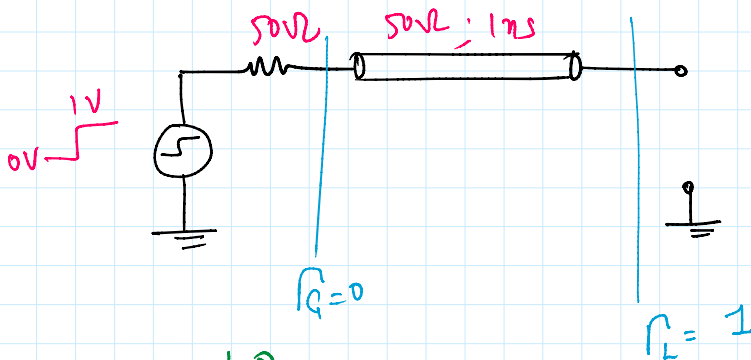


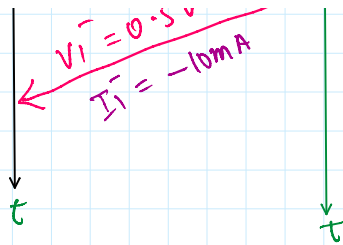

Transmission Line with Inductive Load.

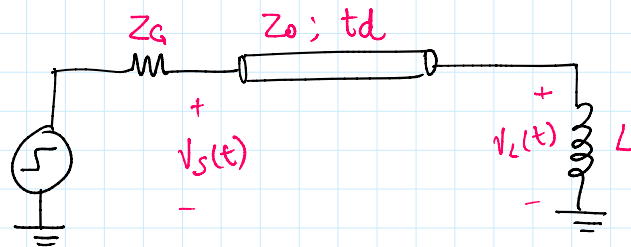

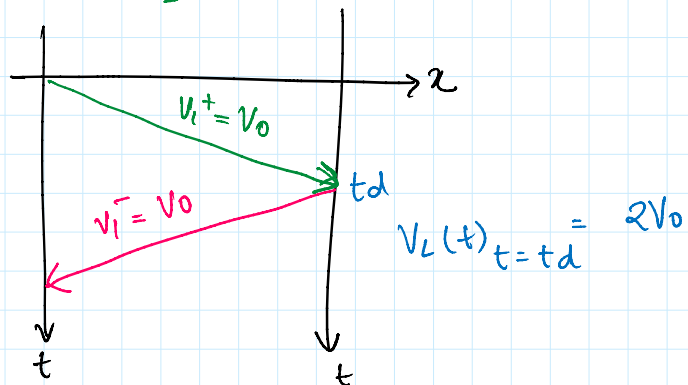- Inductor acts like an open when forward travelling wave reaches the inductor.
- $\left\{ \Gamma_i = 1 \text{ at time } t = t_d \right\}$



$$V_L(t) = L \frac{dI_L(t)}{dt} \quad - (0)$$

$$V_L(t) = V_i^+(t) + V_i^-(t) \quad - (1)$$

$$I_L(t) = I_i^+(t) + I_i^-(t) \quad - (2)$$

$$\begin{aligned} V_i^+ &= V_0 \text{ constant} \\ V_i^- &= V_0 \quad | \quad t = t_d \end{aligned}$$



$$V_i^-(t) = -V_0 + 2V_0 e^{-(Z_0/L)(t-t_d)}$$

$$V_L(t) = V_i^+(t) + V_i^-(t)$$

$$V_L(t) = \underset{\downarrow}{V_0} e^{-(Z_0/L)(t-t_d)}$$

