
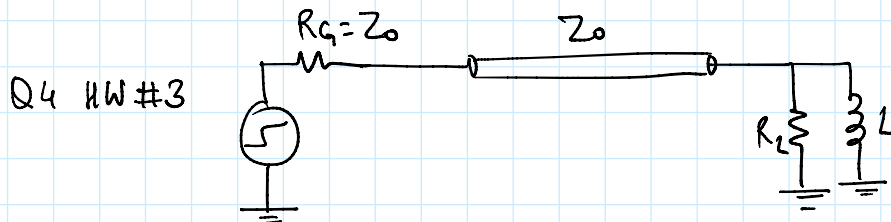


Q1 HW#3 - Fig 2.34 in text book

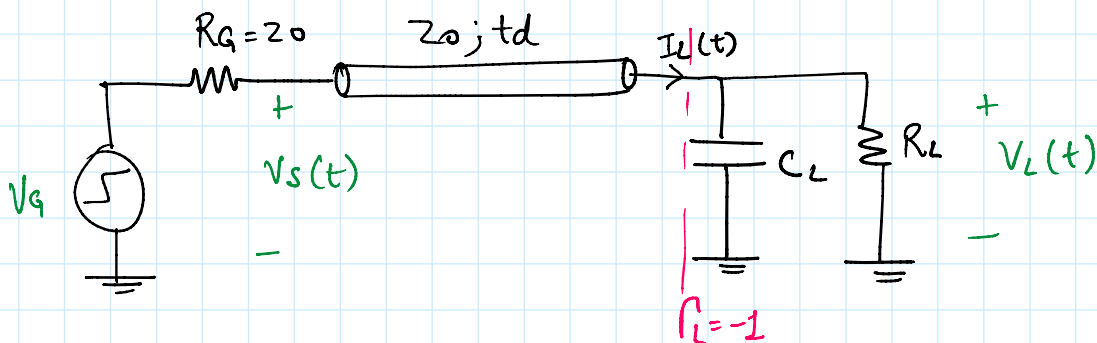

- a) $R_L < Z_0$
- b) $R_L > Z_0$
- c) $R_L = Z_0$

Capacitive Load in a Transmission Line



- Capacitor acts like a short
- $\Gamma_L = -1$ at the time when forward travelling wave hits the capacitor.

$$V_L(t) = V_1^+(t) + V_1^-(t)$$

$$I_L(t) = I_1^+(t) + I_1^-(t)$$

$$I_L(t) = \frac{V_1^+(t)}{Z_0} - \frac{V_1^-(t)}{Z_0}$$

$$\Gamma_L = -1 \Rightarrow V_1^-(t) = -V_1^+(t)$$

$$I_1^-(t) = I_1^+(t)$$

no sign because $I_1(t)$ at $t = t + \tau$ the current

$I_L(t) = \frac{V_L(t)}{Z_0} - \frac{V_L(t)}{Z_0}$

-ve sign because $I_L(t)$ at $t=t_d^+$ the current become twice the current at $t=t_d^-$

$$I_L(t) = \frac{V_L(t)}{R_L} + C \frac{dV_L(t)}{dt} \quad \left\{ \begin{array}{l} V_i^+(t) = V_G/2 \end{array} \right.$$

$$\frac{V_i^+(t)}{Z_0} - \frac{V_i^-(t)}{Z_0} = \frac{V_i^+(t)}{R_L} + \frac{V_i^-(t)}{R_L} + C \left[\frac{dV_i^+}{dt} + \frac{dV_i^-}{dt} \right]$$

$$\frac{dV_i^-}{dt} + \left[\frac{R_L + Z_0}{R_L Z_0} \right] V_i^-(t) - \left[\frac{R_L - Z_0}{R_L Z_0} \right] V_i^+(t) = 0$$

$$V_i^-(t) = K_1 + K_2 e^{-\left[\frac{R_L + Z_0}{R_L Z_0 C} \right] (t - t_d)}$$

\downarrow Const.
 \downarrow Const.

Boundary Condition

- 1) $t = t_d$
- 2) $t = \infty$


$$V_i^- = -V_i^+ = -V_G/2$$


$$V_i^- = \left(\frac{R_L - Z_0}{R_L + Z_0} \right) V_i^+ \quad \text{at } t = \infty$$

$$V_L(t) = \frac{R_L V_G}{R_L + Z_0} \left[1 - e^{-\left[\frac{R_L + Z_0}{R_L Z_0 C} \right] (t - t_d)} \right]$$

$$\tau = \frac{R_L Z_0 C}{R_L + Z_0}$$


$$1 - e^{-t/\tau}$$

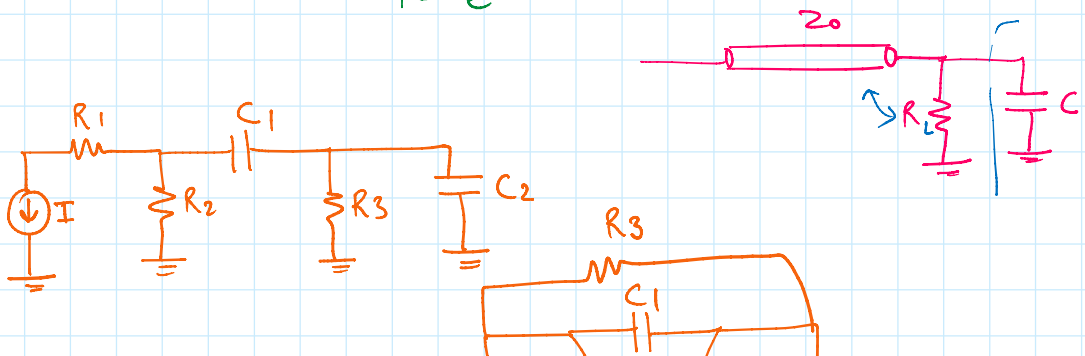


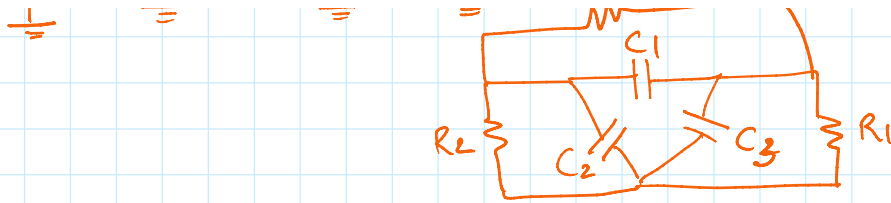


Time Domain Reflectometry (TDR)


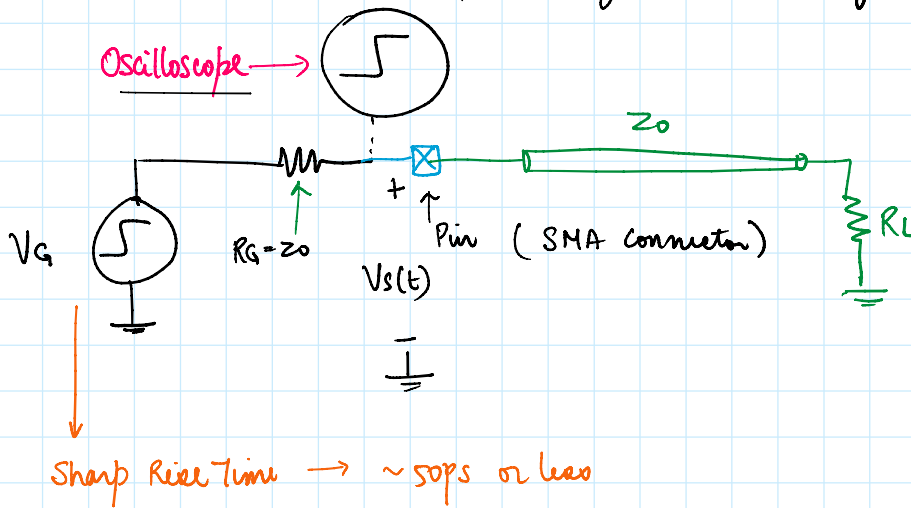
1. Measure the characteristic impedance
2. Determine the nature of the load
3. Detect the presence of discontinuity in the Tx line.




Resistive Termination

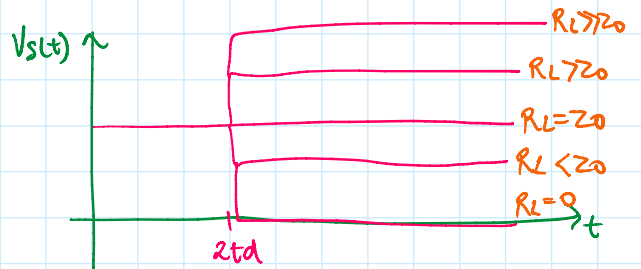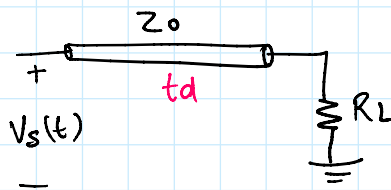

Inductive Termination

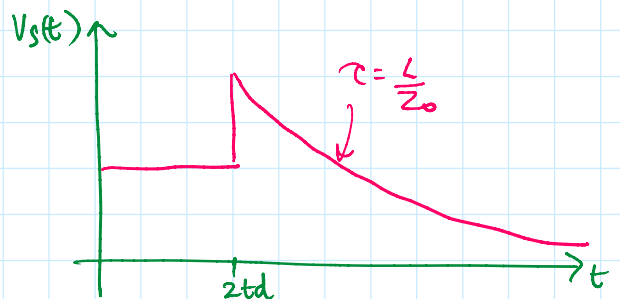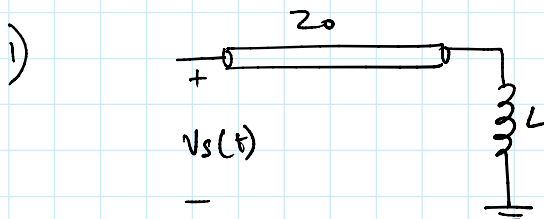

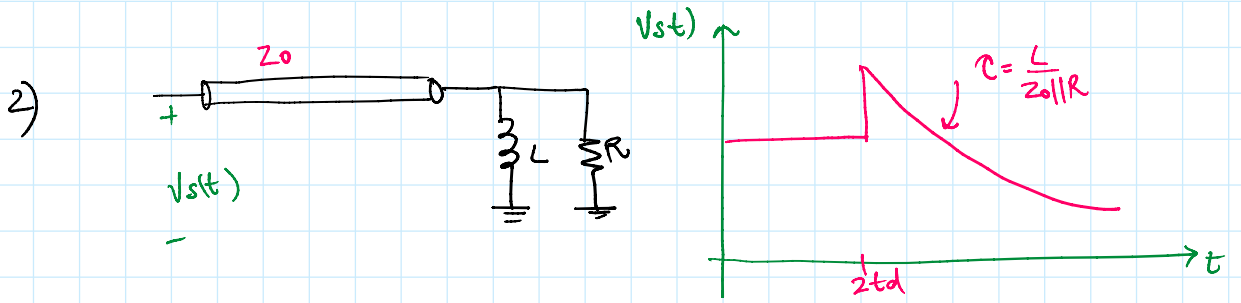

Capacitive Load:

