

Analysis of Transmission line with Analog signal

→ RF

- Assume Loss-less Transmission Line : $R=0; G=0$

$$\gamma = \sqrt{(R+j\omega L)(G+j\omega C)}$$

$$= \alpha + j\beta$$

↓
0

Voltage :

$$V(z) = V^+ e^{j\beta z} + V^- e^{-j\beta z}$$

$$V(z) = V^+ e^{j\beta z} \left[1 + \frac{V^-}{V^+} e^{-j2\beta z} \right]$$

Standing Voltage Equation

$$V(z) = V^+ e^{j\beta z} \left[1 + \Gamma_L e^{-j2\beta z} \right]$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$\Gamma_L = \frac{V^-}{V^+}$$

Complex quantity

$$\Gamma_L = |\Gamma_L| e^{j\phi_L}$$

Current :

$$I(z) = \frac{V^+}{Z_0} e^{j\beta z} - \frac{V^-}{Z_0} e^{-j\beta z}$$



$$I(z) = \frac{V^+}{Z_0} e^{j\beta z} \left[1 - \Gamma_L e^{-j2\beta z} \right]$$

Standing Current Equation.

Phasor representation

$$V(z) = |V^+ e^{j\beta z}| \left[1 + |\Gamma_L| e^{j(\phi_L - 2\beta z)} \right]$$

$$I(z) = \frac{V^+}{Z_0} e^{j\beta z} \left[1 - |\Gamma_L| e^{j(\phi_L - 2\beta z)} \right]$$

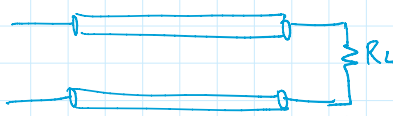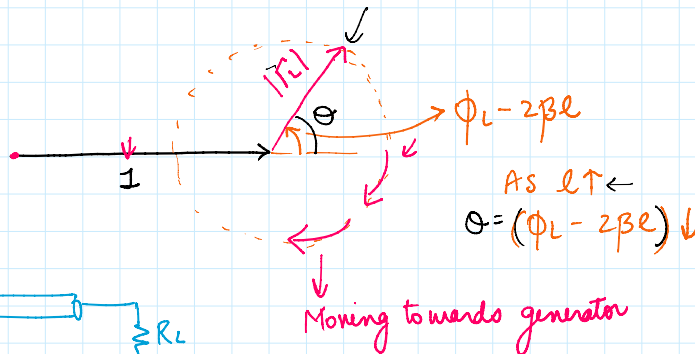

← $l=0$
 l increases

$$V(l) \text{ maximum} = v^+ e^{j\beta l} [1 + |\Gamma|] \quad ; \quad I(l) \text{ minimum} = \frac{v^+}{Z_0} e^{j\beta l} [1 - |\Gamma|]$$

$$V(l) \text{ minimum} = v^+ e^{j\beta l} [1 - |\Gamma|] \quad ; \quad I(l) \text{ maximum} = \frac{v^+}{Z_0} e^{j\beta l} [1 + |\Gamma|]$$

Observation :

1. Point of maximum voltage corresponds to minimum current
2. Point of minimum voltage corresponds to maximum current.

VSWR: Voltage Standing Wave Ratio.

$$\rho = \frac{|V|_{\max}}{|V|_{\min}} = \frac{v^+ e^{j\beta l} [1 + |\Gamma|]}{v^+ e^{j\beta l} [1 - |\Gamma|]} = \frac{1 + |\Gamma|}{1 - |\Gamma|} = \rho$$

The goal should be to have $\rho = 1$

$$1 < \rho < \infty$$

$$-1 \leq \Gamma \leq 1$$

Case 1: Short Circuit Transmission Line.

Standing Wave Pattern

$$\left. \begin{aligned} V(l) &= v^+ e^{j\beta l} + v^- e^{-j\beta l} \\ I(l) &= \frac{v^+}{Z_0} e^{j\beta l} - \frac{v^-}{Z_0} e^{-j\beta l} \end{aligned} \right\} \begin{aligned} \Gamma &= -1 \\ v^- &= -v^+ \end{aligned}$$

$$V(l) = v^+ e^{j\beta l} - v^+ e^{-j\beta l} = v^+ [e^{j\beta l} - e^{-j\beta l}]$$




$$I(l) = \frac{v^+}{Z_0} e^{j\beta l} + \frac{v^+}{Z_0} e^{-j\beta l} = \frac{v^+}{Z_0} [e^{j\beta l} + e^{-j\beta l}]$$

$$I(l) = \frac{V^+}{Z_0} e^{j\beta l} + \frac{V^+}{Z_0} e^{-j\beta l} = \frac{V^+}{Z_0} [e^{j\beta l} + e^{-j\beta l}]$$

$$V(l) = j V^+ Z_0 \sin(\beta l) \leftarrow$$

$$I(l) = \frac{V^+}{Z_0} \cdot Z_0 \cos(\beta l) \leftarrow$$
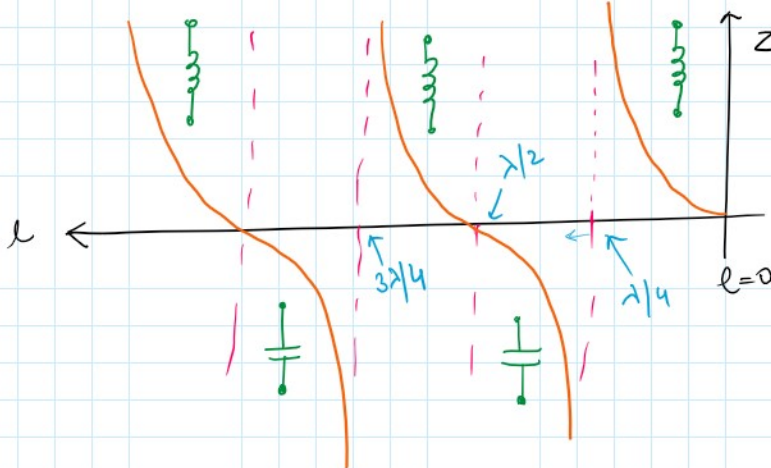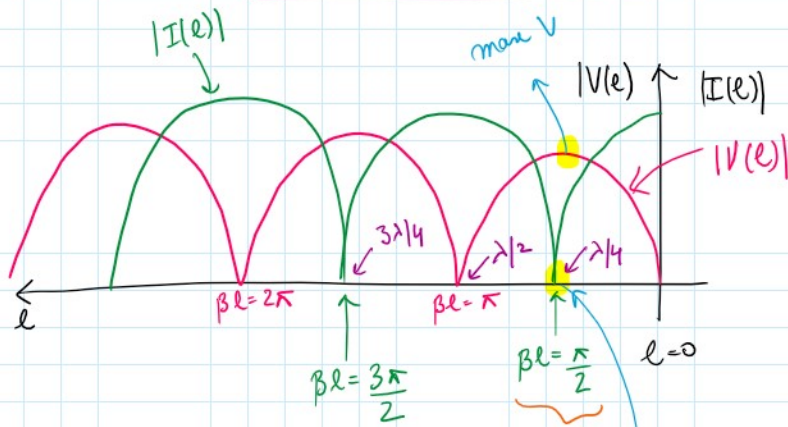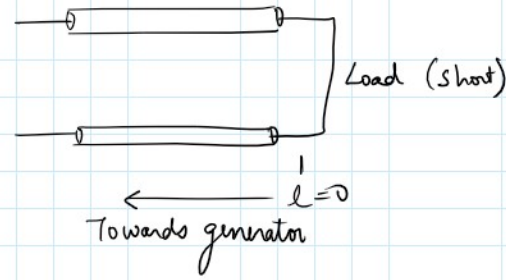
$$Z(l) = \frac{V(l)}{I(l)} = j Z_0 \tan(\beta l)$$



$$\frac{2\pi}{\lambda} \cdot l = \frac{\pi}{2}$$

$$l = \frac{\lambda}{4}$$