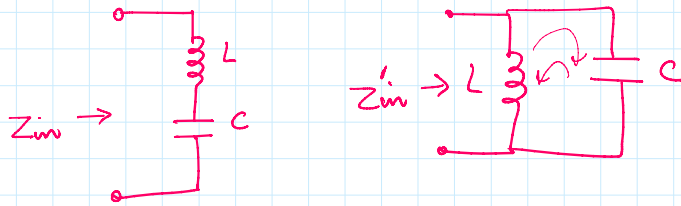


No class on Wednesday (2/19)



$$\omega_{res} = \frac{1}{\sqrt{LC}}$$

$$\omega_{res} = \frac{1}{\sqrt{LC}}$$

$Z_{in} = 0$ at ω_{res}


$Z_{in} = \infty$ at ω_{res}


$$Z_{in} = sL + \frac{1}{sC} = \frac{s^2LC + 1}{sC} \rightarrow 0 \quad \omega = \frac{1}{\sqrt{LC}}$$

$$sL \parallel \frac{1}{sC} = \frac{sL}{sC} = \frac{sL}{s^2LC + 1}$$


$$= \frac{j\omega L}{-\omega^2LC + 1} \rightarrow 0 \quad \omega = \frac{1}{\sqrt{LC}}$$

Parallel LC are used in oscillators.

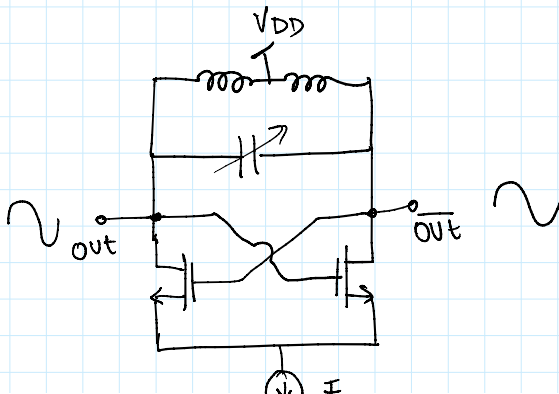

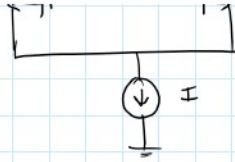

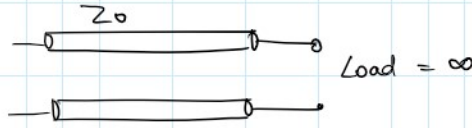Case 2: Standing Wave in Open Circuit Transmission Line.



$$V(l) = v^+ e^{j\beta l} + v^- e^{-j\beta l}$$

$$I(l) = \frac{v^+}{Z_0} e^{j\beta l} - \frac{v^-}{Z_0} e^{-j\beta l}$$

$$\Gamma_L = 1$$

$$v^- = v^+$$



$$V(l) = v^+ (e^{j\beta l} + e^{-j\beta l})$$


$$I(l) = \frac{v^+}{Z_0} (e^{j\beta l} - e^{-j\beta l})$$

$$V(l) = v^+ \cdot 2 \cdot \cos(\beta l)$$

$$I(l) = j \frac{2v^+}{Z_0} \sin(\beta l)$$
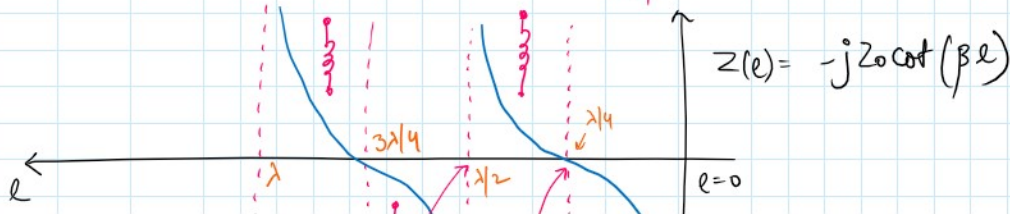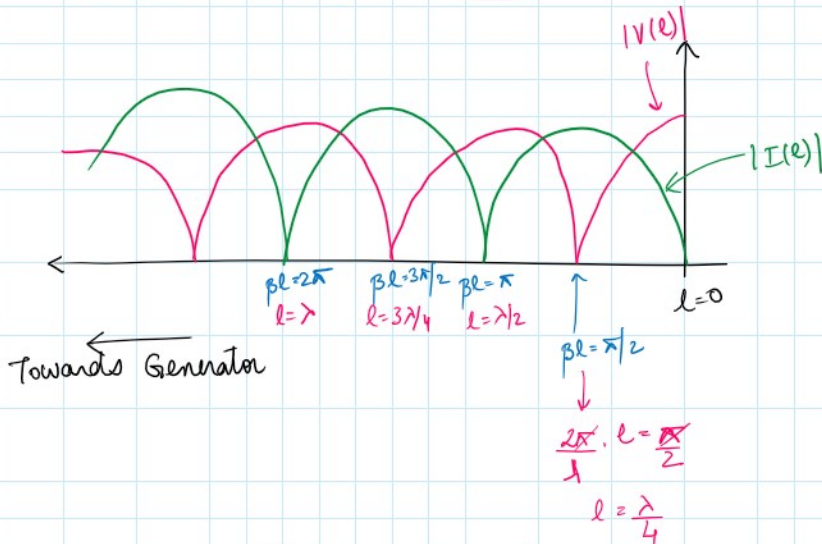
$$Z(l) = \frac{V(l)}{I(l)} = -j Z_0 \cot(\beta l)$$



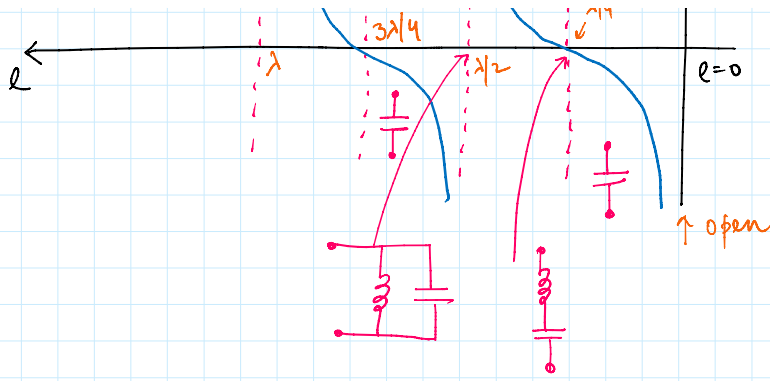


Summary

- 1) $|\leftarrow l < \lambda/4 \rightarrow| \equiv \text{capacitor}$ $l = \lambda/4 \equiv \text{series LC}$
- 2) $l < \lambda/4 \equiv \text{inductor}$ $l = \lambda/4 \equiv \text{parallel LC}$
- 3) $|\leftarrow \lambda/4 < l < \lambda/2 \rightarrow| \equiv \text{inductor}$
- 4) $|\lambda/4 < l < \lambda/2| \equiv \text{capacitor}$

Case 3:

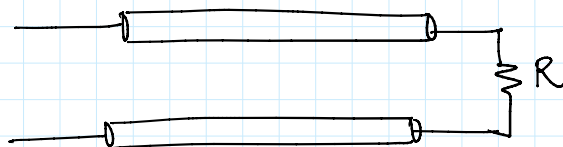VSWR in a transmission line with Resistive Load.



Loss Less Transmission Line : $Z_0 = R_0$
Pure resistive

Loss Less Transmission Line: $Z_0 = R_0$
pure resistive

$$V(z) = v^+ e^{j\beta z} \left(1 + |\Gamma_L| e^{j(\phi_L - 2\beta z)} \right)$$

$$I(z) = \frac{v^+}{Z_0} e^{j\beta z} \left(1 - |\Gamma_L| e^{j(\phi_L - 2\beta z)} \right)$$

$$\Gamma_L = |\Gamma_L| e^{j\phi_L}$$

↓
0

$$\frac{Z_L - Z_0}{Z_L + Z_0} = \frac{R_L - R_0}{R_L + R_0}$$