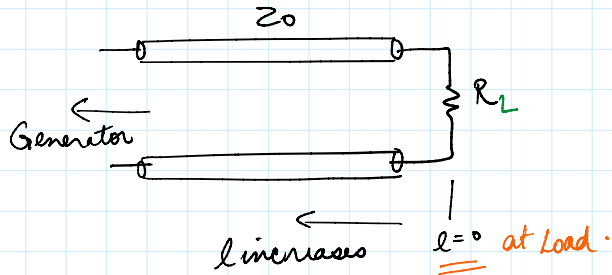


VSWR with a resistive load.



Lossless line $\rightarrow Z_0$ is real

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$R = 0 \\ G = 0$$

$$V(l) = V^+ e^{j\beta l} (1 + |\Gamma_L| e^{j(\phi_L - 2\beta l)}) \\ I(l) = \frac{V^+}{Z_0} e^{j\beta l} (1 - |\Gamma_L| e^{j(\phi_L - 2\beta l)})$$

$$\Gamma_L = \frac{R_L - Z_0}{R_L + Z_0}$$


Real quantity with angle 0

$$\Gamma_L = |\Gamma_L| e^{j\phi_L}$$

$$V(l) = V^+ e^{j\beta l} (1 + \Gamma_L e^{-j2\beta l}) \\ I(l) = \frac{V^+}{Z_0} e^{j\beta l} (1 - \Gamma_L e^{-j2\beta l})$$

$$\text{@ } l=0 \text{ (at Load)} = \begin{aligned} V(0) &= V^+ (1 + \Gamma_L) \\ I(0) &= \frac{V^+}{Z_0} (1 - \Gamma_L) \end{aligned}$$

Phasor for Voltage at $l=0$


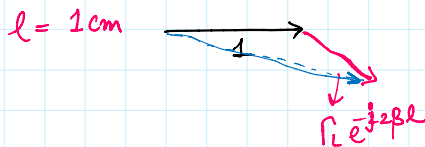


Observation: If $\Gamma_L > 0$
 Γ_L is positive
 $R_L > Z_0$

$|V(0)|$ is maximum at the load



$|V(l)|$ reduces as we move away from the load.



Phasor for Current

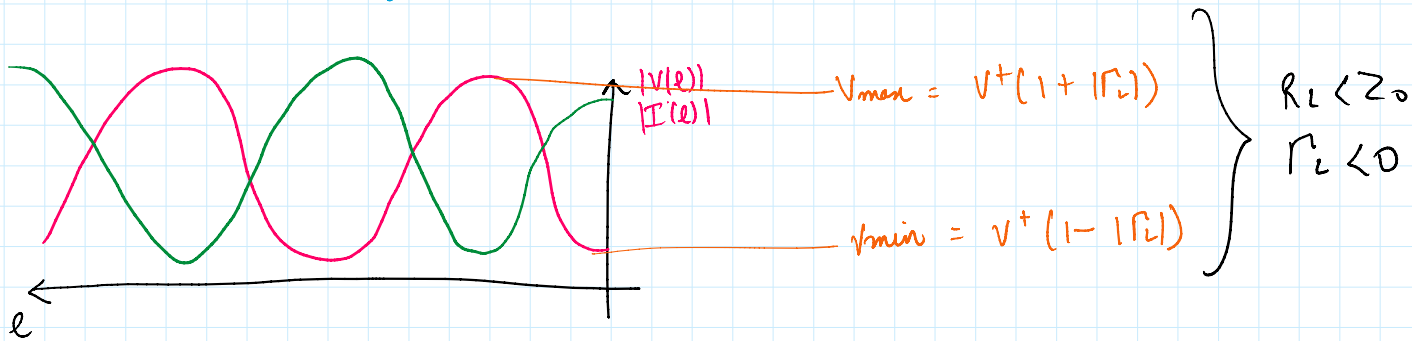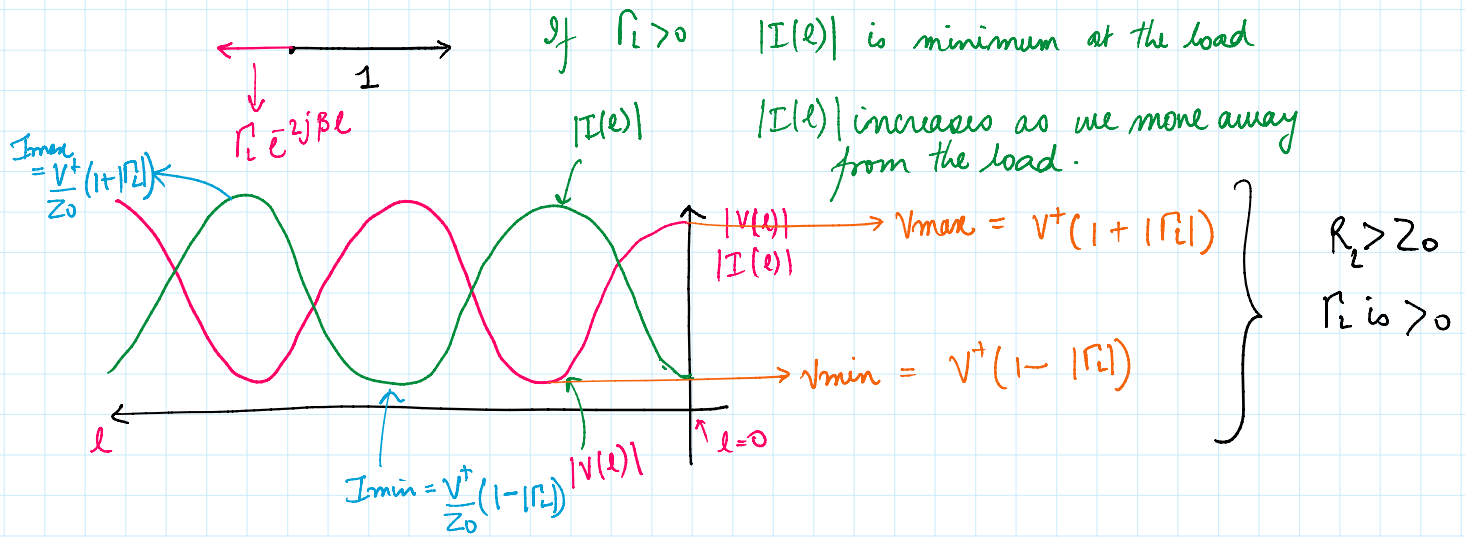


$$V(l) = V^+ e^{j\beta l} (1 + |\Gamma_L| e^{j(\phi_L - 2\beta l)})$$

@ $l=0$

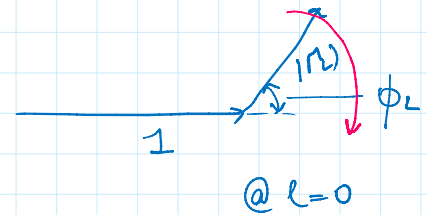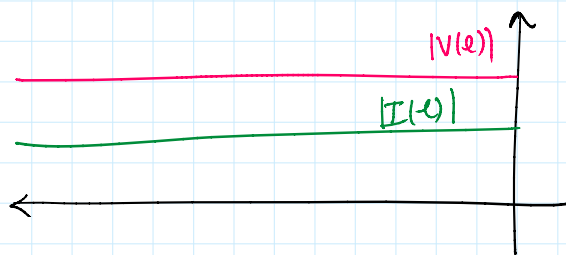

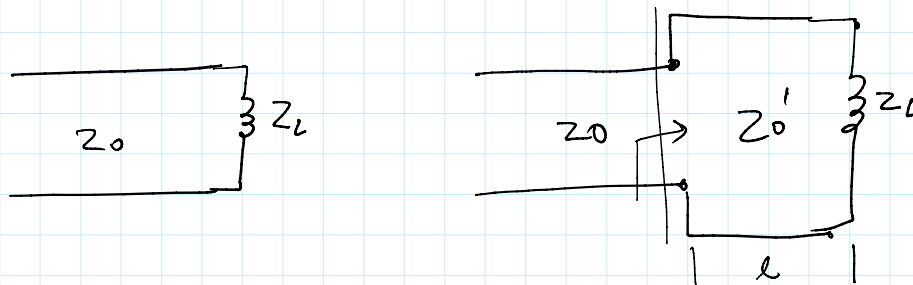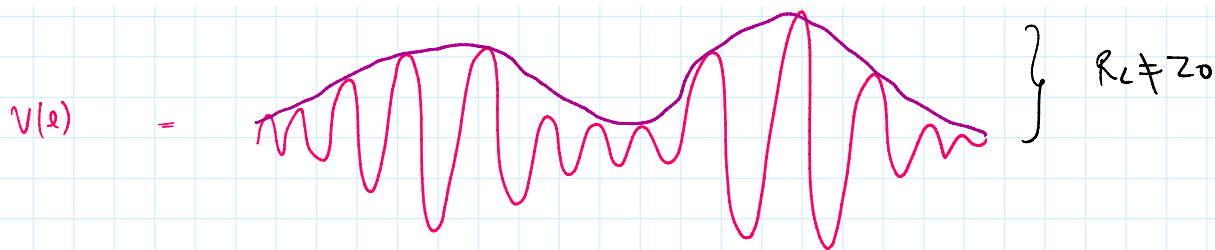

Example: 1

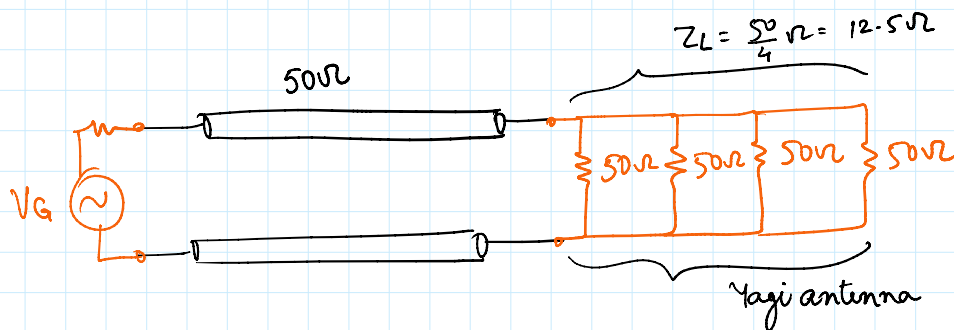

a) $\Gamma_L = \frac{12.5 - 50}{12.5 + 50} = -0.6 = 0.6 e^{j\pi}$

b) Calculate V_{max} , V_{min} , I_{max} , I_{min}

$V^+ = 1V$

$V_{max} = 1.6V \rightarrow V^+ (1 + |\Gamma_L|)$
 $1 + 0.6$

$V_{min} = 0.4 \rightarrow V^+ (1 - |\Gamma_L|)$

$I_{max} = \frac{V^+}{Z_0} (1 + |\Gamma_L|) = \frac{1.6}{50} = 32mA$

$I_{min} = \frac{V^+}{Z_0} (1 - |\Gamma_L|) = \frac{0.4}{50} = 8mA$

c) Sketch $|V(z)|$ & $|I(z)|$ as a function of z/λ starting at $z=0$

$$V(l) = V^+ e^{j\beta l} (1 + 0.6 e^{j\pi - 2j\beta l}) \quad \beta = \frac{2\pi}{\lambda}$$

$$V(l) = \underbrace{V^+}_{1} e^{j\frac{2\pi}{\lambda} l} (1 + 0.6 e^{j\pi(1-4l/\lambda)})$$

↓ take absolute magnitude

$$\rightarrow |V(l)| = \left| (1 + 0.6 \cos[\pi(1-4l/\lambda)] + j0.6 \sin[\pi(1-4l/\lambda)]) \right|$$

$$\frac{l}{\lambda} = 0 \quad |V(l)| = 0.4V$$

$$\frac{l}{\lambda} = \frac{1}{4} \quad = 1.6V$$

$$\frac{l}{\lambda} = \frac{1}{2} \quad = 0.4V$$

$$\frac{l}{\lambda} = \frac{3}{4} \quad = 1.6V$$

$$\frac{l}{\lambda} = 1 \quad = 0.4V$$