

Example


$$v_p = 2.07 \times 10^8 \text{ m/s}$$

Propagation Velocity

$$Z_0 = 50 \Omega$$

- We want 15nH from a TX line short circuited at the output
- We want this inductance @ 3GHz

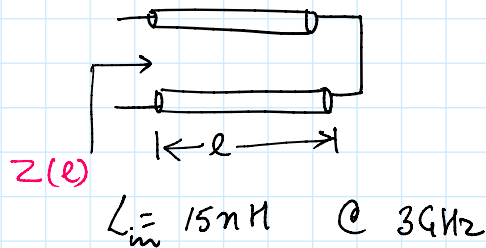Q: What is the length of the transmission line



$$Z(l) = j Z_0 \tan(\beta l)$$

$$\beta = \frac{2\pi}{\lambda}$$

$$j \cdot 2\pi \times 3 \times 10^9 \times 15 \times 10^{-9} = j \cdot 50 \tan\left(\frac{2\pi}{\lambda} \cdot l\right)$$

$$\lambda = \frac{v_p}{f}$$

$$\frac{v_p}{f} \frac{1}{2\pi} \tan^{-1}\left(\frac{2\pi \times 3 \times 10^9 \times 15 \times 10^{-9}}{50}\right) = l$$

$$v_p = \lambda f$$

$$l = 1.53 \text{ cm}$$

(b) If operating frequency changes to 4GHz

What is the impedance seen by 1.53cm (short circuited) transmission line?


Case 4

VSWR on a Complex Load

1)



2)

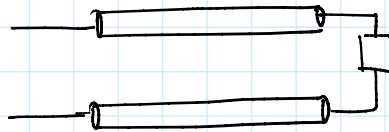


$$Z_L = R_L + jX_L$$

X_L is > 0 for inductance
 X_L is < 0 for capacitance

$$X_L = j\omega L$$

$$X_L = \frac{-j}{\omega C}$$
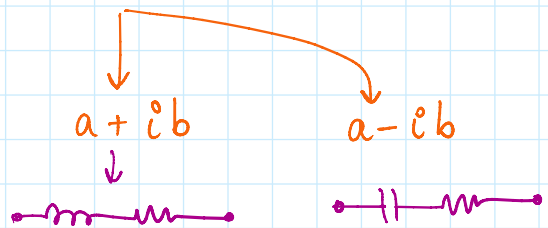
$$\Gamma_L = \frac{R_L + jX_L - Z_0}{R_L + jX_L + Z_0} = \frac{R_L - Z_0 + jX_L}{R_L + Z_0 + jX_L}$$



1) Inductive + Resistive Load.

$$\Gamma_L = |\Gamma_L| e^{j\phi_L}$$


$$\downarrow$$

$$\frac{R_L - Z_0 + jX_L}{R_L + Z_0 + jX_L} = a + ib$$

$$0 < \phi_L < \pi$$


$$V(l) = V^+ e^{j\beta l} \left(1 + \underbrace{|\Gamma_L| e^{j(\phi_L - 2\beta l)}} \right)$$

Phasor at $l=0$
(at the load end)

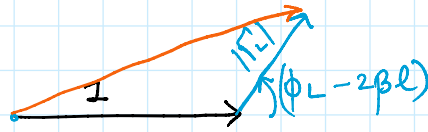


($\beta l = 0$)

$l = 1 \text{ cm}$

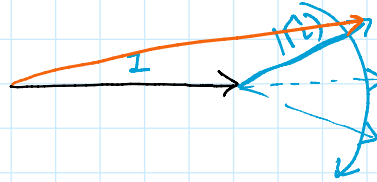

- Observation:
- $|V(l)|$ increases as we go away from the load.
 - $|V(l)|$ will **FIRST** get a maxima away from the load.

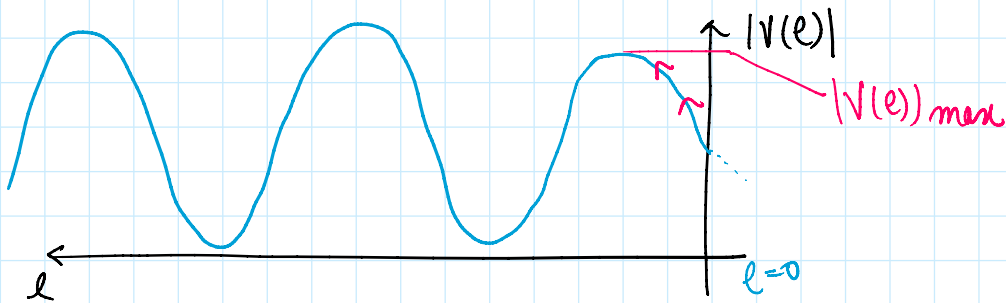

2) Capacitive + Resistive load.

$$\Gamma_L = \frac{R_L - Z_0 + jX_L}{R_L + Z_0 + jX_L} \quad \leftarrow -ve$$

$$|\Gamma_L| e^{j\phi_L}$$

\downarrow


$$-\pi < \phi_L < 0$$

Phasor of $V(l)$
at $l=0$







$l = 1 \text{ cm}$

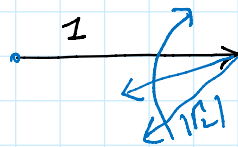

Observation: As we move away from the load $|V(l)|$ will **FIRST** hit a minimum.

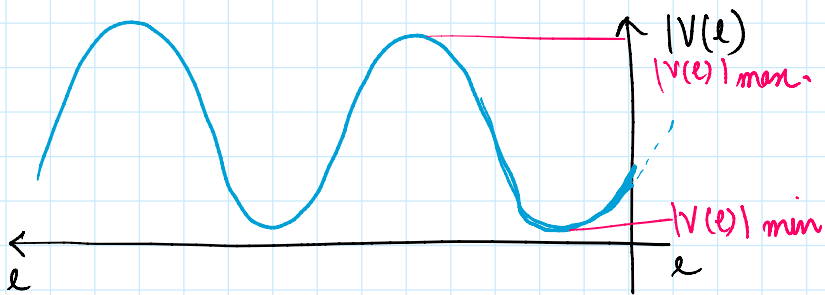

Derivation of V^+

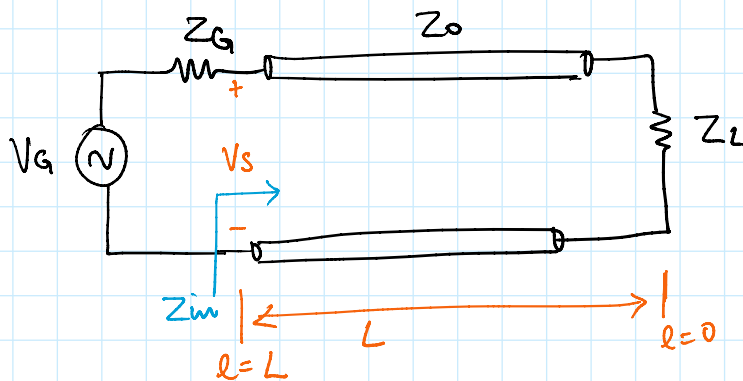

$$V(l) = V^+ e^{j\beta l} (1 + |\Gamma_L| e^{j(\phi_L - 2\beta l)}) \leftarrow$$

$$V_S = V(l) \Big|_{l=L} = \underset{\uparrow}{V^+} e^{j\beta L} (1 + |\Gamma_L| e^{j(\phi_L - 2\beta L)}) \quad \text{--- (1)}$$

$$V_s = \left(\frac{Z_{in}}{Z_{in} + Z_G} \right) V_G \quad - (2) \quad Z_{in} = Z(\ell) \Big|_{\ell=L}$$

↓
 $\frac{V(\ell)}{I(\ell)} \Big|_{\ell=L}$

$$Z_{in} = Z_0 \left(\frac{e^{j\beta\ell} + |\Gamma_L| e^{-j\beta\ell}}{e^{j\beta\ell} - \Gamma_L e^{-j\beta\ell}} \right) \leftarrow$$

Equati (1) & (2)

$$V^+ = \left(\frac{Z_{in}}{Z_{in} + Z_G} \right) V_G \frac{1}{e^{j\beta L} (1 + |\Gamma_L| e^{j(\Phi_L - 2\beta L)})}$$