

HW-4 Due Today
Midterm-2 Next Week



$$\gamma = \sqrt{(R+j\omega L)(G+j\omega C)}$$

$$Z_0 = \sqrt{\frac{R+j\omega L}{G+j\omega C}}$$

$$\gamma \cdot Z_0 = R + j\omega L$$


$$\frac{\gamma}{Z_0} = G + j\omega C$$

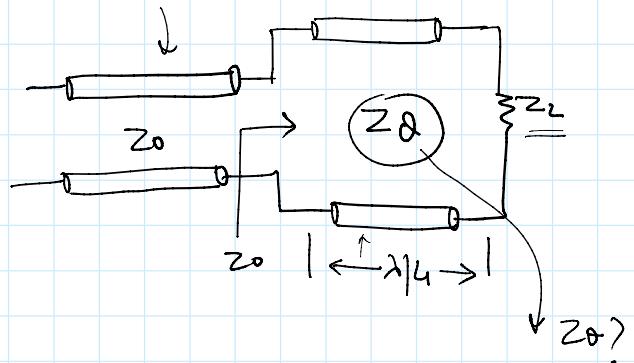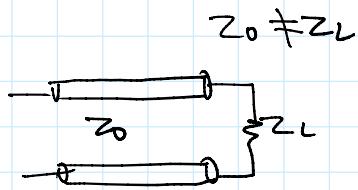Impedance Transformation \rightarrow Quarter wavelength matching .



$$V(l) = V^+ e^{rl} + V^- e^{-rl}$$
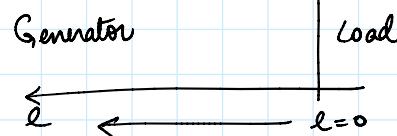
$$I(l) = \frac{V^+}{Z_0} e^{rl} - \frac{V^-}{Z_0} e^{-rl}$$



$$\frac{V(l)}{I(l)} = Z(l) = Z_0 \left\{ \frac{1 + \frac{Z_L e^{-2rl}}{Z_0 e^{2rl}}}{1 - \frac{Z_L e^{-2rl}}{Z_0 e^{2rl}}} \right\}$$

$$Z(l) = \frac{Z_L e^{-2rl}}{Z_L + Z_0}$$

$$z(l) = z_0 \left\{ \frac{1 + \frac{z_L - z_0}{z_L + z_0} e^{-2\gamma l}}{1 - \frac{z_L - z_0}{z_L + z_0} e^{-2\gamma l}} \right\}$$

$$z(l) = z_0 \left\{ \frac{z_L \cosh \gamma l + z_0 \sinh \gamma l}{z_0 \cosh \gamma l + z_L \sinh \gamma l} \right\}$$

$$\cosh \gamma l = \frac{e^{\gamma l} + e^{-\gamma l}}{2}$$

$$\sinh \gamma l = \frac{e^{\gamma l} - e^{-\gamma l}}{2}$$

Normalized Impedance

$$\frac{z(l)}{z_0} = \bar{z}(l) \rightarrow \text{normalize } z(l)$$

$$\frac{z_L}{z_0} = \bar{z}_L \rightarrow \text{normalized load}$$

For a lossless line

$$\begin{aligned} \alpha &= 0 \\ \gamma &= \alpha + j\beta \\ &\downarrow \\ \gamma &= j\beta \end{aligned}$$

$$\underline{z(l)} = z_0 \left\{ \frac{z_L \cosh(j\beta l) + z_0 \sinh(j\beta l)}{z_0 \cosh(j\beta l) + z_L \sinh(j\beta l)} \right\}$$

$$\bar{z}(l) = \frac{\bar{z}_L \cos \beta l + j \sin \beta l}{\cos \beta l + j \bar{z}_L \sin \beta l}$$

- Normalized impedance $\bar{z}(l)$ repeats itself every $\lambda/2$

$$\bar{z}(l) = \bar{z}(l + \lambda/2)$$

$$\beta(l + \lambda/2) = \frac{2\pi}{\lambda} \cdot l + \frac{\pi}{\lambda} \frac{\lambda}{2}$$

$$\beta(l + \lambda/2) = \beta l + \pi$$

$$\begin{aligned} Z(l+\lambda/2) &= \frac{\cancel{Z_L} \cdot \cancel{j} \cdot \cancel{\lambda/2}}{\cancel{\lambda/2}} \\ \beta(l+\lambda/2) &= \beta l + \pi \end{aligned}$$

$$\begin{aligned} \bar{Z}(l+\lambda/2) &= \frac{\bar{Z}_L \cos(\beta l + \pi) + j \sin(\beta l + \pi)}{\cos(\beta l + \pi) + j \bar{Z}_L \sin(\beta l + \pi)} \\ &= \frac{-\bar{Z}_L \cos(\beta l) - j \sin(\beta l)}{-\cos(\beta l) - j \bar{Z}_L \sin(\beta l)} \\ &= \frac{\bar{Z}_L \cos \beta l + j \sin \beta l}{\cos \beta l + j \bar{Z}_L \sin \beta l} = \bar{Z}(l) \end{aligned}$$

2. Normalized impedance **INVERTS** at every $l=\lambda/4$

$$\bar{Z}(l)$$

$$\bar{Z}(l+\lambda/4) = \frac{1}{\bar{Z}(l)}$$

$$\begin{aligned} \beta(l+\lambda/4) &\rightarrow \beta l + \frac{2\pi \cdot \cancel{\lambda}}{\cancel{\lambda}} \cdot \frac{\lambda}{4} \\ &= \beta l + \pi/2 \end{aligned}$$


$$\bar{Z}(l+\lambda/4) = \frac{\bar{Z}_L \cos(\beta l + \pi/2) + j \sin(\beta l + \pi/2)}{\cos(\beta l + \pi/2) + j \bar{Z}_L \sin(\beta l + \pi/2)}$$

$$\begin{aligned} \bar{Z}(l+\lambda/4) &= \frac{-\bar{Z}_L \sin \beta l + j \cos \beta l}{-\sin \beta l + j \bar{Z}_L \cos \beta l} \\ &= \frac{-\cancel{\cos \beta l} - j \bar{Z}_L \sin \beta l}{\cancel{\sin \beta l} + j \bar{Z}_L \cos \beta l} \end{aligned}$$

\downarrow multiply & divide by j

$$= -\frac{\text{coopl} - j\bar{z}_L \sin \beta l}{-\bar{z}_L \text{coopl} - j \sin \beta l}$$
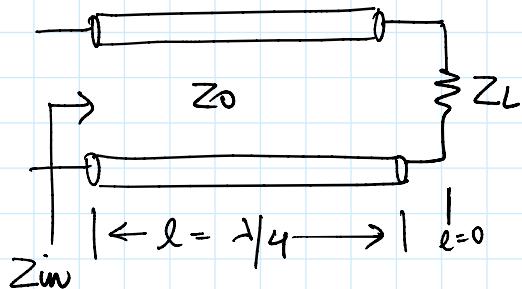
$$\boxed{\bar{z}(l+\lambda/4) = \frac{\text{coopl} + j\bar{z}_L \sin \beta l}{\bar{z}_L \text{coopl} + j \sin \beta l} = \frac{1}{\bar{z}(l)}}$$



$$\bar{z}(l) = \bar{z}_L \quad \text{at } l=0$$

$$Z_{in} = \bar{z}(l=\lambda/4)$$

$$\bar{z}(l=\lambda/4) = \frac{1}{\bar{z}_L}$$

$$\frac{Z_{in}}{Z_0} = \frac{Z_0}{Z_L}$$

$$Z_0^2 = Z_{in} \cdot Z_L$$



$$\rightarrow \boxed{Z_0 = \sqrt{Z_{in} \cdot Z_L}}$$





works out for a resistive load
in hand calculations.

Assume Z_L is resistive

Example:

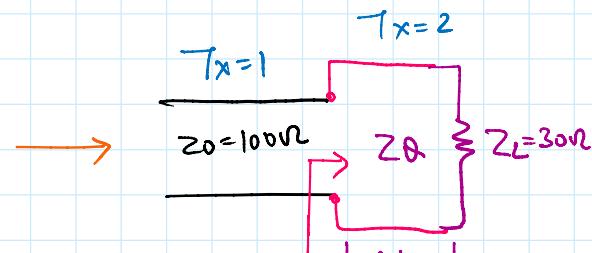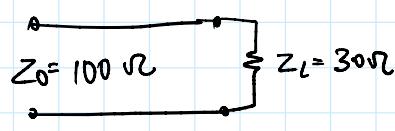

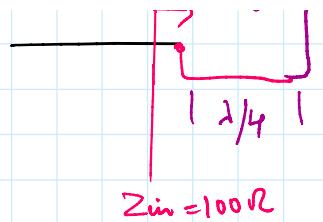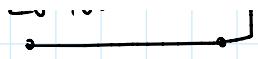

$$Z_Q = \sqrt{100 \times 30}$$

$$Z_Q = \sqrt{3000} \approx 54.8\Omega$$

↓
real

(lossless) \Rightarrow Terms inside sqrt must be real $\Rightarrow Z_L$ must be real

