



Midterm-2 on 03/04/2020

Contents: Lec-8 to Lec-18 (HW-3, HW-4)


Example 2:  $\lambda/4$  matching in complex loads.

$$Z_L = 73 + j42.5 \Omega$$

$$Z_0 = 100 \Omega$$

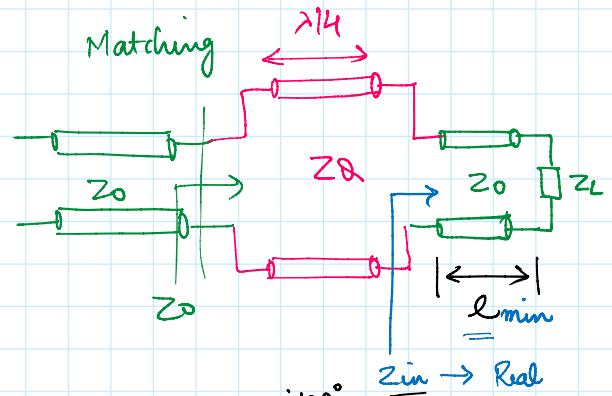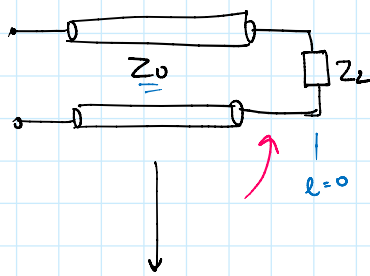
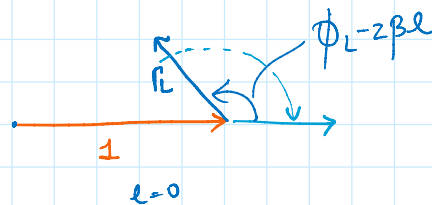
$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{73 + j42.5 - 100}{73 + j42.5 + 100} = 0.283 e^{j109^\circ}$$



$$Z_{in}(l_{min}) = \text{Real}$$



$$\phi_L - 2\beta l = 0$$

$$109^\circ \times \frac{\pi}{180^\circ} - 2 \cdot \frac{2\pi}{\lambda} \cdot l = 0$$

$$l_{min} = 0.151\lambda$$

$$\bar{Z}(l=l_{min}) = \left. \begin{array}{l} \bar{Z}_L \cos \beta l + j \sin \beta l \\ \cos \beta l + j \bar{Z}_L \sin \beta l \end{array} \right\}$$


$$\bar{Z}(l=l_{min}) = 1.79$$

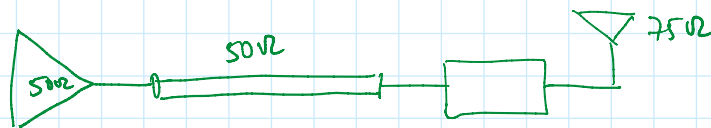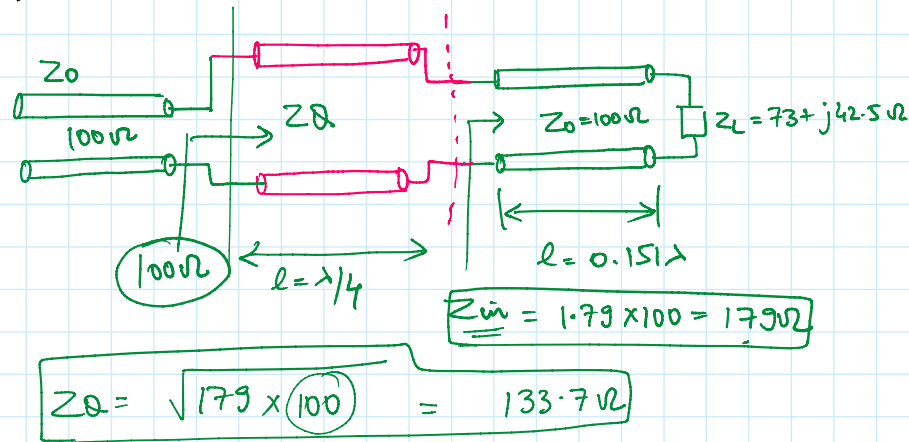

### Smith Chart

- Impedance represented on smith chart are normalized to  $Z_0$   
 $\downarrow$   
 Char Imp

#### 1) Complex Impedance Plane

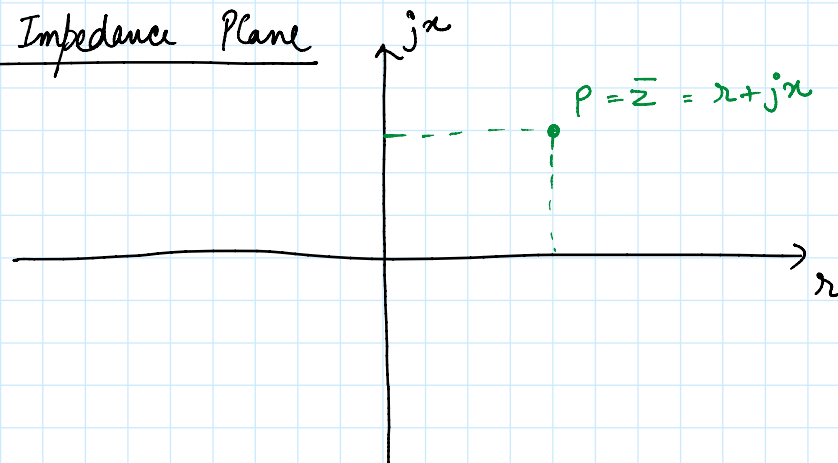

#### Observation

1. All points of  $P$  on the imaginary axis represents reactive load
2. All points on real axis represents real load
3. All points on right half plane represents all possible impedance values on a transmission line.

3. All points on right half plane represents all possible impedance values on a transmission line.

### Reflection Coefficient

$$\Gamma = \frac{Z - Z_0}{Z + Z_0} \quad ; \quad \Gamma(\ell) = \frac{Z(\ell) - Z_0}{Z(\ell) + Z_0}$$


$$\Gamma(\ell) = \frac{\bar{Z}(\ell) - 1}{\bar{Z}(\ell) + 1} = \mu + j\nu$$

$$= \underline{R}e^{j\theta} \quad (\text{Polar representation})$$

$$\bar{Z}(\ell) = \frac{1 + \Gamma(\ell)}{1 - \Gamma(\ell)}$$

#### Observation

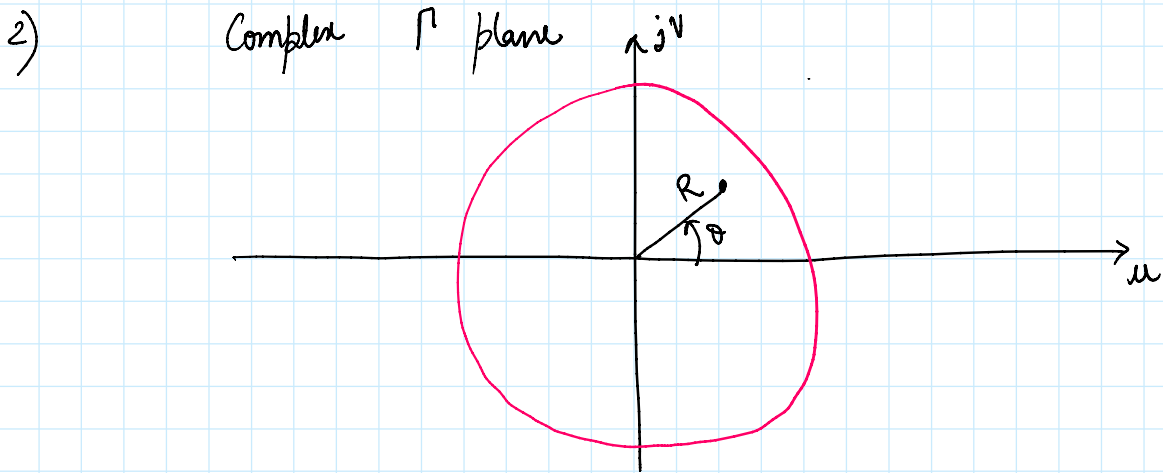1. If we know  $\Gamma(\ell)$ , we can get  $\bar{Z}(\ell)$
2. If we know  $\bar{Z}(\ell)$ , we can get  $\Gamma(\ell)$



- Observation :
1. All possible points of  $\Gamma(\ell)$  are inside the unit circle.
  2. All possible normalized impedance can be mapped on a complex  $\Gamma$  plane inside a unit circle.

Mapping b/w  $\Gamma$  plane and  $\bar{Z}$  plane.

$$\bar{Z} = r + jx = 1 + \Gamma$$

Impedanz  $Z$  in  $u$  und  $v$  - part

$$\bar{Z} = r + jx = \frac{1 + \Gamma}{1 - \Gamma}$$

$$r + jx = \frac{1 + u + jv}{1 - u - jv}$$