
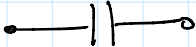
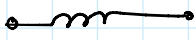


No class on Friday 01/10/2020

Lumped Circuit

322

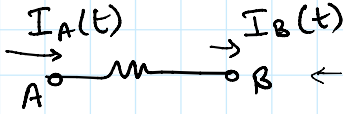


$$I_A(t) = I_B(t)$$

for all time  $t$



Distributed Circuit.

391

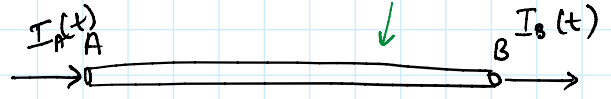


$$|I_A(t)| \neq |I_B(t)|$$


for all time  $t$

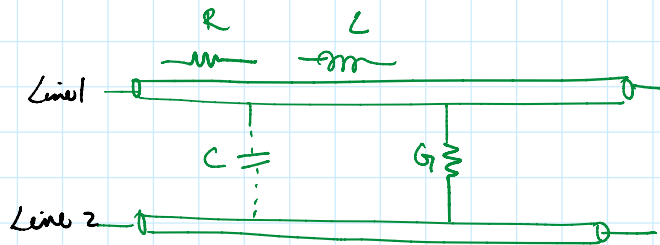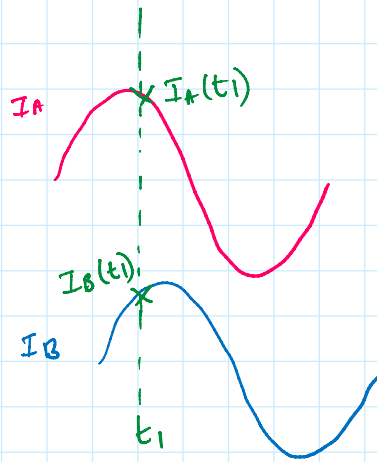

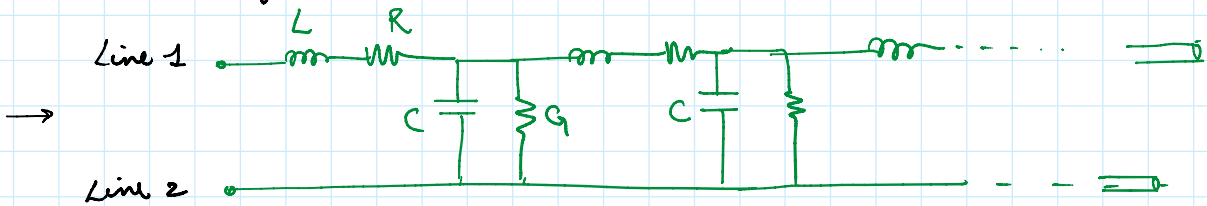Representation of distributed parameters in a transmission line.



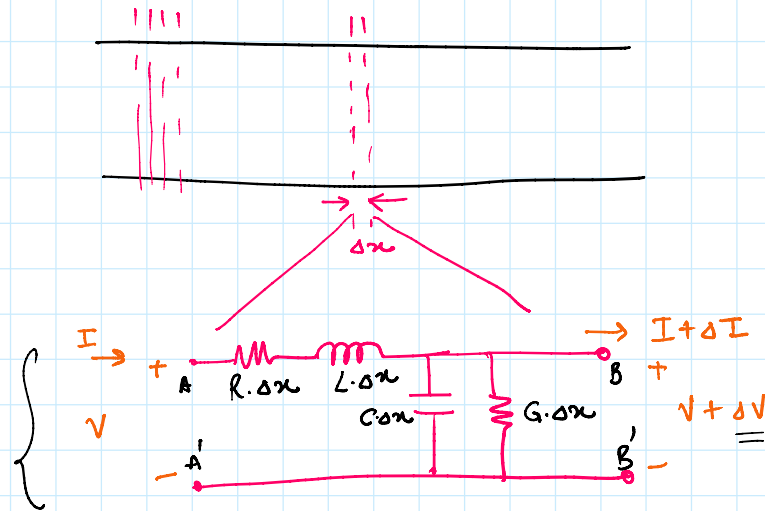- $\left\{ \begin{array}{ll} L: & \text{Inductance / unit length} \quad \text{H/m} \\ C: & \text{Capacitance / unit length} \quad \text{F/m} \\ R: & \text{Resistance / unit length} \quad \text{\Omega/m} \\ G: & \text{Conductance / unit length} \quad \text{S/m} \end{array} \right.$



Let us assume frequency of signal =  $f$  Hz  $\omega$  rad/sec.

Voltage drop b/w AA' & BB'

$$\Delta V = -(R\Delta x + j\omega L\Delta x) I$$

$$\Delta I = -(G\Delta x + j\omega C\Delta x) V$$

$$\lim_{\Delta x \rightarrow 0} \frac{\Delta V}{\Delta x} = -(R + j\omega L) I$$

$$\lim_{\Delta x \rightarrow 0} \frac{\Delta I}{\Delta x} = -(G + j\omega C) V$$

$$\frac{dV}{dx} = -(R + j\omega L) I$$

$$\frac{dI}{dx} = -(G + j\omega C) V$$

Coupled equations

Take a second derivative to uncouple the equations.

$$\frac{d^2V}{dx^2} = -(R + j\omega L) \frac{dI}{dx} \quad \text{--- (1)}$$

$$\frac{d^2I}{dx^2} = -(G + j\omega C) \frac{dV}{dx} \quad \text{--- (2)}$$

$$\frac{d^2 I}{dx^2} = -(G + j\omega C) \frac{dV}{dx} \quad - (2)$$

Substitute  $\frac{dI}{dx}$  in (1) &  $\frac{dV}{dx}$  in (2)

$$\frac{d^2 V}{dx^2} = + (R + j\omega L)(G + j\omega C) \cdot V$$

$$\frac{d^2 I}{dx^2} = + \underbrace{(R + j\omega L)(G + j\omega C)}_{\gamma^2} I$$

Characteristic of a transmission line  
 ↓  
 Constant for a given transmission line

$$\gamma^2 = (R + j\omega L)(G + j\omega C) = \text{Propagation Constant}$$

$$\frac{d^2 V}{dx^2} = \gamma^2 V$$

$$\frac{d^2 I}{dx^2} = \gamma^2 I$$

Solution of the differential equations

$$V(x) = v^+ e^{-\gamma x} + v^- e^{\gamma x}$$

↓ Forward travelling signal  
 ↘ Backward travelling signal.

↳ This voltage solution is wrt distance - x

Multiply the above equation by  $e^{j\omega t}$  to get the instantaneous value of voltage.

$$V(x, t) = V^+ e^{-\gamma x} e^{j\omega t} + V^- e^{\gamma x} e^{j\omega t}$$

Voltage in space & time.

Propagation constant  $\gamma = \alpha + j\beta$  (Complex quantity)  $= \sqrt{(R+j\omega L)(G+j\omega C)}$

- Only consider forward travelling wave

Amp  $V(x, t) = V^+ e^{-\gamma x} e^{j\omega t}$  Phase

$$\text{Re} \{ V(x, t) \} = \text{Re} \left\{ V^+ e^{-\alpha x} e^{-j\beta x} e^{j\omega t} \right\}$$

$$V(x, t) = V^+ e^{-\alpha x} \cos(\omega t - \beta x)$$

$\phi$

