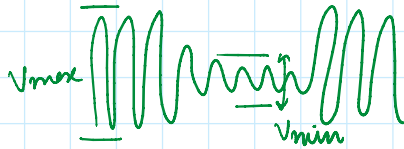


$$VSWR = \frac{|V_{max}|}{|V_{min}|}$$



Example 2: $Z_L = 65 - j75 \Omega$
 $Z_0 = 50 \Omega$

Calculate Γ_L , ϕ_L


Step 1: $\bar{Z}_L = \frac{65 - j75}{50} = 1.3 - j1.5$

Step 2: Draw constant VSWR circle

Step 3: Measure the radius of the VSWR circle : 4.6 cm

Step 4: Measure the radius of the Smith Chart : 8.3 cm

Step 5: Calculate $\Gamma_L = \frac{4.6 \text{ cm}}{8.3 \text{ cm}} = 0.55$

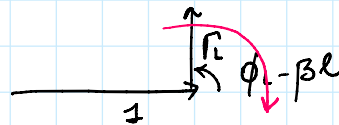


Example 3:


$$Z_0 = 50 \Omega$$

$$\epsilon_r = 2.25$$

$$\ell = 3 \text{ m}$$

(Transmission line length)

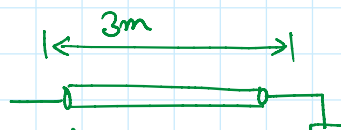

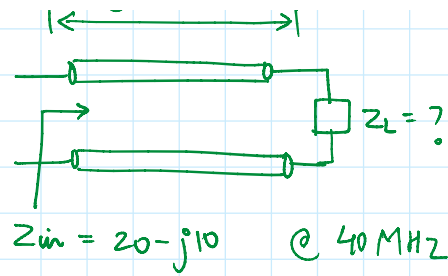

1. $Z_L = ?$,

2. Position of V_{min} in meters from the load.

Steps 1: Normalize the $Z_{in} \rightarrow \bar{Z}_{in} = \frac{20 - j10}{50} = 0.4 - j0.2$

Step 2: $\lambda = \frac{c}{\sqrt{\epsilon_r} f}$

$$\lambda = \frac{3 \times 10^8}{\sqrt{2.25} \cdot 40 \times 10^6} = 5 \text{ m}$$

$$l \text{ (in } \lambda) = \frac{3 \text{ m}}{5 \text{ m}} = 0.6 \lambda$$

Step 3: Go towards the load \rightarrow Counter clockwise rotation $\rightarrow 0.6 \lambda$

$$l = 0.5 \lambda + 0.1 \lambda$$

$$2\beta l = 2\pi$$

$$2 \cdot \frac{2\pi}{\lambda} \cdot l = 2\pi$$

$$l = \lambda/2$$

Step 4: Draw a line A & measure λ at \bar{Z}_{in} : $\lambda = 0.036$

Step 5: Find a point on the dial (towards load) at $\lambda = 0.136$

Step 6: Draw a line from centre to $\lambda = 0.136$ — line - B

Step 7: Draw a constant VSWR circle intersect line B and read out
 $\bar{Z}_L = 0.73 - j0.82$

Step 8: $Z_L = 50(0.73 - j0.82) \Omega$

$$Z_L = 36.5 - j41 \Omega$$

Maxima & Minima of Voltage

$$V_{max} = V^+(1 + |\Gamma_L|)$$

$$V_{min} = V^+(1 - |\Gamma_L|)$$

Step 1: Identify the position of V_{min} → Intersection of VSWR circle & the horizontal line
(left side)

Step 2: Measure the distance b/w \bar{Z}_L & V_{min} point in terms of λ

$$\lambda = 0.136$$

$$\left\{ \lambda = 5m \right\}$$

Distance of V_{min} from load = $5m \times 0.136 = 0.68m$ from load.