

V^+ - Amplitude of forward travelling wave: Generator to Load

V^- - Amplitude of reverse travelling wave: Load to generator.

Example 2 Continued:

$$v(t) = \operatorname{Re} \left\{ V^+ e^{-\alpha x} \frac{e^{-j\beta x + \omega t}}{e} \right\}$$

$$= \rightarrow \underset{\uparrow}{V^+} e^{-\alpha x} \cos(\beta x - \omega t + \phi_0)$$

$$\begin{aligned} x=0; t=0 \\ v(t) = 8.66V \\ \phi_0 = 30^\circ \end{aligned}$$

Substitute $x=0$ & $t=0$

$$8.66 = V^+ \cdot 1 \cos(\phi_0)$$

$$V^+ = \frac{8.66}{\cos 30^\circ} = \frac{8.66 \cdot 2}{\sqrt{3}}$$

$$\boxed{V^+ = 10V}$$

Step 2: Calculate the voltage at $t = 100ns$ $f = 1GHz$
 $x = 1m$

$$v(t) = V^+ e^{-\alpha x} \cos(\omega t - \beta x + \phi_0)$$

$$\alpha = 2.23 \text{ nepers/m}$$

$$\beta = 28.2 \text{ rad/m}$$

$$v(t) = -0.88V \}$$

- More analysis on the differential equations of Transmission Line

$$\frac{dV}{dx} = -(R+j\omega L)I$$

$$V = V^+ e^{-\gamma x} + V^- e^{\gamma x}$$

$$I = I^+ e^{-\gamma x} + I^- e^{\gamma x}$$

$$\frac{d}{dx} (V^+ e^{-\gamma x} + V^- e^{\gamma x}) = -(R+j\omega L) [I^+ e^{-\gamma x} + I^- e^{\gamma x}]$$

$$V^+ (-\gamma) e^{-\gamma x} + V^- (\gamma) e^{\gamma x} = -(R+j\omega L) [I^+ e^{-\gamma x} + I^- e^{\gamma x}]$$

Separate out the forward travelling & reverse travelling components.

$$V^+ (-\gamma) e^{-\gamma x} = -(R+j\omega L) I^+ e^{-\gamma x}$$

$$\frac{V^+}{I^+} = \frac{R+j\omega L}{\gamma}$$


$$\frac{V^-}{I^-} = -\frac{(R+j\omega L)}{\gamma}$$

$$\gamma = \sqrt{(R+j\omega L)(G+j\omega C)}$$


$$\frac{V^+}{I^+} = \sqrt{\frac{R+j\omega L}{G+j\omega C}} \quad \frac{V^-}{I^-} = -\sqrt{\frac{R+j\omega L}{G+j\omega C}}$$

Z_0 : Characteristic Impedance

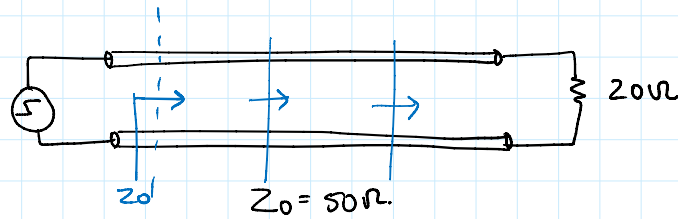Impedance seen by the forward travelling or reverse travelling wave



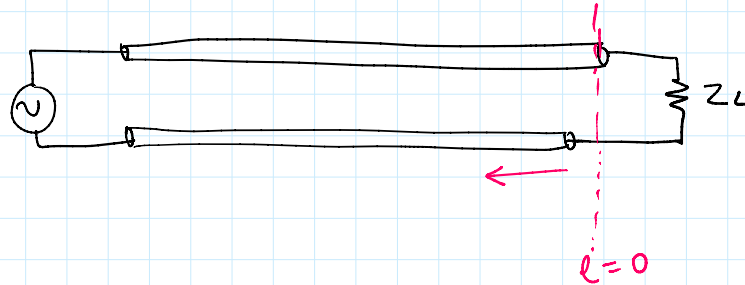Boundary Conditions on a Transmission Line



$$\left. \begin{aligned} V &= V^+ e^{+\gamma l} + V^- e^{-\gamma l} \quad (1) \\ I &= I^+ e^{+\gamma l} + I^- e^{-\gamma l} \quad (2) \end{aligned} \right\} \begin{array}{l} l \text{ is made negative because we are} \\ \text{assuming } l \text{ increases from right to} \\ \text{left.} \end{array}$$

Boundary Condition: At $l=0$ $Z = Z_L$ (load)

Take ratio of (1) & (2) & apply the boundary condition.

$$Z_L = \left. \frac{V}{I} \right|_{l=0} = \frac{V^+ + V^-}{I^+ + I^-}$$

$$\left\{ \begin{array}{l} \frac{V^+}{I^+} = Z_0 \\ \frac{V^-}{I^-} = -Z_0 \end{array} \right\}$$

$$Z_L = \left(\frac{V^+ + V^-}{V^+ - V^-} \right) Z_0$$

Characteristic Impedance

$$I^+ = \frac{V^+}{Z_0}; \quad I^- = \frac{V^-}{-Z_0}$$

Reflection Coefficient:

$$\Gamma(l) = \frac{V^- e^{-\gamma l}}{V^+ e^{+\gamma l}}$$

$$\Gamma(l=0) \text{ at load} = \frac{V^-}{V^+}$$

Re write

Re write

$$\frac{Z_L}{Z_0} = \frac{1 + \frac{V^-}{V^+}}{1 - \frac{V^-}{V^+}} = \left(\frac{1 + \Gamma(0)}{1 - \Gamma(0)} \right)$$

$$\frac{Z_L}{Z_0} = \frac{1 + \Gamma(0)}{1 - \Gamma(0)}$$

$$\frac{Z_L - Z_0}{Z_L + Z_0} = \Gamma(0)$$

$$\left\{ \begin{array}{l} \frac{a}{b} = \frac{c}{d} \\ \frac{a-b}{a+b} = \frac{c-d}{c+d} \end{array} \right\}$$

$$\Gamma(0) = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$\Gamma(0) = \frac{V^-}{V^+}$$

Ideally we don't want anything to reflect from the load.

→ V^- should ideally be 0

↓ The requires

$$Z_L = Z_0$$

- Terminate the transmission line with the characteristic impedance.